

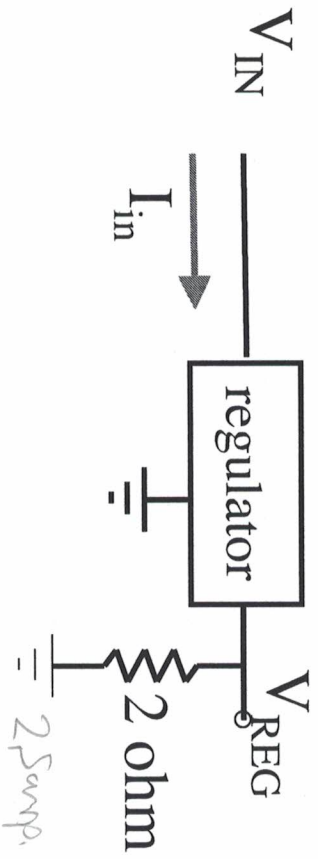
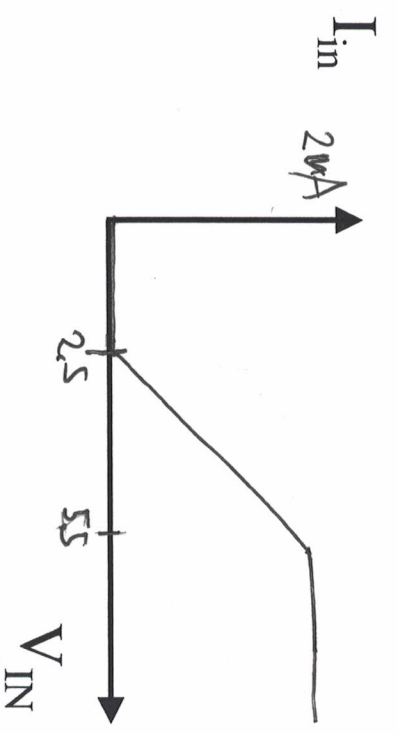



# Approximate voltage regulator behavior

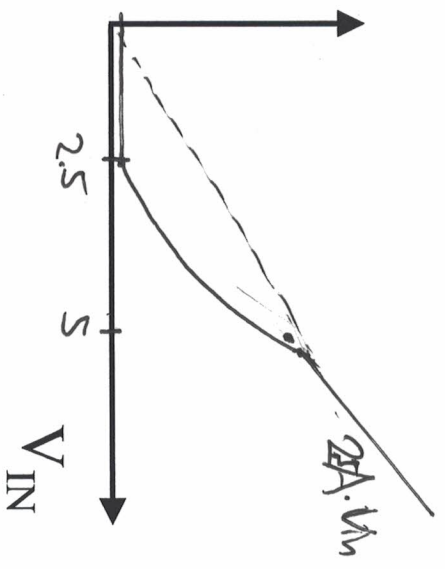




Linear Regulator  
nominal output 5V,

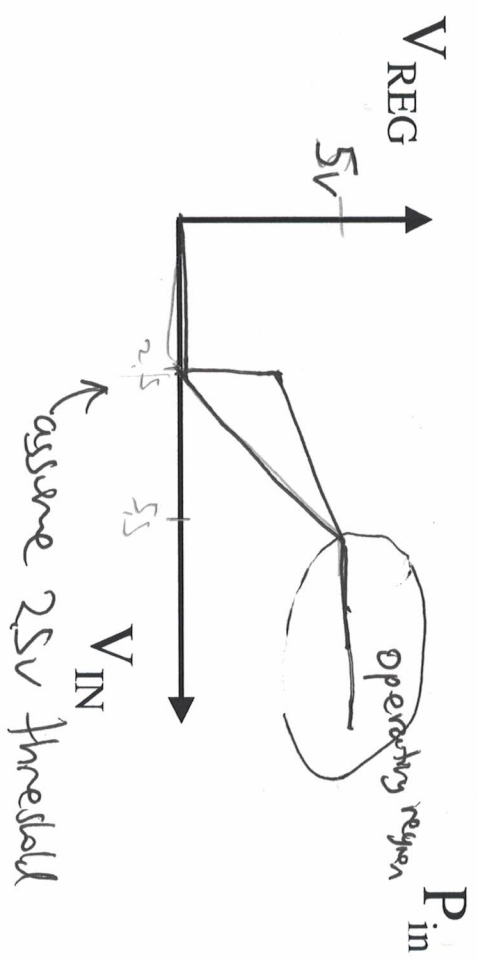

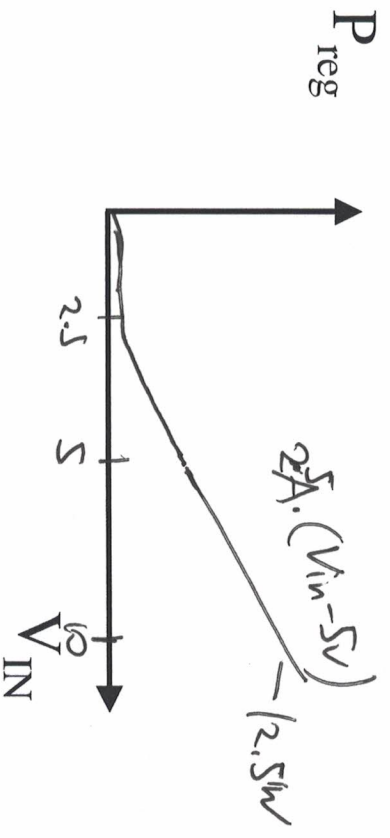
Power dissipated in regulator =  $I_{in} (V_{in} - V_{REG})$




# Approximate voltage regulator behavior

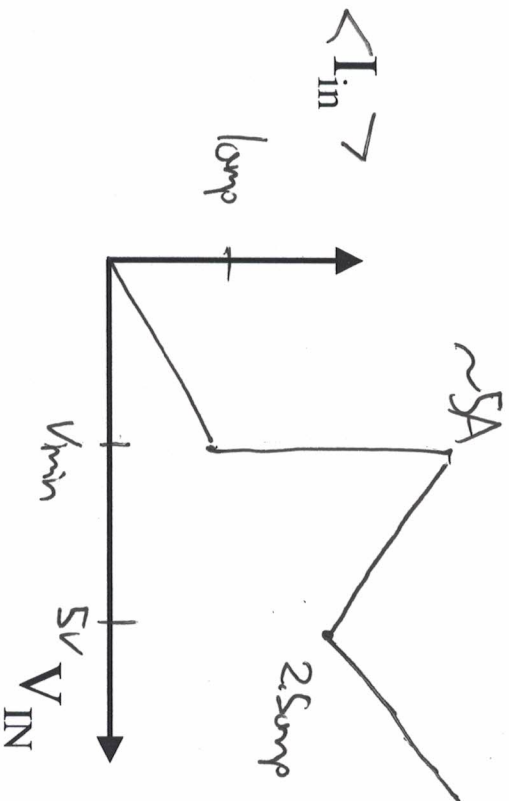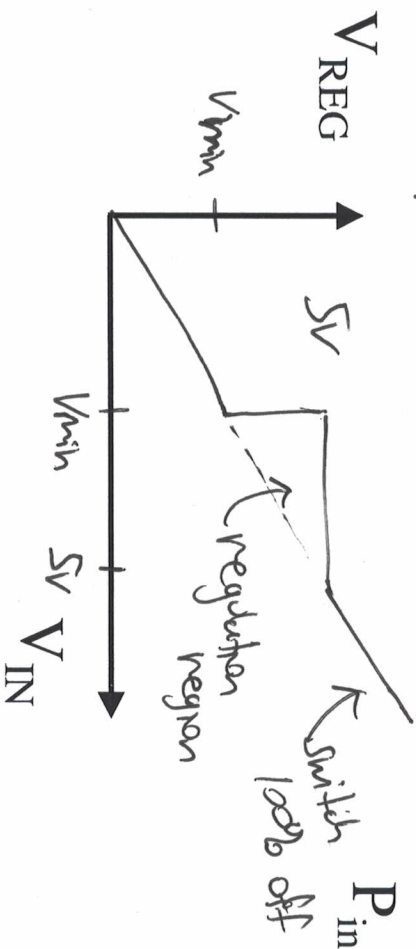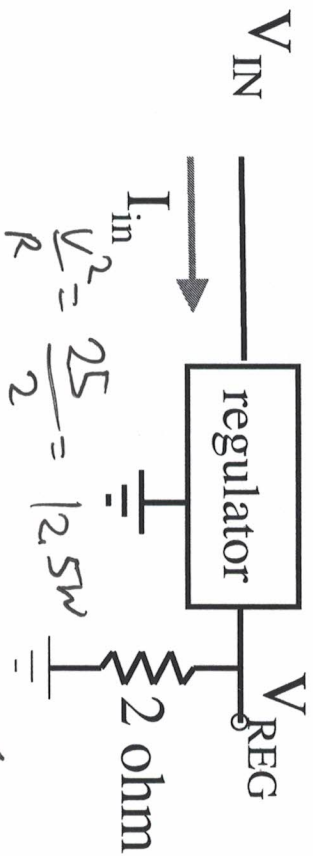

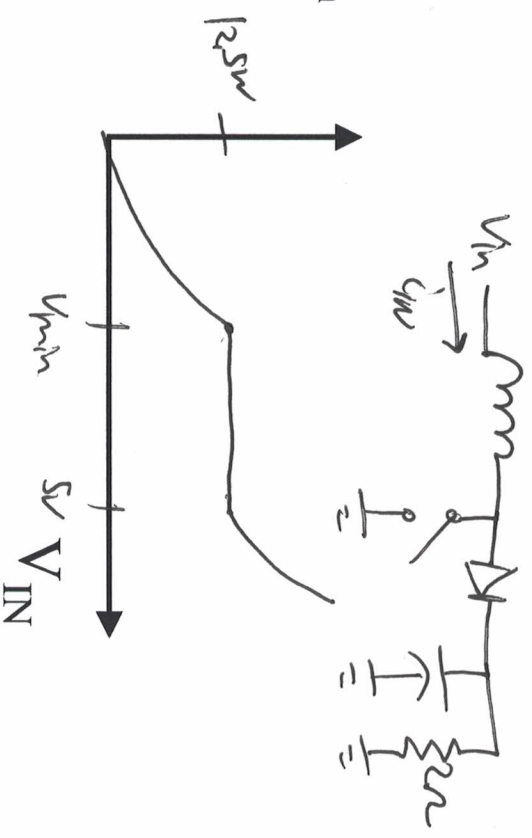Boost Converter, nominal  
Output 5V,  $V_{IN} < V_{REG}$






Power dissipated in regulator


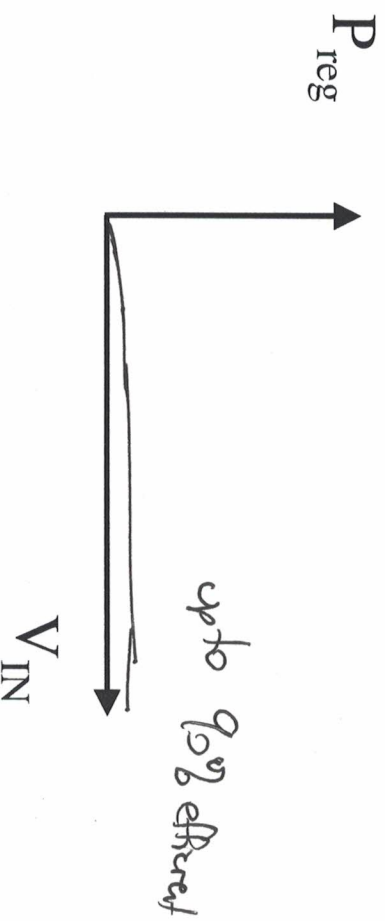


assumption: switch only cycles when  $V_{in} < V_{in} < 5V$   
2.5V


# Approximate voltage regulator behavior

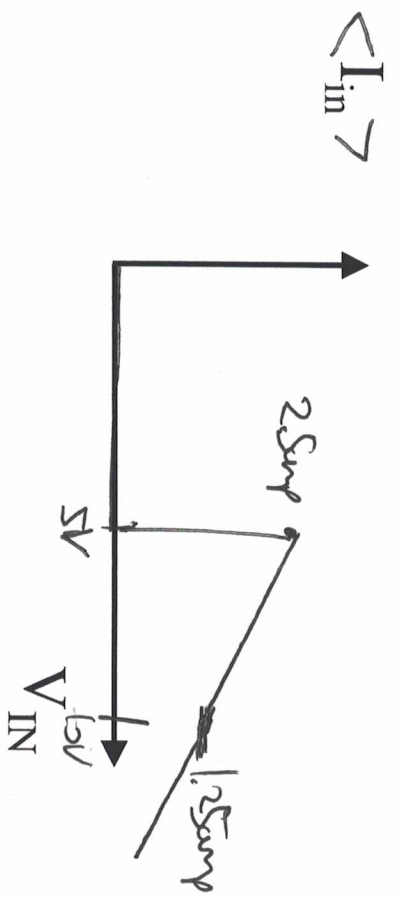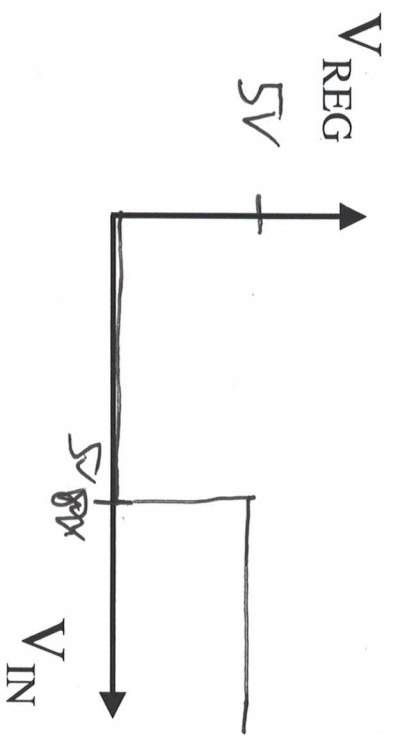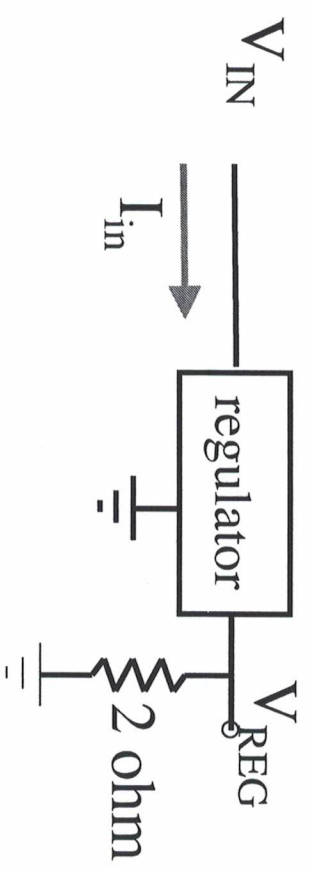

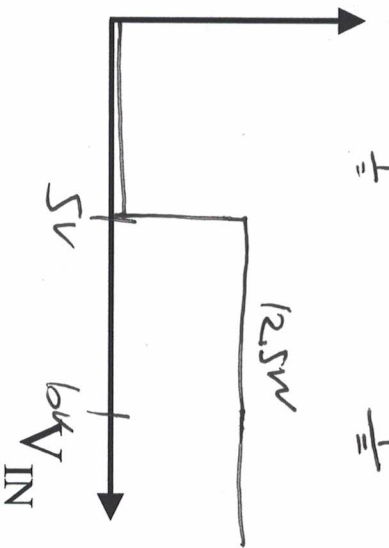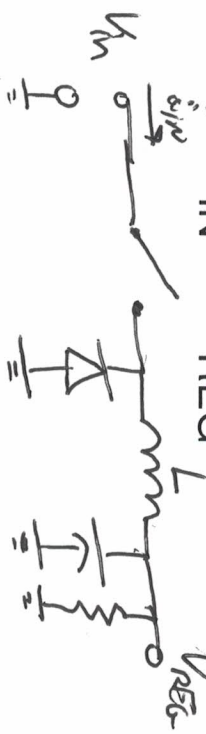Buck Converter, nominal  
Output 5V,  $V_{IN} > V_{REG}$



Power dissipated in regulator

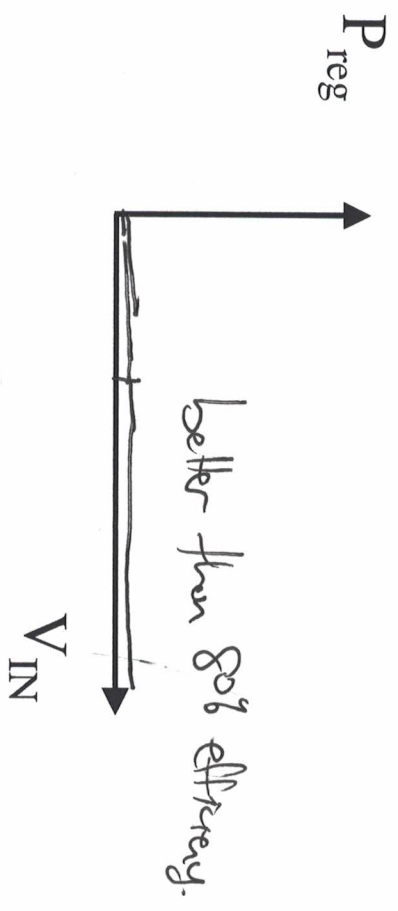

better than 80% efficiency.

Assumption  $V_{in} > 5V$  for switch operation  
(LM2678 recommends 8V). Assume 100% eff.