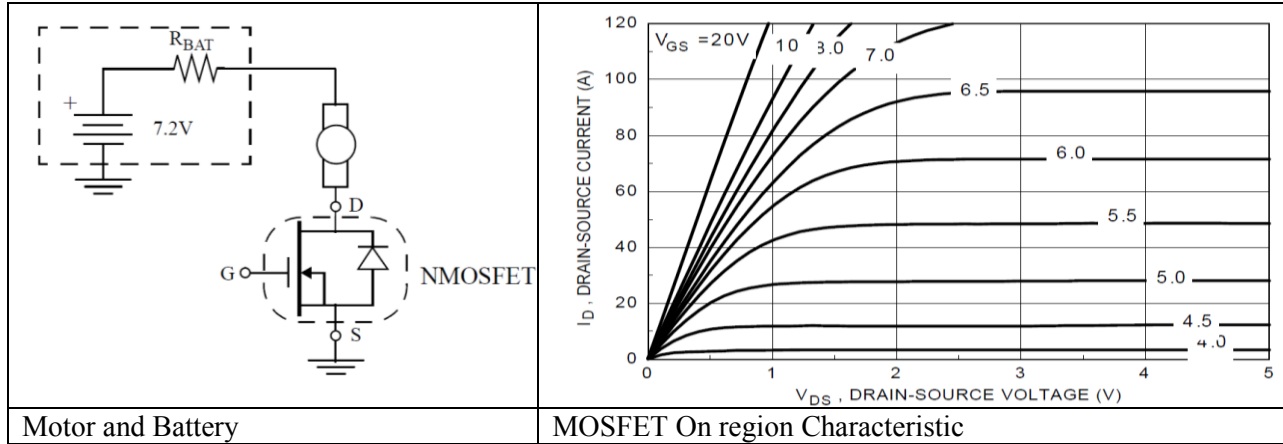


\*\*\* For practice, not collected or graded \*\*\*



Given:  $R_{BAT} = 0.06$  Ohms,  $R_m = 0.06$  ohms. Neglect motor inductance, assume static case. (Motor is stalled).

1. If  $V_{DS} = 0.0$  V, what is motor current? What is power dissipated in motor? What is battery voltage? What is power supplied by battery?
2. If MOSFET gate is driven such that  $V_{DS} = 2.4$  V, what is the motor current? What is the power dissipated in the motor? What is power dissipated in the MOSFET?
3. If  $V_{GS} = 5.5$  V, what is  $I_{DS}$ ? What is  $V_{DS}$ ? (Hint: loadline). What is power dissipated in motor? What is power dissipated in MOSFET?
4. Repeat 2, but now  $V_{GS} = 20$  V.