

EECS 192: Mechatronics Design Lab

Discussion 4: Project Proposal Feedback & Power Systems


GSI: Ducky Lin, Derek Chou

7 & 8 Feb 2017 (Week 4)

Project Proposal Feedback

- ▶ Beaglebone Blue pins
- ▶ Sensors
 - ▶ Line scan camera(s)
 - ▶ encoder/ back emf sensor
- ▶ Links
 - ▶ Line Scan Camera 1, Line Scan Camera 2
 - ▶ Optical encoder coming soon


Functional Block Diagram

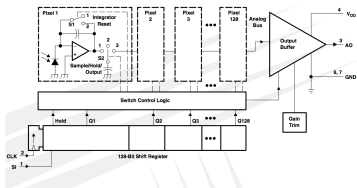

NC - No internal connection
Package Drawing is Not to Scale

TSL1401CL


BLOCK DIAGRAM AND FUNCTIONS

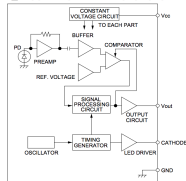


Optical Encoder

Motor Drive

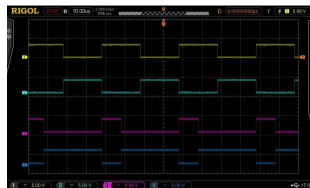- ▶ G_en
 - ▶ Needs 5V!!!!
 - ▶ Pull down resistor (6.8k good)
- ▶ Shoot through protection
 - ▶ Logic protection circuit
 - ▶ Inverted PWM via code
- ▶ General
 - ▶ Heatsinks
 - ▶ Layout



Complimentary PWM

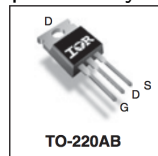


Mosfet Package

Switching Power Supply

DC-DC Converter

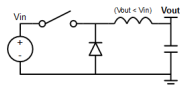
- ▶ 3 Cell LiPo Battery provides 11-12V
 - ▶ Good for motor, driver chip/ op amp
- ▶ We also need 5V?
 - ▶ Servo, optical encoder, camera, etc.
- ▶ How to consistently get 5V?
 - ▶ DC-DC converter!
 - ▶ **Step Down**
 - ▶ Buck Converter, Linear Regulator
 - ▶ Step Up
 - ▶ Boost Converter



Buck Converter

Buck Converter Circuit

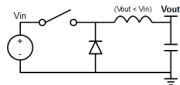
- ▶ DC-to-DC switching power supply generating output voltage lower than input
- ▶ Uses inductor as storage element
- ▶ Efficient, no losses in ideal case
 - ▶ Non-idealities: wire resistance, diode and transistor losses
- ▶ Capacitive filter to smooth output voltage



Buck Converter


Buck Converter Operation

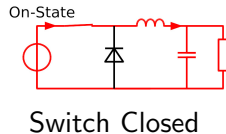- ▶ Inductor charges when switch is closed
 - ▶ Energy stored in inductor by magnetic field, current through inductor increases
 - ▶ Diode does nothing here



Buck Converter Operation

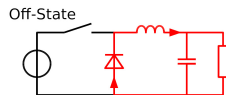
- ▶ Inductor charges when switch is closed
 - ▶ Energy stored in inductor by magnetic field, current through inductor increases
 - ▶ Diode does nothing here
- ▶ Inductor discharges when switch is open
 - ▶ Magnetic field dissipates, current through inductor decreases
 - ▶ Inductor voltage polarity reversed, generating voltage over input
 - ▶ Current flows through diode, output capacitor charged




Switch Open

Buck Converter Control

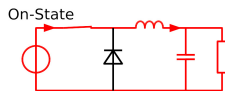- ▶ If switch cycled fast enough, inductor does not fully discharge
- ▶ Output voltage is function of duty cycle D and efficiency η (link)
 - ▶ $V_{out} = \eta D V_{in}$




Inductor charging

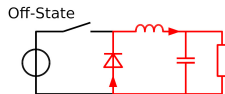

Inductor discharging

Check your Understanding

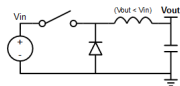
- ▶ I've got a buck converter set up...
- ▶ A magic chip (LM2678) regulates the output to 5v
 - ▶ Duty cycle is adjusted to maintain voltage
 - ▶ Remember: $V_{out} = \eta DV_{in}$
- ▶ What happens if I...



Buck Circuit

Check your Understanding

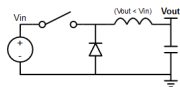
- ▶ I've got a buck converter set up...
- ▶ A magic chip (LM2678) regulates the output to 5v
 - ▶ Duty cycle is adjusted to maintain voltage
 - ▶ Remember: $V_{out} = \eta DV_{in}$
- ▶ What happens if I...
 - ▶ Increase the input voltage?



Buck Circuit

Check your Understanding

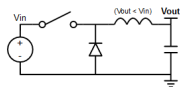
- ▶ I've got a buck converter set up...
- ▶ A magic chip (LM2678) regulates the output to 5v
 - ▶ Duty cycle is adjusted to maintain voltage
 - ▶ Remember: $V_{out} = \eta DV_{in}$
- ▶ What happens if I...
 - ▶ Increase the input voltage?
 - ▶ Duty cycle decreases, current decreases



Buck Circuit

Check your Understanding

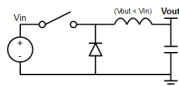
- ▶ I've got a buck converter set up...
- ▶ A magic chip (LM2678) regulates the output to 5v
 - ▶ Duty cycle is adjusted to maintain voltage
 - ▶ Remember: $V_{out} = \eta DV_{in}$
- ▶ What happens if I...
 - ▶ Increase the input voltage?
 - ▶ Duty cycle decreases, current decreases
 - ▶ Decrease the input voltage?



Buck Circuit

Check your Understanding

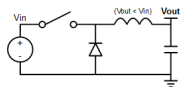
- ▶ I've got a buck converter set up...
- ▶ A magic chip (LM2678) regulates the output to 5v
 - ▶ Duty cycle is adjusted to maintain voltage
 - ▶ Remember: $V_{out} = \eta DV_{in}$
- ▶ What happens if I...
 - ▶ Increase the input voltage?
 - ▶ Duty cycle decreases, current decreases
 - ▶ Decrease the input voltage?
 - ▶ Duty cycle increases, current increases



Buck Circuit

Boost Converter Circuit (for your reference)

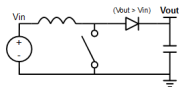- ▶ DC-to-DC switching power supply generating output voltage *lower* than input
- ▶ Similar principle to buck converter
 - ▶ $V_{out} = \frac{1}{1-D} V_{in}$
- ▶ Also exists buck-boost converters, where output can be greater than, equal to, or less than the input



Boost Converter

Questions?



got it?

power supply pros, right?

Practical Application

Automatic Feedback Control

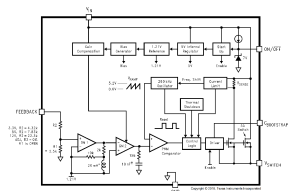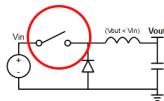- ▶ So, what is the switch-controlling magic?
- ▶ Feedback control: chip has logic to regulate the voltage on the feedback pin to an internal $V_{FB} = 1.21V$ reference
- ▶ $V_{out} = V_{FB}(1 + \frac{R_2}{R_1})$
- ▶ $R_1 \approx 1k\Omega$ recommended



LM2678 Block Diagram

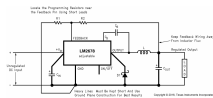



Figure 27. Basic Circuit for Adjustable Output Voltage Applications

Application circuit

Problematic?

- ▶ What happens if the switch get stuck in the closed position?

On-State

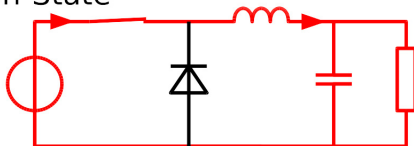

Boost Circuit

Layout is Important!!!

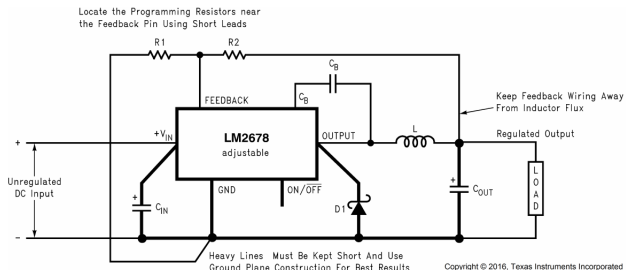


Figure 22. Basic Circuit for Adjustable Output Voltage Applications

Circuit

Layout Guidelines

- ▶ Switching power supplies are layout sensitive
 - ▶ Part placement and routing matters!
- ▶ Tips from the datasheet:
 - ▶ Keep diode and filter capacitor connections as short as possible
 - ▶ Minimize high frequency current path (switch, diode, capacitor)
- ▶ Read the datasheet!

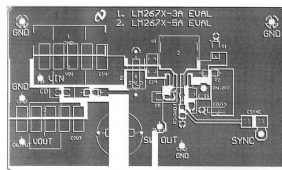


Figure 24. Top Layer Foil Pattern of Printed-Circuit Board

Recommended layout
(uses surface-mount components)
source: datasheet, Linear Technology

Supporting Componentets

- ▶ Capacitors
 - ▶ Ceramic, film, polarized (tantalum, aluminum, etc.)...
- ▶ Diodes
 - ▶ Shottky
- ▶ Inductor
 - ▶ Toroid



Toroid Inductor

Summary

Summary

- ▶ Buck converters step down a DC voltage to a lower DC voltage
- ▶ LM2678 uses feedback control to do voltage regulation
- ▶ Follow recommended layout guidelines during PCB design
- ▶ Very difficult to make work on perfboard- just design it on the pcb.

Parts Handout Office hours for the rest of the section