

EE 240B – Spring 2018

Advanced Analog Integrated Circuits Lecture 3: Gain-Bandwidth Limited Amplifier Design Methodology




Elad Alon
Dept. of EECS

Preliminaries

- **This will be the first in a series of design methodologies we will develop**
 - To keep the discussion manageable, will generally assume that only a couple of specifications are critical
 - And that all other specs will “automatically” be met
 - In practice, can inspect specs and technology capabilities to figure out which constraints are really active, and utilize the appropriate methodology
- **Will largely ignore biasing details for now**
 - But will patch this later

CS Amplifier Design Methodology

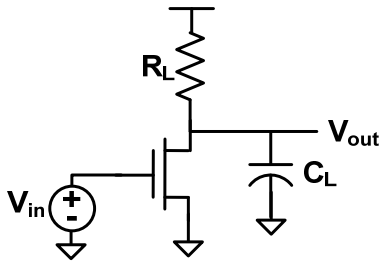


- **Input specifications:**
 - Minimum small signal gain A_v
 - Minimum 3dB bandwidth ω_{bw}
 - Fixed capacitive load C_L
 - Supply voltage V_{dd}
- **Goal: minimize power**
- **What are our design variables?**

EE 240B

Lecture 3

3

Small Signal Model and Analysis

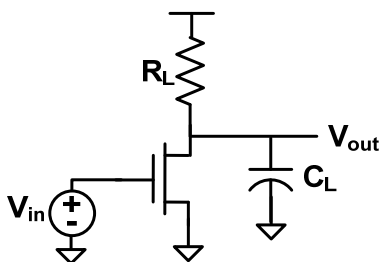

EE 240B

Lecture 3

4

Power and g_m

EE 240B

Lecture 3

5

First Pass Methodology

EE 240B

Lecture 3

6

Side Discussion: Digital vs. Analog Power

$$P_{digital} = \alpha_{0 \rightarrow 1} C_L V_{DD}^2 f_{clk} \quad P_{analog} = \frac{1}{2} C_L V_{DD} V^* A_v \omega_{bw}$$

- What needs to be true for analog to be lower power than digital?

g_m vs. GBW revisited (1)

g_m vs. GBW revisited (2)

EE 240B

Lecture 3

9

g_m vs. GBW revisited (3)

EE 240B

Lecture 3


10

Direct Implication

$$I_D = \frac{1}{2} \left(\frac{A_V \omega_{bw} V^* C_L}{1 - A_V \omega_{bw} / (\omega_T / \gamma)} \right)$$

- **For a given V^* , there is a maximum GBW you can achieve**

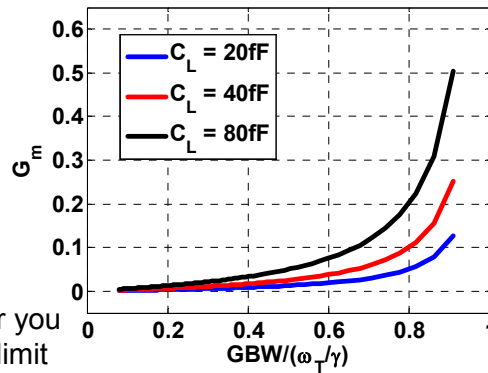- No matter how much power you spend, cannot exceed this limit (with this topology)



Methodology Take 2

Methodology Take 2`

EE 240B

Lecture 3

13

What about r_o ?

EE 240B

Lecture 3

14

Bias Point

EE 240B

Lecture 3

15

Extension #1: Differential Amplifier

EE 240B

Lecture 3

16

Extension #2: Multi-Stage Amplifier

EE 240B

Lecture 3

17

Extension #3: “Inverter” Amplifier

EE 240B

Lecture 3

18