

EE 240B – Spring 2018

Advanced Analog Integrated Circuits Lecture 5: Noise and SNR Analysis



Elad Alon
Dept. of EECS

General Noise Analysis

- **Method:**
 - 1) Create small-signal model
 - 2) All inputs = 0 (linear superposition)
 - 3) Pick output v_o or i_o
 - 4) For each noise source v_x, i_x
Calculate $H_x(s) = v_o(s) / v_x(s)$ (... i_o, i_x)
 - 5) Total noise at output is:

$$\overline{v_{on,T}^2(f)} = \sum_x |H_x(s)|_{s=2\pi jf}^2 \overline{v_x^2(f)}$$

$$\overline{v_{on,T}^2} = \int_0^\infty \overline{v_{on,T}^2(f)} df$$

Tedious but simple ...

Important Integrals

$$\int_0^{\infty} \left| \frac{1}{1 + \frac{s}{\omega_o}} \right|^2 df = \frac{\omega_o}{4}$$

$$\int_0^{\infty} \left| \frac{1}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \right|^2 df = \int_0^{\infty} \left| \frac{\frac{s}{\omega_o}}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \right|^2 df = \frac{\omega_o Q}{4}$$


$$\int_0^{\infty} \left| \frac{\frac{s}{\omega_z} + 1}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \right|^2 df = \frac{\omega_o Q}{4} \left(\frac{\omega_o^2}{\omega_z^2} + 1 \right)$$

EE 240B

Lecture 5

3

Noise in a Real Circuit: RC

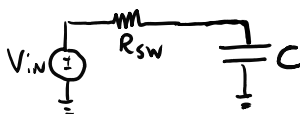

- **Noise on the capacitor:**

$$\overline{v_{on}^2(f)} = 4k_B T R \left| \frac{1}{1 + sRC} \right|^2$$

$$\rightarrow \overline{v_{oT}^2} = 4k_B T R \frac{1}{4RC} = \frac{k_B T}{C}$$

- **Note that effective bandwidth is:**



$$\Delta f = \frac{1}{4RC} = \frac{\omega_o}{4} = \frac{\pi}{2} f_o$$

EE 240B

Lecture 5

4

Noise PSD

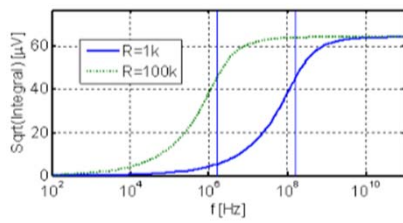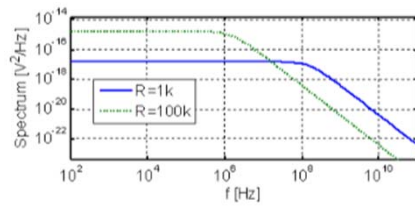

EE 240B

Lecture 5

5


Equipartition Theorem

EE 240B

Lecture 5

6

CS Amplifier Noise

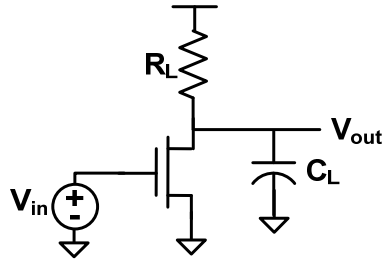

$$\begin{aligned} \overline{v_{on}^2(f)} &= 4k_B T \left(\frac{1}{R_L} + \gamma g_m \right) \left| \frac{R_L}{1 + sR_L C_L} \right|^2 \\ \overline{v_{oT}^2} &= 4k_B T \left(\frac{1}{R_L} + \gamma g_m \right) R_L^2 \int_0^\infty \left| \frac{1}{1 + sR_L C_L} \right|^2 df \\ &= 4k_B T \left(\frac{1}{R_L} + \gamma g_m \right) R_L^2 \frac{1}{4R_L C_L} \\ &= \frac{k_B T}{C_L} (1 + \gamma g_m R_L) \\ &= \frac{k_B T}{C_L} (1 + \gamma |A_{vo}|) \\ &= \frac{k_B T}{C_L} n_F \end{aligned}$$

EE 240B

Lecture 5

7

Optional: Two-Stage Amplifier

EE 240B

Lecture 5

8

Signal-To-Noise Ratio

- **SNR:**
$$SNR = \frac{P_{sig}}{P_{noise}}$$

- **Signal Power (sinusoidal source):**

$$P_{sig} = \frac{1}{2} V_{zero-peak}^2$$

- **Noise Power (assuming thermal noise dominates):**

$$P_{noise} = \frac{k_B T}{C} n_f$$

- **So:**

$$SNR = \frac{\frac{1}{2} C V_{zero-peak}^2}{n_f k_B T}$$

SNR $\uparrow +6dB$
 \downarrow
 C $\uparrow \times 4$

SNR versus Bits

- **Quantization “noise”**

- Quantizer step size: Δ

- Box-car pdf variance: $S_Q = \frac{\Delta^2}{12}$

N	dB
8	50
16	98
24	146

- **SNR of N-Bit sinusoidal signal**

- Signal power
$$P_{sig} = \frac{1}{2} \left(\frac{1}{2} 2^{N_{bits}} \Delta \right)^2$$

- SNR
$$SNR = \frac{P_{sig}}{S_Q} = 1.5 \times 2^{2N_{bits}}$$

- 6.02 dB per Bit
$$= [1.76 + 6.02 N_{bits}] \text{ dB}$$

SNR versus C_L

- For a 1V sinusoidal signal at 100°C:

Bits	SNR [dB]	C
3.0	20	4.1 aF
6.3	40	412 aF
9.7	60	41 fF
13.0	80	4.1 pF
16.3	100	412 pF
19.6	120	41 nF
23.0	140	4.1 μ F

SNR versus Power


- 1 Bit \rightarrow 6dB \rightarrow 4x SNR
- 4x SNR \rightarrow 4x C
- Circuit bandwidth $\sim g_m/C \rightarrow$ 4x g_m
- Keeping V^* constant \rightarrow 4x I_D , 4x W

- Thermal noise limited circuit:
 - Each bit QUADRUPLES power!

- Comparison vs. digital circuits...

Input and Output Referred Noise


Output

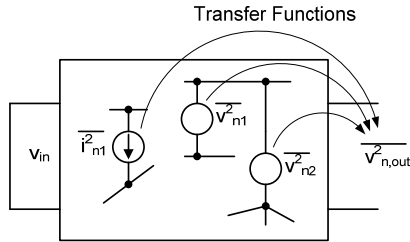

$$v_{out} = H_i \cdot S_{n,i}$$

$$\overline{v_{n,out}^2} = \sum_i |H_i|^2 \overline{S_{n,i}^2}$$

Input

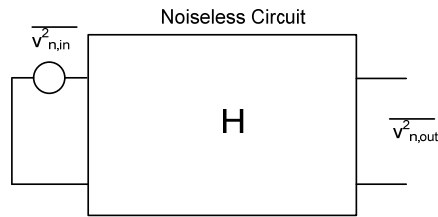

$$v_{out} = H \cdot v_{in}$$


$$v_{n,in}^2(\omega) = \frac{\overline{v_{n,out}^2}(\omega)}{|H|^2}$$

EE 240B

Lecture 5

13

Noise Example

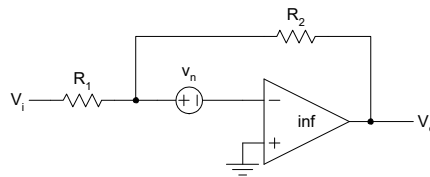

- Ignoring noise from R_1 , R_2 :

$$v_o = -v_i \underbrace{\frac{R_2}{R_1}}_{-A_{v0}} + v_n \left(1 + \frac{R_2}{R_1} \right) = -v_i \frac{R_2}{R_1} + v_n \frac{R_1 + R_2}{R_1}$$

$$\overline{v_{ieq}^2} = \overline{v_n^2} \left(\frac{R_1 + R_2}{R_1} \frac{R_1}{R_2} \right)^2 = \overline{v_n^2} \left(\frac{R_1 + R_2}{R_2} \right)^2 = \overline{v_n^2} \left(1 + \frac{1}{|A_{v0}|} \right)^2$$

- “Ideal” feedback, why is $v_{ieq}^2 > v_n^2$?

EE 240B

Lecture 5

14

Source Impedance
