


# EE 240B – Spring 2018

## Advanced Analog Integrated Circuits Lecture 6: Noise- and SNR-Limited Amplifier Design Methodology



Elad Alon  
Dept. of EECS

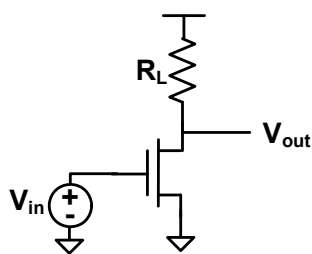
## Noise Density Limited Amplifier Design Methodology



- **Input specifications:**
  - Minimum small signal gain  $A_v$
  - Supply voltage  $V_{dd}$
  - Fixed  $V^*$
  - Maximum input-referred noise spectral density  $v_{i,n}^2/\Delta f$
- **Goal: minimize power**

## Small Signal Model and Noise Analysis

---

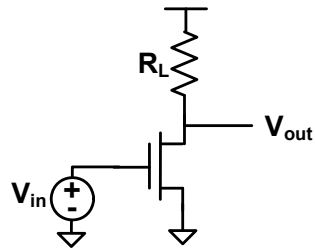

EE 240B

Lecture 6

3

## Resulting Design

---

EE 240B

Lecture 6

4

## Discussion (1)

---


- Why did we not even specify the capacitive load?

## Discussion (2)

---

- If you could exactly set  $a_{v0}$ , what value would you pick?

## Integrated Noise-Limited Amplifier

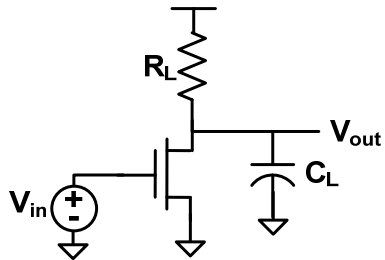

- **Input specifications:**
  - Minimum small signal gain  $A_v$
  - Minimum 3dB bandwidth  $\omega_{bw}$
  - Supply voltage  $V_{dd}$
  - Fixed  $V^*$
  - Maximum noise variance  $v_{o,n}^2$
- **Goal: minimize power**

EE 240B

Lecture 6

7

## Required $C_L$ , $g_m$ , and $I_D$

EE 240B

Lecture 6

8

## Discussion (1)

---

- For both noise-density and integrated noise-limited amplifiers, what  $V^*$  should you pick?


## Discussion (2)

---

- How would one know the  $v_{i,n}^2/\Delta f$  or  $v_{o,n}^2$  spec?

## Signal Swing Limitations

---

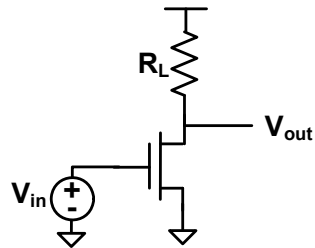

EE 240B

Lecture 6

11

## Why Linearity Matters

---

- **Option 1: Retaining the original shape of the input inherently matters**
  - E.g., oscilloscope, spectrum analyzer
  - (Actually also often matters in communication systems)
- **Option 2: Need to be able to discern a (small) signal out of the combination of many others**
  - E.g., RF, neural front-ends
  - “Other” signals could
- **Precise linearity metric depends on usage scenario**
  - More next time – will use simplified metric for now

EE 240B

Lecture 6

12

## Sources of Non-Linearity

---

- Output limited:  
Non-linear  $Z_{out}$  ( $r_o$ )
- Input limited:  
Non-linear  $g_m$


EE 240B

Lecture 6

13

## Input Non-Linearity with a Diff. Pair

---

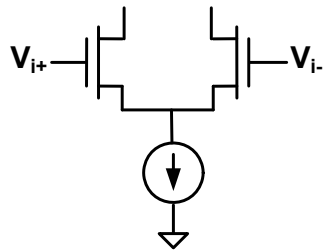


EE 240B

Lecture 6

14

## Full Circle: SNR-Limited Design (noise density)

---

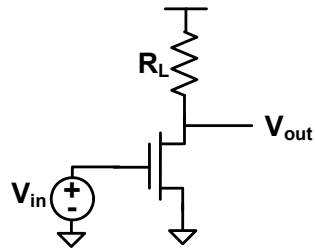

- **Input specifications:**
  - Minimum small signal gain  $A_v$
  - Supply voltage  $V_{dd}$
  - Input-referred maximum linear amplitude  $V_{i,max}$
  - Signal shape (usually sinusoid) and amplitude  $V_{sig}$
  - Externally determined bandwidth  $f_{bw}$
  - Minimum signal-to-noise ratio  $SNR_{min}$
- **Goal: minimize power**

EE 240B

Lecture 6

15

## Required $v_{i,n}/\Delta f$

---

EE 240B

Lecture 6

16



## Required $V^*$

---


EE 240B

Lecture 6

17

## SNR-Limited Design (total noise)

---

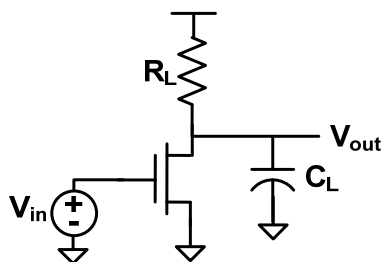

- **Input specifications:**
  - Minimum small signal gain  $A_v$
  - Minimum 3dB bandwidth  $\omega_{bw}$
  - Supply voltage  $V_{dd}$
  - Input-referred maximum linear amplitude  $V_{i,max}$
  - Signal shape (usually sinusoid) and amplitude  $V_{sig}$
  - Minimum signal-to-noise ratio  $SNR_{min}$
- **Goal: minimize power**

EE 240B

Lecture 6

18

# Discussion

---