

EE 240B – Spring 2018



Advanced Analog Integrated Circuits Lecture 7: Operational Transconductance Amplifiers (I)



Elad Alon
Dept. of EECS



OpAmps and OTAs

OpAmp

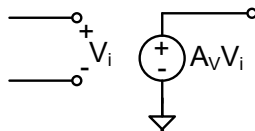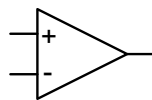


- High voltage gain, high input impedance
- Voltage source output (low impedance)

OTA

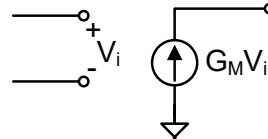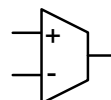

- High “voltage” gain, high input impedance
- Current source output (high impedance)

Opamp & OTA in CMOS

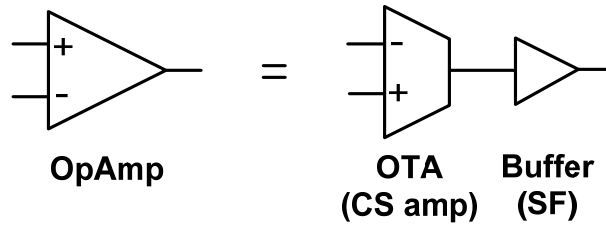


EE 240B

Lecture 7

3

Opamp vs. OTA Noise

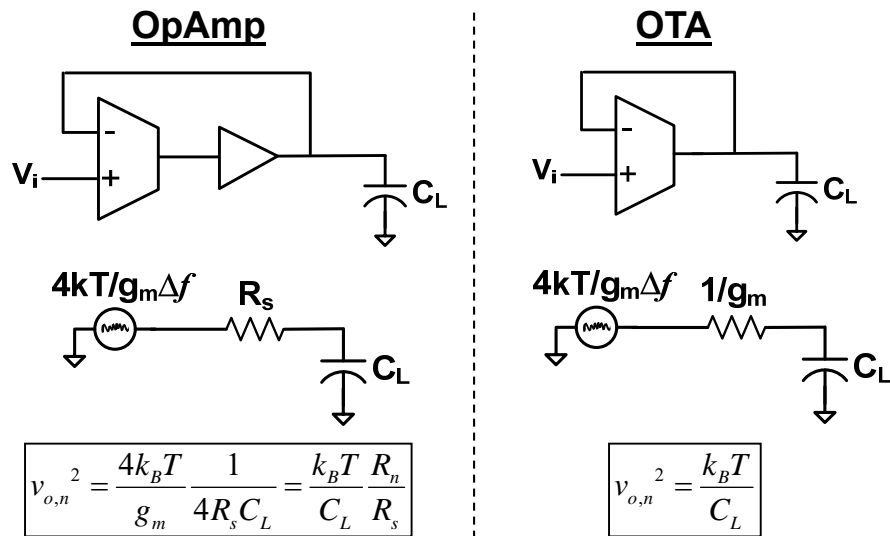

EE 240B

Lecture 7

4


Simplest Single-Ended OTA

EE 240B

Lecture 7

5

Differential Input?

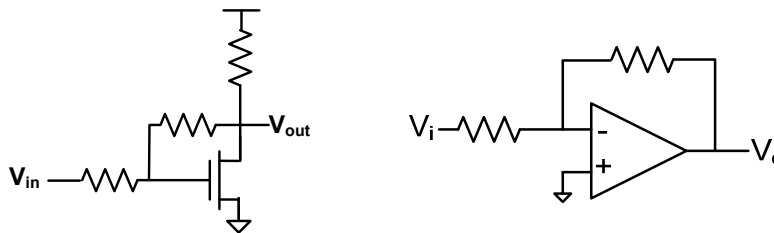


- **Why use a differential input?**
 - Diff. version has extra device(s) – more power, noise, etc.
- **Real reason is systematic offset**
 - All voltages are relative
- **If used a differential input, often might as well use differential output too...**

EE 240B

Lecture 7

6

Simple Diff. Input OTA

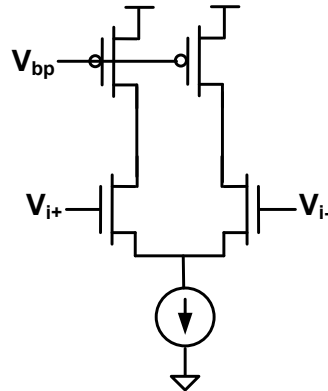


EE 240B

Lecture 7

7

Simple Diff. Input OTA: Noise (1)

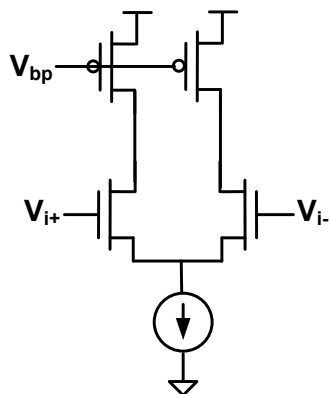


EE 240B

Lecture 7

8

Simple Diff. Input OTA: Noise (2)

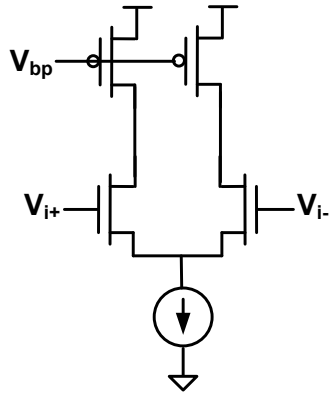

EE 240B

Lecture 7

9

Simple Diff. Input OTA: Noise (2)

EE 240B

Lecture 7

10

More Careful Look at Noise...

EE 240B

Lecture 7

11

More Careful Look at Noise...

EE 240B

Lecture 7

12

Real R vs. Current Source (1)

EE 240B

Lecture 7

13


Real R vs. Current Source (2)

EE 240B

Lecture 7

14

Limitations of Simple OTA

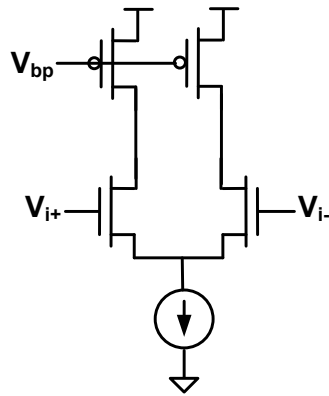


EE 240B

Lecture 7

15

Telescopic Cascoded OTA

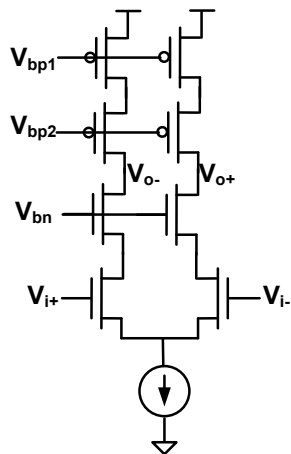

EE 240B

Lecture 7

16


Why Cascoding Helps

EE 240B

Lecture 7

17

Cascode Sizing for r_o

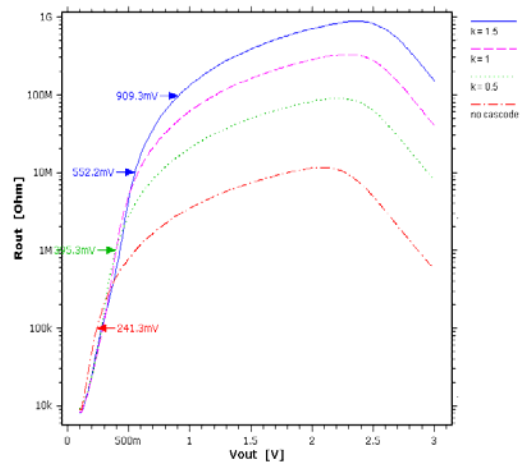

EE 240B

Lecture 7

18

Cascode Noise?

EE 240B

Lecture 7

19

Cascode Noise?

EE 240B

Lecture 7

20

More Complete Analysis

EE 240B

Lecture 7

21

More Complete Analysis

EE 240B

Lecture 7

22

Cascode Sizing
