

EE 240B – Spring 2018

Advanced Analog Integrated Circuits Lecture 8: Operational Transconductance Amplifiers (II)



**Elad Alon
Dept. of EECS**

Closer Look at Cascode Dynamics

Aside: Useful TF Properties

EE 240B

Lecture 8

3

Cascode Z_{out} vs. f

EE 240B

Lecture 8

4

Pole-Zero Doublets

EE 240B

Lecture 8

5

Discussion

- **Doublet generally not important in “simple” cascode since it shows up at high frequencies**
- **But, doublets can show up in similar circuits**
 - In particular, when you try and increase the gain beyond what a simple cascode can support

EE 240B

Lecture 8

6

Gain Boosting

- **Use feedback to further increase R_{out}**
 - No increase of V_{min} (unlike double cascode)
- **References:**
 - B. J. Hosticka, "Improvement of the gain of MOS amplifiers," JSSC, Dec. 1979 , pp. 1111-4.
 - E. Sackinger and W. Guggenbuhl, "A high-swing high-impedance MOS cascode circuit", JSSC, Feb. 1990, pp. 289-298.
 - K. Bult, G. Geelen, "A fast-settling CMOS op-amp for SC circuits with 90-dB DC gain," JSSC, Dec. 1990 , pp. 1379-84.

EE 240B

Lecture 8

7

Stability?

EE 240B

Lecture 8


8

Gain-Boosted Z_{out}

If it works, do it again!


2144

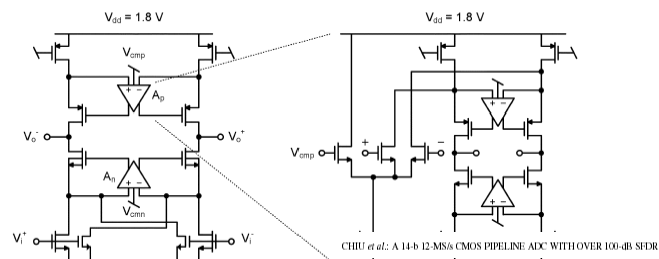IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 39, NO. 12, DECEMBER 2004



- Since in advanced scaled CMOS $g_m r_o$ is small, we can use nested gain boosting for higher output impedance.
- Watch out for pole-zero doublets!

Telescopic OTA: Common Mode vs. Swing

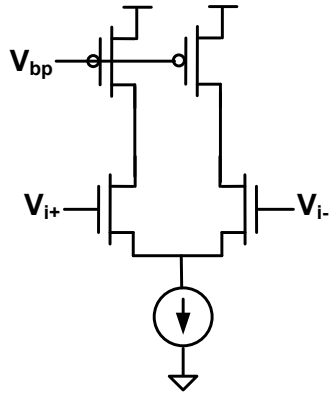


EE 240B

Lecture 8

11

Folded-Cascode Schematic

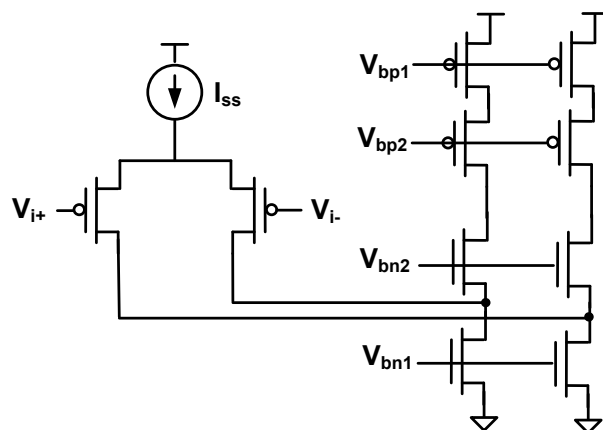


EE 240B

Lecture 8

12

Folded-Cascode Noise

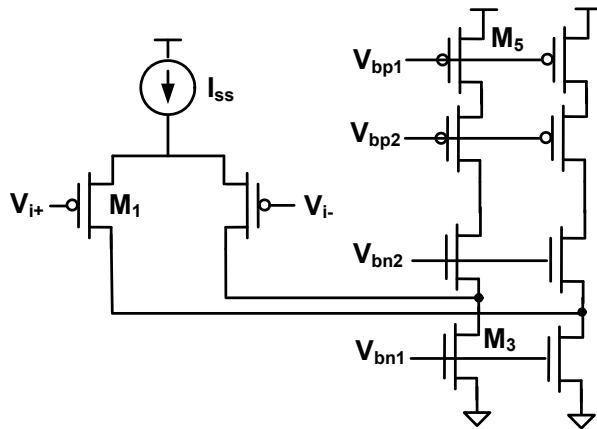


EE 240B

Lecture 8

13

Low Frequency Gain: a_v and A_v

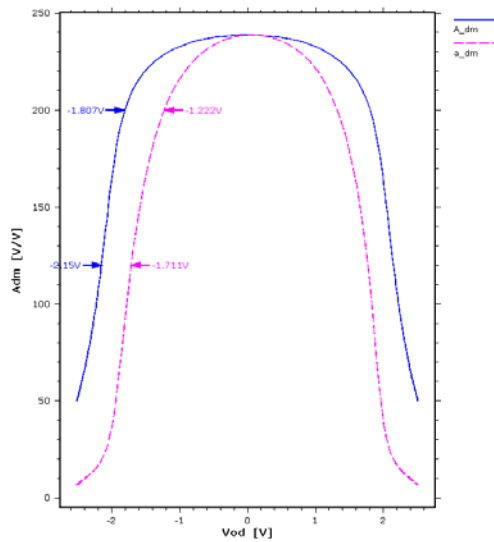


EE 240B

Lecture 8


14

Output Resistance

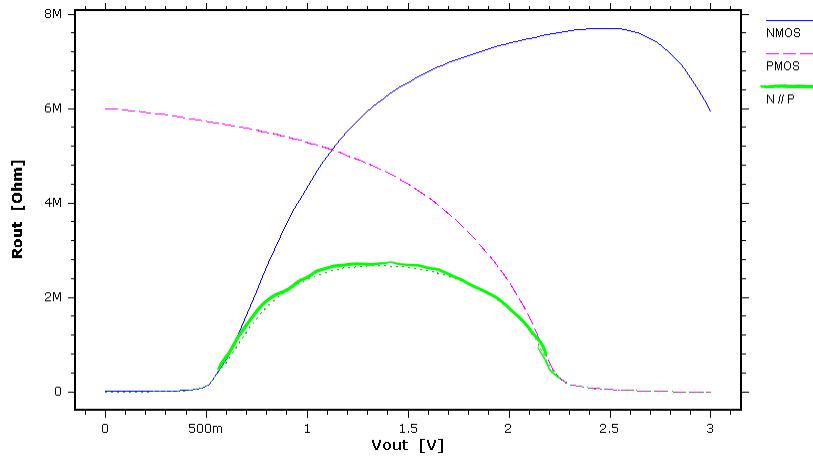


Beware of r_o imbalance between NMOS and PMOS current sources

Simulation Schematic

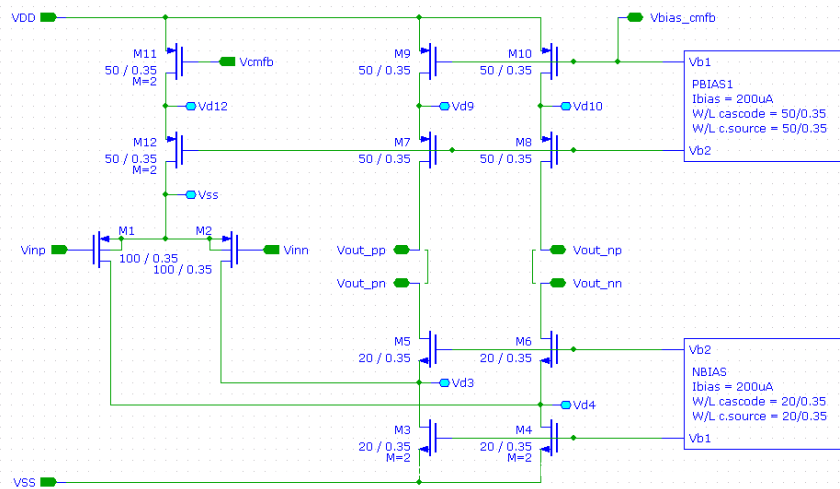

Input Cascode

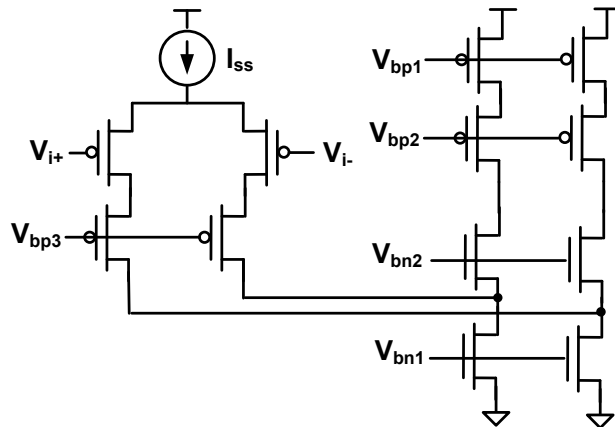

EE 240B

Lecture 8

17

Reminder: Cascode Z_{in}

EE 240B

Lecture 8

18

Biasing and Parasitic Feedback

