

# **EE 240B – Spring 2018**

---

## **Advanced Analog Integrated Circuits**


### **Lecture 14: Photonic Link Overview**



**Elad Alon**  
**Dept. of EECS**


# Why Photonic Links?

---

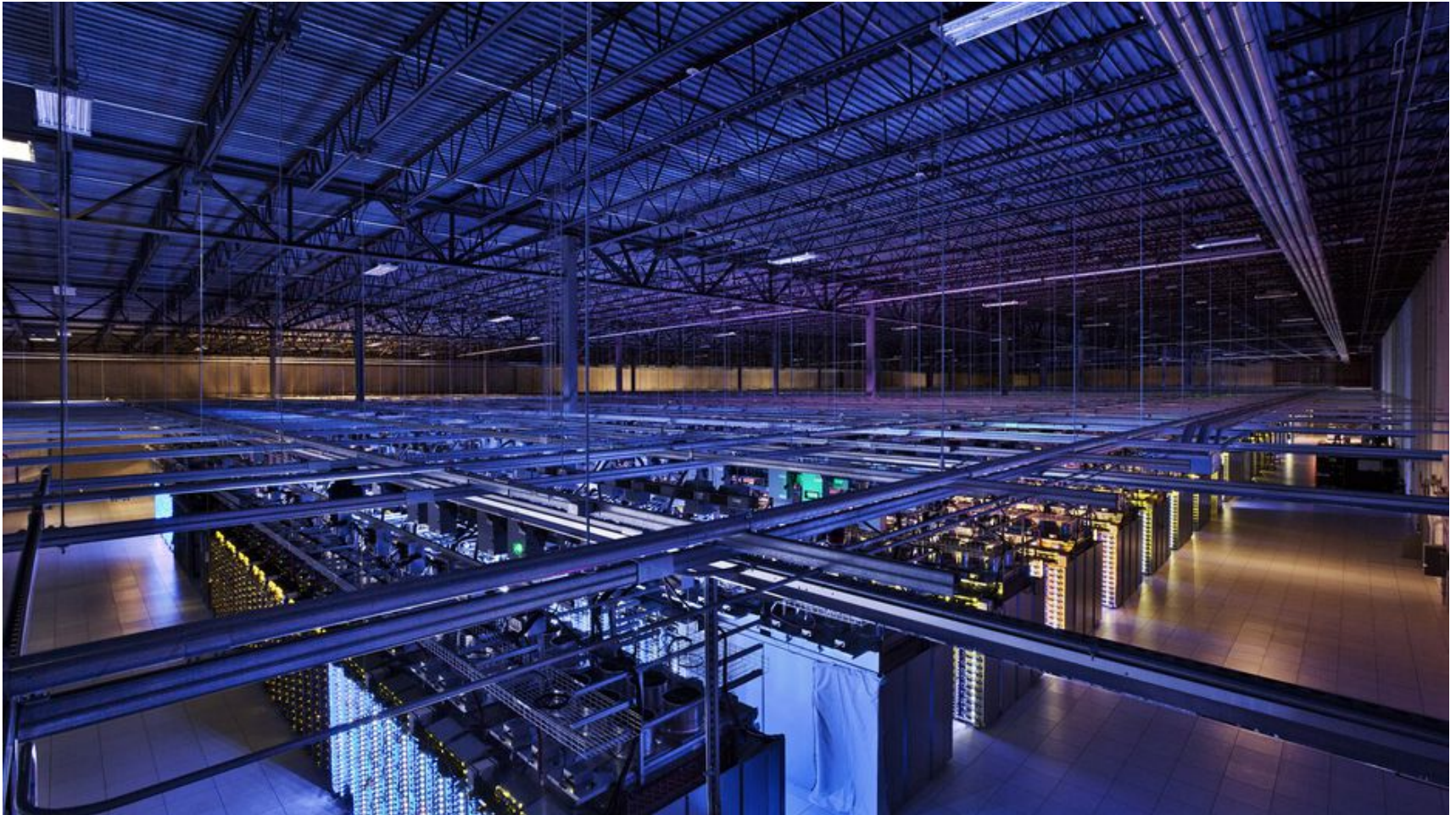

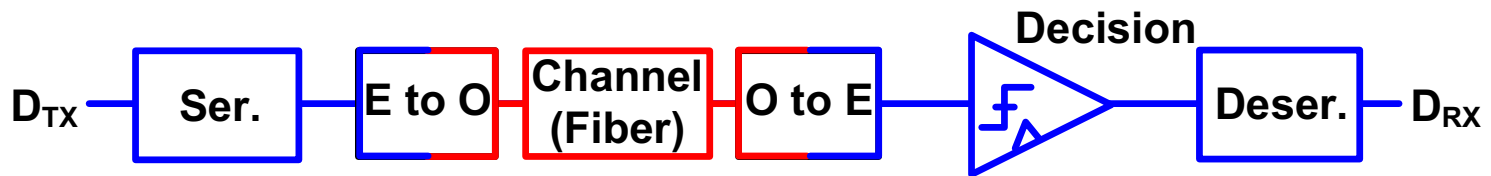
# Basic Link Issues

- Signaling: getting bits from the TX to the RX



- Timing: determining which bit is which

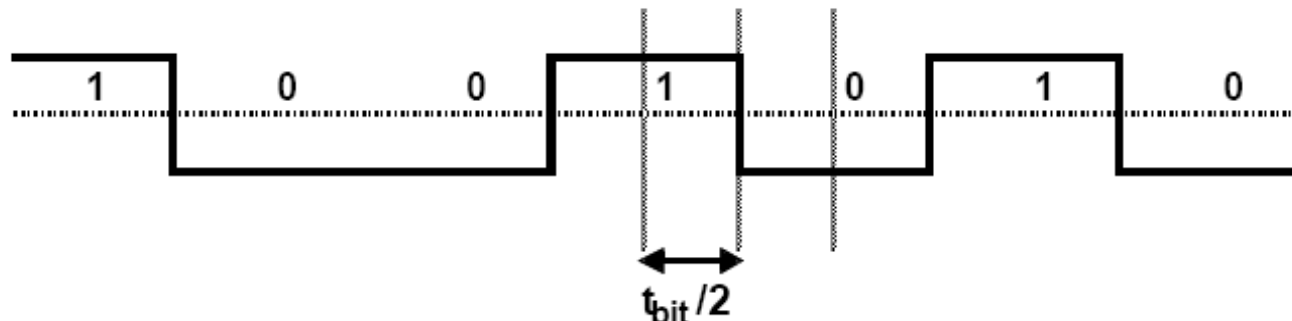

# TX: E to O (1)

---

# TX: E to O (2)

---

# RX: O to E

---

# RX: O to E Model

---

# Photonic RX: Attempt #1




---



# Photonic RX: Attempt #2



---

# Noise $\rightarrow$ BER

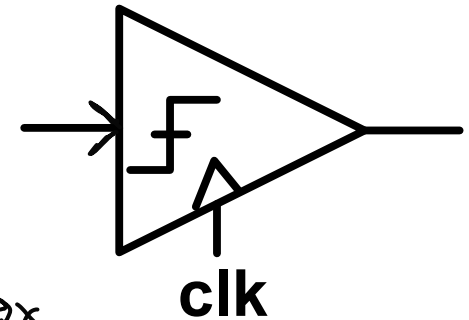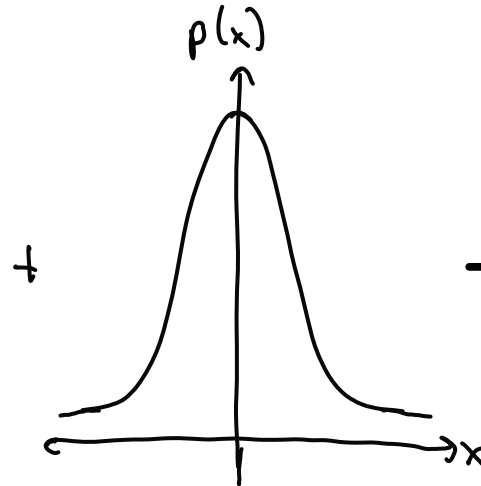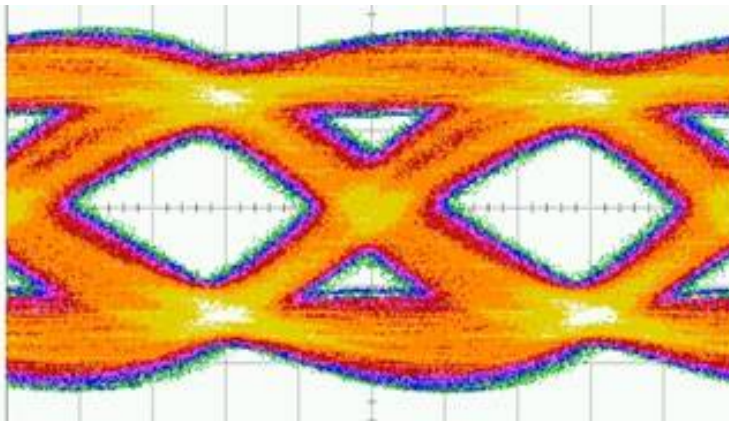

- **RX circuits always have noise**
  - If noise is ever larger than the input signal (at sampling point), RX will decode the bit incorrectly
- **BER = Bit Error Rate**
  - I.e., average # of incorrectly received bits / total transmitted bits

# Min. Signal Amplitude

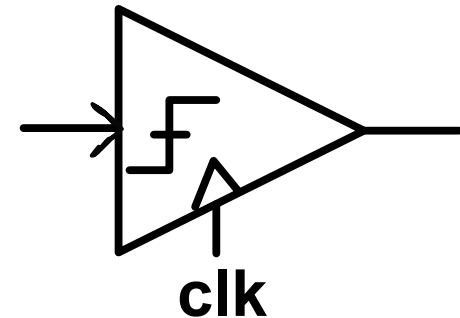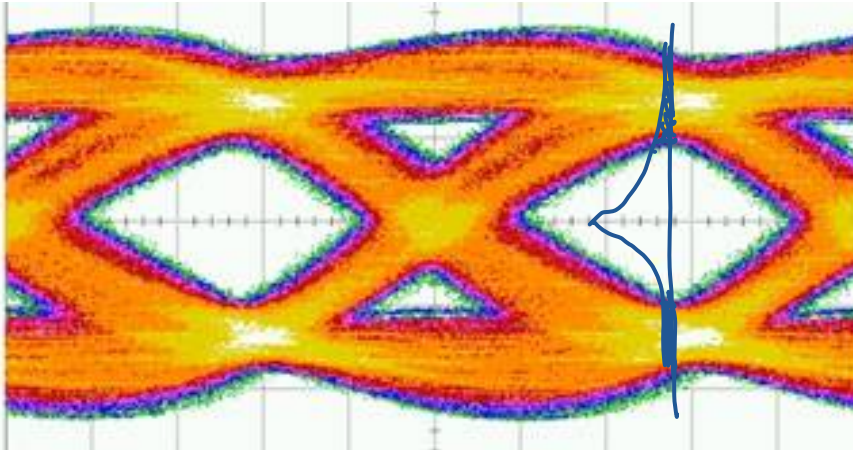

- **Min. signal set by noise  $\sigma$  and residual offset:**

$$BER = \frac{1}{2} \operatorname{erfc} \left( \frac{V_{in,ampl} - V_{off}}{\sqrt{2}\sigma_{noise}} \right)$$

- **$BER = 10^{-12}$ :  $(V_{in,ampl} - V_{off}) = 7\sigma_n$**
- **$BER = 10^{-20}$ :  $(V_{in,ampl} - V_{off}) = 9.25\sigma_n$**

# So What?

---

- **Why not just hit the RX with a larger signal?**
  - (Not a stupid question – this is often what people do)
- **Simple (hand wavy) answers:**
  - Generating optical power can be (very) expensive
    - Wall-plug efficiency usually ~1-10%
  - Larger swing doesn't help with ISI...

# Intersymbol Interference (ISI)

---

# ISI continued

---

# Receiver Design Revisited

---

# TIA-Based Front-End

---



# TIA-Based Receiver

---

# Front-end Bandwidth


---

# Performance Limits

---


# Overcoming PD Bandwidth Limit: Multi-Level Signaling

## 2PAM:

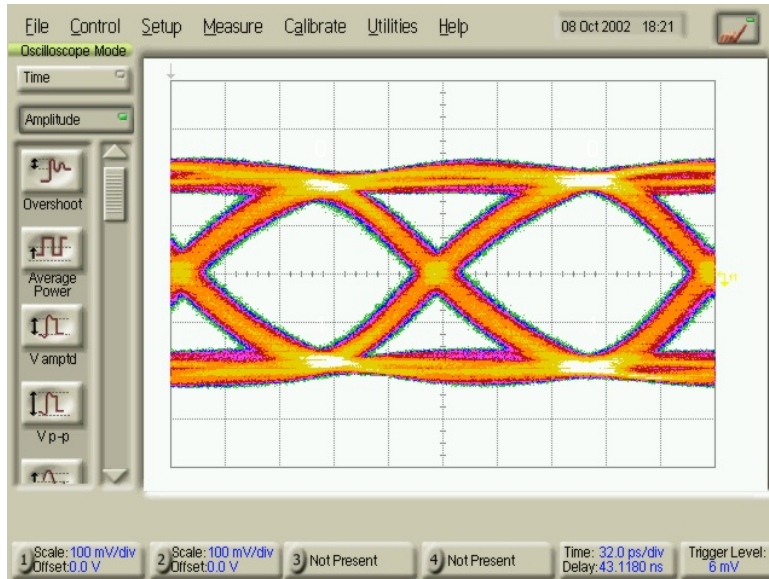

**1 bit/symbol**

## 4PAM:

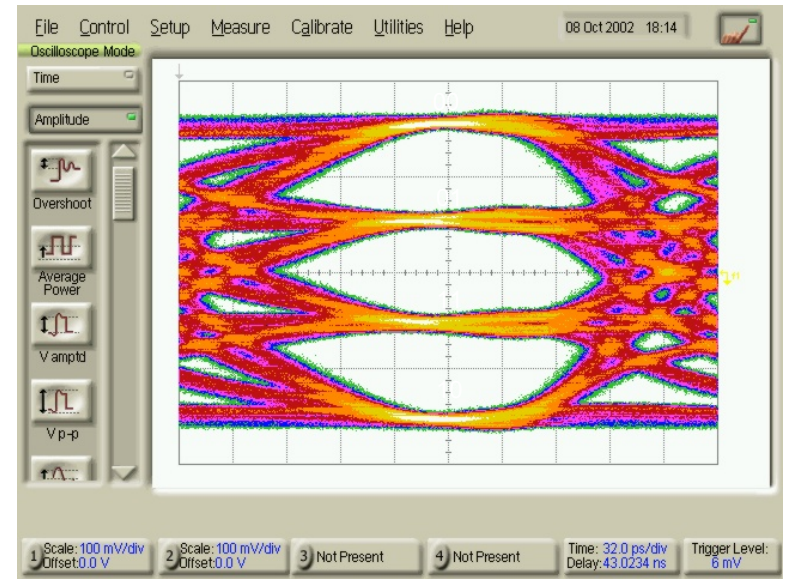

**2 bits/symbol**

# 4PAM RX

---