


# EE 240B – Spring 2018

## Advanced Analog Integrated Circuits Lecture 16: Comparators I



Elad Alon  
Dept. of EECS

## Comparator

 

- **Specs and issues:**

- Clock rate  $f_s$
- Offset
- Resolution
- Hysteresis
- Input cap
- Power dissipation
- CM rejection
- Kickback noise
- ...


## Comparator Gain-Bandwidth

### Example:

- 10Gb/s link
- Minimum  $\Delta V$ : 1mV
- Vdd = 1V

→  $A_v > 1V / 1mV = 1000$  in  $< 100ps!$


## Operational Amplifier?

 

$$f_{-3dB} = \frac{f_u}{A_{vo}} = \frac{2}{3} \frac{1}{T_{bit}}$$

$$\begin{aligned} f_u &= \frac{2A_{vo}}{3T_{bit}} \\ &= \frac{2}{3} \frac{1000}{100ps} = \underline{6.67THz} \end{aligned}$$

## Open-Loop Amplifier Cascade

 

EE 240B

Lecture 16

5

## Cascaded Amplifier

- **Simplified bandwidth analysis:**
  - Open-circuit time constants
  - (Not most accurate, but leads to nearly the right answer for design optimization)

EE 240B

Lecture 16

6

## **Bandwidth/Gain Optimization**

EE 240B

Lecture 16

7

## **Bandwidth/Gain Optimization**

EE 240B

Lecture 16

8

## **Power Consumption**

---

EE 240B

Lecture 16

9

## **Regenerative Latch**

---

EE 240B

Lecture 16

10

## **CML Comparator (Latch)**

EE 240B

Lecture 16

11

## **CML Comparator Analysis (1)**

EE 240B

Lecture 16

12

## **CML Comparator Analysis (2)**

EE 240B

Lecture 16

13

## **CML Comparator Design**

EE 240B

Lecture 16

14