

# EE 240B – Spring 2018

---

## Advanced Analog Integrated Circuits Lecture 17: Comparators II



Elad Alon  
Dept. of EECS

## CML Comparator Power Revisited

---

- **Gain spec driven by smallest signal you need to resolve**
  - But real inputs will often be larger than this
- **For larger inputs, diff. output will clip at  $\pm I_{\text{bias}} R_L$** 
  - I.e., dissipating  $I_{\text{bias}}$  just to produce a constant voltage
  - Can we modify the comparator to spend power only when it is actually providing (regenerative) gain?

## **CMOS Comparator**

EE 240B

Lecture 17

3

## **StrongArm Comparator (Latch)**

EE 240B

Lecture 17

4

## **StrongArm Analysis (1)**

EE 240B

Lecture 17

5

## **StrongArm Analysis (2)**

EE 240B

Lecture 17

6

## **StrongArm Analysis (3)**

EE 240B

Lecture 17

7

## **Hysteresis**

EE 240B

Lecture 17

8

# **Kickback**

---

EE 240B

Lecture 17

9

# **Kickback cont'd**

---

EE 240B

Lecture 17

10

## **Kickback cont'd**

---

EE 240B

Lecture 17

11

## **Overdrive Recovery**

---

EE 240B

Lecture 17

12