

UC Berkeley


Noise Sources

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 12

UC Berkeley

Thermal Noise

- **Thermal Noise in Electronics:** (Johnson noise, Nyquist noise)
 - ↳ Produced as a result of the thermally excited random motion of free e-'s in a conducting medium
 - ↳ Path of e-'s randomly oriented due to collisions
- **Thermal Noise in Mechanics:** (Brownian motion noise)
 - ↳ Thermal noise is associated with all dissipative processes that couple to the thermal domain
 - ↳ Any damping generates thermal noise, including gas damping, internal losses, etc.
- **Properties:**
 - ↳ Thermal noise is white (i.e., constant w/ frequency)
 - ↳ Proportional to temperature
 - ↳ Not associated with current
 - ↳ Present in any real physical resistor




EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 13

UC Berkeley

Circuit Representation of Thermal Noise

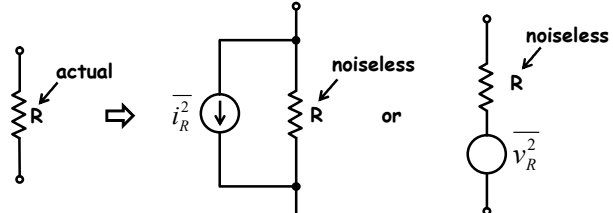- Thermal Noise can be shown to be represented by a series voltage generator $\overline{v_R^2}$ or a shunt current generator $\overline{i_R^2}$



$$\frac{\overline{i_R^2}}{\Delta f} = \frac{4kT}{R}$$

$$\frac{\overline{v_R^2}}{\Delta f} = 4kTR$$

where $4kT = 1.66 \times 10^{-20} V \cdot C$ and where these are spectral densities.


Note: These are one-sided mean-square spectral densities! To make them 2-sided, must divide by 2.

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 14

UC Berkeley


Noise in Capacitors and Inductors?

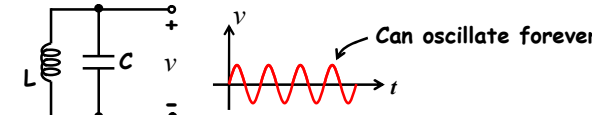- Resistors generate thermal noise
- Capacitors and inductors are noiseless → why?



Can oscillate forever

- Now, add a resistor:

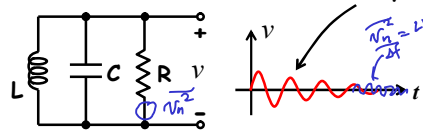

Decays to zero

$\frac{d\overline{v_n^2}}{dt} = 4kTR$

But this violates the laws of thermodynamics, which require that things be in constant motion at finite temperature


Need to add a forcing function, like a noise voltage $\overline{v_R^2}$ to keep the motion going → and this noise source is associated with R

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 15

Back to Determining Sensor Resolution


EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 23

MEMS-Based Tuning Fork Gyroscope

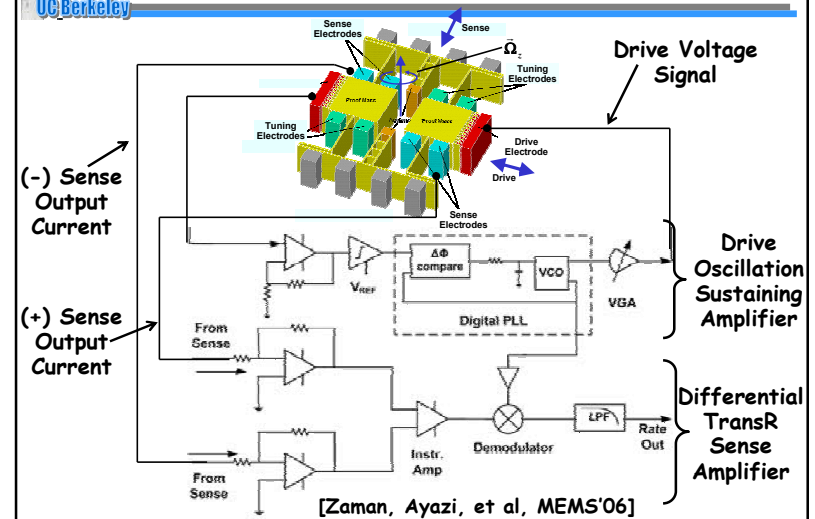


EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 24

Drive Axis Equivalent Circuit

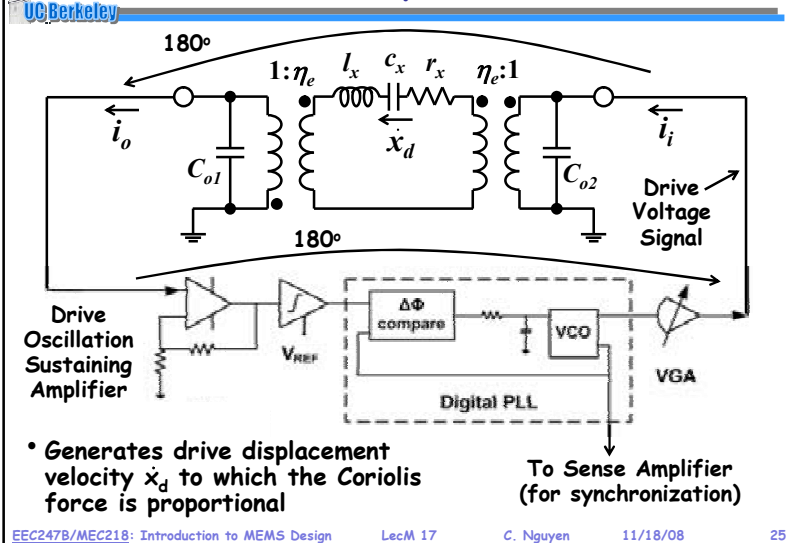


EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 25

Drive-to-Sense Transfer Function

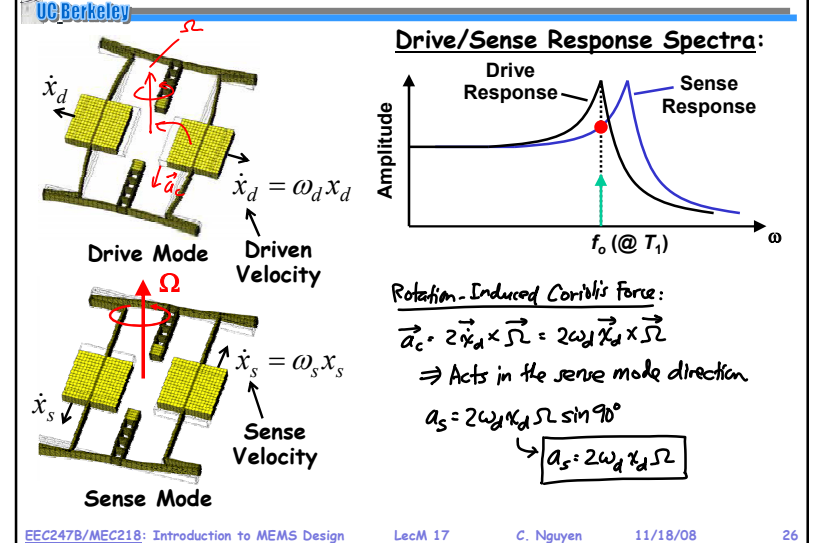


EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 26

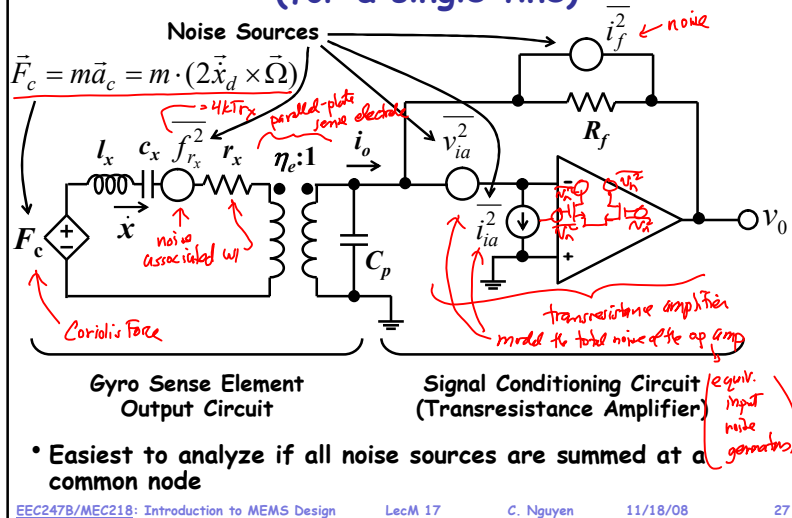Gyro Readout Equivalent Circuit (for a single tine)



Minimum Detectable Signal (MDS)

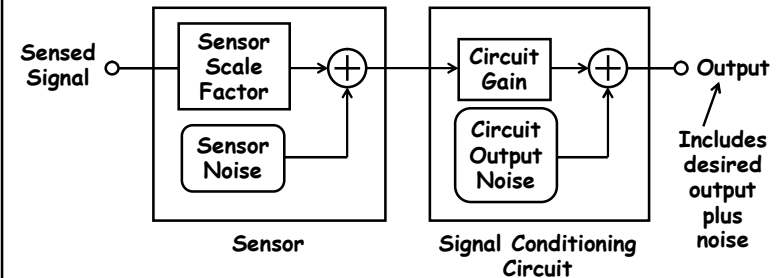
- **Minimum Detectable Signal (MDS):** Input signal level when the signal-to-noise ratio (SNR) is equal to unity



- The sensor scale factor is governed by the sensor type
- The effect of noise is best determined via analysis of the equivalent circuit for the system

Move Noise Sources to a Common Point

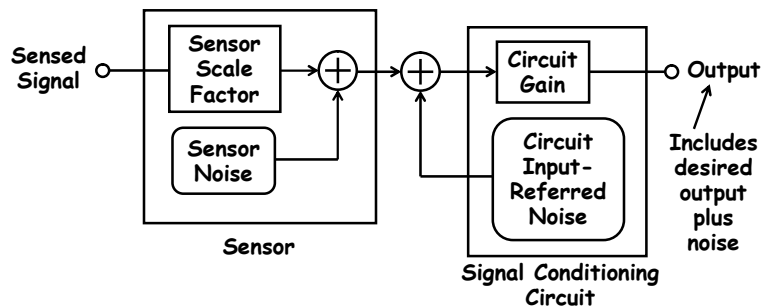- Move noise sources so that all sum at the input to the amplifier circuit (i.e., at the output of the sense element)
- Then, can compare the output of the sensed signal directly to the noise at this node to get the MDS



Equivalent Input-Referred Voltage and Current Noise Sources

Equivalent Input v, i Noise Generators

- Take a noisy 2-port network and represent it by a noiseless network with input v and i noise generators that generate the same total output noise

- Remarks:**
 - Works for linear time-invariant networks
 - v_{eq} and i_{eq} are generally correlated (since they are derived from the same sources)
 - In many practical circuits, one of v_{eq} and i_{eq} dominates, which removes the need to address correlation
 - If correlation is important → easier to return to original network with internal noise sources

EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 31

Calculation of v_{eq}^2 and i_{eq}^2

a) To get v_{eq}^2 for a two-port:

Case I

Case II

- Short input, find v_{0I}^2 (or i_{0I}^2)
- For eq. network, short input, find v_{0II}^2 (or i_{0II}^2)

$f(v_{eq}^2) \parallel f(i_{eq}^2)$

- Set $v_{0I}^2 = v_{0II}^2 \rightarrow$ solve for v_{eq}^2 (or $i_{0I}^2 = i_{0II}^2$)

EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 32

Calculation of v_{eq}^2 and i_{eq}^2 (cont)

b) To get i_{eq}^2 for a 2-port:

- Open input, find v_{0I}^2 (or i_{0I}^2)
- Open input for eq. circuit, find v_{0II}^2 (or i_{0II}^2)
- Set $v_{0I}^2 = v_{0II}^2 \rightarrow$ solve for i_{eq}^2 (or $i_{0I}^2 = i_{0II}^2$)

- Once the equivalent input-referred noise generators are found, noise calculations become straightforward as long as the noise generators can be treated as uncorrelated

EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 33

Cases Where Correlation Is Not Important

- There are two common cases where correlation can be ignored:
 - Source resistance R_s is **small** compared to input resistance $R_i \rightarrow$ i.e., voltage source input
 - Source resistance R_s is **large** compared to input resistance $R_i \rightarrow$ i.e., current source input


1) $R_s = \text{small}$ (ideally = 0 for an ideal voltage source):

\therefore For $R_s = \text{small}$, i_{eq}^2 can be neglected \rightarrow only v_{eq}^2 is important!
(Thus, we need not deal with correlation)

EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 34

Cases Where Correlation Is Not Important

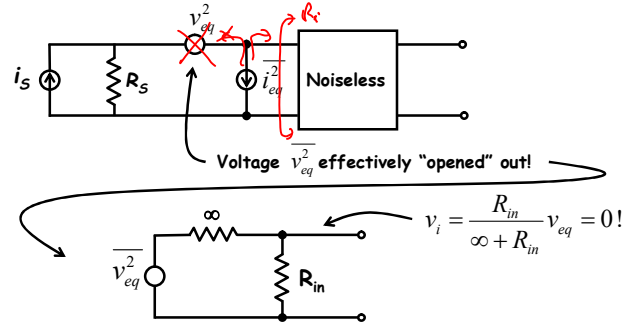2) $R_s = \text{large}$ (Ideally $= \infty$ for an ideal current source)



\therefore For $R_S = \underline{\hspace{1cm}}$, $\overline{v_{eq}^2}$ can be neglected!

→ only i_{eq}^2 is important!

(... and again, we need not deal with correlation)