

Lecture 26w: Equivalent Input NoiseLecture 26: Equivalent Input NoiseAnnouncements:

- HW#6 due Thursday, April 27
- Project Slide Set #3 due Friday, April 28
- Module 17 on Noise & MDS has been online

Reading: Senturia Chpt. 16Lecture Topics:

↳ Minimum Detectable Signal

↳ Noise

— Circuit Noise Calculations

— Noise Sources

— Equivalent Input-Referred Noise


↳ Gyro MDS

— Equivalent Noise Circuit

— Example ARW Determination

Last Time:Circuit noise calculationsNow, move to noise sources and examples ...Systematic Noise Calculation Procedure

General
Ckt.
 ω_l
Several
Noise
Sources

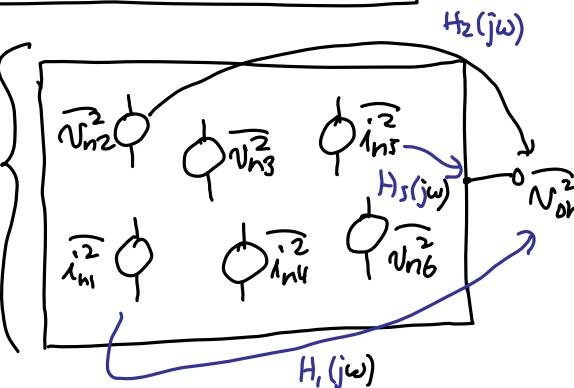

Assume noise sources are ^{un}correlated.

① For i_{n1}^2 , replace w/ a source i_{n1} .

② Calculate $N_{on1}(w) = i_{n1}(w) H_i(w)$
(treating it like a deterministic signal)

③ Determine $\overline{N_{on1}} = \overline{i_{n1}^2} \cdot |H_i(w)|^2$

④ Repeat for each noise source:

$$\overline{N_{on2}} = f(\overline{V_{n2}^2}), \quad \overline{N_{on3}} = f(\overline{V_{n3}^2}), \dots$$

⑤ Add noise power (mean-square values)

$$\overline{N_{onTOT}} = \overline{N_{on1}^2} + \overline{N_{on2}^2} + \overline{N_{on3}^2} + \overline{N_{on4}^2} + \dots$$

$$\overline{N_{onTOT}} = \sqrt{\overline{N_{on1}^2} + \overline{N_{on2}^2} + \overline{N_{on3}^2} + \overline{N_{on4}^2} + \dots}$$

total rms value

Lecture 26w: Equivalent Input Noise

Why $\frac{\overline{V_R^2}}{\Delta f} = 4kT R$? (a heuristic argument)

Consider an RC ckt:

$$E = \frac{1}{2} kT = \frac{1}{2} C \overline{V_c^2} \rightarrow \overline{V_c^2} = \frac{kT}{C}$$

integrated noise over all freqs.

(total mean-square voltage integrated over all freqs.)

Question: What value of $\frac{\overline{V_R^2}}{\Delta f}$ gives us this (assume white noise)


$$\overline{V_c^2} = \int_0^\infty \left| \frac{1}{1+j\omega RC} \right|^2 \frac{\overline{V_R^2}}{\Delta f} d\omega = \frac{kT}{C}$$


[noise is white] $\rightarrow = \frac{1}{2\pi} \frac{\overline{V_R^2}}{\Delta f} \int_0^\infty \frac{\omega_b^2}{\omega_b^2 + \omega^2} d\omega$

$(\omega_b = \frac{1}{RC})$

$$\left[\int \frac{dx}{x^2+a^2} = \frac{1}{a} \tan^{-1}\left(\frac{x}{a}\right) \right]$$

$$= \frac{1}{2\pi} \frac{\overline{V_R^2}}{\Delta f} \frac{\omega_b^2}{\omega_b} \tan^{-1}\left(\frac{\omega}{\omega_b}\right) \Big|_0^\infty$$
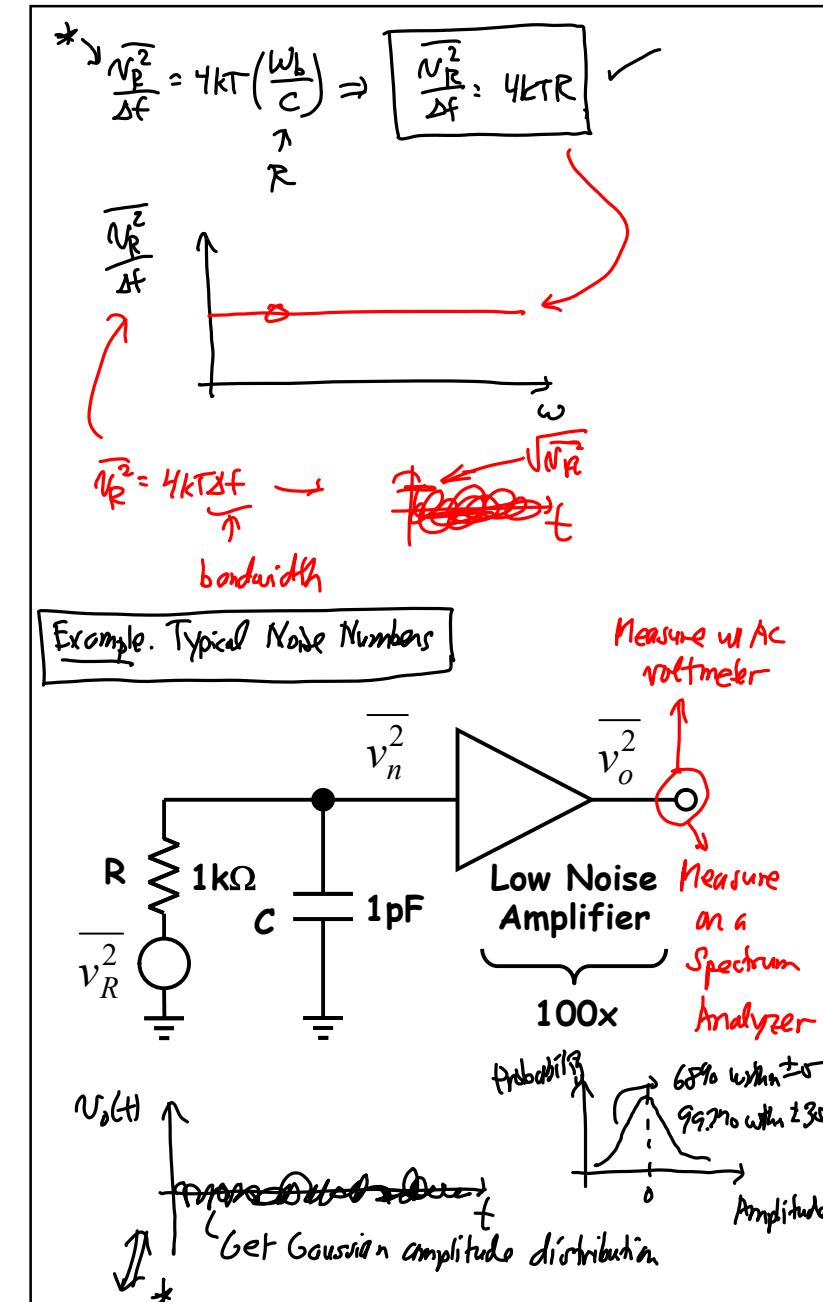
$$= \frac{1}{2\pi} \frac{\overline{V_R^2}}{\Delta f} \left(\frac{1}{2} \omega_b - 0 \right) = \frac{1}{4} \omega_b \frac{\overline{V_R^2}}{\Delta f} = \frac{kT}{C}$$

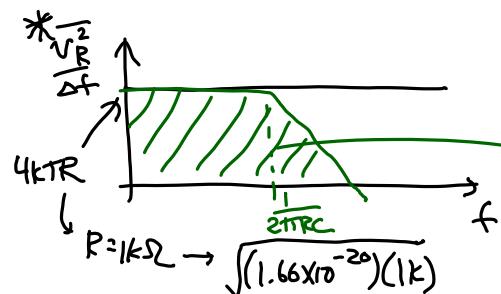
Lecture 26w: Equivalent Input Noise



$$1k\Omega: 4nV/\sqrt{Hz} \quad (\text{for every } 1k \text{ of } R)$$

$$1PF: \sqrt{\frac{kT}{C}} = 64 \mu V \text{ rms}$$

Case: AC Voltmeter

$$\sqrt{N_o^2} = (100)(64 \mu V \text{ rms}) = \underline{\underline{6.4 mV \text{ rms}}}$$

Case: Spectrum Analyzer

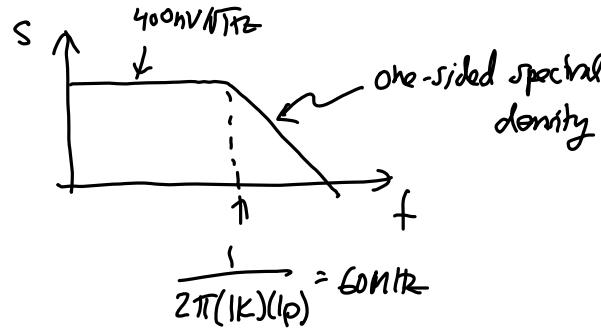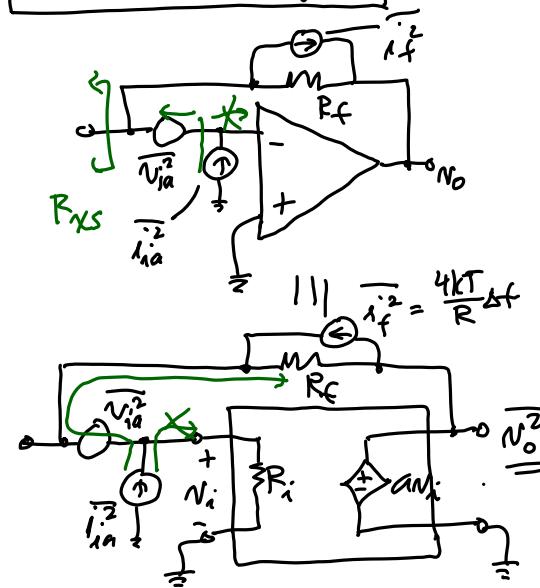Noise in a Transf. Amplifier

Get $\overline{N_o^2}$: use superposition \rightarrow handle one noise source at a time

$$\overline{N_o^2}: N_{o1} = i_{ia} R_f \rightarrow \overline{N_{o1}^2} = \overline{i_{ia}^2} R_f^2$$