

# EE 247B / ME 218 Discussion 1

---

Kieran Peleaux

# Introductions

---

Kieran Peleaux

- B.S.E.E. from University of Pittsburgh (2014)
- Worked for Powercast in Pittsburgh for ~1.5 years
- 2<sup>nd</sup> year PhD student in Prof. Clark Nguyen's group
- Interests
  - Vibrating RF MEMS
  - MEMS-CMOS integration
  - MEMS filter design
  - All-mechanical transceivers
  - My cats
  - Cooking
  - Video games

*Come introduce yourself  
during office hours!*

# Office Hours & Discussion

---

## Office Hours

*Mondays 3:30 – 5 pm, 212 Cory Hall*

*Wednesdays 1 – 2 pm, 212 Cory Hall (557 Cory this week!)*

## Discussion


*Currently scheduled for Wednesdays 12 – 1 pm*

***This conflicts with one of my classes, please go to [this poll](#) and list your availability ASAP. Thanks in advance!***

# Op-Amp Review

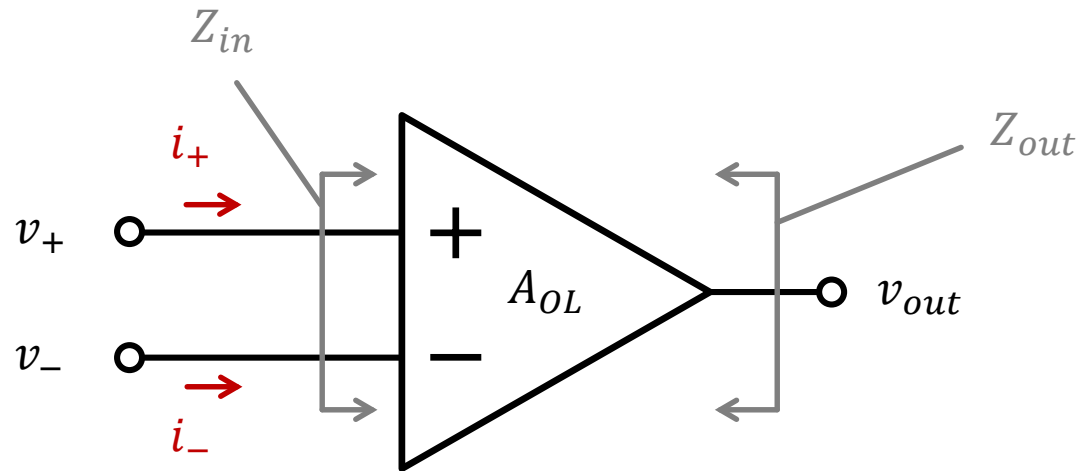
## Ideal Op-amp Laws

- $Z_{in} = \infty$ 
  - $i_+ = i_- = 0$
- $A_{OL} = \infty$ 
  - $v_+ = v_-$
- $Z_{out} = 0$



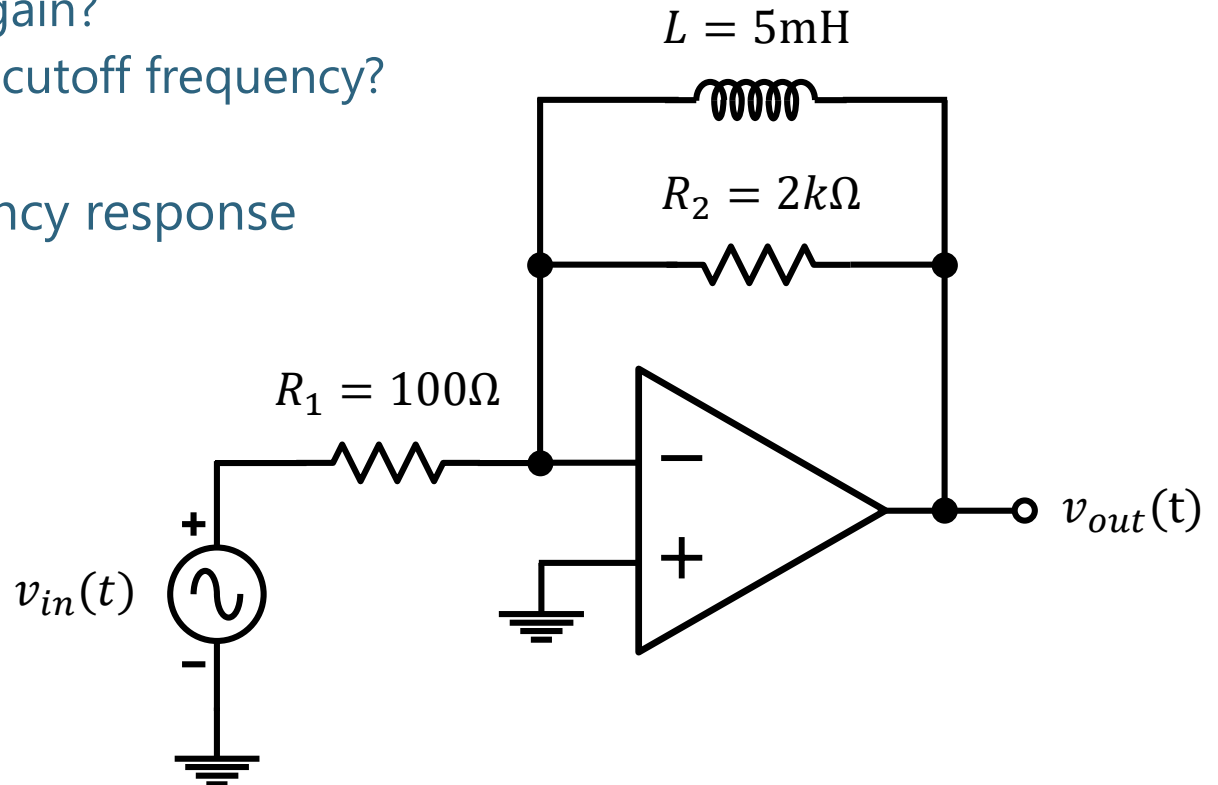
# Op-Amp Example

- What is the transfer function  $\frac{v_o(s)}{v_i(s)}$ ?
  - what's the DC gain?
  - what's the 3dB cutoff frequency?
- Sketch the frequency response
  - magnitude
  - phase



# Op-Amp Example (cont.)

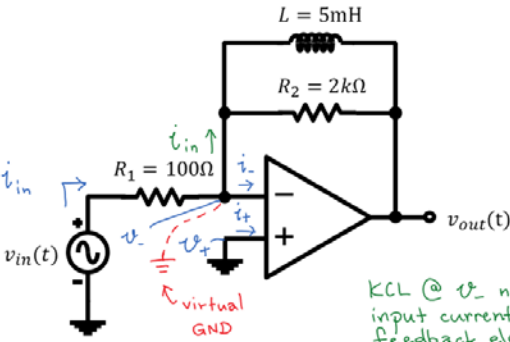

$$A_{OL} = \infty$$

$$v_o = A_{OL} (v_+ - v_-)$$

$$\therefore \text{if } v_o < \infty, (v_+ - v_-) = 0$$

$$v_+ = v_-$$

$$Z_{in} = \infty$$

$$i_+ = \frac{v_+}{Z_{in}} = \frac{v_+}{\infty} = 0$$

$$i_- = \frac{v_-}{Z_{in}} = \frac{v_-}{\infty} = 0$$

since  $v_+$  is grounded,  
 $v_+ = v_- = 0V$

KCL @  $v_-$  node shows all input current flows thru feedback elements.

KVL btwn.  $v_i$  &  $v_-$ :

$$v_i - i_{in} \cdot R_1 = v_-$$

$$i_{in} = \frac{(v_i - v_-)}{R_1}$$

$$i_{in} = \frac{v_i}{R_1} \quad (1)$$

KVL btwn.  $v_-$  &  $v_o$ :

$$v_- - i_{in} \cdot Z_{fb} = v_o$$

$$v_o = -i_{in} \cdot Z_{fb}$$

plug in (1) & (2)

$$v_o = -\left(\frac{v_i}{R_1}\right) \left(\frac{R_2 \cdot sL}{R_2 + sL}\right)$$

$$\frac{v_o}{v_i} = -\left(\frac{R_2}{R_1}\right) \cdot \frac{s \frac{L}{R_2}}{s \frac{L}{R_2} + 1}$$

one zero @  $s = 0$   
 $\omega_z = 0 \frac{\text{rad}}{\text{sec}}$   
 $f_z = 0 \text{ Hz}$

one pole:  $s \frac{L}{R_2} = 1$   
 $\omega_p = \frac{R_2}{L} = \frac{2 \text{ k}\Omega}{5 \text{ mH}}$

$\omega_p = 400 \text{ krad/sec}$   
 $f_p = \frac{\omega_p}{2\pi} = 63.7 \text{ kHz}$   
 this is 3dB cutoff frequency

max gain (not @ DC!):

$$|A_{cl, \text{max}}| = \frac{R_2}{R_1} = \frac{2 \text{ k}\Omega}{100 \Omega}$$

$$|A_{cl, \text{max}}| = 20 \frac{V}{V}$$

$$A_{cl, \text{max, dB}} = 20 \log(20 \frac{V}{V})$$

$$A_{cl, \text{max, dB}} = 26 \text{ dB}$$

$$|A_{DC}| = 0 \frac{V}{V}$$

$Z_{fb}$ :


$$Z_{fb} = (Z_{R2} \parallel Z_L)$$

$$= \frac{(Z_{R2} \cdot Z_L)}{(Z_{R2} + Z_L)}$$


$$Z_{fb} = \frac{R_2 \cdot sL}{R_2 + sL} \quad (2)$$

Remember:  
 $Z_L = sL$  where  
 $Z_C = \frac{1}{sC}$   $s = j\omega$

$\frac{|v_o(s)|}{|v_i(s)|}$

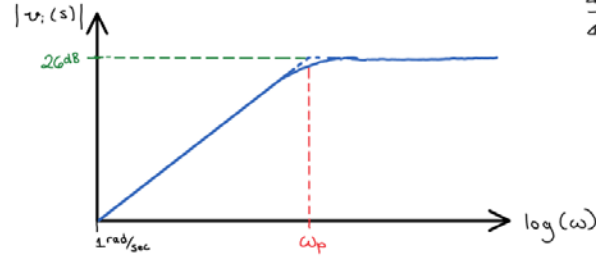

$\angle v_o(s)$

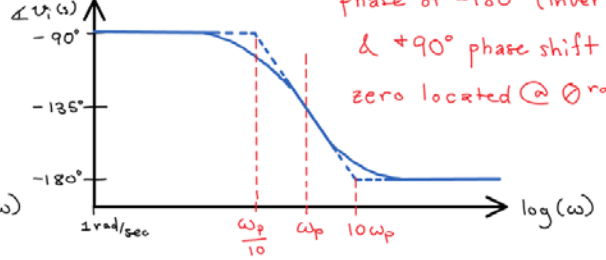



\* note that phase plot begins @  $-90^\circ$  due to initial phase of  $-180^\circ$  (inverting config.) &  $+90^\circ$  phase shift due to the zero located @  $0 \text{ rad/sec}$

# Intro to Thermal Circuits

- Modeling a thermal body/excitation as circuit elements
- Can then apply circuit analysis techniques to non-electrical problems—or hybrid electromechanical problems
- Common theme in this course, will see more complex modeling

Electrical	Thermal
Voltage, $V$ (V)	Temperature, $T$ (°C or K)
Current, $I$ (A)	Power, $P$ (W)
Resistance, $R$ ( $\Omega$ or V/A)	Thermal Resistance, $R_{th}$ (K/W)
Capacitance (F or C/V)	Heat Capacity, $C_{th}$ (J/K)

# Resistance : Electrical vs. Thermal

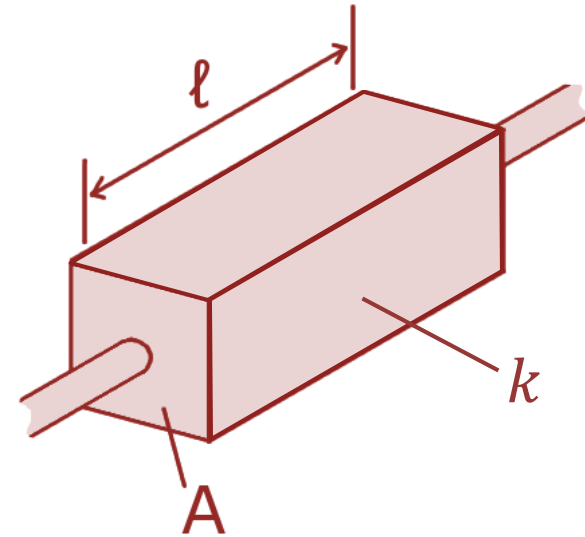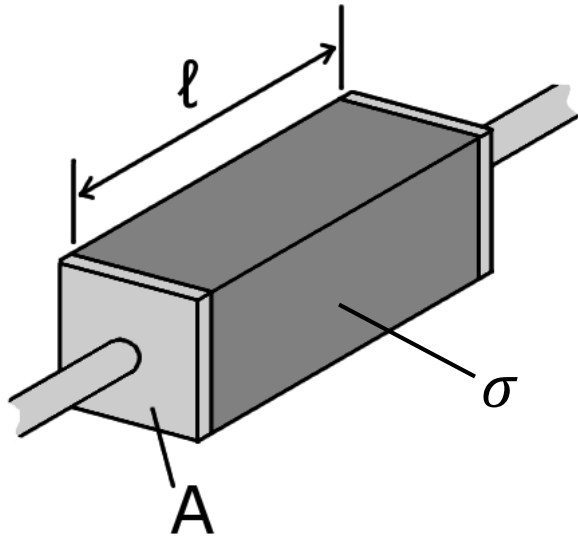

resistance ( $\Omega$ )

$$R = \frac{l}{\sigma \cdot A}$$

length (m)

conductivity ( $(\Omega \cdot m)^{-1}$ )

cross-sectional area ( $m^2$ )

thermal resistance ( $K/W$ )

$$R_{th} = \frac{l}{k \cdot A}$$


length (m)

thermal conductivity ( $\frac{W}{K \cdot m}$ )

cross-sectional area ( $m^2$ )



# Capacitance : Electrical vs. Thermal

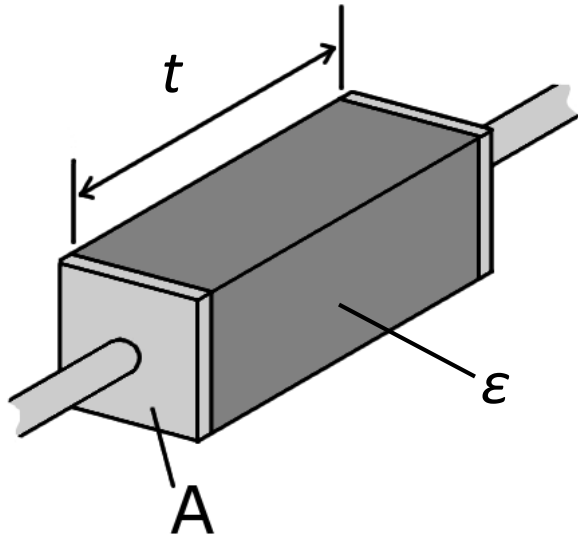


capacitance (F)

permittivity of dielectric ( $\frac{F}{m}$ )

area of plate ( $m^2$ )

thickness of dielectric (m)

$$C = \epsilon \cdot \frac{A}{t}$$

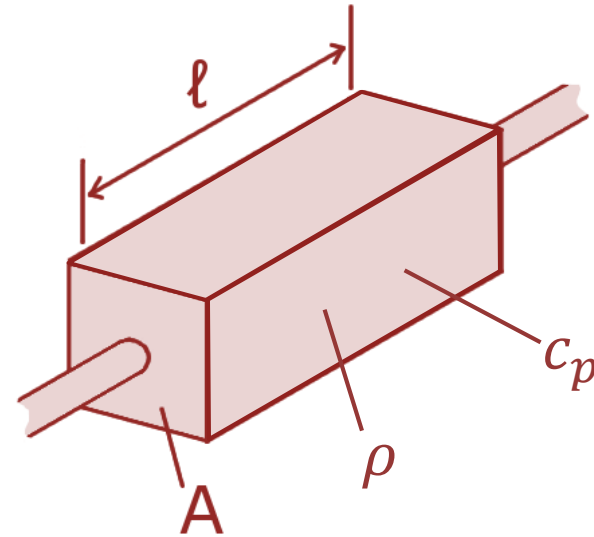

thermal capacitance (J/K)

length (m)


specific heat ( $\frac{J}{kg \cdot K}$ )

density ( $\frac{kg}{m^3}$ )

cross-sectional area ( $m^2$ )


$$C_{th} = \rho \cdot l \cdot A \cdot c_p$$

# Distributed Thermal Model

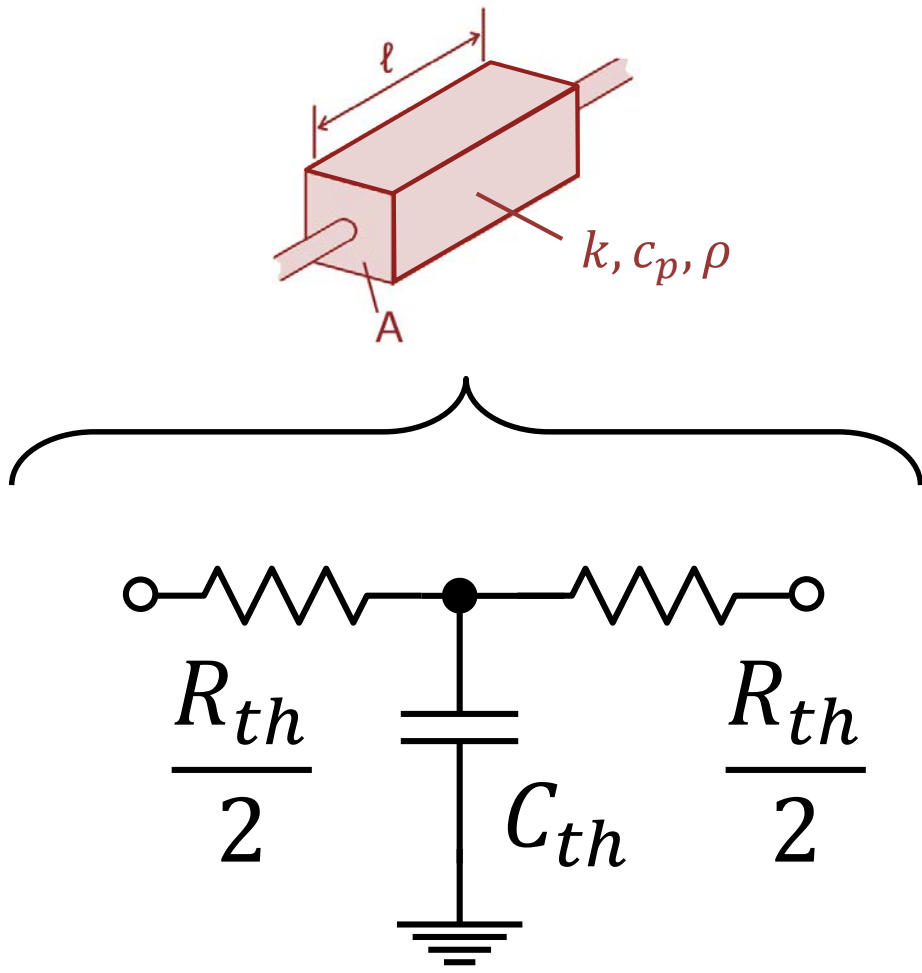

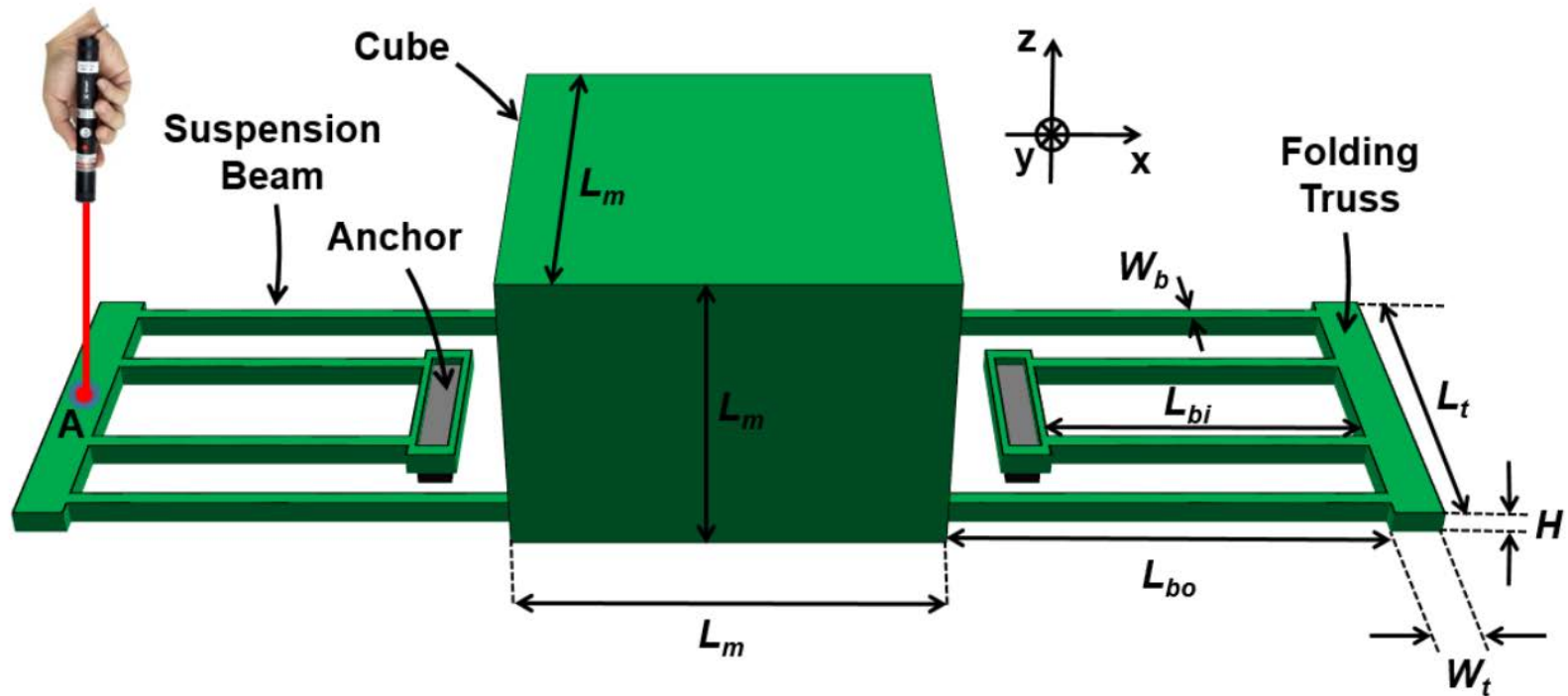
# Thermal Ckt. Example

- Draw the full thermal circuit model (include effects of laser!)
- What approximations can you make?




# Thermal Ckt. Example (cont.)

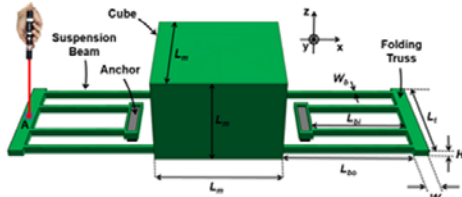

$L_{bi} = 50 \mu\text{m}$     $L_t = 50 \mu\text{m}$     $k = 30 \text{ W/m}\cdot\text{K}$   
 $L_{bo} = 75 \mu\text{m}$     $W_t = 6 \mu\text{m}$     $c_p = 770 \text{ J/kg}\cdot\text{K}$   
 $W_b = 2 \mu\text{m}$     $L_m = 50 \mu\text{m}$     $\rho = 2,300 \text{ kg/m}^3$   
 $H = 2 \mu\text{m}$

$$R_{th,bi} = \frac{L_{bi}}{k(W_b \cdot H)} = \frac{50 \mu\text{m}}{(30 \frac{\text{W}}{\text{m}\cdot\text{K}})(2 \mu\text{m})^2} = 4.17 \times 10^5 \text{ K/W}$$
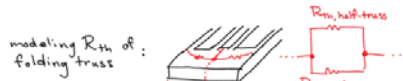
$$R_{th,bo} = \frac{L_{bo}}{k(W_b \cdot H)} = \frac{75 \mu\text{m}}{(30 \frac{\text{W}}{\text{m}\cdot\text{K}})(2 \mu\text{m})^2} = 6.25 \times 10^5 \text{ K/W}$$



$$R_{th,t} = R_{th, \text{half-truss}} \parallel R_{th, \text{half-truss}} = \frac{R_{th, \text{half-truss}}}{2}$$

$$= \frac{1}{2} \frac{L_t/2}{k(W_t \cdot H)} = \frac{(50 \mu\text{m})}{2(30 \frac{\text{W}}{\text{m}\cdot\text{K}})(6 \mu\text{m})(2 \mu\text{m})}$$


$$R_{th,t} = 3.47 \times 10^4 \text{ K/W} \ll R_{th,bi}, R_{th,bo}$$

$\therefore$  can neglect  $R_{th,t}$ !


$$R_{th,m} = \frac{L_m}{k(L_m)^2} = \frac{50 \mu\text{m}}{(30 \frac{\text{W}}{\text{m}\cdot\text{K}})(50 \mu\text{m})^2} = 667 \text{ K/W}$$

$\hookrightarrow$  can also neglect  $R_{th,m}$ !

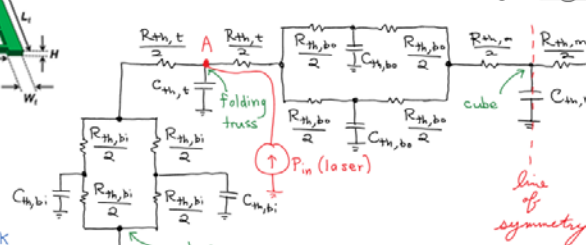Can start w/  $1/2$  of thermal ckt. due to symmetry:




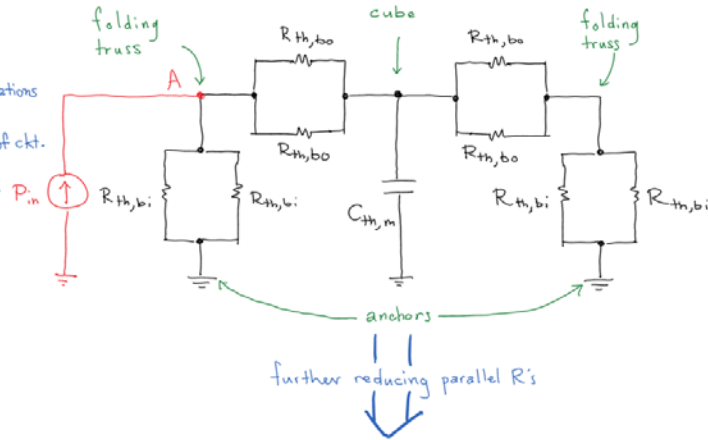applying approximations & adding  $2^{nd}$  half of ckt.



further reducing parallel R's

Fully simplified final circuit:

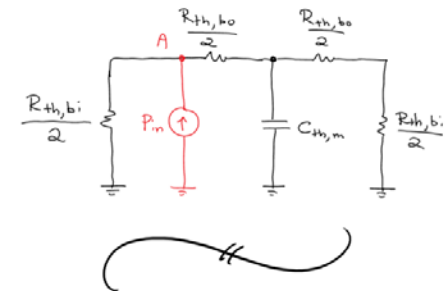

$$C_{th,bi} = \rho(L_{bi} \cdot W_b \cdot H) c_p = (2.3 \times 10^3 \frac{\text{kg}}{\text{m}^3})(50 \mu\text{m})(2 \mu\text{m})^2 (770 \text{ J/kg}\cdot\text{K})$$

$$C_{th,bi} = 3.54 \times 10^{-10} \text{ J/K}$$

$$C_{th,bo} = \rho(L_{bo} \cdot W_b \cdot H) c_p = (2.3 \times 10^3 \frac{\text{kg}}{\text{m}^3})(75 \mu\text{m})(2 \mu\text{m})^2 (770 \text{ J/kg}\cdot\text{K})$$

$$C_{th,bo} = 5.31 \times 10^{-10} \text{ J/K}$$

$$C_{th,t} = \rho(L_t \cdot W_t \cdot H) c_p = (2.3 \times 10^3 \frac{\text{kg}}{\text{m}^3})(50 \mu\text{m})(6 \mu\text{m})(2 \mu\text{m})(770 \text{ J/kg}\cdot\text{K})$$

$$C_{th,t} = 1.06 \times 10^{-9} \text{ J/K}$$

$$C_{th,m} = \rho(L_m)^3 c_p = (2.3 \times 10^3 \frac{\text{kg}}{\text{m}^3})(50 \mu\text{m})^3 (770 \text{ J/kg}\cdot\text{K})$$

$$C_{th,m} = 2.21 \times 10^{-7} \text{ J/K} \gg C_{th,bi}, C_{th,bo}, C_{th,t}$$

$\therefore$  can neglect all  $C_{th}$ 's except  $C_{th,m}$ !