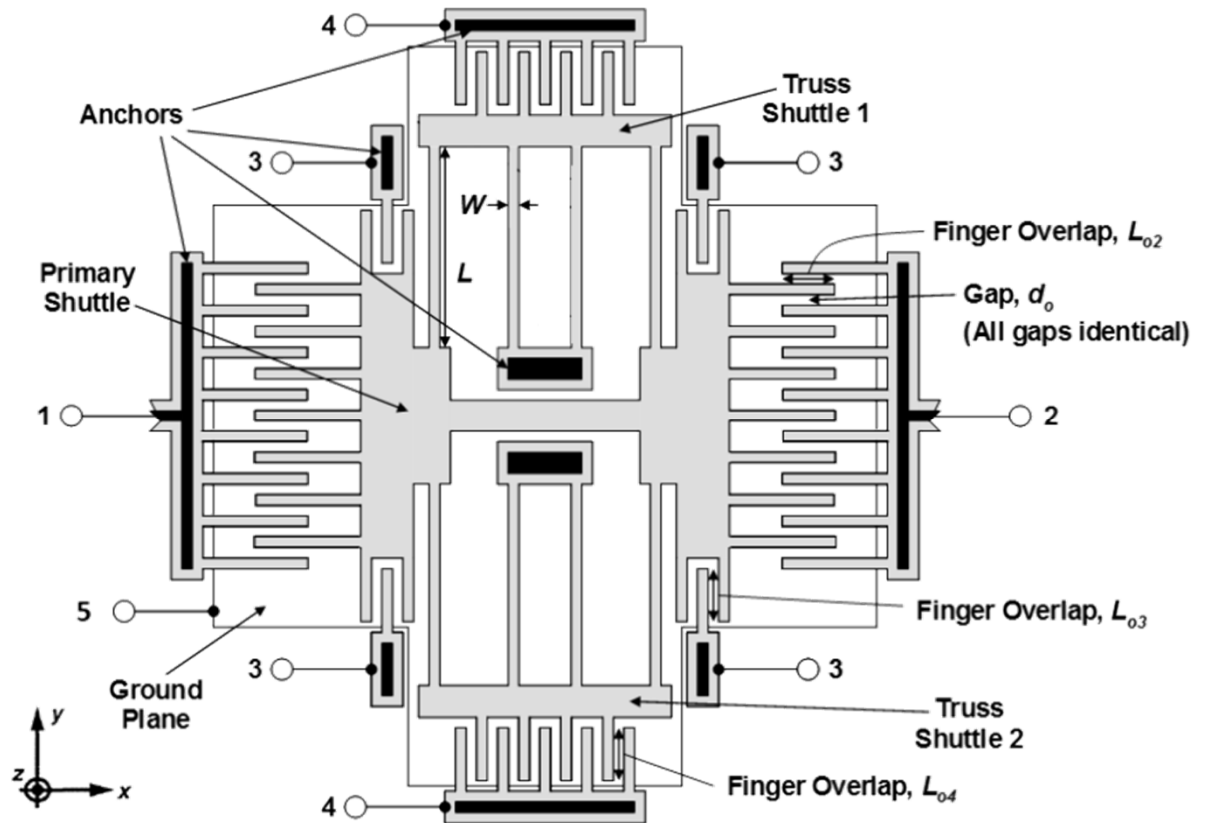


EE 247B / ME 218 Discussion 12

Kieran Peleaux

Equivalent Circuits & Sensing

Let's do some analysis on the resonance behavior of this comb-drive structure



Structural Material Properties:

Young's Modulus, $E = 150 \text{ GPa}$; Density, $\rho = 2,300 \text{ kg/m}^3$

Poisson ratio, $\nu = 0.226$; $Q = 100,000$

Geometric Dimensions:

$L = 50 \mu\text{m}$; $W = 2 \mu\text{m}$; Thickness, $h = 2 \mu\text{m}$; All Finger Gaps, $d_o = 1 \mu\text{m}$

All Finger Overlaps, $L_o = 10 \mu\text{m}$, Truss Shuttle 1 Area = $300 \mu\text{m}^2$

Truss Shuttle 2 Area = $300 \mu\text{m}^2$, Primary Shuttle Area = $4,000 \mu\text{m}^2$

x-Direction Resonance Frequency

First, let's find f_0 when all ports are grounded

$$\omega_0 = \sqrt{\frac{k_s}{m_s}}$$

$$k_s = k_c = \frac{2Ew^3h}{L^3} = \frac{2(150G)(2\mu)(2\mu)}{(50\mu)^3} = 38.4 \text{ N/m}$$


$$m_s = M_s + \frac{1}{4}M_t + \frac{12}{35}M_b = 20.35 \text{ ng}$$

$$M_s = \rho h A_s = 18.4 \text{ ng}$$


$$M_t = 2\rho h A_t = 2.76 \text{ ng}$$

$$M_b = 8\rho h L W = 3.68 \text{ ng}$$
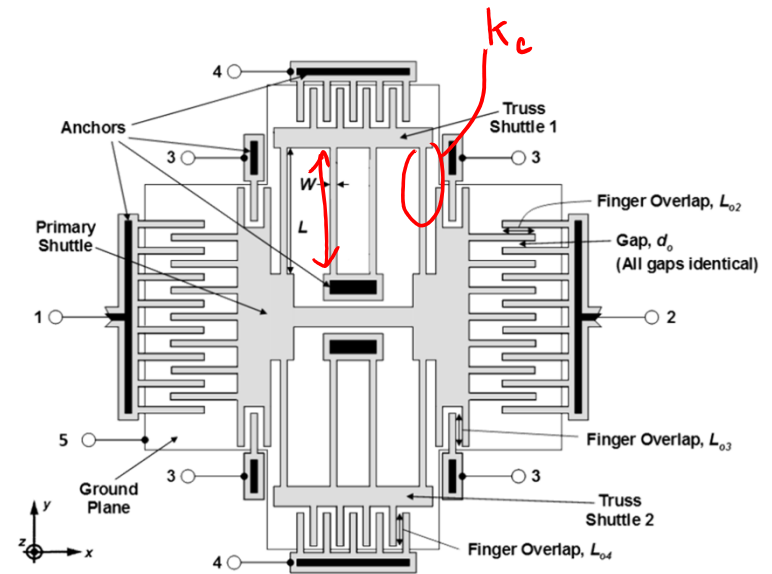
$$\omega_0 = \sqrt{\frac{38.4}{20.3 \text{ n}}} = 1.37 \frac{\text{Mrad}}{\text{s}} \Rightarrow f_0 = 218.618 \text{ kHz}$$



x-Direction Resonance Frequency

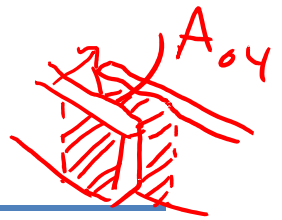

Now, let's find f_0 when ports 1, 2 & 4 are grounded, and all other ports are biased to 50 V

$$f_0' = f_0 \left(1 - \frac{k_{e4}}{k_t} \right)^{\frac{1}{2}}$$

electrical stiffness from port 4
stiffness @ truss

$$k_{e4} = V_p^2 \frac{C_0}{d_0^2} = V_p^2 \frac{\epsilon_0 A_{04}}{d_0^3} = \frac{V_p^2 \epsilon_0 (2N_{f4} h L_0)}{d_0^3}$$

$$= \frac{(50)^2 (8.85 \times 10^{-12}) (2)(8)(2 \mu\text{m})(10 \mu\text{m})}{(1 \mu\text{m})^3} = 7.08 \text{ N/m}$$

$$\frac{1}{2} m_t v_t^2 = \frac{1}{2} m_s v_s^2$$

$$m_t = \left(\frac{v_s^2}{v_t^2} \right) m_s = 4 m_s \Rightarrow k_t = 4 k_s = 4(38.4 \text{ N/m})$$


$$v_t = \frac{1}{2} v_s \quad \omega_{0t} = \omega_{0s}$$

$$k_t = 153.6 \text{ N/m}$$

$$f_0' = (218 \text{ k}) \left(1 - \frac{7.08}{153.6} \right)^{\frac{1}{2}}$$



$$f_0 = 0.9767 f_0'$$

$$= 213.517 \text{ kHz}$$

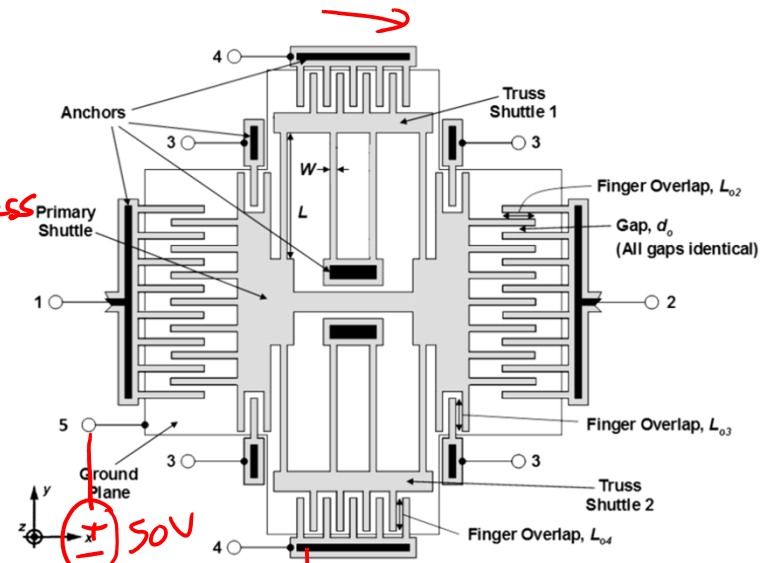

Equivalent Circuit

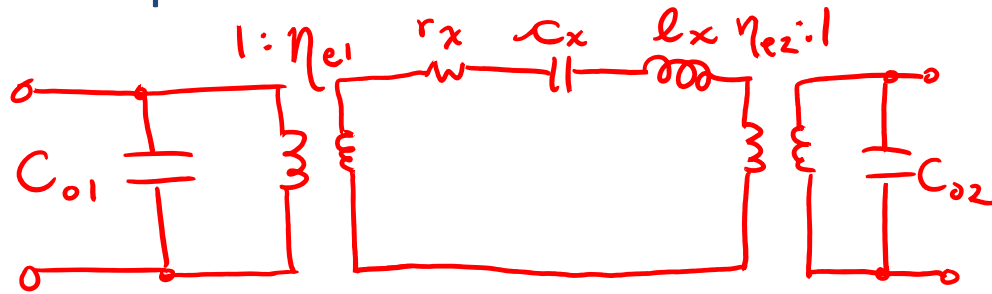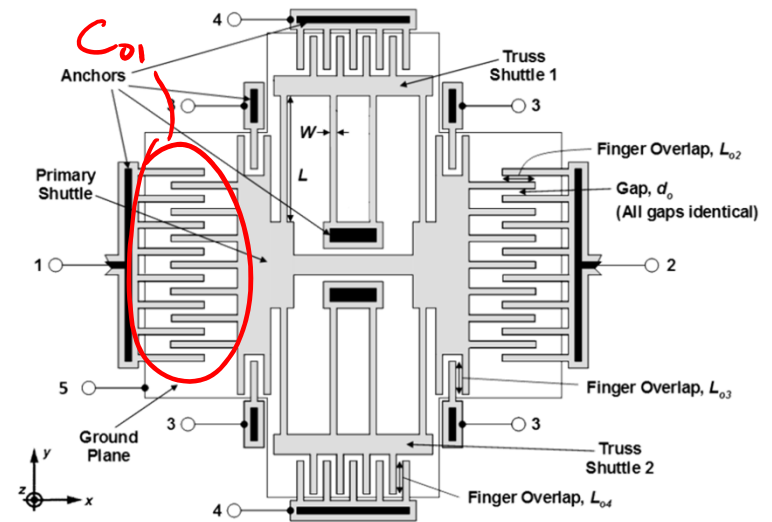Now draw the transformer-based equivalent circuit (between ports 1 & 2) when ports 1, 2 & 4 are grounded and all other ports are biased to 50 V



$$\eta_{e1} = \eta_{e2} = V_p \frac{\partial c}{\partial x} = V_p \frac{2N_f \epsilon_0 (2\mu)}{l_\mu}$$

$$\eta_{e1} = 1.24 \times 10^{-8} \text{ C/m}$$

$$C_{o1} = C_{o2} = \frac{\epsilon_0 h L_o (2N_f)}{d_o}$$

$$C_{o1} = 2.48 \text{ fF} = C_{o2}$$


$$l_x = m_s = 2.035 \times 10^{-11} \text{ kg (or It)}$$

$$c_x = \frac{1}{k_s} = 0.026 \frac{\text{m}}{\text{N}} \text{ (or F)}$$

$$r_x = b_x = \frac{\sqrt{k_s m_s}}{Q} = 0.2795 \frac{\text{nkg}}{\text{s}} \text{ (or n}\Omega\text{)}$$

Equivalent Circuit

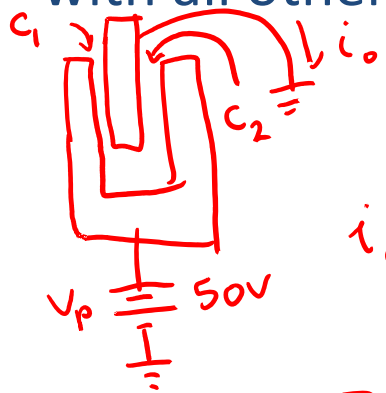Next, draw the transformer-based equivalent circuit between ports 1 & 3 with all other ports are biased to 50 V




$$\frac{\partial C_1}{\partial x} \approx \frac{C_0}{d_0} \quad \frac{\partial C_2}{\partial x} \approx -\frac{C_0}{d_0}$$


$$i_0 = V_p \left(\frac{\partial C_1}{\partial x} + \frac{\partial C_2}{\partial x} \right) \frac{dx}{dt} = 0$$

$$F_d = V_p \left(\frac{\partial C_1}{\partial x} + \frac{\partial C_2}{\partial x} \right) \sigma_i = 0$$

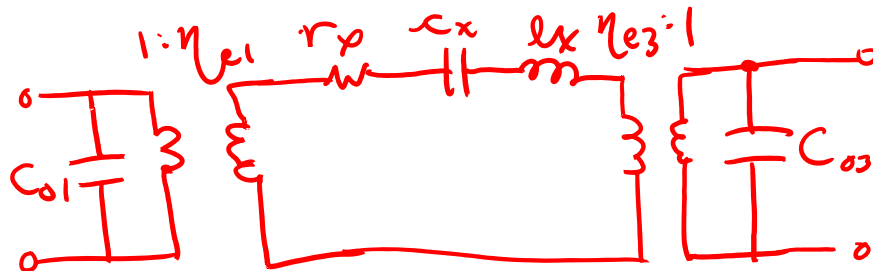
$$\eta_{e3} = V_p \left(\frac{\partial C_1}{\partial x} + \frac{\partial C_2}{\partial x} \right) = 0$$


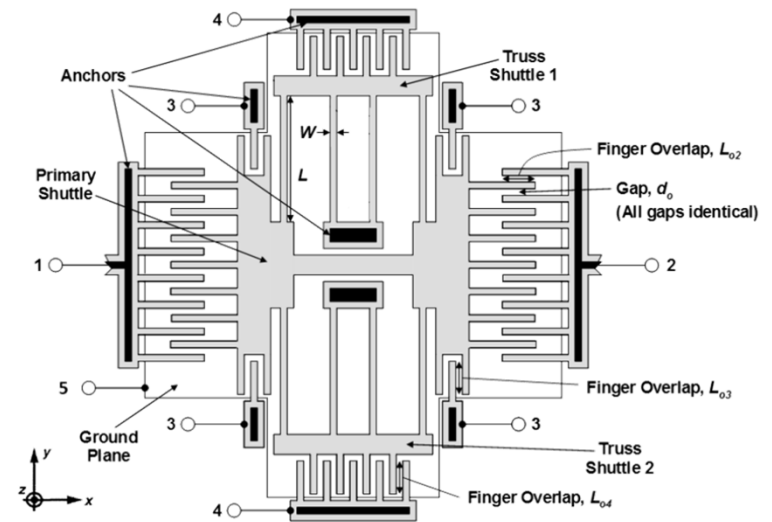
$$C_{03} = \frac{2 N_p^2 \epsilon_0 h L_0}{d_0}$$



Sensing

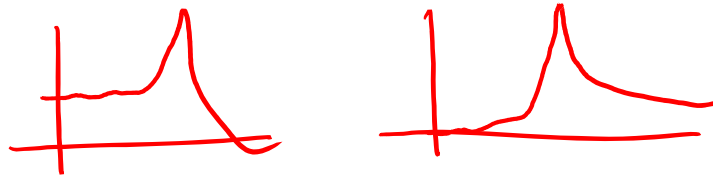

find $\left| \frac{v_o(s)}{v_i(s)} \right|$ $\frac{v_o(s)}{v_i(s)} = \underbrace{\frac{C_x/C_D}{1 - C_x/C_D}}_{\text{DC gain}} \underbrace{\frac{(\omega_o')^2}{s^2 + \left(\frac{\omega_o'}{Q'}\right)s + (\omega_o')^2}}_{\text{low-pass biquad}}$

$$\omega_o' = \omega_o \sqrt{1 + \frac{C_x}{C_D}}$$


$$Q' = Q \sqrt{1 + \frac{C_x}{C_D}}$$

$$C_x = \eta_{ei}^2 C_x = 4 \text{ aF}$$

$$\omega_o' = 227.2 \text{ kHz}$$

$$Q' = 104,000$$

$$\frac{C_x/C_D}{1 - C_x/C_D} = 0.074$$

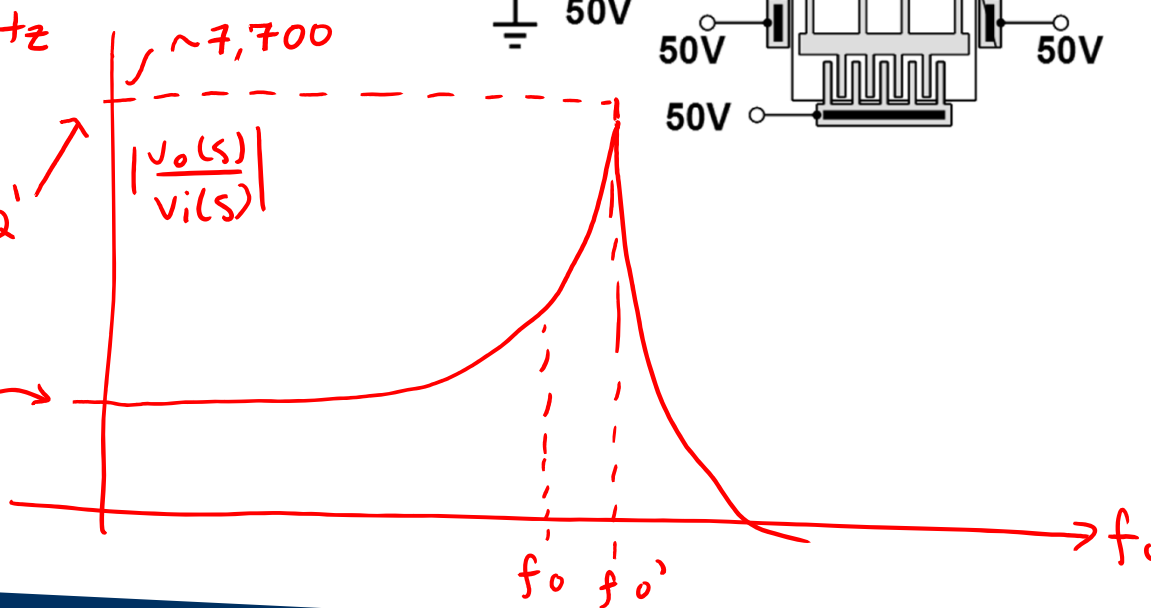

Sensing

$$C_{\text{eff}} = C_p + (1 + A_o)C_f$$

$$f_o' = f_o \left(1 + \frac{C_x}{C_{\text{eff}}} \right) \uparrow \Rightarrow \Delta f_o \downarrow$$

$$\left| \frac{v_o(s)}{v_i(s)} \right| = \frac{C_x / C_{\text{eff}}}{1 + C_x / C_{\text{eff}}} \frac{(\omega_o')^2}{s^2 + \left(\frac{\omega_o'}{Q'} \right) s + (\omega_o')^2}$$

