

# EE 247B / ME 218 Discussion 2

---

Kieran Peleaux

# Logistics


---

- Discussion will remain Wednesdays 12 – 1pm
- I will be out the next two weeks – back on Feb. 16<sup>th</sup>
- Will be available via Piazza, email, Skype (if need be), etc.
- OH & discussion will still be held
  - Led by Alper Ozgurluk
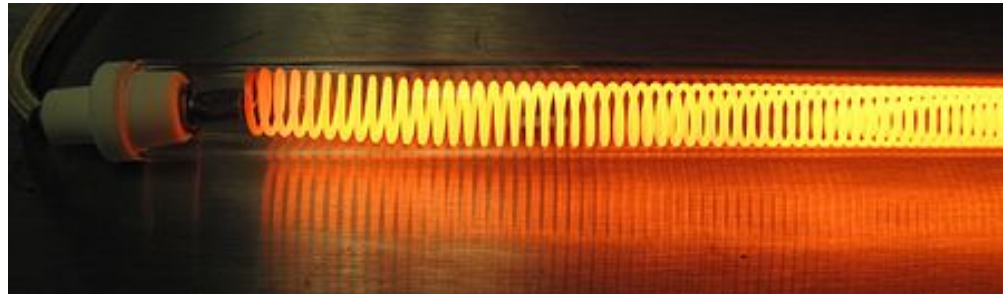
# Thermal/Electrical Hybrid Circuits

---

- The circuit problems we've looked at have been mostly thermal
- Inputs have been convenient power sources (like lasers)
- Is this actually useful? How is thermal energy typically coupled into a thermal body/MEMS?




Electrical power through resistive heating!

# Power Dissipated in a Resistor

- Remember Ohm's law!

$$V = I \cdot R, \quad I = \frac{V}{R}$$

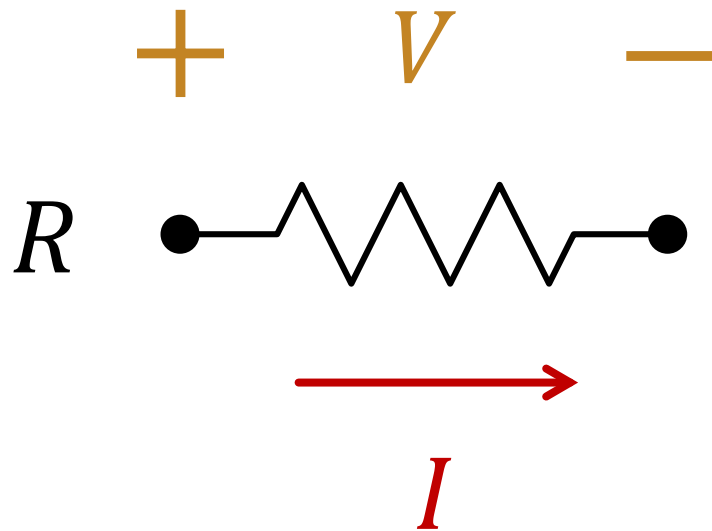


$$P = I \cdot V$$

$$P = \frac{V^2}{R} = I^2 R$$

Most of this energy is thermal!

# Reminder: Electrical Resistance

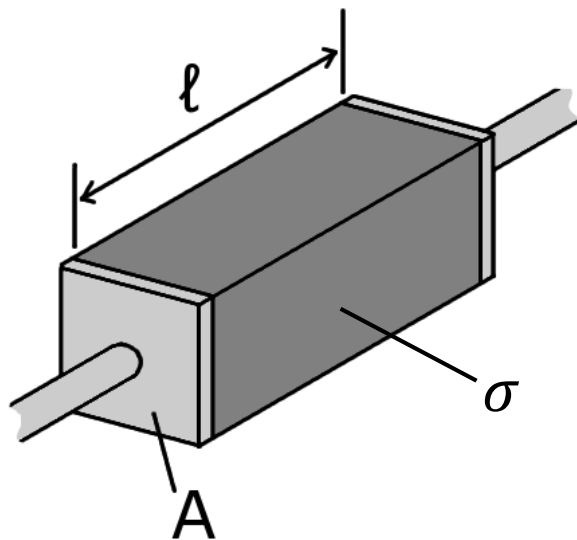

$$R = \frac{l}{\sigma \cdot A}$$

resistance ( $\Omega$ )

length ( $m$ )

conductivity ( $(\Omega \cdot m)^{-1}$ )


cross-sectional area ( $m^2$ )

# Reminder: Superposition

---

*How do we handle circuits with multiple inputs (i.e., sources)?*

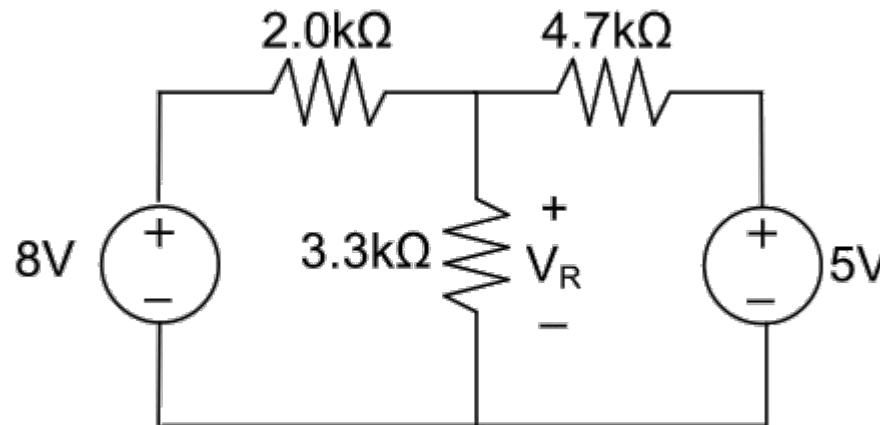1. Pick a source to analyze
2. Suppress (turn off) all other inputs
  - Set either  $V$  or  $I$  to zero
  - This means short-circuiting voltage sources & open-circuiting current sources
3. Find the output of interest for the modified circuit
4. Repeat steps 1-3 for all sources
5. Sum all resultant outputs to find total output due to all sources



# Thermal Ckt. Example

- $V_A$  represents a step function voltage source (can think of it as switching the voltage on at some time,  $t$ )
- Find the time-constant of the circuit
- Find the steady-state temperature on the shuttle if the final value of  $V_A$  is 1V

