

# EE 247B / ME 218 Discussion 1

---

Kieran Peleaux

# Introductions

---

## Kieran Peleaux

- B.S.E.E. from University of Pittsburgh (2014)
- Worked for Powercast in Pittsburgh for ~1.5 years
- 4<sup>th</sup> year PhD student in Prof. Clark Nguyen's group
- Interests
  - Vibrating RF MEMS
  - MEMS-CMOS integration
  - MEMS filter design
  - MEMS oscillators
  - My pets
  - Cooking
  - Video games

*Come introduce yourself  
during office hours!*

# Office Hours & Discussion

---

## Office Hours

*Mondays, 3:30 – 5 pm, 367 Cory Hall*

*Wednesdays, 10 – 11 am, 367 Cory Hall*


## Discussion

*Fridays, 10 – 11 am, 9 Evans Hall (hopefully we're here now)*

# Op-Amp Review

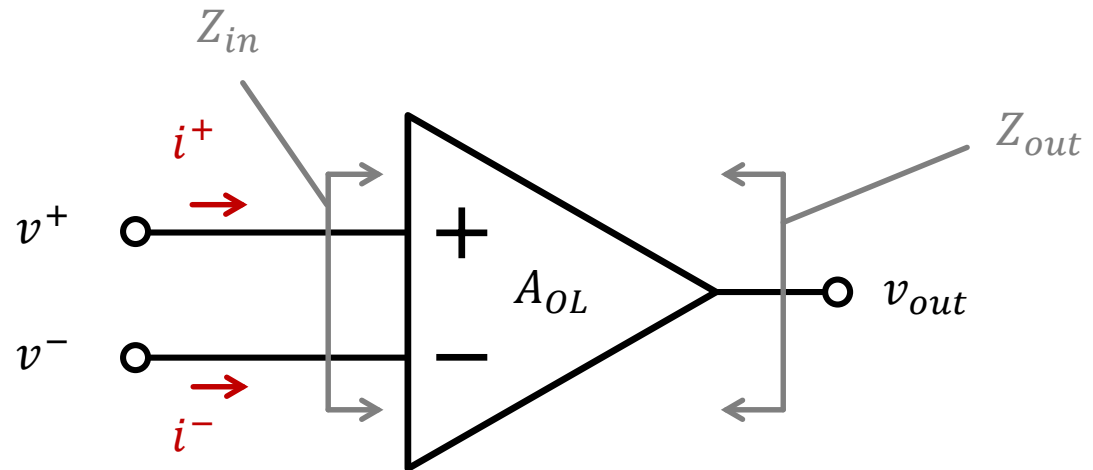
## Ideal Op-amp Laws

- $Z_{in} = \infty$ 
  - $i^+ = i^- = 0$
- $A_{OL} = \infty$ 
  - $v^+ = v^-$
- $Z_{out} = 0$



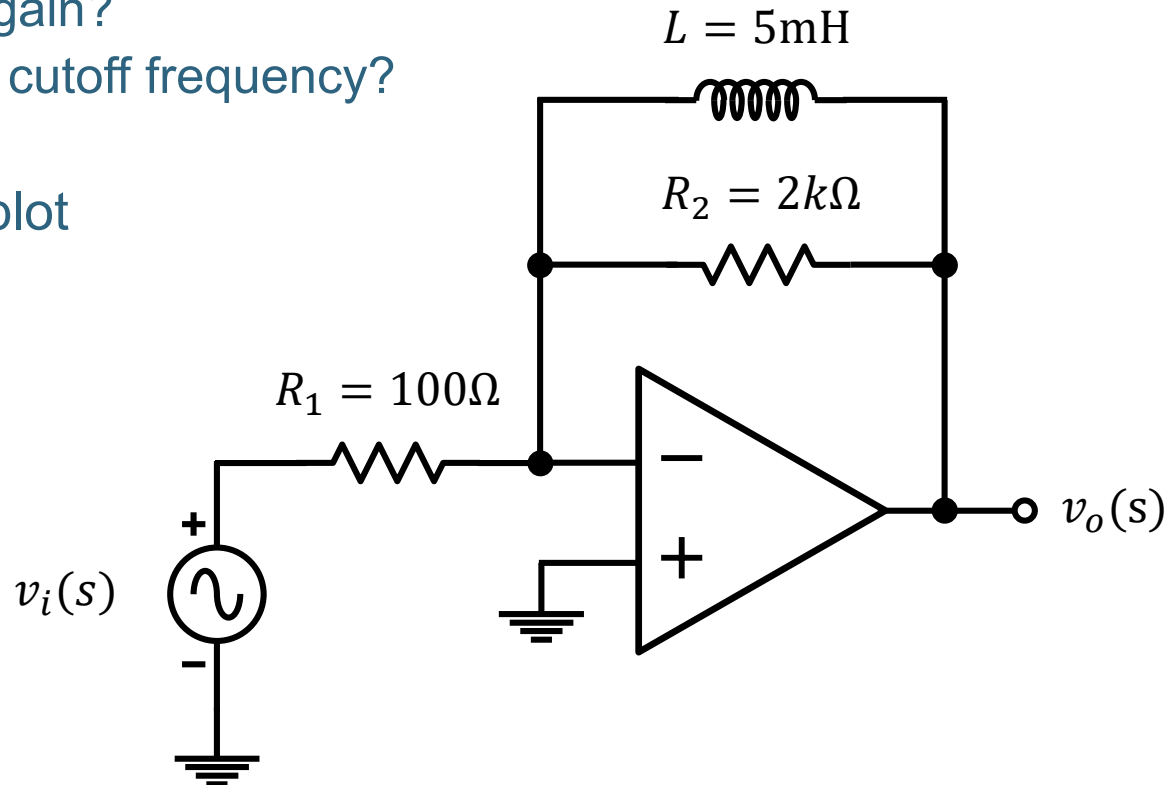
# Op-Amp Example

- What is the transfer function  $\frac{v_o(s)}{v_i(s)}$ ?
  - what's the DC gain?
  - what's the 3dB cutoff frequency?
- Sketch the Bode plot
  - magnitude
  - phase



# Op-Amp Example (cont.)

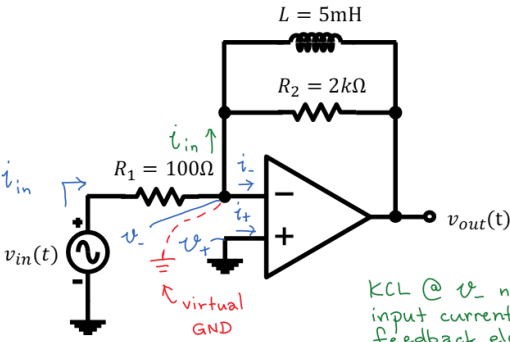

$A_{OL} = \infty$   
 $v_o = A_{OL}(v_+ - v_-)$   
 $\therefore$  if  $v_o < \infty$ ,  $(v_+ - v_-) = 0$   
 $v_+ = v_-$

$Z_{in} = \infty$   
 $i_+ = \frac{v_+}{Z_{in}} = \frac{v_+}{\infty} = 0$   
 $i_- = \frac{v_-}{Z_{in}} = \frac{v_-}{\infty} = 0$

since  $v_+$  is grounded,  
 $v_+ = v_- = 0V$

KCL @  $v_-$  node shows all input current flows thru feedback elements.

KVL btwn.  $v_i$  &  $v_-$ :

$v_i - i_{in} \cdot R_1 = v_-$   
 $i_{in} = \frac{(v_i - v_-)}{R_1}$   
 $i_{in} = \frac{v_i}{R_1} \quad (1)$

KVL btwn.  $v_-$  &  $v_o$ :

$v_- - i_{in} \cdot Z_{fb} = v_o$   
 $v_o = -i_{in} \cdot Z_{fb}$   
 plug in (1) & (2)

$v_o = -\left(\frac{v_i}{R_1}\right) \left(\frac{R_2 \cdot sL}{R_2 + sL}\right)$

$\frac{v_o}{v_i} = -\left(\frac{R_2}{R_1}\right) \cdot \frac{s \frac{L}{R_2}}{s \frac{L}{R_2} + 1}$

one zero @  $s = 0$   
 $\omega_z = 0 \frac{\text{rad}}{\text{sec}}$   
 $f_z = 0 \text{ Hz}$   
 one pole:  $s \frac{L}{R_2} = 1$   
 $\omega_p = \frac{R_2}{L} = \frac{2k\Omega}{5mH}$



$\omega_p = 400 \text{ krad/sec}$   
 $f_p = \frac{\omega_p}{2\pi} = 63.7 \text{ kHz}$   
 this is 3dB cutoff frequency

max gain (not @ DC!):  
 $|A_{CL, \text{max}}| = \frac{R_2}{R_1} = \frac{2k\Omega}{100\Omega}$

$|A_{CL, \text{max}}| = 20 \frac{V}{V}$   
 $A_{CL, \text{max, dB}} = 20 \log(20 \frac{V}{V})$   
 $A_{CL, \text{max, dB}} = 26 \text{ dB}$   
 $|A_{DC}| = 0 \frac{V}{V}$

$Z_{fb}$ :  
 $Z_{fb} = (Z_{R2} \parallel Z_L)$   
 $= \frac{(Z_{R2} \cdot Z_L)}{(Z_{R2} + Z_L)}$   
 $Z_{fb} = \frac{R_2 \cdot sL}{R_2 + sL} \quad (2)$

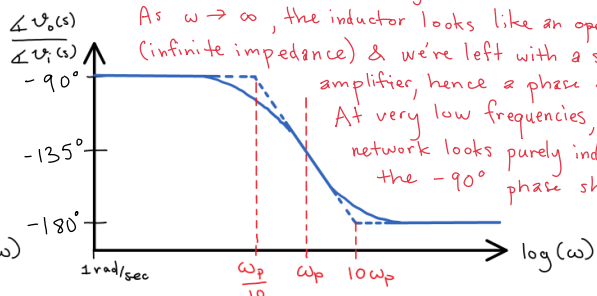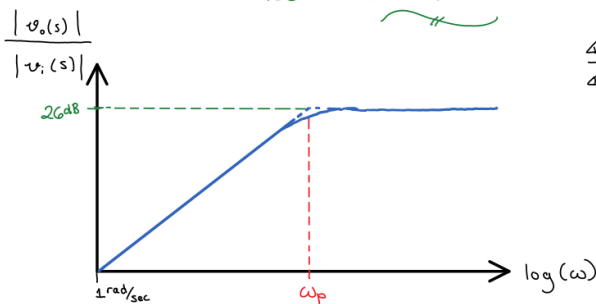Remember:  
 $Z_L = sL$  where  
 $Z_C = \frac{1}{sC}$   $s = j\omega$



☆ To determine the phase at low/high frequencies (i.e.  $\omega_p/10$  &  $10\omega_p$ ) analyze the circuit as  $\omega \rightarrow 0$  or  $\infty$ . As  $\omega \rightarrow \infty$ , the inductor looks like an open-circuit (infinite impedance) & we're left with a standard inverting amplifier, hence a phase shift of  $-180^\circ$ . At very low frequencies, the feedback network looks purely inductive, hence the  $-90^\circ$  phase shift.



$v = (j\omega L)I$

# Intro to Thermal Circuits

- Modeling a thermal body/excitation as circuit elements
- Can then apply circuit analysis techniques to non-electrical problems—or hybrid electromechanical problems
- Common theme in this course, will see more complex modeling

Electrical	Thermal
Voltage, $V$ (V)	Temperature, $T$ (°C or K)
Current, $I$ (A)	Power, $P$ (W)
Resistance, $R$ ( $\Omega$ or V/A)	Thermal Resistance, $R_{th}$ (K/W)
Capacitance, $C$ (F or C/V)	Heat Capacity, $C_{th}$ (J/K)

# Resistance : Electrical vs. Thermal

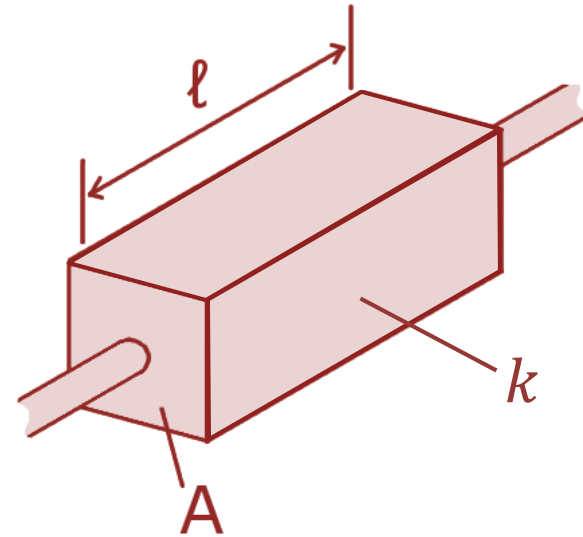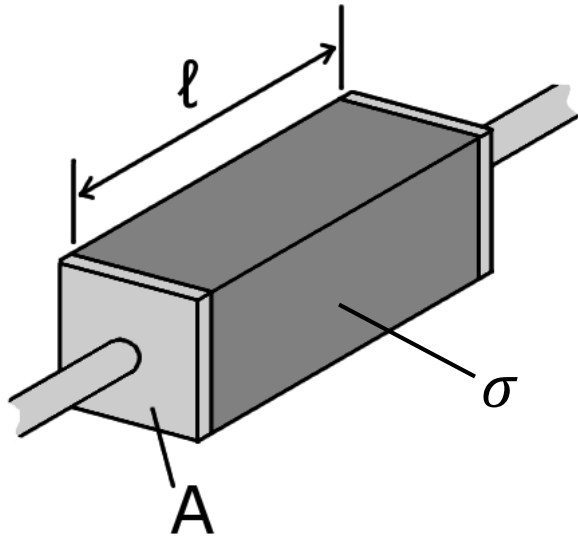

resistance ( $\Omega$ )

$$R = \frac{l}{\sigma \cdot A}$$

length (m)

conductivity ( $(\Omega \cdot m)^{-1}$ )

cross-sectional area ( $m^2$ )

thermal resistance ( $K/W$ )

$$R_{th} = \frac{l}{k \cdot A}$$


length (m)

thermal conductivity ( $\frac{W}{K \cdot m}$ )

cross-sectional area ( $m^2$ )



# Capacitance : Electrical vs. Thermal

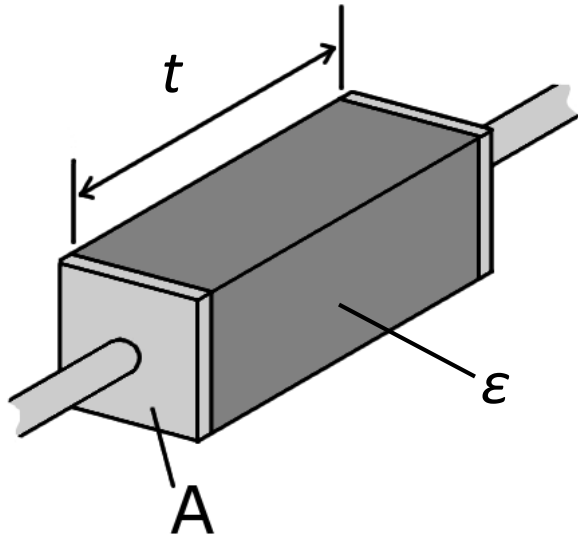


capacitance (F)

permittivity of dielectric ( $\frac{F}{m}$ )

area of plate ( $m^2$ )

thickness of dielectric (m)

$$C = \epsilon \cdot \frac{A}{t}$$

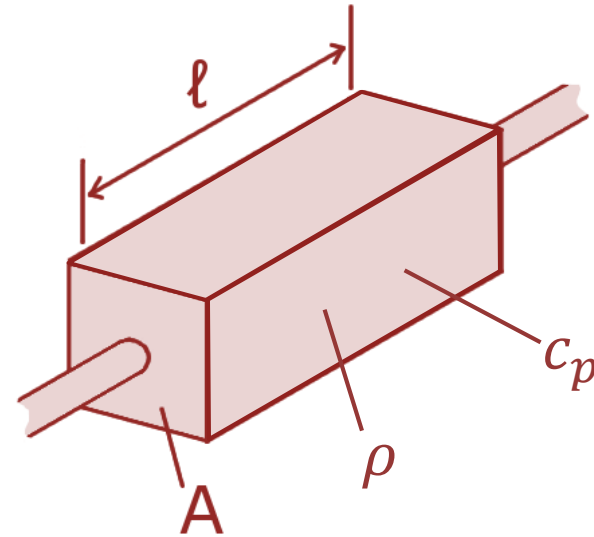

thermal capacitance ( $\frac{J}{K}$ )

length (m)


specific heat ( $\frac{J}{kg \cdot K}$ )

density ( $\frac{kg}{m^3}$ )

cross-sectional area ( $m^2$ )


$$C_{th} = \rho \cdot l \cdot A \cdot c_p$$

# Distributed Thermal Model

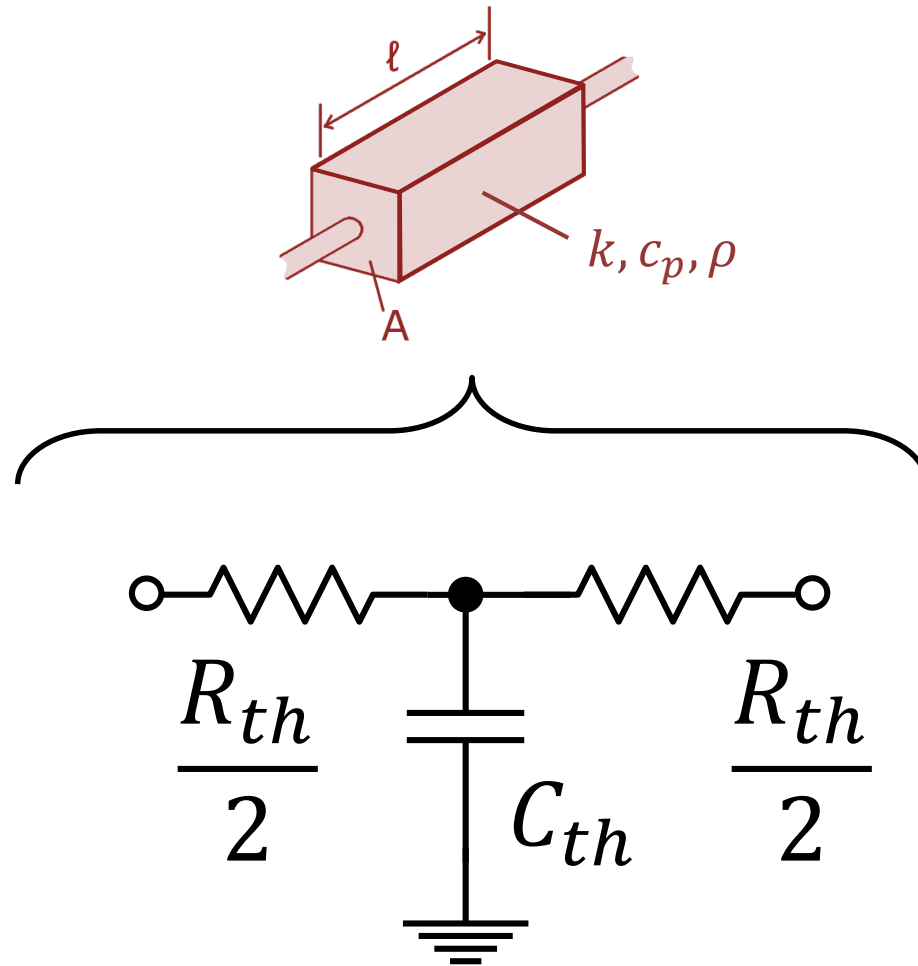

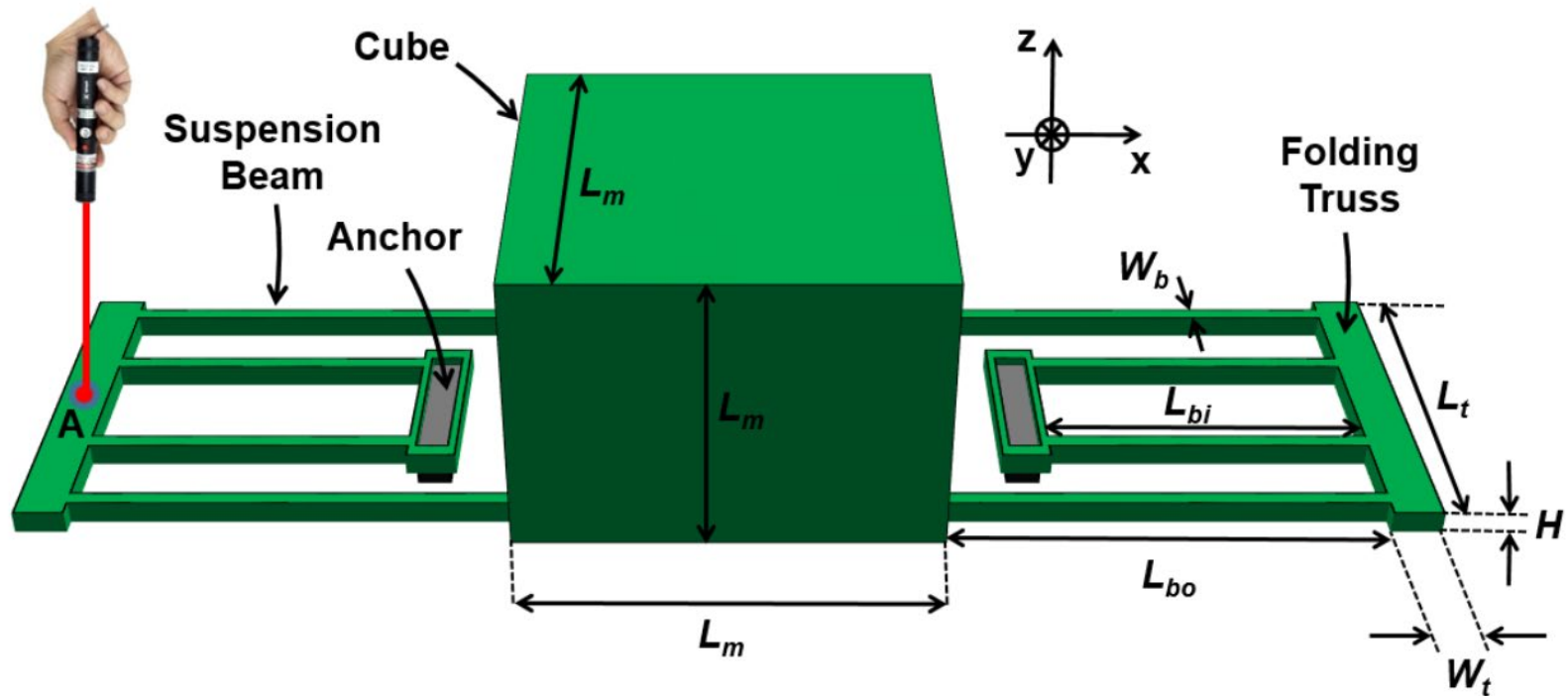
# Thermal Ckt. Example


- Draw the full thermal circuit model (include effects of laser!)
- What approximations can you make?




# Thermal Ckt. Example (cont.)

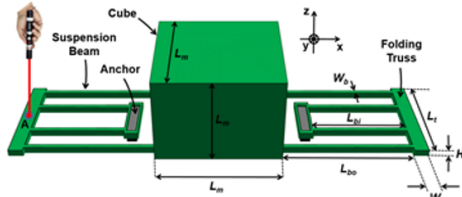

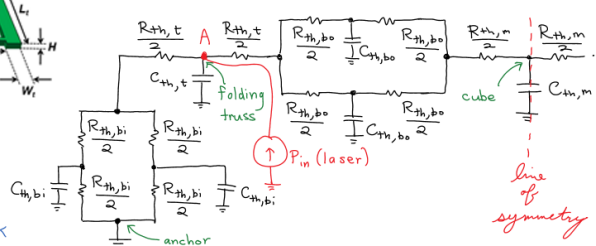Can start w/ 1/2 of thermal ckt. due to symmetry:




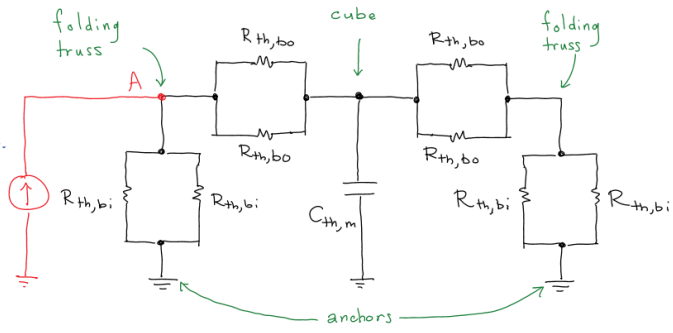applying approximations  
adding 2nd half of ckt.



further reducing parallel R's

Fully simplified final circuit:

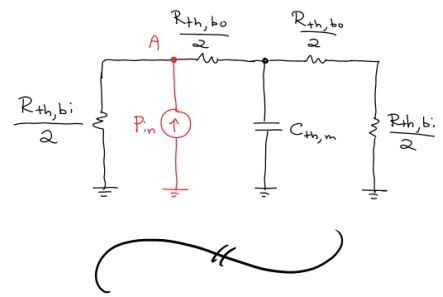

$$L_{bi} = 50 \mu\text{m} \quad L_t = 50 \mu\text{m} \quad k = 30 \text{ W/m}\cdot\text{K}$$


$$L_{bo} = 75 \mu\text{m} \quad W_t = 6 \mu\text{m} \quad c_p = 770 \text{ J/kg}\cdot\text{K}$$

$$W_b = 2 \mu\text{m} \quad L_m = 50 \mu\text{m} \quad \rho = 2,300 \text{ kg/m}^3$$

$$H = 2 \mu\text{m}$$

$$R_{th,bi} = \frac{L_{bi}}{k(W_b \cdot H)} = \frac{50 \mu\text{m}}{(30 \frac{\text{W}}{\text{m}\cdot\text{K}})(2 \mu\text{m})^2} = 4.17 \times 10^5 \text{ K/W}$$
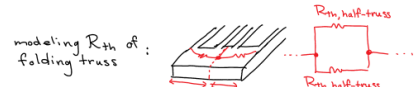
$$R_{th,bo} = \frac{L_{bo}}{k(W_b \cdot H)} = \frac{75 \mu\text{m}}{(30 \frac{\text{W}}{\text{m}\cdot\text{K}})(2 \mu\text{m})^2} = 6.25 \times 10^5 \text{ K/W}$$



$$R_{th,t} = R_{th, \text{half-truss}} \parallel R_{th, \text{half-truss}} = \frac{R_{th, \text{half-truss}}}{2}$$

$$= \frac{1}{2} \frac{L_t/2}{k(W_t \cdot H)} = \frac{(50 \mu\text{m})}{2(4)(30 \frac{\text{W}}{\text{m}\cdot\text{K}})(6 \mu\text{m})(2 \mu\text{m})}$$

$$R_{th,t} = 3.47 \times 10^4 \text{ K/W} \ll R_{th,bi}, R_{th,bo}$$

∴ can neglect  $R_{th,t}$ !

$$R_{th,m} = \frac{L_m}{k(L_m)^2} = \frac{50 \mu\text{m}}{(30 \frac{\text{W}}{\text{m}\cdot\text{K}})(50 \mu\text{m})^2} = 667 \text{ K/W}$$

∴ can also neglect  $R_{th,m}$ !

$$C_{th,bi} = \rho(L_{bi} \cdot W_b \cdot H) c_p = (2.3 \times 10^3 \frac{\text{kg}}{\text{m}^3})(50 \mu\text{m})(2 \mu\text{m})^2 (770 \text{ J/kg}\cdot\text{K})$$

$$C_{th,bi} = 3.54 \times 10^{-10} \text{ J/K}$$

$$C_{th,bo} = \rho(L_{bo} \cdot W_b \cdot H) c_p = (2.3 \times 10^3 \frac{\text{kg}}{\text{m}^3})(75 \mu\text{m})(2 \mu\text{m})^2 (770 \text{ J/kg}\cdot\text{K})$$

$$C_{th,bo} = 5.31 \times 10^{-10} \text{ J/K}$$

$$C_{th,t} = \rho(L_t \cdot W_t \cdot H) c_p = (2.3 \times 10^3 \frac{\text{kg}}{\text{m}^3})(50 \mu\text{m})(6 \mu\text{m})(2 \mu\text{m})(770 \text{ J/kg}\cdot\text{K})$$

$$C_{th,t} = 1.06 \times 10^{-9} \text{ J/K}$$

$$C_{th,m} = \rho(L_m)^3 c_p = (2.3 \times 10^3 \frac{\text{kg}}{\text{m}^3})(50 \mu\text{m})^3 (770 \text{ J/kg}\cdot\text{K})$$

$$C_{th,m} = 2.21 \times 10^{-7} \text{ J/K} \gg C_{th,bi}, C_{th,bo}, C_{th,t}$$

∴ can neglect all  $C_{th}$ 's except  $C_{th,m}$ !