

Lecture 26: Gyro Minimum Detectable Signal

- Announcements:
- HW#6 online and due Friday, 5/1, at 8 a.m.
- Project Out-Briefs Sign-Up (google) sheet shared with you; out-briefs will be on Thursday & Friday of RRR week
- Final Exam info sheet today
  - ↳ Will also be online with some sample exams
- Course wrap up
- Course evaluations
- -----
- Reading: Senturia Chpt. 16
- Lecture Topics:
  - ↳ Minimum Detectable Signal
  - ↳ Noise
    - Circuit Noise Calculations
    - Noise Sources
    - Equivalent Input-Referred Noise
  - ↳ Gyro MDS
    - Example ARW Determination
- -----
- Last Time:
- Started example angle random walk (ARW) determination
- Now continue with this ...

Gyroscope Drive-to-Sense Xfer Fcn

**Drive Mode**  
 $\dot{x}_d = \omega_d x_d$   
 Driven Velocity

**Sense Mode**  
 $\dot{x}_s = \omega_s x_s$   
 Sense Velocity

**Rotation-Induced Coriolis Force:**  
 $\vec{a}_c = 2\vec{\dot{x}}_d \times \vec{\Omega}$

$\vec{a}_c = 2\omega_d \dot{x}_d \Omega \sin 90^\circ$   
 acts in the sense mode direction

$a_s = a_c = 2\omega_d \dot{x}_d \Omega \sin 90^\circ$

$a_s = 2\omega_d \dot{x}_d \Omega$   
 (rotation rate (what we want to measure))

drive radian frequency  
 drive displacement amplitude

$F_c = m a_s = m a_c$   
 Coriolis Force

**Drive/Sense Response Spectra:**  
 Amplitude vs  $\omega$   
 Drive Response (black curve)  
 Sense Response (blue curve)  
 Resonance frequency  $f_0$  (@  $T_1$ )

**Determine MDS**

Noise Sources

$$\vec{F}_c = m\vec{a}_c = m \cdot (2\dot{\vec{x}}_d \times \vec{\Omega})$$

Gyro Sense Element Output Circuit      Signal Conditioning Circuit (Transresistance Amplifier)

① Determine  $\overline{N_{on}}^2$ :  
 ⇒ use superposition (handle one source at a time)

large "virtual ground" due to neg. FB:  $N_i = 0$

$N_{o1} = i_{ia} R_f \rightarrow \overline{N_{o1}}^2 = i_{ia}^2 R_f^2$   
 (ignore the "-" sign, since it doesn't matter for noise)

$N_{o2} = i_f R_f \rightarrow \overline{N_{o2}}^2 = i_f^2 R_f^2 = \frac{4kT}{R_f} R_f^2 = 4kTR_f \Delta f$

$\overline{N_{ia}}^2$ :

⇒ unity gain buffer  
 $N_{o3} = N_{ia} \rightarrow \overline{N_{o3}}^2 = \overline{N_{ia}}^2$

$\overline{f_{rx}}^2$ :  $N_{o4} = i_e \eta_e R_f = \frac{f_{rx}}{r_x} \odot (j\omega_d) \eta_e R_f$   
 $\left[ i_e = \frac{f_{rx}}{r_x} \odot (j\omega_d) \right]$  drive freq.

$\overline{N_{o4}}^2 = \frac{\overline{f_{rx}}^2}{r_x^2} \odot | \odot (j\omega_d) |^2 \eta_e^2 R_f^2$   
 $\left[ \overline{f_{rx}}^2 = 4kTr_x \Delta f \right] \Rightarrow \overline{N_{o4}}^2 = 4kT \odot | \odot (j\omega_d) |^2 \eta_e^2 \frac{R_f^2}{r_x}$

$\therefore \overline{N_{on}}^2 = \overline{N_{ia}}^2 R_f^2 + \overline{N_{io}}^2 + 4kTR_f \left( 1 + \eta_e^2 \odot | \odot (j\omega_d) |^2 \frac{R_f}{r_x} \right) \Delta f$

Get from the op amp data sheet.

Total Output Mean-Square Voltage Noise

② Get the scale factor, i.e., find  $N_0$  in terms of rotation rate  $\Omega$ :

Noise Sources

$\vec{F}_c = m\vec{a}_c = m \cdot (2\dot{\vec{x}}_d \times \vec{\Omega})$

Gyro Sense Element Output Circuit

Signal Conditioning Circuit (Transresistance Amplifier)

$\Rightarrow$  Find the rotation-to- $i_o$  transfer function:

$$\dot{x}_s = F_c \left( \frac{1}{r_x} \mathcal{H}_s(j\omega_d) \right) = \frac{\omega_s Q_s \cdot 2\omega_d r_x \Omega_m}{k_s} \mathcal{H}_s(j\omega_d)$$

$[F_c = m a_c = 2\omega_d r_x \Omega_m] \left[ \frac{1}{r_x} = \frac{\omega_s Q_s}{k_s} \right] \left[ \frac{1}{k_s} = \frac{1}{\omega_s^2} \right]$

$$\dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s r_x \mathcal{H}_s(j\omega_d) \cdot \Omega$$

$\mathcal{H}(s) = \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2}$

$s=0: \mathcal{H}(0) = 0$

$s=j\omega_0: \mathcal{H}(j\omega_0) = 1$

$s=\infty: \mathcal{H}(\infty) = 0$

5

$$i_o = \eta_e \dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s r_x \eta_e \mathcal{H}_s(j\omega_d) \cdot \Omega$$

rotation rate

$$\therefore |N_0| = i_o R_f = 2 R_f \frac{\omega_d}{\omega_s} Q_s r_x \eta_e \mathcal{H}_s(j\omega_d) \cdot \Omega$$

$A \triangleq \text{scale factor} \rightarrow |N_0| = A \Omega$

③  $\Omega = \Omega_{\min}$  when  $|N_0| = \sqrt{N_{0n}^2}$

$\uparrow$  rms noise voltage

minimum detectable rotation rate (MDS)

$$2 R_f \frac{\omega_d}{\omega_s} Q_s r_x \eta_e \mathcal{H}_s(j\omega_d) \cdot \Omega_{\min} = \sqrt{N_{0n}^2}$$

$$\sqrt{1_{ia}^2 R_f^2 + N_{io}^2 + 4kTR_f(1 + \eta_e^2 |\mathcal{H}_s(j\omega_d)|^2 \frac{R_f}{r_x}) \Delta f}$$

Solve for  $\Omega_{\min}$ :

$$\Omega_{\min} = \frac{\sqrt{1_{ia}^2 R_f^2 + N_{io}^2 + 4kTR_f(1 + \eta_e^2 |\mathcal{H}_s(j\omega_d)|^2 \frac{R_f}{r_x}) \Delta f}}{2 R_f \frac{\omega_d}{\omega_s} Q_s r_x \eta_e \mathcal{H}_s(j\omega_d)}$$

Often most interested in spectral density:

$$\sqrt{\frac{\Omega_{\min}^2}{\Delta f}} = \Omega_{\min} \times \left( \frac{1}{\sqrt{\Delta f}} \right) \left( \frac{3600 s}{hr} \right) \left( \frac{180^\circ}{\pi} \right) \rightarrow [(\%hr)/\sqrt{Hz}]$$

\*

6

↓ \*

Angle Random Walk (ARW) =  $\frac{1}{60} \Omega_{\text{max}} \left[ \frac{\circ}{\sqrt{\text{hr}}} \right]$

↓  
Easier to determine directional error as a function of elapsed time.

- Go through Module 17, slides 36-49.