



# EE C247B - ME C218 Introduction to MEMS Design Fall 2020

Prof. Clark T.-C. Nguyen

Dept. of Electrical Engineering & Computer Sciences  
University of California at Berkeley  
Berkeley, CA 94720

## Module 17: Noise & MDS

EEC247B/MEC218: Introduction to MEMS Design

LecM 17

C. Nguyen

11/18/08

1

1



## Lecture Outline

- Reading: Senturia Chpt. 16
- Lecture Topics:
  - ↳ Minimum Detectable Signal
  - ↳ Noise
    - Circuit Noise Calculations
    - Noise Sources
    - Equivalent Input-Referred Noise
  - ↳ Gyro MDS
    - Equivalent Noise Circuit
    - Example ARW Determination

EEC247B/MEC218: Introduction to MEMS Design


LecM 17

C. Nguyen


11/18/08

2

2

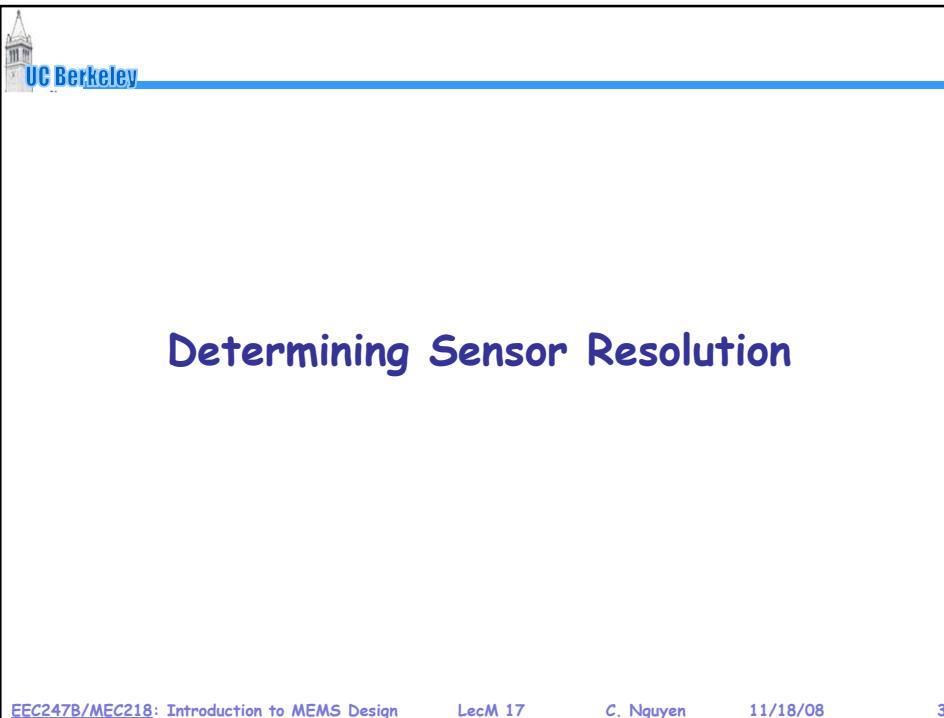

3

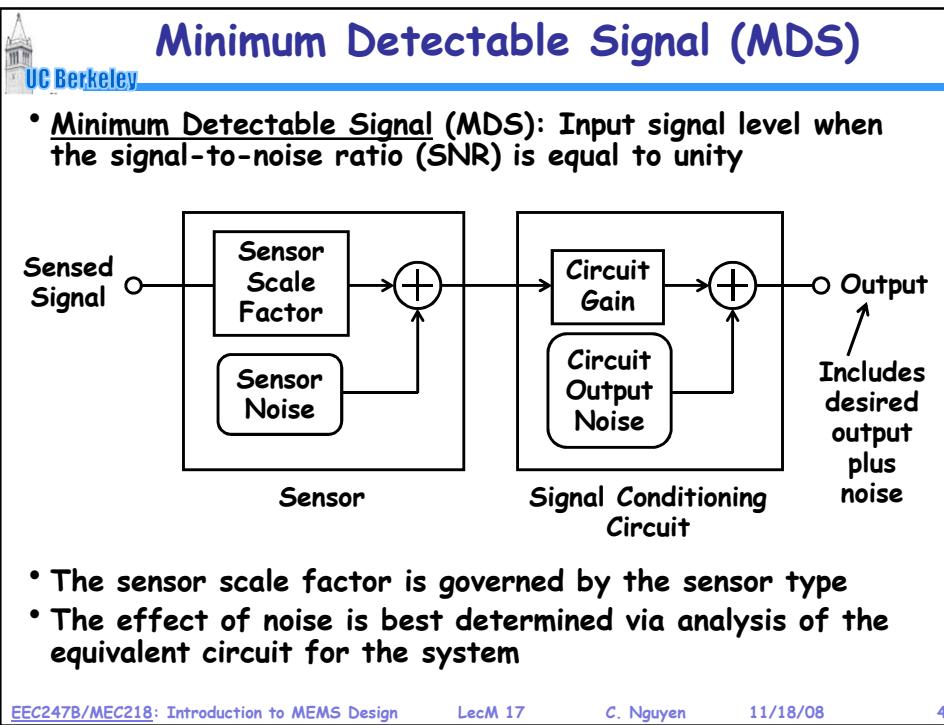

4




## Noise



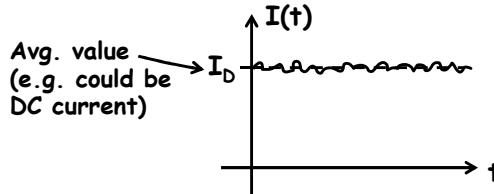
## Noise

- **Noise:** Random fluctuation of a given parameter  $I(t)$
- In addition, a noise waveform has a zero average value
  - We can't handle noise at instantaneous times
  - But we can handle some of the averaged effects of random fluctuations by giving noise a power spectral density representation
  - Thus, represent noise by its mean-square value:




$$\text{Let } i(t) = I(t) - I_D$$

$$\text{Then } \overline{i^2} = \overline{(I - I_D)^2} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T |I - I_D|^2 dt$$

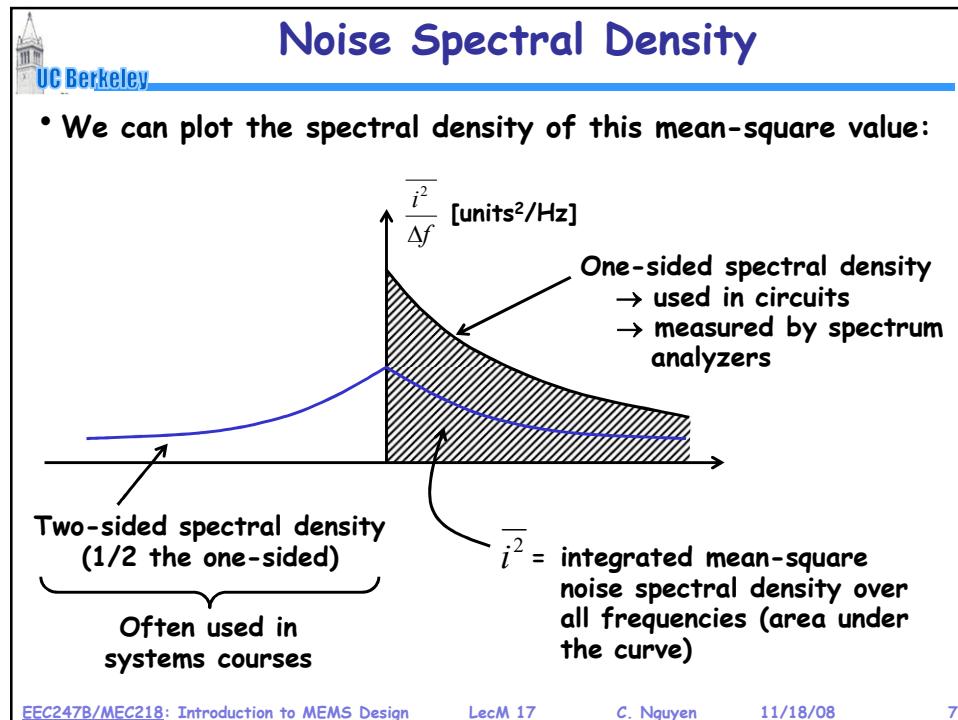

7

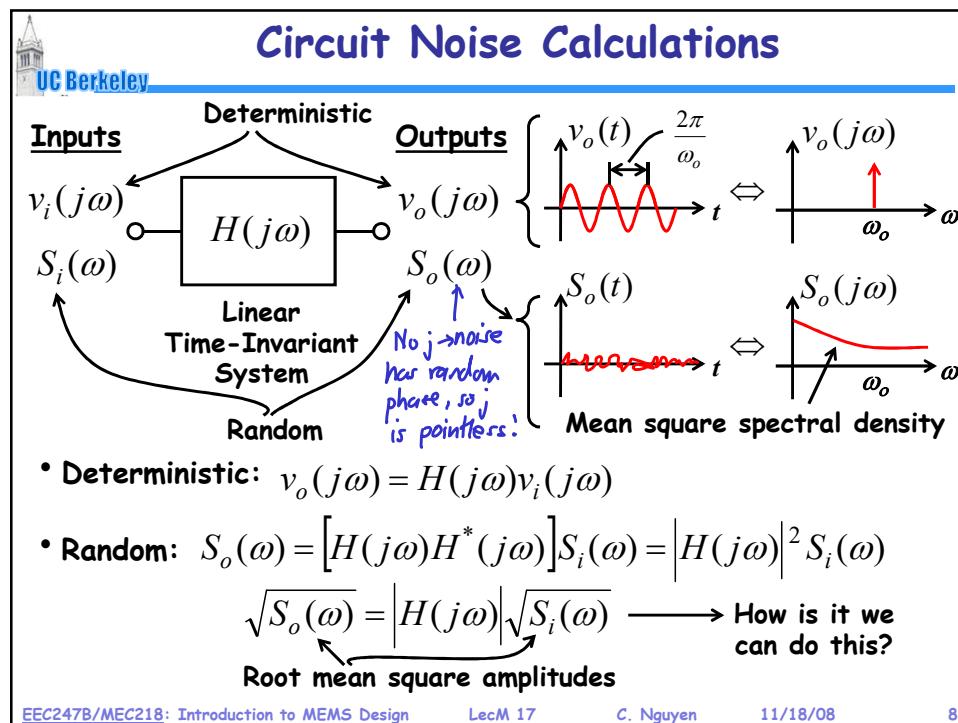

8

## Handling Noise Deterministically

**UC Berkeley**

- Can do this for noise in a tiny bandwidth (e.g., 1 Hz)

$\frac{v_{n1}^2}{\Delta f} = S_1(f) \rightarrow v_{n1} = \sqrt{S_1(f) \cdot B}$  → Can approximate this by a sinusoidal voltage generator (especially for small B, say 1 Hz)

$S_n(j\omega)$

$v_o(t) \sim |A| \cos \omega_o t$

$\tau \sim \frac{1}{B}$

[This is actually the principle by which oscillators work → oscillators are just noise going through a tiny bandwidth filter]

Why? Neither the amplitude nor the phase of a signal can change appreciably within a time period  $1/B$ .

EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    9

9

## Systematic Noise Calculation Procedure

**UC Berkeley**

General Circuit With Several Noise Sources

$H_2(j\omega)$

$H_5(j\omega)$

$H_1(j\omega)$

$v_{n2}^2$

$v_{n3}^2$

$i_{n5}^2$

$i_{n1}^2$

$i_{n4}^2$

$v_{n6}^2$

$v_{on}^2$

- Assume noise sources are uncorrelated
- 1. For  $i_{n1}^2$ , replace w/ a deterministic source of value

$$i_{n1} = \sqrt{\frac{i_{n1}^2}{\Delta f}} \cdot (1 \text{ Hz})$$

EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    10

10

## Systematic Noise Calculation Procedure



2. Calculate  $v_{on1}(\omega) = i_{n1}(\omega)H(j\omega)$  (treating it like a deterministic signal)
3. Determine  $v_{on1}^2 = i_{n1}^2 \cdot |H(j\omega)|^2$
4. Repeat for each noise source:  $i_{n1}^2, v_{n2}^2, v_{n3}^2$
5. Add noise power (mean square values)

$$\overline{v_{onTOT}^2} = \overline{v_{on1}^2} + \overline{v_{on2}^2} + \overline{v_{on3}^2} + \overline{v_{on4}^2} + \dots$$

$$v_{onTOT} = \sqrt{\overline{v_{on1}^2} + \overline{v_{on2}^2} + \overline{v_{on3}^2} + \overline{v_{on4}^2} + \dots}$$

Total rms value



## Noise Sources

## Thermal Noise

**UC Berkeley**

- **Thermal Noise in Electronics:** (Johnson noise, Nyquist noise)
  - ↳ Produced as a result of the thermally excited random motion of free e's in a conducting medium
  - ↳ Path of e's randomly oriented due to collisions
- **Thermal Noise in Mechanics:** (Brownian motion noise)
  - ↳ Thermal noise is associated with all dissipative processes that couple to the thermal domain
  - ↳ Any damping generates thermal noise, including gas damping, internal losses, etc.
- **Properties:**
  - ↳ Thermal noise is white (i.e., constant w/ frequency)
  - ↳ Proportional to temperature
  - ↳ Not associated with current
  - ↳ Present in any real physical resistor

EEC247B/MEC218: Introduction to MEMS Design      LecM 17      C. Nguyen      11/18/08      13

13

## Circuit Representation of Thermal Noise

**UC Berkeley**

- Thermal Noise can be shown to be represented by a series voltage generator  $\overline{v_R^2}$  or a shunt current generator  $\overline{i_R^2}$

Note: These are one-sided mean-square spectral densities! To make them 2-sided, must divide by 2.

$$\frac{\overline{i_R^2}}{\Delta f} = \frac{4kT}{R}$$

$$\frac{\overline{v_R^2}}{\Delta f} = 4kTR$$

where  $4kT = 1.66 \times 10^{-20} V \cdot C$   
 and where these are spectral densities.

EEC247B/MEC218: Introduction to MEMS Design      LecM 17      C. Nguyen      11/18/08      14

14

## Noise in Capacitors and Inductors?

UC Berkeley

- Resistors generate thermal noise
- Capacitors and inductors are noiseless → why?

Now, add a resistor:

Need to add a forcing function, like a noise voltage  $v_R^2$  to keep the motion going → and this noise source is associated with R

EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    15

15

## Why $4kT\Delta f$ ?

UC Berkeley

- Why is  $\overline{v_R^2} = 4kT\Delta f$  (a heuristic argument)
- The Equipartition Theorem of Statistical Thermodynamics says that there is a mean energy  $(1/2)kT$  associated w/ each degree of freedom in a given system
- An electronic circuit possesses two degrees of freedom:
  - ↳ Current,  $i$ , and voltage,  $v$
  - ↳ Thus, we can write:
$$\frac{1}{2}Li^2 = \frac{1}{2}k_B T \quad , \quad \underbrace{\frac{1}{2}Cv^2}_{\text{Energy}} = \frac{1}{2}k_B T$$
- Similar expressions can be written for mechanical systems
  - ↳ For example: for displacement,  $x$
$$\text{Spring constant } \frac{1}{2}kx^2 = \frac{1}{2}k_B T$$


EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    16

16
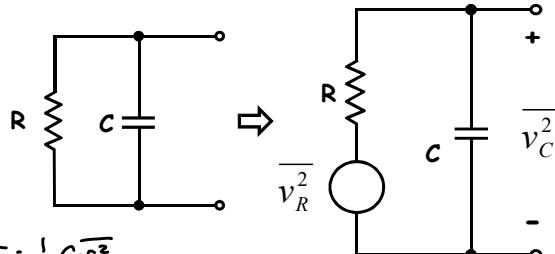
## Why $4kT\Delta f$ ? (cont)



- Why is  $\overline{v_R^2} = 4kT\Delta f$ ? (a heuristic argument)
- Consider an RC circuit:



$$E = \frac{1}{2} kT = \frac{1}{2} C \overline{v_c^2}$$

$$\therefore \overline{v_c^2} = \frac{kT}{C}$$

$\leftarrow$  integrated noise over all freqs.  
 (total mean square voltage integrated over all freqs.)

Question: What value of  $\frac{\overline{v_R^2}}{\Delta f}$  (assuming white noise) gives us this?

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 17

17

## Why $4kT\Delta f$ ? (cont)




Question: What value of  $\frac{\overline{v_R^2}}{\Delta f}$  (assuming white noise) gives us  $\overline{v_c^2} = \frac{kT}{C}$ ?

$$\overline{v_c^2} = \int_0^\infty \left| \frac{1}{1+j\omega RC} \right|^2 \frac{\overline{v_R^2}}{\Delta f} d\omega$$

[noise is white]  $\rightarrow = \frac{1}{2\pi} \frac{\overline{v_R^2}}{\Delta f} \int_0^\infty \frac{\omega_b^2}{\omega_b^2 + \omega^2} d\omega$

$\left[ \int \frac{dx}{x^2+a^2} = \frac{1}{a} \tan^{-1}\left(\frac{x}{a}\right) \right]$

$$= \frac{1}{2\pi} \frac{\overline{v_R^2}}{\Delta f} \frac{\omega_b^2}{\omega_b} \tan^{-1}\left(\frac{\omega}{\omega_b}\right) \Big|_0^\infty = \frac{1}{2\pi} \frac{\overline{v_R^2}}{\Delta f} \left( \frac{\pi}{2} - 0 \right)$$
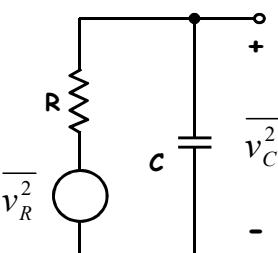
$$= \frac{1}{4} \omega_b \frac{\overline{v_R^2}}{\Delta f} = \frac{kT}{C} \rightarrow \frac{\overline{v_R^2}}{\Delta f} = 4kT \left( \frac{C}{\omega_b} \right) \Rightarrow \boxed{\frac{\overline{v_R^2}}{\Delta f} = 4kT R}$$


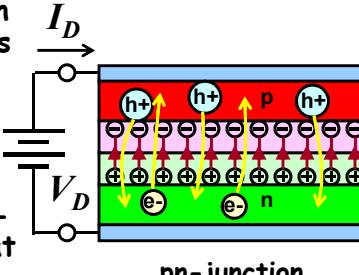
EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 18

18

## Shot Noise

**UC Berkeley**

- Associated with direct current flow in diodes and bipolar junction transistors
- Arises from the random nature by which e<sup>-</sup>'s and h<sup>+</sup>'s surmount the potential barrier at a pn junction
- The DC current in a forward-biased diode is composed of h<sup>+</sup>'s from the p-region and e<sup>-</sup>'s from the n-region that have sufficient energy to overcome the potential barrier at the junction  
 → noise process should be proportional to DC current
- Attributes:**
  - Related to DC current over a barrier
  - Independent of temperature
  - White (i.e., const. w/ frequency)
  - Noise power  $\sim I_D$  & bandwidth



$$\frac{\overline{i_n^2}}{\Delta f} = 2qI_D$$

Charge on an e<sup>-</sup>  
 $(=1.6 \times 10^{-19} C)$

DC Current


EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    19

19

## Flicker (1/f) Noise

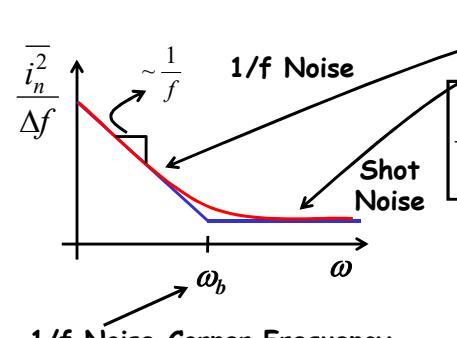**UC Berkeley**

- In general, associated w/ random trapping & release of carriers from "slow" states
- Time constant associated with this process gives rise to a noise signal w/ energy concentrated at low frequencies
- Often, get a mean-square noise spectral density that looks like this:



$$\frac{\overline{i_n^2}}{\Delta f} = 2qI_D + K\left(\frac{I_D^a}{f^b}\right)$$

$I_D$  = DC current  
 $K$  = const. for a particular device  
 $a = 0.5 \rightarrow 2$   
 $b \sim 1$

EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    20

20

**Example: Typical Noise Numbers**

UC Berkeley

- Hookup the circuit below and make some measurements

Measure w/ AC voltmeter  
 Measure w/ spectrum analyzer  
 Get Gaussian amplitude distribution

Probability

Amplitude

68% within  $\pm \sigma$   
 99.7% within  $\pm 3\sigma$

$\frac{N_R^2}{\Delta f} = 4kT$

$\frac{1}{2\pi RC}$

$\sqrt{(1.66 \times 10^{-10})(1k)}$

$\frac{1k\Omega}{1pF} \cdot \sqrt{\frac{kT}{C}} = 64 \mu V \text{ rms}$

EEC247B/MEC218: Introduction to MEMS Design      LecM 17      C. Nguyen      11/18/08      21

21

**Example: Typical Noise Numbers**

UC Berkeley

- Hookup the circuit below and make some measurements

Measure w/ AC voltmeter  
 Measure w/ spectrum analyzer

AC Voltmeter

$$\sqrt{N_o^2} = (100)(64 \mu V \text{ rms}) = 6.4 mV \text{ rms}$$

Spectrum Analyzer

$$\frac{1}{(2\pi)(1k)(1p)} = 60 \text{ MHz}$$


400 nV/V $\sqrt{\text{Hz}}$

20 dB/dec


one-sided spectral density

EEC247B/MEC218: Introduction to MEMS Design      LecM 17      C. Nguyen      11/18/08      22


22

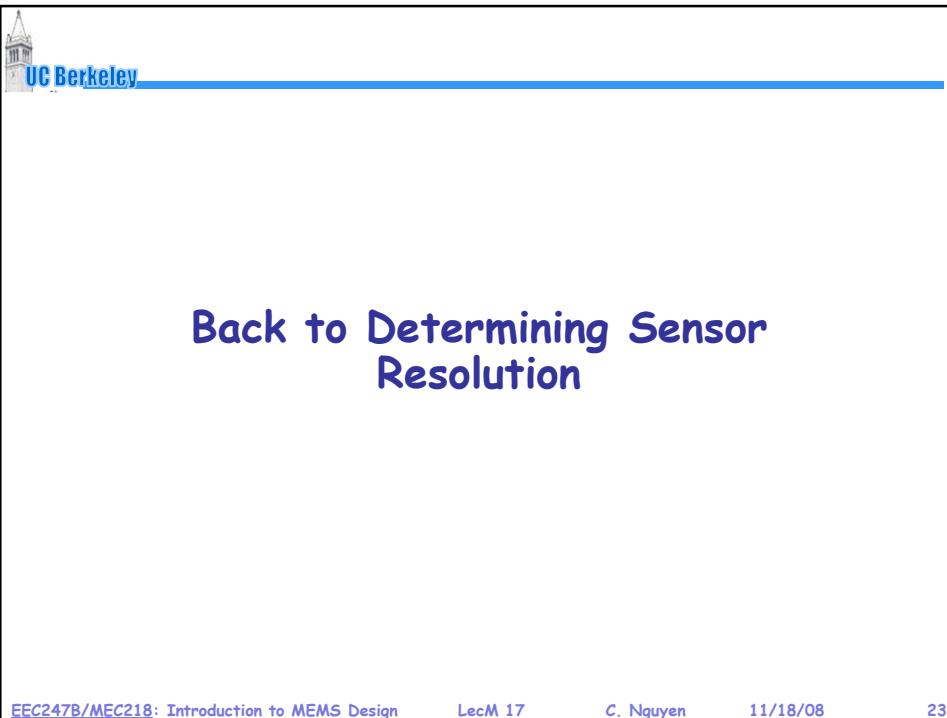


23

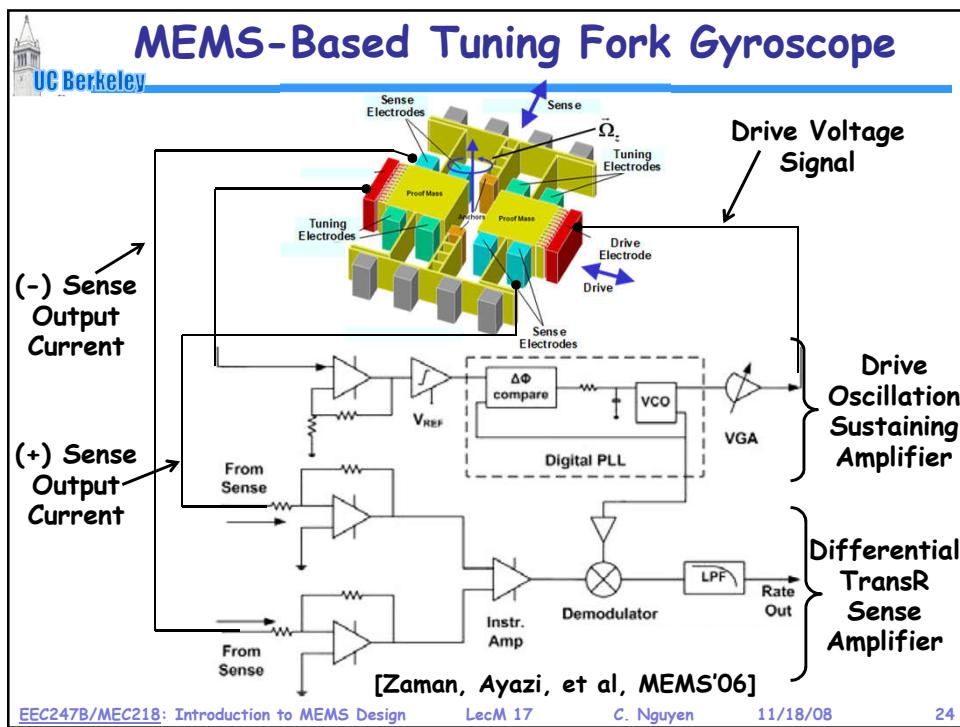


24

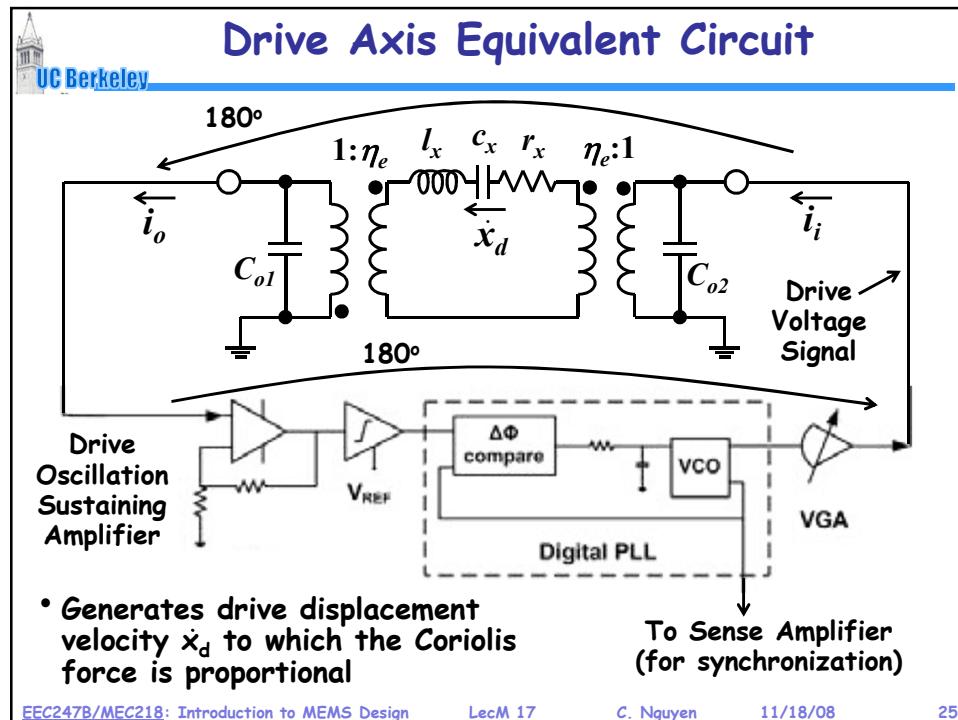


25

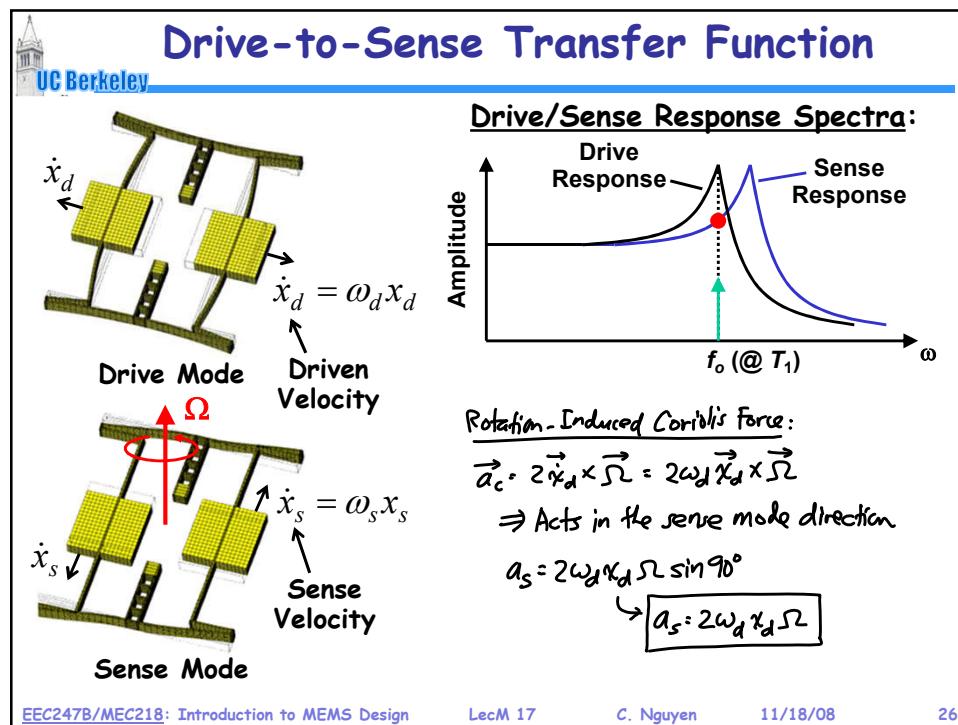

26

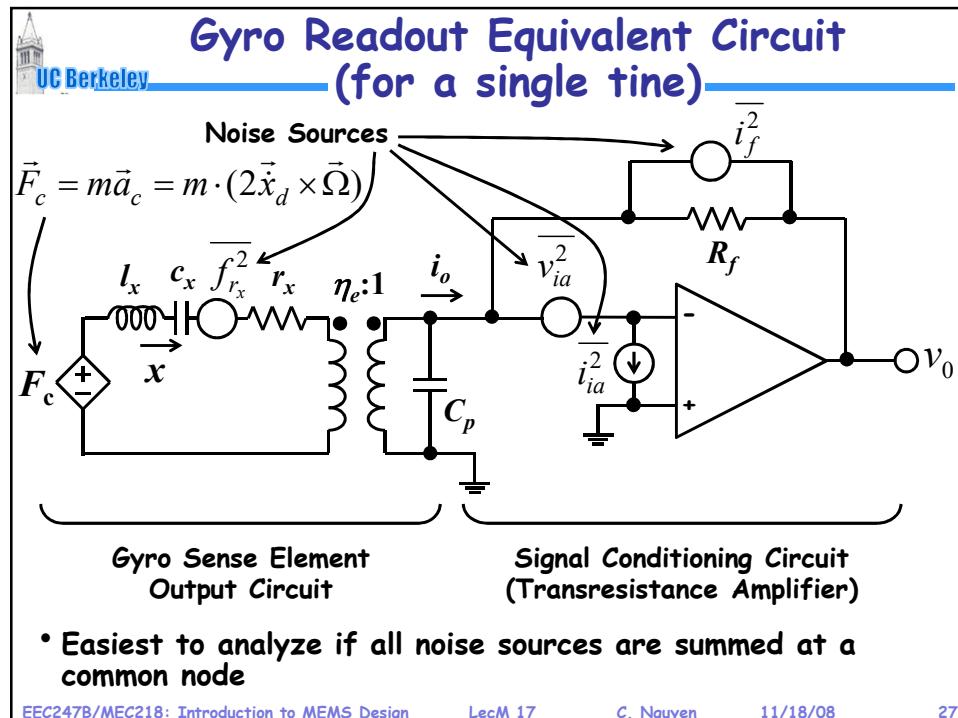

27

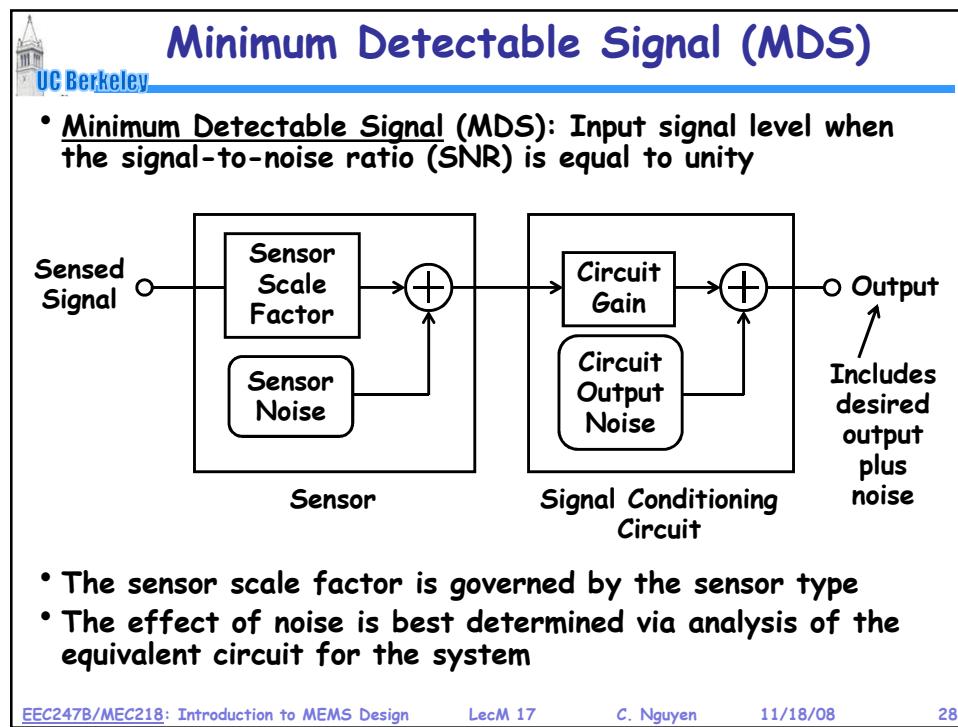


28
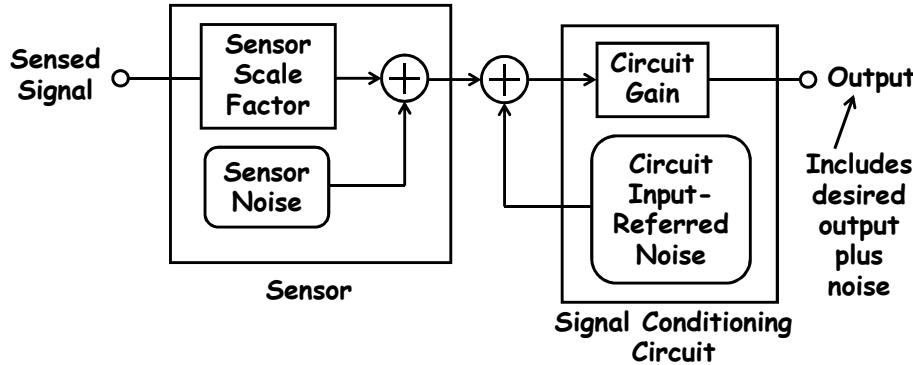
## Move Noise Sources to a Common Point



- Move noise sources so that all sum at the input to the amplifier circuit (i.e., at the output of the sense element)
- Then, can compare the output of the sensed signal directly to the noise at this node to get the MDS




## Equivalent Input-Referred Voltage and Current Noise Sources
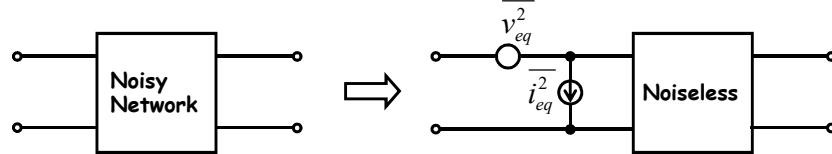
## Equivalent Input $v$ , $i$ Noise Generators



- Take a noisy 2-port network and represent it by a noiseless network with input  $v$  and  $i$  noise generators that generate the same total output noise



- Remarks:


- Works for linear time-invariant networks
- $v_{eq}$  and  $i_{eq}$  are generally correlated (since they are derived from the same sources)
- In many practical circuits, one of  $v_{eq}$  and  $i_{eq}$  dominates, which removes the need to address correlation
- If correlation is important → easier to return to original network with internal noise sources

## Calculation of $\overline{v_{eq}^2}$ and $\overline{i_{eq}^2}$




a) To get  $\overline{v_{eq}^2}$  for a two-port:

Case I

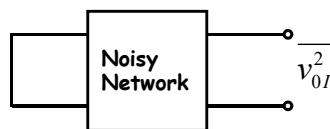

Case II

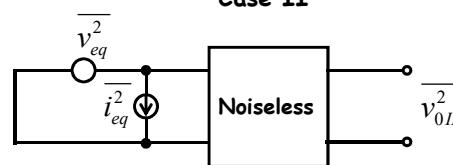

1) Short input, find  $\overline{v_{0I}^2}$  (or  $\overline{i_{0I}^2}$ )

2) For eq. network, short input, find  $\overline{v_{0II}^2}$  (or  $\overline{i_{0II}^2}$ )

$$f\left(\overline{v_{eq}^2}\right) \quad f\left(\overline{v_{eq}^2}\right)$$

3) Set  $\overline{v_{0I}^2} = \overline{v_{0II}^2} \rightarrow$  solve for  $\overline{v_{eq}^2}$  (or  $\overline{i_{0I}^2} = \overline{i_{0II}^2}$ )

**Calculation of  $\overline{v_{eq}^2}$  and  $\overline{i_{eq}^2}$  (cont)**

b) To get  $\overline{i_{eq}^2}$  for a 2-port:

1) Open input, find  $\overline{v_{0I}^2}$  (or  $\overline{i_{0I}^2}$ )  
 2) Open input for eq. circuit, find  $\overline{v_{0II}^2}$  (or  $\overline{i_{0II}^2}$ )  
 3) Set  $\overline{v_{0I}^2} = \overline{v_{0II}^2}(\overline{i_{eq}^2}) \rightarrow \text{solve for } \overline{i_{eq}^2} (\text{or } \overline{i_{0I}^2} = \overline{i_{0II}^2}(\overline{i_{eq}^2}))$

- Once the equivalent input-referred noise generators are found, noise calculations become straightforward as long as the noise generators can be treated as uncorrelated

EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    33

33

**Cases Where Correlation Is Not Important**

There are two common cases where correlation can be ignored:

- Source resistance  $R_s$  is **small** compared to input resistance  $R_i \rightarrow$  i.e., voltage source input
- Source resistance  $R_s$  is **large** compared to input resistance  $R_i \rightarrow$  i.e., current source input

1)  $R_s$  = small (ideally = 0 for an ideal voltage source):

$\overline{i_{eq}^2}$  Current shorted out!

.. For  $R_s$  small,  $\overline{i_{eq}^2}$  can be neglected  $\rightarrow$  only  $\overline{v_{eq}^2}$  is important!  
 (Thus, we need not deal with correlation)

EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    34

34

### Cases Where Correlation Is Not Important

**UC Berkeley**

2)  $R_s = \text{large}$  (Ideally =  $\infty$  for an ideal current source)

$$v_i = \frac{R_{in}}{\infty + R_{in}} v_{eq}^2 = 0!$$

$\therefore$  For  $R_s = \text{large}$ ,  $v_{eq}^2$  can be neglected!  
 → only  $i_{eq}^2$  is important!

(... and again, we need not deal with correlation)

EEC247B/MEC218: Introduction to MEMS Design

LecM 17

C. Nguyen

11/18/08

35

35

### Example: TransR Amplifier Noise

**UC Berkeley**

Input-referred current noise:  
 Open inputs; equate output voltage noise.

Case I:  
 $N_{OI} = i_{ia}^2 R_f$   
 $N_{OII} = i_f^2 R_f$   
 $N_{OI3} = N_{ia} \sqrt{i_{ia}^2 + i_f^2 R_f^2}$

Case II:  
 $N_{OI}^2 = i_{eq}^2 R_f^2 + i_f^2 R_f^2 + N_{ia}^2$   
 $N_{OII}^2 = i_{eq}^2 R_f^2$

$i_{eq}^2 = i_{ia}^2 + i_f^2 + \frac{N_{ia}^2}{R_f^2}$

EEC247B/MEC218: Introduction to MEMS Design


LecM 17

C. Nguyen


11/18/08

36


36

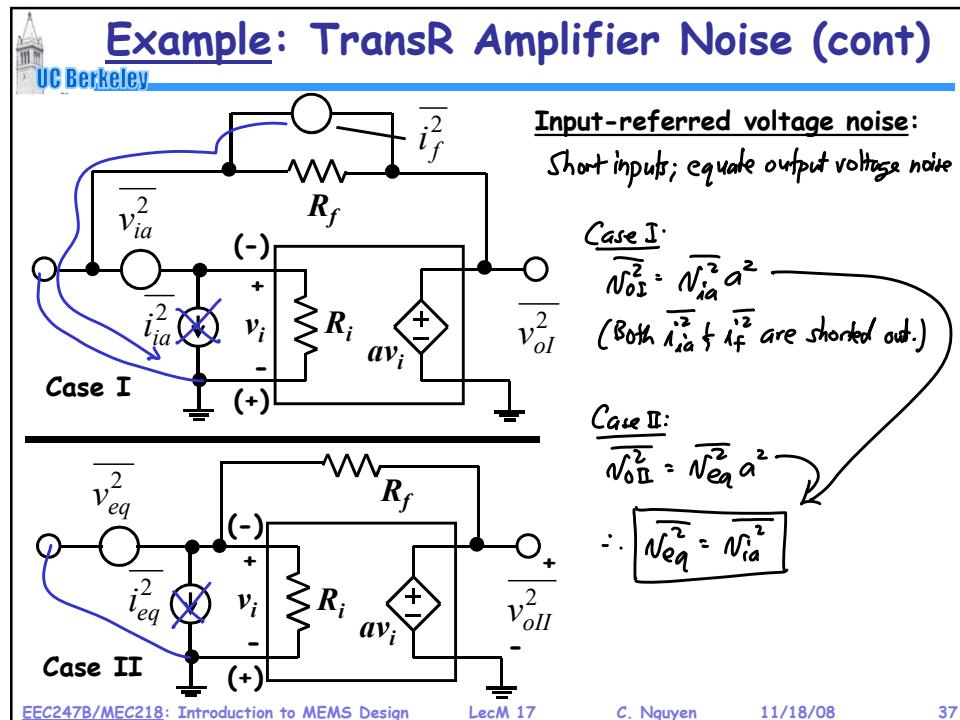


37

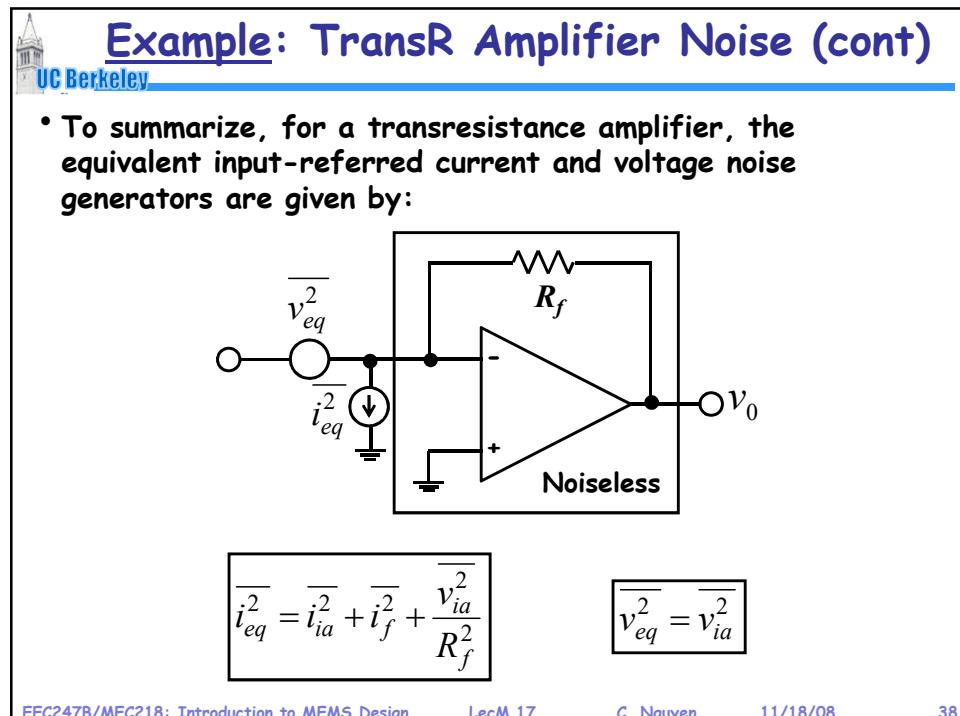

38

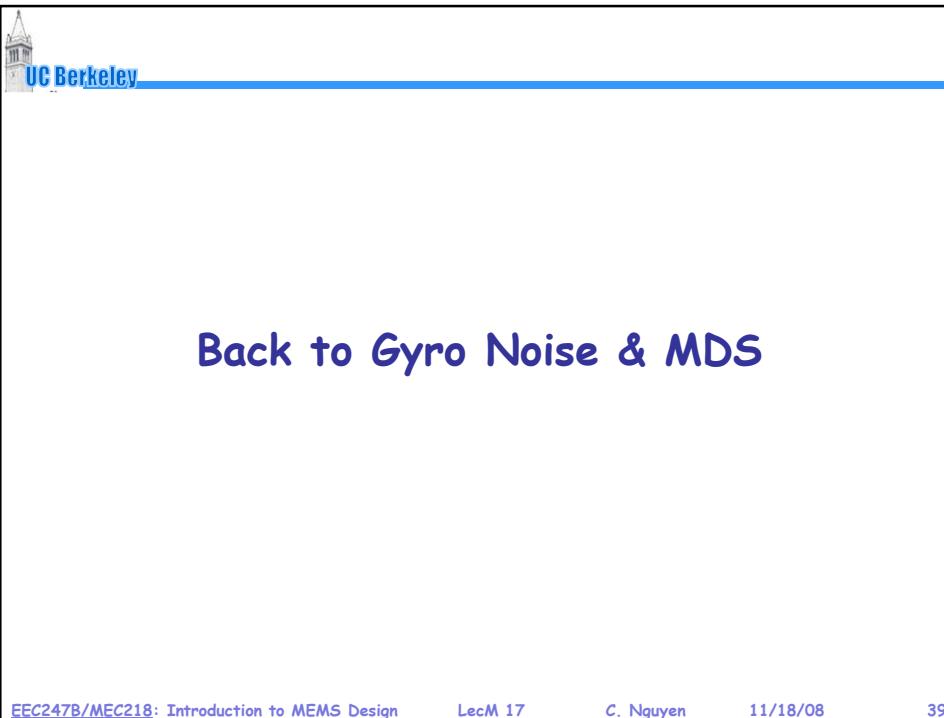

39

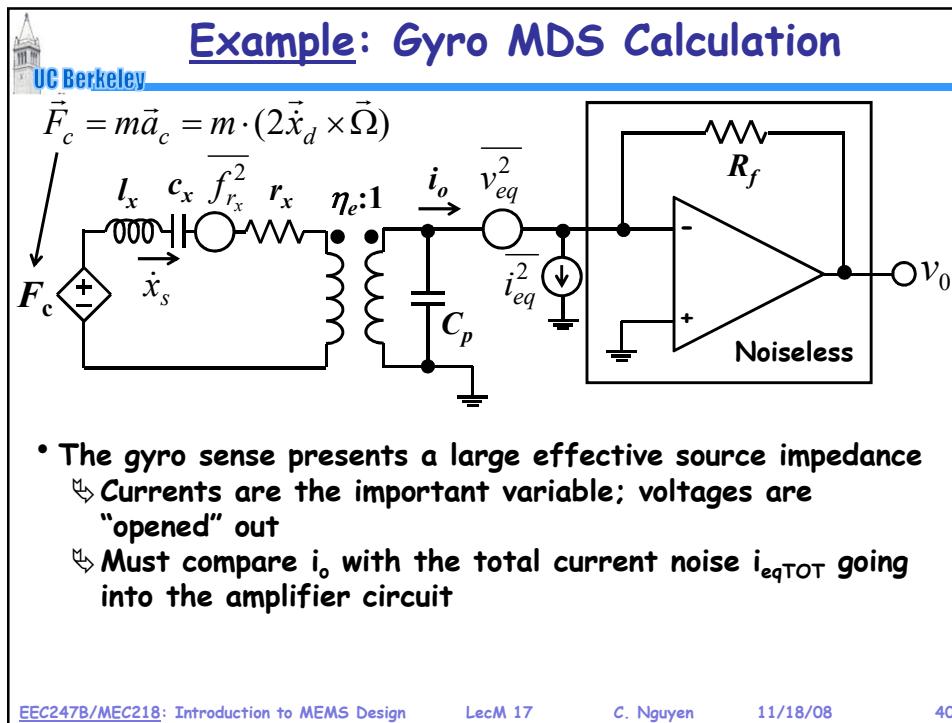

40

**Example: Gyro MDS Calculation (cont)**

$$F_c = m \vec{a}_c = m \cdot (2 \vec{x}_d \times \vec{\Omega})$$

$$\dot{x}_s = \frac{i_o}{\eta_e : 1}$$

$$i_o = \eta_e \dot{x}_s$$

$$v_{eq}^2 = \frac{r_x}{l_x + r_x} i_o^2$$

$$i_{eq}^2 = \frac{v_{eq}^2}{C_p}$$

$$v_0 = -R_f i_{eq}^2$$

• First, find the rotation to  $i_o$  transfer function:

$$\dot{x}_s = \frac{\omega_s Q_s H_s(j\omega_d)}{k_s} F_s = \frac{\omega_s Q_s \cdot 2\omega_d \chi_d \zeta_m}{k_s} H_s(j\omega_d)$$

$$[F_s = F_c = 2\omega_d \chi_d \zeta_m]$$

$$\dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s \chi_d H_s(j\omega_d) \cdot \zeta_m$$

**Example: Gyro MDS Calculation (cont)**

$$i_o = \eta_e \dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s \chi_d H_s(j\omega_d) \cdot \zeta_m \rightarrow i_o = A \zeta_m$$

$$A \equiv \text{scale factor}$$

$$A = 2 \frac{\omega_d}{\omega_s} Q_s \chi_d H_s(j\omega_d)$$

When  $\zeta_m = \zeta_{min} \equiv MDS$ ,  $i_o = i_{eq,TOT}$   $\leftarrow$  input-referred noise current entering the sense amplifier  $\rightarrow$  in  $pA/\sqrt{Hz}$

$$\therefore i_{eq,TOT} = A \zeta_{min} \rightarrow \zeta_{min} = \frac{i_{eq,TOT}}{A} \left( \frac{3600\pi}{hr} \right) \left( \frac{180^\circ}{\pi} \right) \left[ (\%hr)/\sqrt{Hz} \right]$$

$$\text{Angle Random Walk} = \text{ARW} = \frac{1}{60} \zeta_{min} [\%/hr]$$

Easier to determine directional error as a function of elapsed time.

**Example: Gyro MDS Calculation (cont)**

The diagram shows a mechanical system with a sense element and a noiseless electronic circuit. The mechanical system consists of a mass-spring-damper system with parameters  $F_c = m\vec{a}_c = m \cdot (2\vec{x}_d \times \vec{\Omega})$ ,  $l_x$ ,  $c_x$ ,  $f_{rx}^2$ ,  $r_x$ , and  $\eta_e : 1$ . The sense element is represented by a voltage source  $i_s$ . The noiseless electronic circuit includes a resistor  $R_f$  and an operational amplifier.

Equation for  $i_{eqTOT}$ :

$$i_{eqTOT} = i_s + i_{eq} \rightarrow i_{eqTOT} = \overline{i_s^2} + \overline{i_f^2} + \overline{i_{ia}^2} + \frac{\overline{N_{ia}^2}}{R_f^2} \quad \frac{\overline{f_{rx}^2}}{\Delta f} = 4kT r_x$$

Annotations:

- $R_s$ : large  $\therefore N_{eq}^2$  "opened" out
- Now, find the  $i_{eqTOT}$  entering the amplifier input:

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 43

43

**Example: Gyro MDS Calculation (cont)**

Detailed circuit diagram showing noise contributions:

$$\overline{i_s^2} = \frac{N_{Rx}^2}{R_x} = 4kT R_x$$

$$\overline{i_{ia}^2} = \frac{N_{ia}^2}{R_f^2} = \frac{4kT}{R_f^2} |(\Theta_s(j\omega_d))|^2$$

$$\overline{i_f^2} = \frac{4kT}{R_x} |(\Theta_s(j\omega_d))|^2$$

Thus:

$$\frac{\overline{i_{eqTOT}^2}}{\Delta f} = \frac{4kT}{R_x} |(\Theta_s(j\omega_d))|^2 + \frac{4kT}{R_f^2} + \frac{\overline{i_{ia}^2}}{\Delta f} + \frac{N_{ia}^2}{\Delta f} \left( \frac{1}{R_f^2} \right)$$

Learn to get these from EE240.  
 or just get them from a data sheet ...

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 44

44

## LF356 Op Amp Data Sheet

**UC Berkeley**

### LF155/LF156/LF256/LF257/LF355/LF356/LF357

#### JFET Input Operational Amplifiers

##### General Description

These are the first monolithic JFET input operational amplifiers to incorporate well matched, high voltage JFETs on the same chip with standard bipolar transistors (Bi-FET™ Technology). These amplifiers feature low input bias and offset currents/low offset voltage and offset voltage drift, coupled with offset adjust which does not degrade drift or common-mode rejection. The devices are also designed for high slew rate, wide bandwidth, extremely fast settling time, low voltage and current noise and a low  $1/f$  noise corner.

##### Features

- Replace expensive hybrid and module FET op amps
- Rugged JFETs allow blow-out free handling compared with MOSFET input devices
- Excellent for low noise applications using either high or low source impedance—very low  $1/f$  corner
- Offset adjust does not degrade drift or common-mode rejection as in most monolithic amplifiers
- New output stage allows use of large capacitive loads (5,000 pF) without stability problems
- Internal compensation and large differential input voltage capability

##### Applications

- Precision high speed integrators
- Fast D/A and A/D converters
- High impedance buffers
- Wideband, low noise, low drift amplifiers

**Common Features**

- Low input bias current: 30 pA
- Low Input Offset Current: 3 pA
- High input impedance:  $10^{12} \Omega$
- Low input noise current:  $0.01 \text{ pA}/\sqrt{\text{Hz}}$
- High common-mode rejection ratio: 100 dB
- Large dc voltage gain: 106 dB

**Uncommon Features**

	LF155/ LF355	LF156/ LF256	LF257/ LF357	Units
Extremely fast settling time to 0.01%	4	1.5	1.5	μs
Fast slew rate	5	12	50	V/μs
Wide gain bandwidth	2.5	5	20	MHz
Low input noise voltage	20	12	12	nV/ $\sqrt{\text{Hz}}$

*(Handwritten notes:  $i_{ia} = 0.01 \text{ pA}/\sqrt{\text{Hz}}$  and  $v_{ia} = 12 \text{ nV}/\sqrt{\text{Hz}}$ )*


EEC247B/MEC218: Introduction to MEMS Design      LecM 17      C. Nguyen      11/18/08      45

45

## Example ARW Calculation

**UC Berkeley**

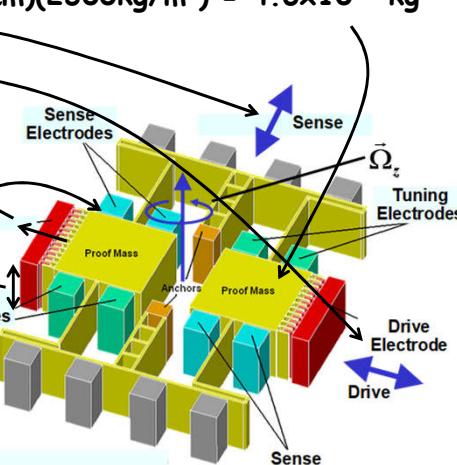- Example Design:**
  - Sensor Element:**
 $m = (100\mu\text{m})(100\mu\text{m})(20\mu\text{m})(2300\text{kg/m}^3) = 4.6 \times 10^{-10}\text{kg}$ 
 $\omega_s = 2\pi(15\text{kHz})$ 
 $\omega_d = 2\pi(10\text{kHz})$ 
 $k_s = \omega_s^2 m = 4.09 \text{ N/m}$ 
 $x_d = 20 \mu\text{m}$ 
 $Q_s = 50,000$ 
 $V_p = 5\text{V}$ 
 $h = 20 \mu\text{m}$ 
 $d = 1 \mu\text{m}$
  - Sensing Circuitry:**
 $R_f = 100\text{k}\Omega$ 
 $i_{ia} = 0.01 \text{ pA}/\sqrt{\text{Hz}}$ 
 $v_{ia} = 12 \text{ nV}/\sqrt{\text{Hz}}$



EEC247B/MEC218: Introduction to MEMS Design      LecM 17      C. Nguyen      11/18/08      46

46

**Example ARW Calculation (cont)**

Get rotation rate to output current scale factor:

$$A = 2 \frac{w_d}{w_s} Q_s \eta_e |\Theta(j\omega_d)| = 2 \left( \frac{10k}{15k} \right) (50k) (20\mu) (5) (2000 \epsilon_0) (0.000024) = \underline{2.83 \times 10^{-12} C}$$

$$\left[ \Theta_s(j\omega_d) = \frac{(j\omega_d)(w_s/Q_s)}{-\omega_d^2 + j\omega_d w_s + \omega_s^2} = \frac{j(10k)(15k)/(50k)}{(15k)^2 - (10k)^2 + j(10k)(15k)/50k} = \frac{j(3k)}{1.25 \times 10^8 + j(3k)} \right]$$

$$\rightarrow |\Theta_s(j\omega_d)| = \frac{3k}{\sqrt{(1.25 \times 10^8)^2 + (3k)^2}} = \frac{0.000024}{8.854 \times 10^{-8} F/m}$$

$$\left[ \frac{\partial C}{\partial x} = \frac{C_0}{d} = \frac{\epsilon_0 h w_p}{d} = \frac{\epsilon_0 (20\mu)(100\mu)}{(1\mu)^2} = 2000 \epsilon_0 \rightarrow \eta_e = V_p \frac{\partial C}{\partial x} = \frac{5(2000 \epsilon_0)}{8.854 \times 10^{-12} F/m} \right]$$

Assume electrode covers the whole sidewall.

Then, get noise:

$$\frac{i_{eq,TOT}^2}{\Delta f} = \frac{4kT}{R_X} |\Theta_s(j\omega_d)|^2 + \frac{4kT}{R_f} + \frac{i_{ia}^2}{\Delta f} + \frac{N_{ia}^2}{\Delta f} \left( \frac{1}{R_f^2} \right)$$

EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    47

47

**Example ARW Calculation (cont)**

$R_X = \frac{w_s m}{Q_s \eta_e} = \frac{2\pi(15k)(4.6 \times 10^{-10})}{(50k)(8.854 \times 10^{-8})^2} = 110.6 k\Omega$

$$\frac{i_{eq,TOT}^2}{\Delta f} = \frac{(1.66 \times 10^{-29})}{(110.6k)} (0.000024)^2 + \frac{(1.66 \times 10^{-29})}{1M} + (0.01\rho)^2 + \frac{(12\mu)^2}{(1M)^2}$$

$\xrightarrow{8.64 \times 10^{-75} A^2/Hz}$  sensor element noise insignificant

$\xrightarrow{1.66 \times 10^{-26} A^2/Hz}$   $\xrightarrow{1 \times 10^{-28} A^2/Hz}$  noise from  $R_f$  dominates!

$$\therefore \frac{i_{eq,TOT}^2}{\Delta f} = 1.68 \times 10^{-26} A^2/Hz \rightarrow i_{eq,TOT} = \sqrt{\frac{i_{eq,TOT}^2}{\Delta f}} = 1.30 \times 10^{-13} A/\sqrt{Hz}$$

$$\therefore S2_{min} = \frac{i_{eq,TOT}}{A} \left( \frac{3600\pi}{hr} \right) \left( \frac{180}{\pi} \right) = \frac{1.30 \times 10^{-13}}{2.83 \times 10^{-12}} (3600) \left( \frac{180}{\pi} \right) = \underline{9448 (\%/hr) / \sqrt{Hz}}$$

And finally:  
 $ARW = \frac{1}{60} S2_{min} = \frac{1}{60} (9448) = \boxed{157 \%/\sqrt{hr} = ARW}$   $\Rightarrow$  almost turned around in 1 hour!

EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    48

48

**What if  $\omega_d = \omega_s$ ?**

UC Berkeley

If  $\omega_d = \omega_s = 15\text{kHz}$ , then  $|H_s(j\omega_d)| = 1$  and

$$A = 2 \frac{\omega_d}{\omega_s} Q_s \chi_d \eta_e |H_s(j\omega_d)| = 2 Q_s \chi_d \eta_e = 2(50k)(20\mu)(5)(2000\epsilon_0) = 1.77 \times 10^{-7} \text{C}$$

$$\frac{i_{eq,TOT}^2}{\Delta f} = \underbrace{\frac{(1.66 \times 10^{-29})}{(110.6k)} (1)^2}_{1.51 \times 10^{-25} \text{A}^2/\text{Hz}} + \underbrace{\frac{(1.66 \times 10^{-29})}{1M}}_{1.66 \times 10^{-26} \text{A}^2/\text{Hz}} + \underbrace{(0.01\rho)^2}_{1 \times 10^{-28} \text{A}^2/\text{Hz}} + \underbrace{\frac{(12n)^2}{(1M)^2}}_{1.44 \times 10^{-28} \text{A}^2/\text{Hz}}$$

Now, the sensor element dominates!

$$\therefore \frac{i_{eq,TOT}^2}{\Delta f} = 1.67 \times 10^{-25} \text{A}^2/\text{Hz} \rightarrow i_{eq,TOT} = \sqrt{\frac{i_{eq,TOT}^2}{\Delta f}} = 4.08 \times 10^{-13} \text{A}/\sqrt{\text{Hz}}$$

$$\therefore \Sigma_{min} = \frac{i_{eq,TOT}}{A} \left( \frac{3600\pi}{hr} \right) \left( \frac{180^\circ}{\pi} \right) = \frac{4.08 \times 10^{-13}}{1.77 \times 10^{-7}} (3600) \left( \frac{180}{\pi} \right) = 0.476 (\%/\text{hr})/\sqrt{\text{Hz}}$$

And finally:

$$ARW = \frac{1}{60} \Sigma_{min} = \frac{1}{60} (0.476) = 0.0079 \%/\sqrt{\text{hr}} = ARW \Rightarrow \text{Navigation grade!}$$

EEC247B/MEC218: Introduction to MEMS Design    LecM 17    C. Nguyen    11/18/08    49