

UC Berkeley

EE C245 - ME C218 Introduction to MEMS Design Fall 2010

Prof. Clark T.-C. Nguyen

Dept. of Electrical Engineering & Computer Sciences
 University of California at Berkeley
 Berkeley, CA 94720

Lecture Module 13: Equivalent Circuits II

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 1

UC Berkeley

Lecture Outline

- Reading: Senturia, Chpt. 6, Chpt. 14
- Lecture Topics:
 - ↪ Input Modeling
 - Force-to-Velocity Equiv. Ckt.
 - Input Equivalent Ckt.
 - ↪ Current Modeling
 - Output Current Into Ground
 - Input Current
 - Complete Electrical-Port Equiv. Ckt.
 - ↪ Impedance & Transfer Functions

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 2

UC Berkeley

Input Modeling

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 3

UC Berkeley

Electromechanical Analogies

$F(t) = F \cos(\omega t) \rightarrow x(t) = X \cos \omega t$
 Equation of Motion:
 $m_{eq} \ddot{x} + c_{eq} \dot{x} + k_{eq} x = F(t)$
 \Rightarrow using phasor concepts:
 $F = j\omega m_{eq} \dot{x} + \frac{k_{eq}}{j\omega} x + c_{eq} \dot{x}$
 \Rightarrow by analogy:

$F \rightarrow N$	$m_{eq} \rightarrow l_x$	$c_{eq} \rightarrow r_x$
$\dot{x} \rightarrow \dot{q}$	$k_{eq} \rightarrow \frac{1}{c_x}$	

Impedance looking in:
 $\frac{N}{\dot{q}} = j\omega l_x + \frac{1}{j\omega c_x} + r_x$
 $N = j\omega l_x \dot{q} + \frac{(\dot{q} c_x)}{j\omega} + r_x \dot{q}$

Parameter Relationships in the Current Analogy

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 4

Bandpass Biquad Transfer Function

$$F = j\omega m_{eq} \dot{x} + \frac{k_{eq}}{j\omega} x + C_{eq} \dot{x}$$

$$\Rightarrow \text{Converting to full phasor form:}$$

$$F = (j\omega)(j\omega x) m_{eq} + \frac{k_{eq}}{j\omega} (j\omega x) + C_{eq} (j\omega x)$$

$$\frac{X}{F}(j\omega) = \frac{1}{k_{eq}} \left[-\omega^2 \frac{m_{eq}}{k_{eq}} + 1 + j \frac{C_{eq}\omega}{k_{eq}} \right]^{-1} = \frac{1}{k_{eq}} \left[-\left(\frac{\omega}{\omega_0}\right)^2 + 1 + j \frac{\omega}{Q\omega_0} \right]^{-1}$$

$$\left[\frac{k_{eq}}{m_{eq}} = \omega_0^2, Q = \frac{m_{eq}\omega_0}{C_{eq}} = \frac{k_{eq}}{\omega_0 C_{eq}} \rightarrow \frac{k_{eq}}{C_{eq}} = Q\omega_0 \right]$$

$$\left| \frac{X}{F}(j\omega) \right|$$

$$X = \frac{F}{k_{eq}}$$

$$X = \frac{QF}{k_{eq}}$$

$$\frac{X}{F}(j\omega) = \frac{k_{eq}^{-1}}{1 - (\frac{\omega}{\omega_0})^2 + j \frac{\omega}{Q\omega_0}}$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 5

Force-to-Velocity Relationship

- The relationship between input voltage v_1 and force F_{d1} :

$$F_{d1} \approx -V_P \frac{\partial C_1}{\partial x} v_1$$
- When displacement x is the mechanical output variable:

$$\frac{X(s)}{F_{d1}(s)} = \frac{1}{k} \frac{\omega_o^2}{s^2 + (\omega_o/Q)s + \omega_o^2}$$
- When velocity v is the mechanical output variable:

$$\frac{v(s)}{F_{d1}(s)} = \frac{sX(s)}{F_{d1}(s)} = \frac{1}{k} \frac{\omega_o^2 s}{s^2 + (\omega_o/Q)s + \omega_o^2}$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 6

Force-to-Velocity Equiv. Ckt.

- Combine the previous lumped LCR mechanical equivalent circuit with a circuit modeling the capacitive transducer \rightarrow circuit model for voltage-to-velocity

$$U = -\dot{x} \quad | \quad x = m \quad | \quad r_x = b$$

$$\epsilon_x = 1/k$$

Electrical | Mechanical

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 7

Equiv. Circuit for a Linear Transducer

- A transducer ...
 - converts energy from one domain (e.g., electrical) to another (e.g., mechanical)
 - has at least two ports
 - is not generally linear, but is virtually linear when operated with small signals (i.e., small displacements)

Electrical | Mechanical

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 8