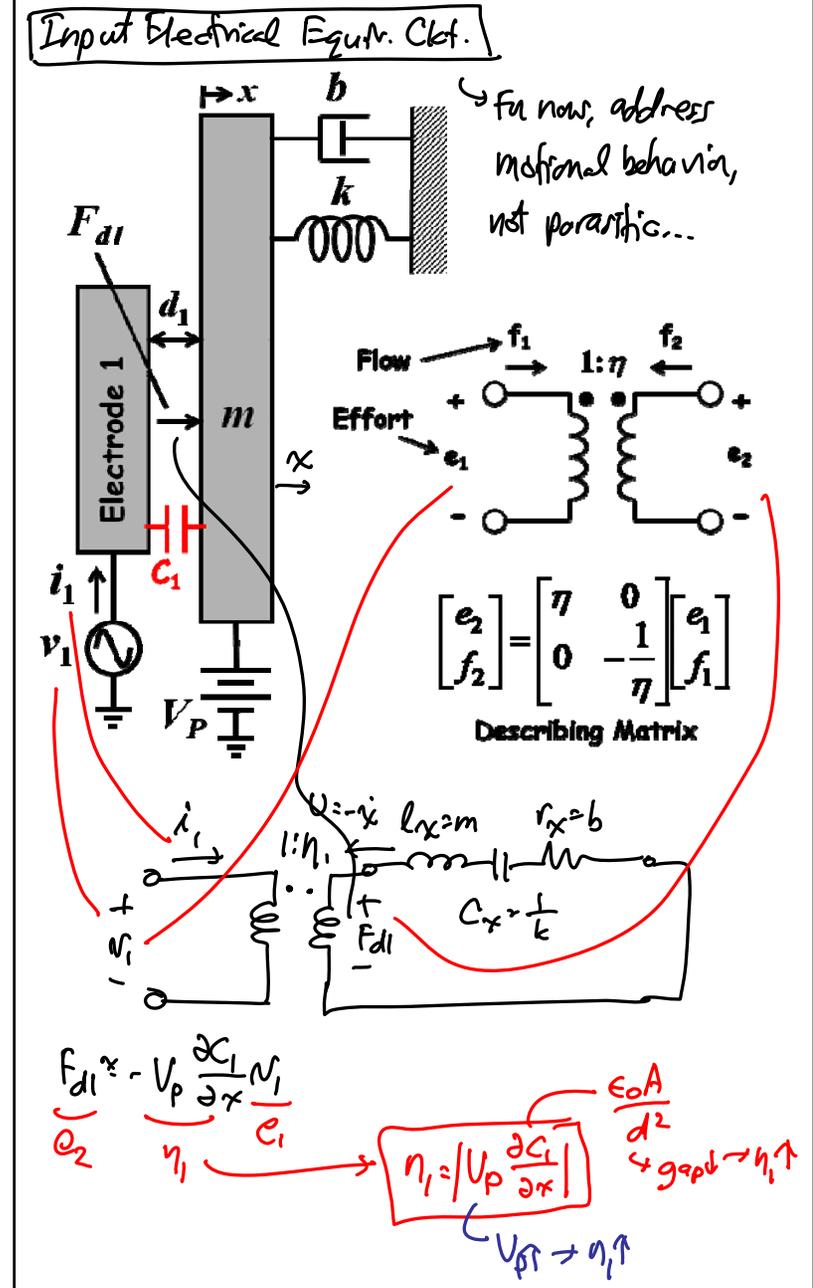


Lecture 24: Equivalent Circuits II

- Announcements:
- HW#7 will be online soon (tomorrow morning)
 - ↳ It's color, so will not be handed out
 - ↳ Get it from the website
- Reminder: 3rd project slide due Dec. 3
- No class Thursday (Thanksgiving)
-
- Reading: Senturia, Chpt. 6, Chpt. 14
- Lecture Topics:
 - ↳ Input Modeling
 - Force-to-Velocity Equiv. Ckt.
 - Input Equivalent Ckt.
 - ↳ Current Modeling
 - Output Current Into Ground
 - Input Current
 - Complete Electrical-Port Equiv. Ckt.
 - ↳ Impedance & Transfer Functions
-
- Last Time:
 - ↳ Started electrical equivalent circuits using Module 13



Output Current Into Ground

Want this model.

$[q = CV]$

$i = \frac{dq}{dt} = C \frac{dV}{dt} + V \frac{dC}{dt}$

$i_2 = C_2 \frac{dV_2(t)}{dt} + V_2(t) \frac{dC_2(x,t)}{dt}$

$[V_2(t) = -V_P] \Rightarrow i_2 = -V_P \frac{dC_2}{dt} = -V_P \frac{\partial C}{\partial x} \frac{\partial x}{\partial t}$

In phasor form: $I_2(j\omega) = -V_P \frac{\partial C_2}{\partial x} (j\omega X)$

$I_2(j\omega) = -j\omega V_P \frac{\partial C_2}{\partial x} X$

\leftarrow motional current

$I_2(j\omega) = \cancel{j\omega} V_P \frac{\partial C_2}{\partial x} \cancel{X} = -V_P \frac{\partial C_2}{\partial x} U$

\uparrow \uparrow \uparrow
90° phase lag (t) (t) \rightarrow velocity

Velocity $\rightarrow U = \dot{x} \leftarrow f_2$

$f_2 = \frac{1}{n_2} f_1 \rightarrow f_1 = -n_2 f_2$

$[f_1 = I_2, f_2 = U] \Rightarrow I_2 = -n_2 U$

$\therefore n_2 = \left| V_P \frac{\partial C_2}{\partial x} \right|$

Input Current Expression

Get $I_i(j\omega)$:

$$i_i(t) = C_1(x,t) \frac{dV_1(t)}{dt} + V_1(t) \frac{dC_1(x,t)}{dt}$$

$$[V_1(t) = V_1 - V_P] \Rightarrow i_i = C_1 \frac{dV_1}{dt} + (V_1 - V_P) \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t}$$

$\therefore I_i(j\omega) = j\omega C_1 V_1 + j\omega m \frac{\partial C_1}{\partial x} X - j\omega V_P \frac{\partial C_1}{\partial x} X$

Feedthrough Current (under $j\omega C_1 V_1$)
Motional Current (under $j\omega m \frac{\partial C_1}{\partial x} X - j\omega V_P \frac{\partial C_1}{\partial x} X$)

due to mass motion! (circled around the motional current terms)

@ DC: $x = \frac{F_{dl}}{k} = -\frac{1}{k} V_P \left(\frac{\partial C_1}{\partial x} \right) V_1$

@ resonance: $x = \frac{Q F_{dl}}{jk} = -\frac{Q}{jk} V_P \frac{\partial C_1}{\partial x} V_1 = X$

\uparrow
90° phase lag

Thus: (@ resonance) ω_0

$$I_i(j\omega) = j\omega_0 C_1 V_1 + j\omega_0 \left(V_P \frac{\partial C_1}{\partial x} \right)^2 \frac{Q}{jk} V_1$$

$i_p = j\omega_0 C_1 V_1$ (circled)
 $i_x = \omega_0 \frac{Q}{k} \eta e_1^2 V_1$ (circled)

90° phase shifted from V_1
In phase w/ V_1 .

This is a capacitor in shunt at the input!
This is an effective resistance seen "looking into electrode 1" @ ω_0

Motional Resistance: \leftarrow Over \rightarrow



Motional Resistance:

$$R_{x1} = \frac{V_1}{I_1} = \frac{k}{\omega_0 Q \eta_{e1}^2} = \frac{m \omega_0}{Q \eta_{e1}^2} = \frac{b}{\eta_{e1}^2} = R_{x1}$$

↑
"motion"

The equivalent def. better
get this right!

Input Impedance Into Port 1

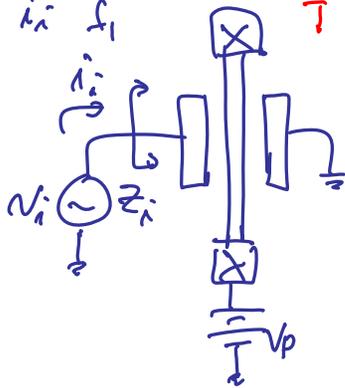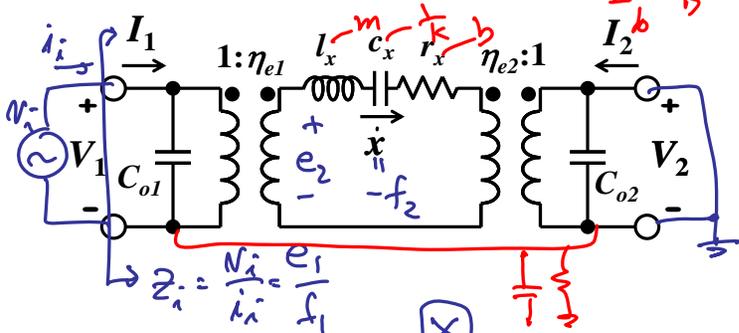

$$\begin{bmatrix} e_2 \\ f_2 \end{bmatrix}, \begin{bmatrix} \eta & 0 \\ 0 & -\frac{1}{\eta} \end{bmatrix} \begin{bmatrix} e_1 \\ f_1 \end{bmatrix} \Rightarrow \left. \begin{aligned} e_2 &= \eta e_1 \rightarrow e_1 = -\frac{e_2}{\eta} \\ f_2 &= -\frac{1}{\eta} f_1 \rightarrow f_1 = -\eta f_2 \end{aligned} \right\}$$

$$\frac{e_1}{f_1} = \frac{e_2}{\eta} \left(-\frac{1}{\eta f_2} \right) = -\frac{1}{\eta^2} \frac{e_2}{f_2} \rightarrow \frac{V_1}{I_1} = Z_i = -\frac{1}{\eta_{e1}^2} \frac{F_{d2}}{(-x_2)}$$

$$= \frac{1}{\eta_{e1}^2} Z_x$$

$$Z_i = \frac{1}{\eta_{e1}^2} (j\omega L_x + \frac{1}{j\omega C_x} + R_x)$$

$$= j\omega \underbrace{\left(\frac{L_x}{\eta_{e1}^2} \right)}_{L_{x1}} + \frac{1}{j\omega \underbrace{(\eta_{e1}^2 C_x)}_{C_{x1}}} + \underbrace{\frac{R_x}{\eta_{e1}^2}}_{R_{x1}}$$

