

EE43/EE100 — LAB #4

Op Amps Guide

Motivation / Objectives

In this lab, we will be learning about operational amplifiers (op amps), and simple circuits involving op amps. We will compare the op amp theoretical analysis developed in the lectures with actual measured values, and real-world (non-ideal) op amps. In addition, the circuits used in this lab will also reinforce previous concepts, such as voltage dividers and superposition.

Important Notes

- Please set the current limit on the DC power supply to 300mA or less, on both the 6V and $\pm 25V$ outputs, to prevent damage to the op amps.
- These circuits are complicated. Good breadboard practices will be key in completing this lab.

Part 1: Op Amp Setup

1. Set the current limit on the 6V, 25V, and -25V outputs of the DC power supply to 300mA. Set the power supply to have outputs of +5V, +10V, and -10V. Be sure to use the same ground node for the ground of the 6V and $\pm 25V$ outputs.
2. We will be using the LM741 op amp. The pinout of the LM741 package is shown in Figure 1.

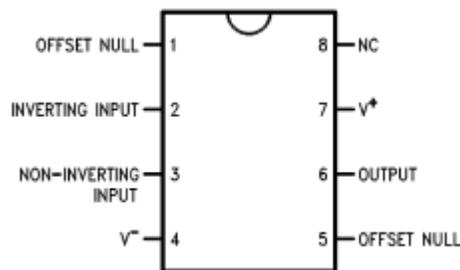


Figure 1: Pinout of LM741 package (Source: National Semiconductor LM741 datasheet)

Part 2: The Voltage Follower

3. On your breadboard, build the op amp circuit shown in Figure 2. The numbers correspond to the appropriate pin of the LM741. V_{DD} and V_{SS} will be supplied by the DC power supply. Set $V_{DD} = 10V$ and $V_{SS} = -10V$.

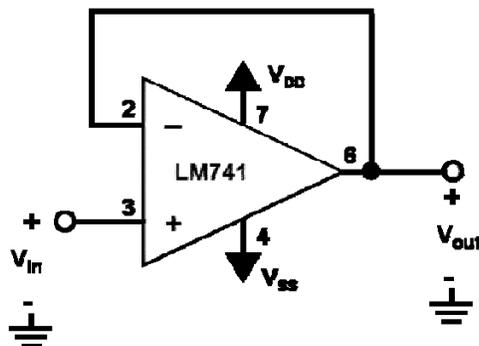


Figure 2: The voltage follower

- Apply a 5V DC voltage to v_{in} . Measure this value using the DMM. What is the expected value of v_{out} ? Verify by measuring v_{out} with the DMM.

Part 3: The Inverting Amplifier

- On your breadboard, build the op amp circuit shown in Figure 3. The numbers correspond to the appropriate pin of the LM741. The circuit element labeled R is an adjustable resistor, which is realized by using a potentiometer.

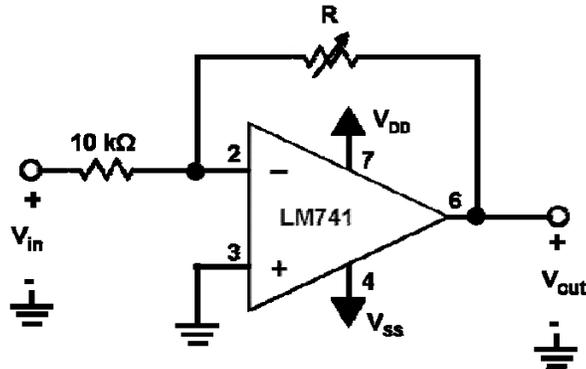


Figure 3: The inverting amplifier

- Set R to approximately 20k Ω . Use the DMM to measure the exact value of R . Using the 6V output of the DC power supply, apply a 1V DC signal at v_{in} . Using the measured value of R , calculate the expected value of v_{out} . Verify by measuring the value of v_{out} using the DMM. What is the gain of this circuit?
- Increase R to approximately 50k Ω . Use the DMM to measure the exact value of R . Using the measured value of R , calculate the expected value of v_{out} . Verify by measuring the value of v_{out} using the DMM. What is the gain of this circuit?
- Disconnect the 1V DC input. Use the function generator to apply a 1kHz, 0.5Vpp sine wave to v_{in} . Measure v_{in} using the oscilloscope to obtain a more precise value. Using the measured value of v_{in} , what should v_{out} be? Using the second channel of the oscilloscope, measure v_{out} and display it on the screen along with v_{in} . Plot the input and output waveforms (using the same scales for both signals). What is the gain of this circuit?

Part 4: The Non-inverting Amplifier

- On your breadboard, build the op amp circuit shown in Figure 4.

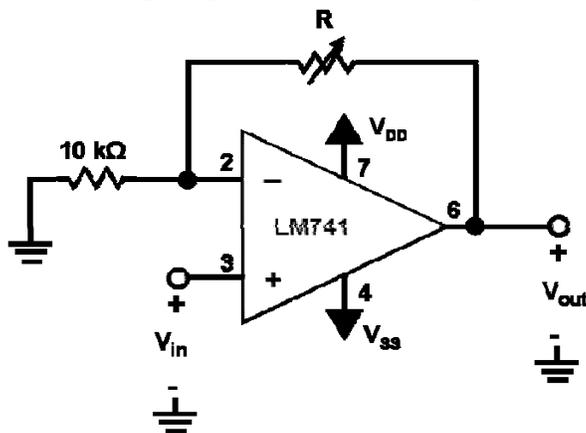


Figure 4: The non-inverting amplifier

10. Set R to approximately $20\text{k}\Omega$. Use the DMM to measure the exact value of R . Using the 6V output of the DC power supply, apply a 1V DC signal at v_{in} . Using the measured value of R , calculate the expected value of v_{out} . Verify by measuring the value of v_{out} using the DMM. What is the gain of this circuit?
11. Increase R to approximately $50\text{k}\Omega$. Use the DMM to measure the exact value of R . Using the measured value of R , calculate the expected value of v_{out} . Verify by measuring the value of v_{out} using the DMM. What is the gain of this circuit?
12. Disconnect the 1V DC input. Use the function generator to apply a 1kHz, 0.5Vpp sine wave to v_{in} . Measure v_{in} using the oscilloscope to obtain a more precise value. Using the measured value of v_{in} , what should v_{out} be? Using the second channel of the oscilloscope, measure v_{out} and display it on the screen along with v_{in} . Plot the input and output waveforms (using the same scales for both signals). What is the gain of this circuit?

Part 5: The Summing Amplifier

13. On your breadboard, build the op amp circuit shown in Figure 5.

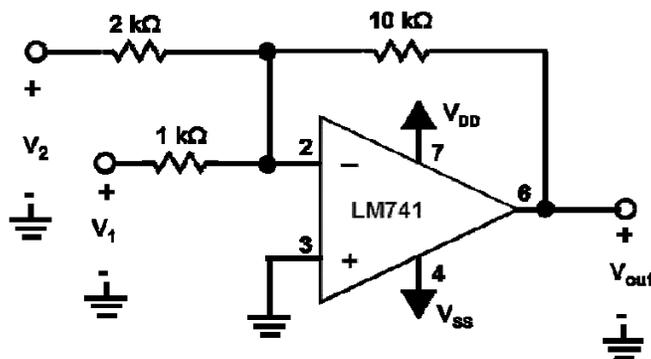


Figure 5: The summing amplifier

14. Leaving v_2 disconnected, use the 6V output of the DC power supply to apply a 0.5V DC signal to v_1 . What value do you expect for v_{out} ? Verify by measuring the value of v_{out} using the DMM.
15. Now disconnect v_1 , and use the 6V output of the DC power supply to apply a 0.5V DC signal to v_2 . What value do you expect for v_{out} ? Verify by measuring the value of v_{out} using the DMM.
16. Use the superposition principle to calculate v_{out} for the case where $v_1 = v_2 = 0.5\text{V}$. Apply a 0.5V signal to both v_1 and v_2 . Measure the value of v_{out} using the DMM. You have now witnessed the superposition principle in practice.

Part 6: The Non-Ideal Op Amp

17. One condition of the ideal op amp is that the open-loop gain is infinite. Let's see how a real op amp behaves. Build the circuit shown in Figure 6.

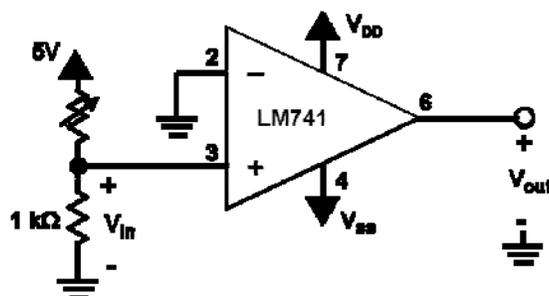


Figure 6: Open-loop op amp

18. Set $R = 4 \text{ k}\Omega$. Use the DMM to measure the exact value of R . Using the measured value of R , calculate the expected value of v_{in} . Verify by measuring the value of v_{in} using the DMM. What is the expected value of v_{out} ? Measure the actual value of v_{out} using the DMM.
19. Set $R = 1 \text{ k}\Omega$. Use the DMM to measure the exact value of R . Using the measured value of R , calculate the expected value of v_{in} . Verify by measuring the value of v_{in} using the DMM. What is the expected value of v_{out} ? Measure the actual value of v_{out} using the DMM. Review your results for $R = 4 \text{ k}\Omega$ and $R = 1 \text{ k}\Omega$. Why is the measured value of v_{out} not equal to the expected value?

Part 7: The Differential Amplifier

20. Build the op amp circuit show in Figure 7.

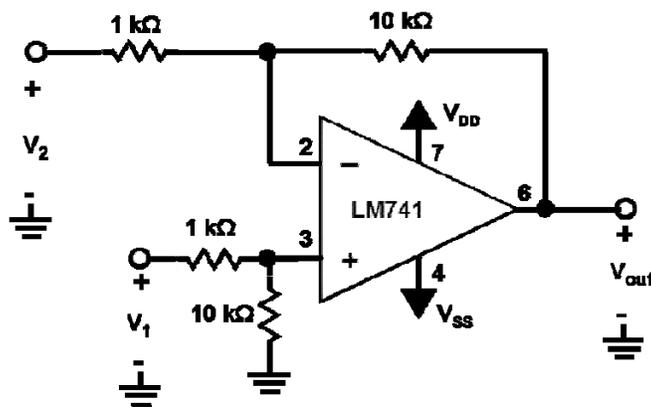


Figure 7: The differential amplifier

21. Using the 6V output of the DC power supply, apply a 1V DC signal to v_1 . Using the function generator, apply a 1kHz, 1Vpp sine wave to v_2 . What do you expect the output of the differential amplifier to be?
22. Measure the output of the differential amplifier using the oscilloscope. Plot the output waveform.