

Name: Solutions

Lab TA: Dan _____
Bart _____
Nir _____
Konrad _____
Yu Ching _____

EE 40

Midterm 2

October 17, 2002

PLEASE WRITE YOUR NAME ON EACH ATTACHED PAGE

PLEASE SHOW YOUR WORK TO RECEIVE PARTIAL CREDIT

Problem 1: 10 Points Possible _____

Problem 2: 5 Points Possible _____

Problem 3: 15 Points Possible _____

Problem 4: 10 Points Possible _____

Problem 5: 10 Points Possible _____

Problem 6: 15 Points Possible _____

Problem 7: 15 Points Possible _____

Problem 8: 5 Points Possible _____


Problem 9: 15 Points Possible _____

Problem 10: 10 Points Possible _____

TOTAL: 110 Points Possible _____

Name: Solutions**Problem 1:** 10 Points Possible

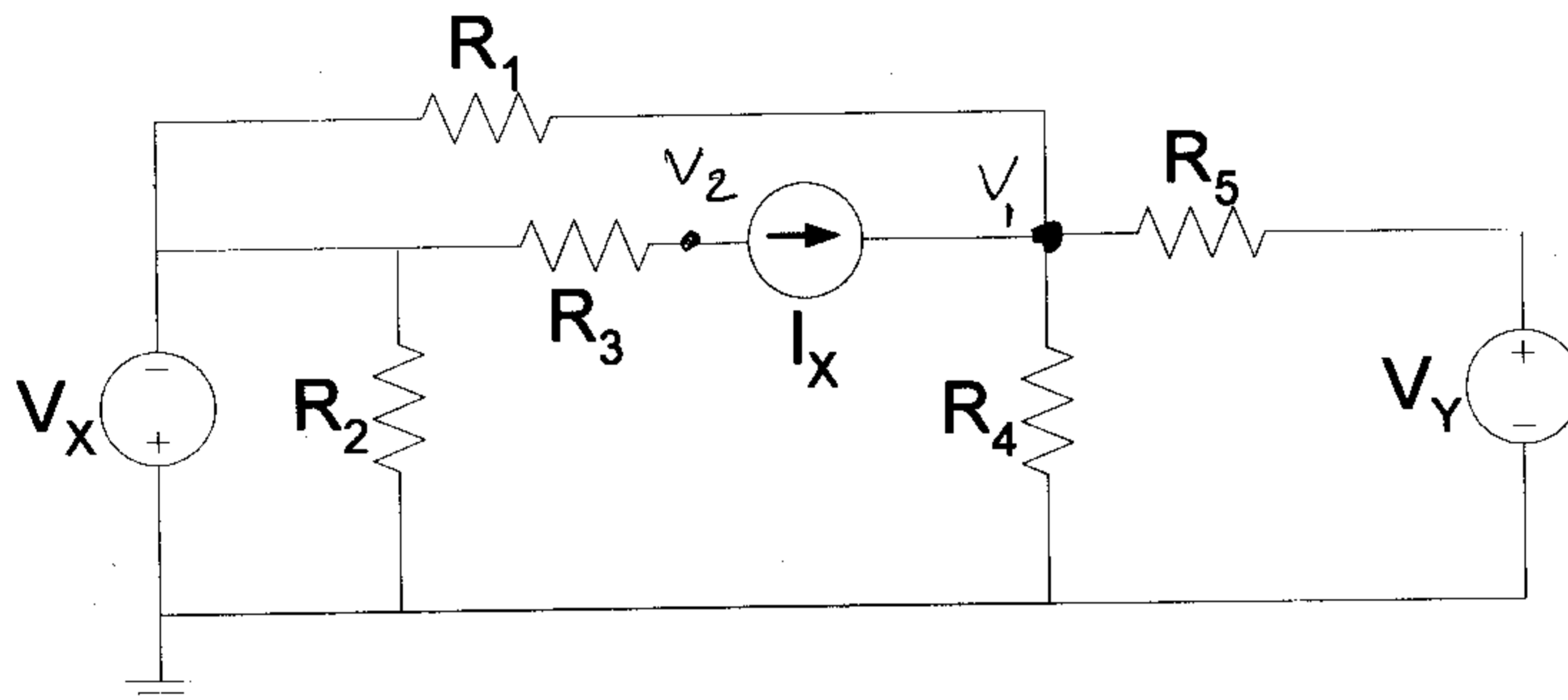Perform nodal analysis on the circuit below. This means write a KCL equation for each node with unknown voltage. DO NOT SIMPLIFY the circuit. DO NOT SOLVE the KCL equations.



Required: KVL @ V_1 :

$$\frac{V_1 - V_x}{R_1} - I_x + \frac{V_1}{R_4} + \frac{V_1 - V_y}{R_5} = 0$$

Optional: KVL @ V_2 :

$$\frac{V_2 - V_x}{R_3} + I_x = 0$$

Problem 2: 5 Points Possible


In nodal analysis, when is a supernode needed? Why is a supernode needed?

A supernode is needed when there is a "floating" voltage source (neither terminal of the source is at ground). The source makes it difficult to write KCL equations at its terminal nodes because it has no $V-I$ relationship (current is unknown). KCL is possible after enclosing the source in a supernode.

Name: Solutions

Problem 3: 15 Points Possible


Revisiting the circuit from Problem 1,

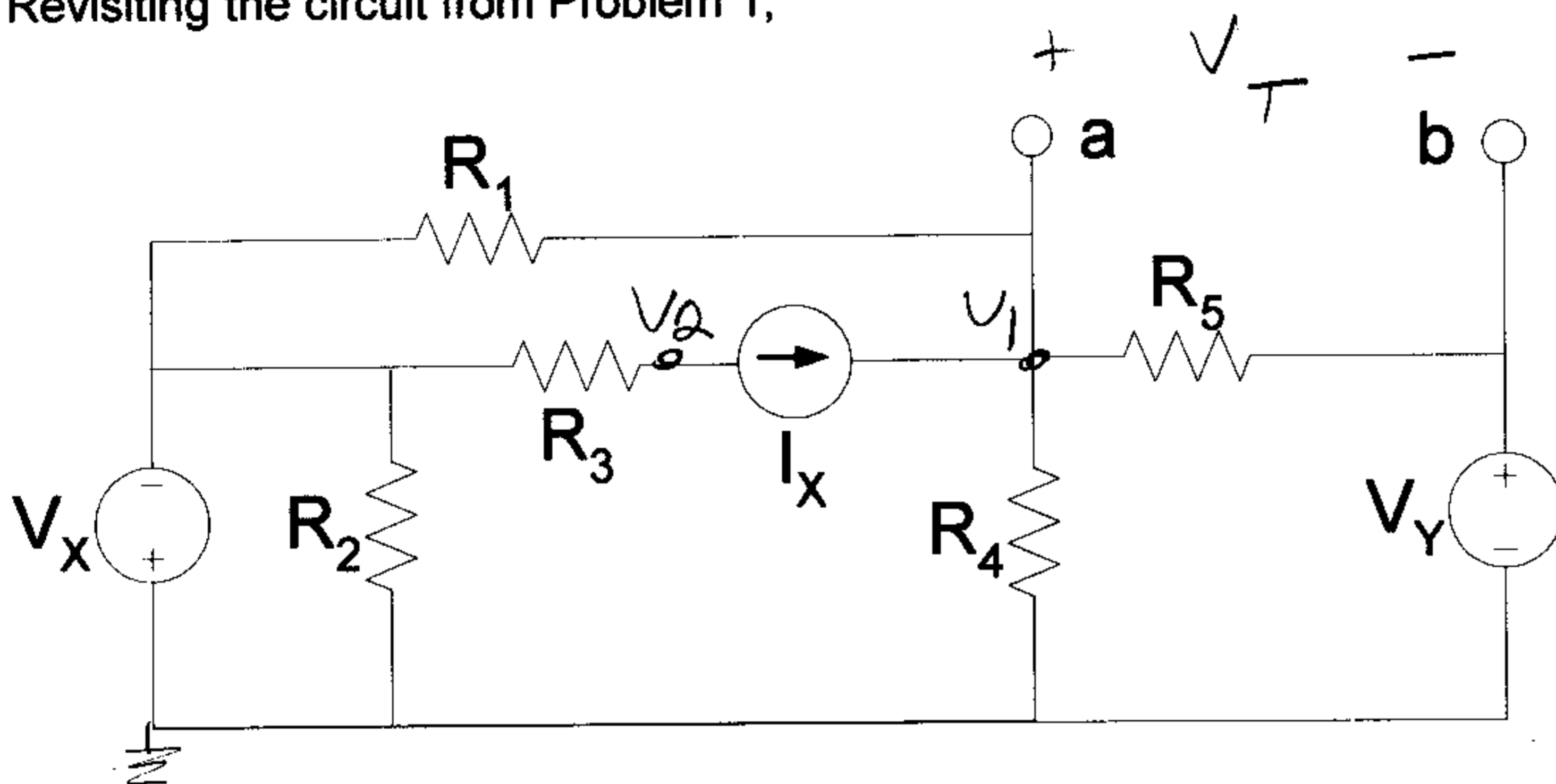


- Find the Thevenin equivalent voltage V_T with respect to a and b. Express V_T in terms of node voltages. (5 Points Possible)
- Find the Thevenin equivalent resistance R_T . DO NOT INCLUDE \parallel symbol in final answer; write the full mathematical expression. (10 Points Possible)

a) $V_T = V_{ab} = V_1 - V_Y$

b) Deactivate independent sources

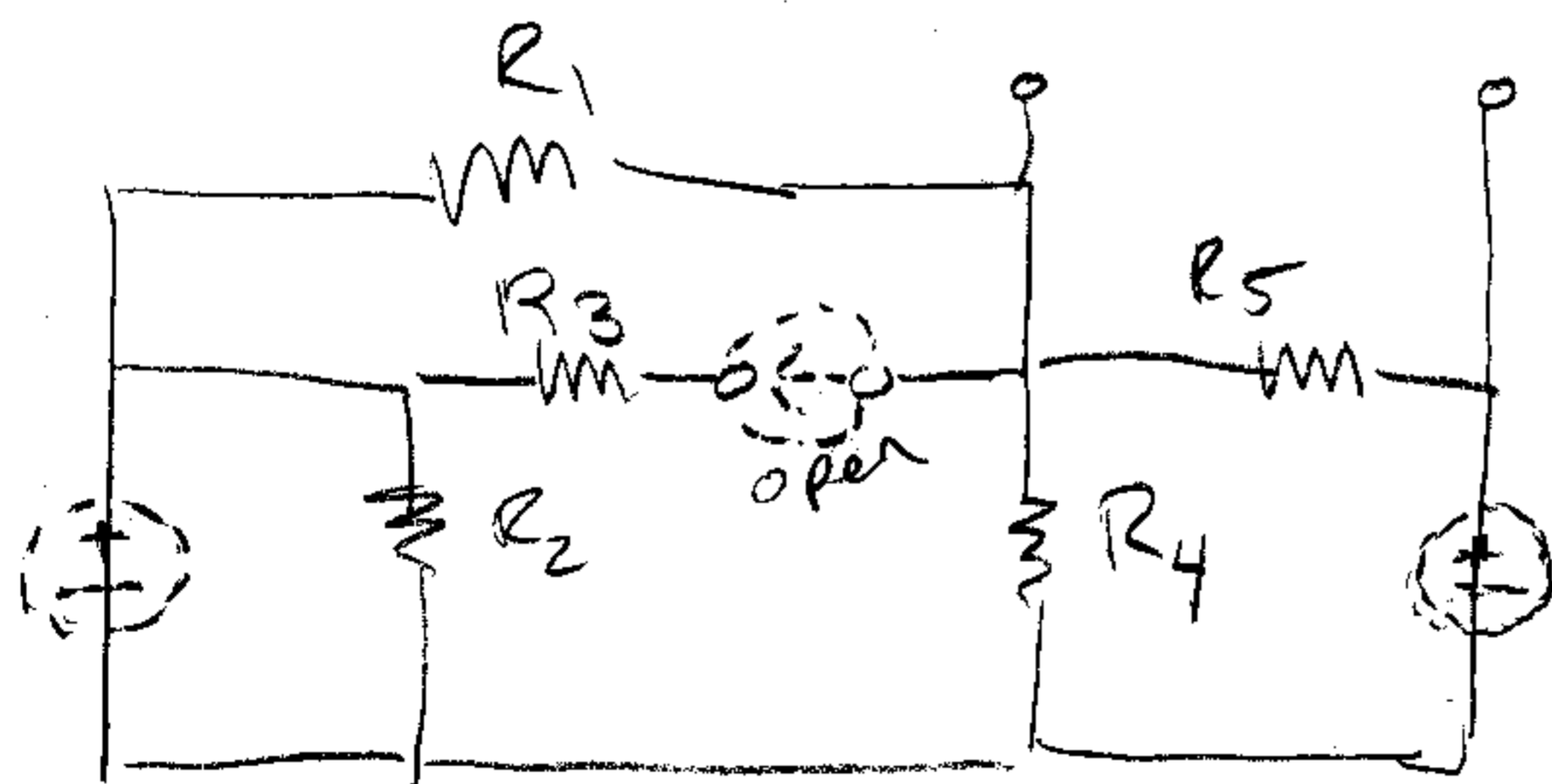

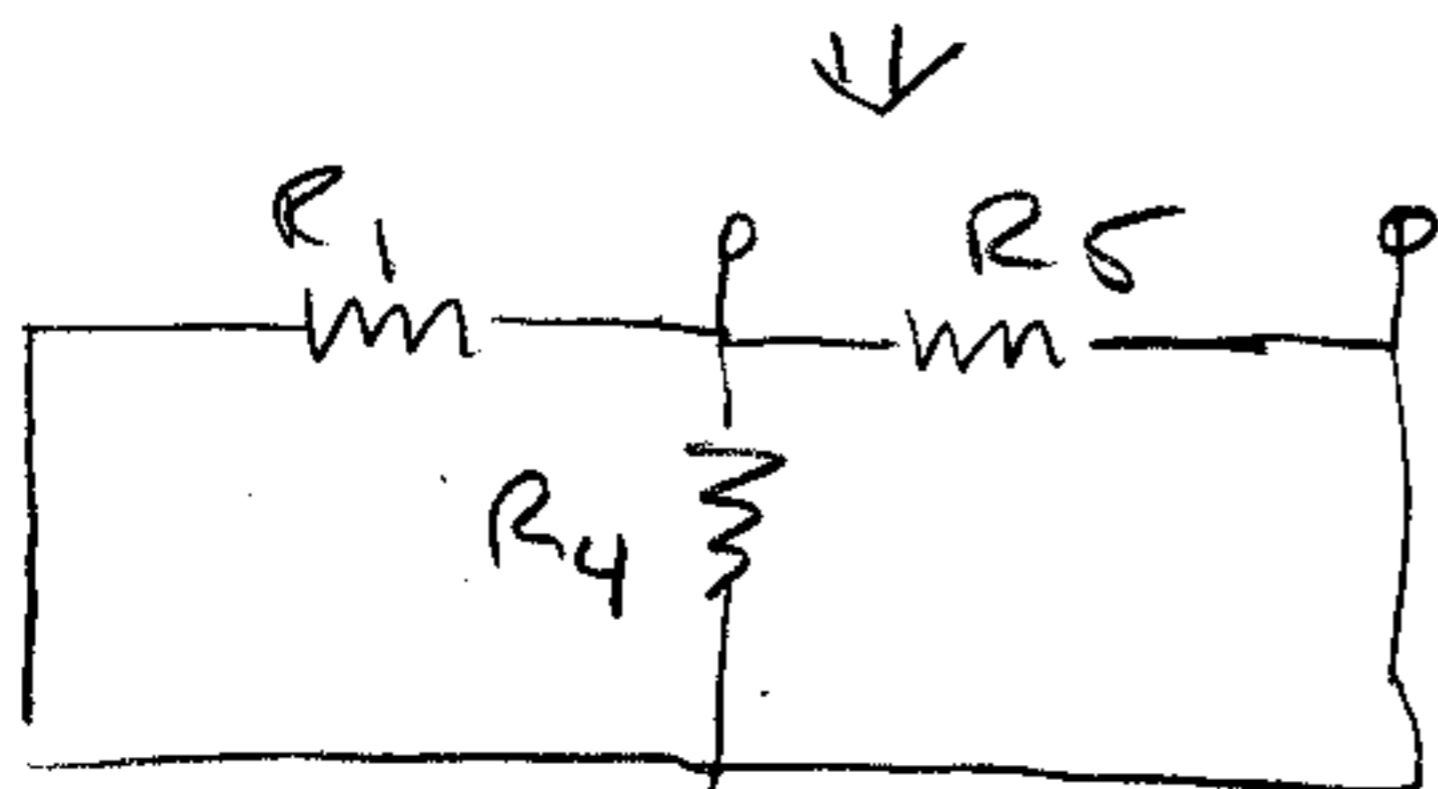R_3 carries no current (series w/ open circuit)
 R_2 carries no current (shorted out) parallel w/ wire




$$R_T = R_1 \parallel R_4 \parallel R_5$$

$$= (R_1^{-1} + R_4^{-1} + R_5^{-1})^{-1}$$

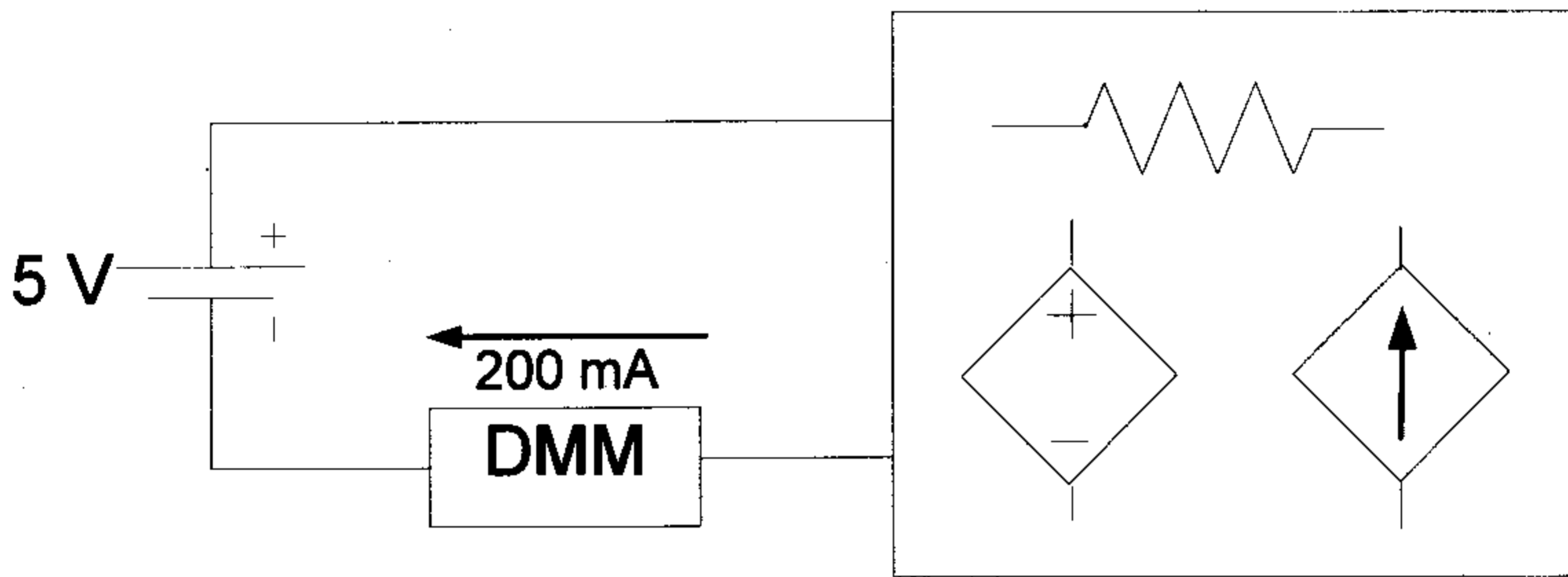Problem 4: 10 Points Possible

Suppose I have a black-box circuit (I can't see exactly what's inside) but I know it only contains resistors and linear dependent sources. The controlling voltages and currents for the dependent sources are also in the box.


I perform one experiment: When I attach a 5 V battery as shown, I measure a 200 mA current in the direction shown. The internal resistance of the battery is 4 Ω and the internal resistance of the DMM is 1 Ω .



Can I find the Thevenin equivalent of the black-box circuit with this information? If yes, find the Thevenin equivalent. If no, explain why not.

Since there are only dependent sources & resistors, No independent sources,


$$V_T = 0$$

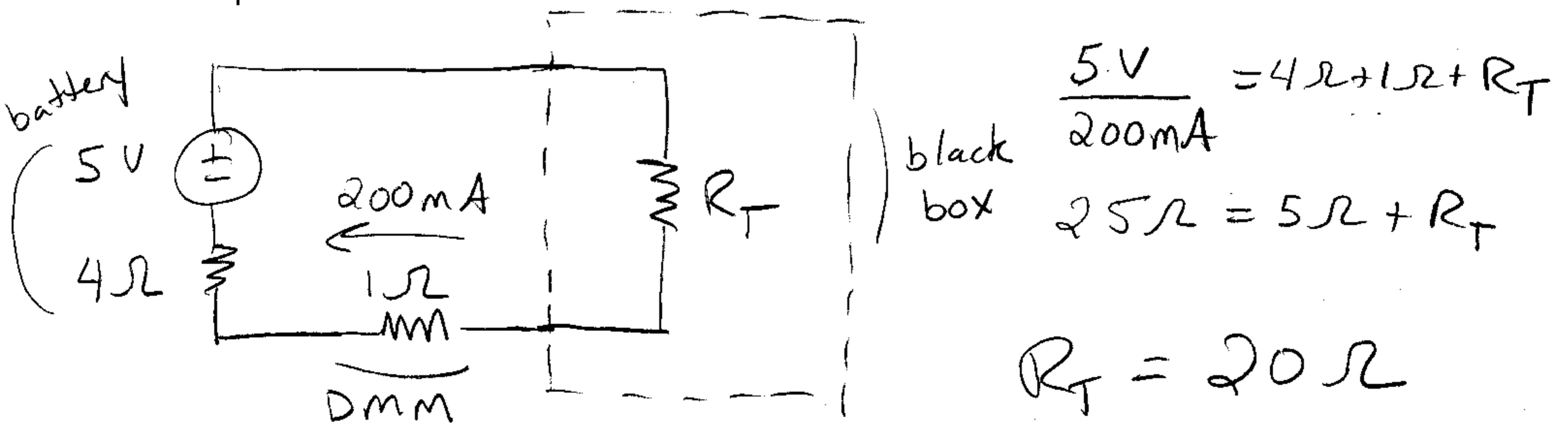


Name: Solutions

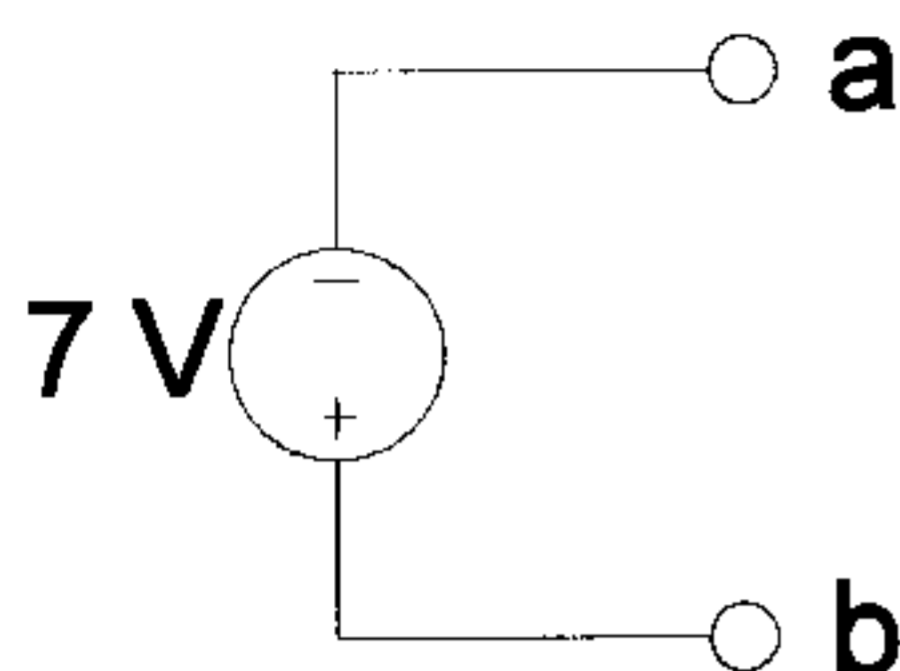Problem 5: 10 Points Possible

Find the Thevenin and Norton equivalents (if possible) for the following circuits:
(3 Points Possible for each Thevenin, 2 Points Possible for each Norton)



I-V graph

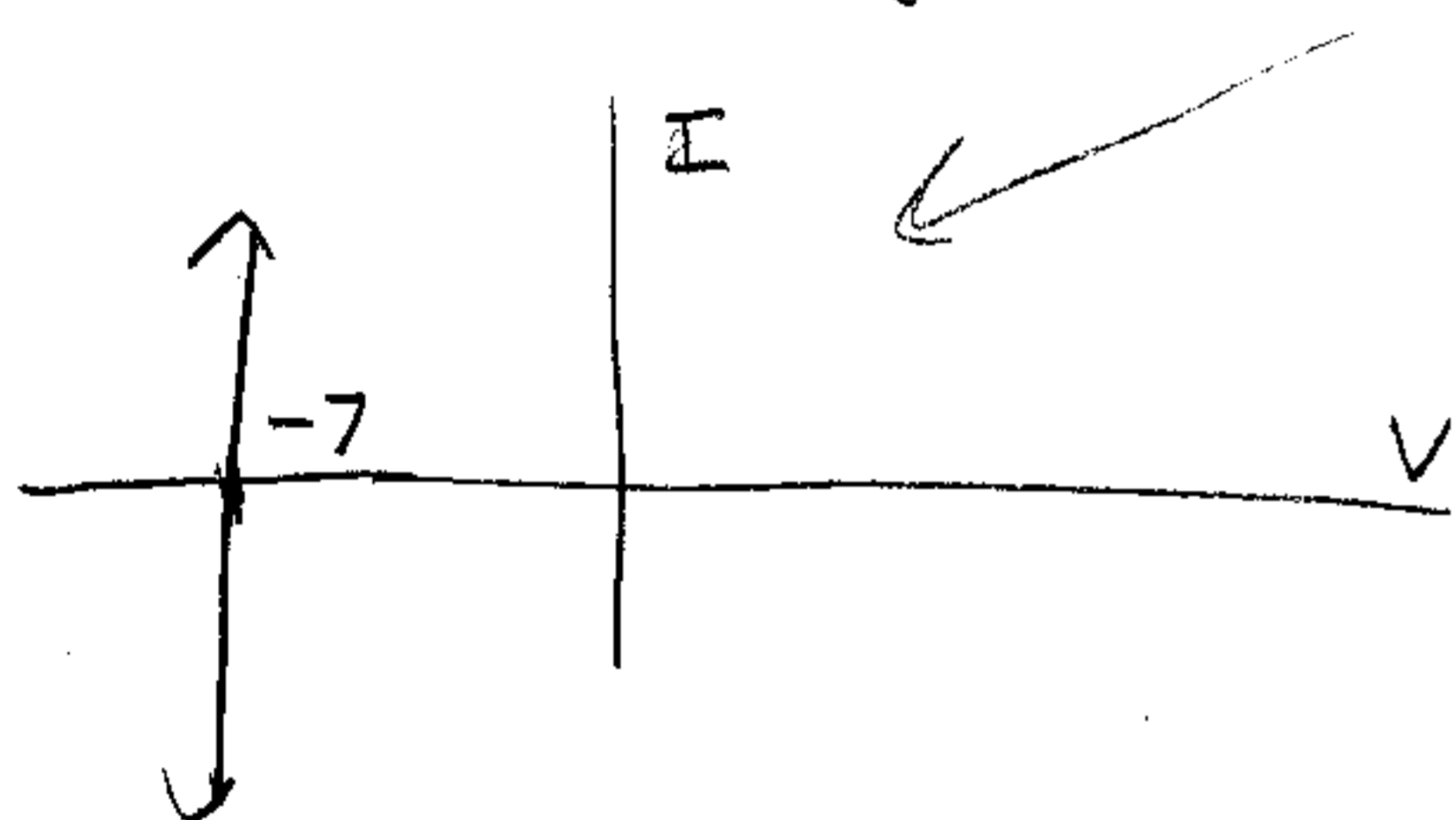


This is the Thevenin equiv.


$$V_T = -7V \quad R_T = 0\Omega$$

No y-intercept $\Rightarrow I_N$ does not exist

Norton equiv does not exist!

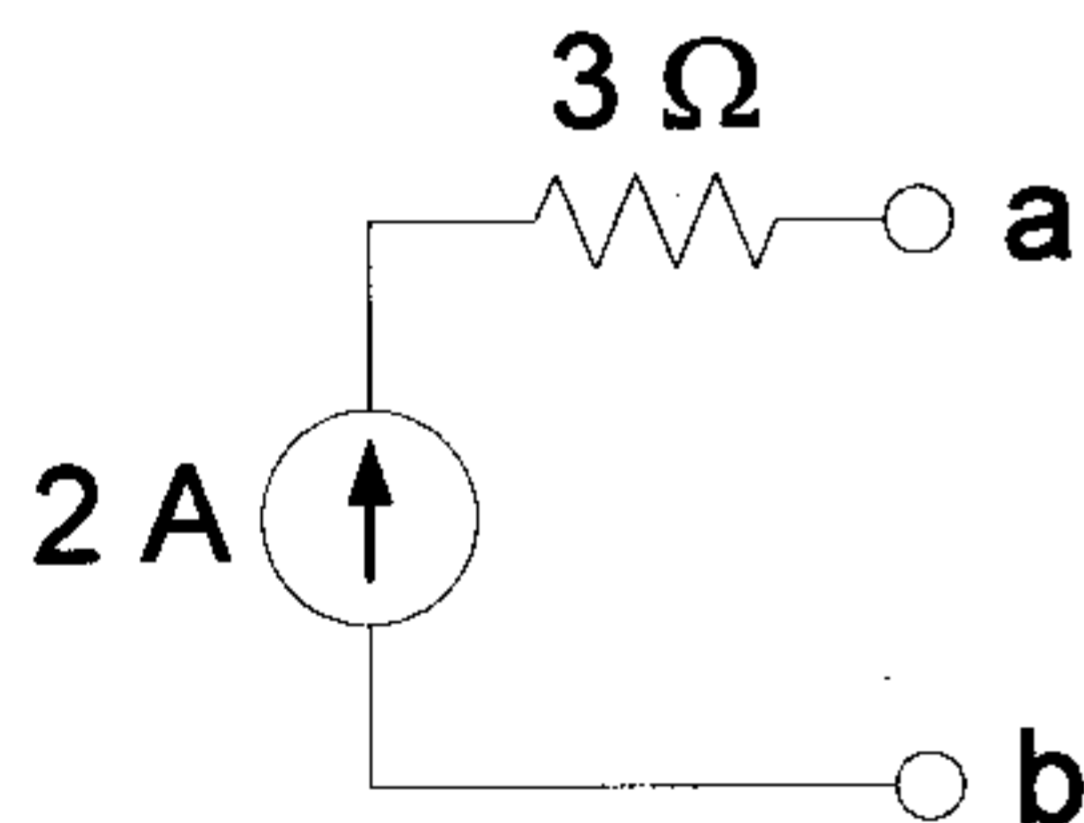


I-V graph

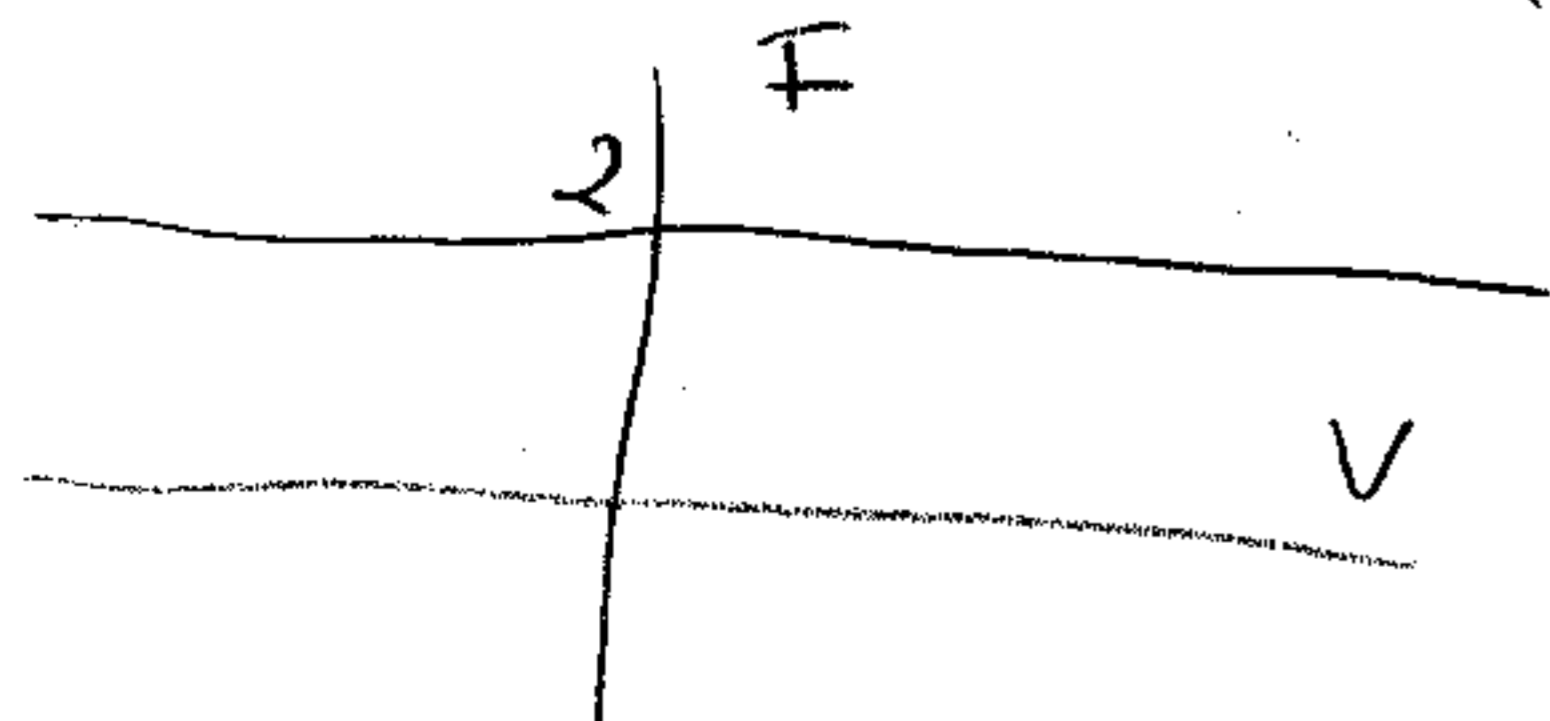

I-V graph same as 2A source alone without resistor

Norton equivalent:

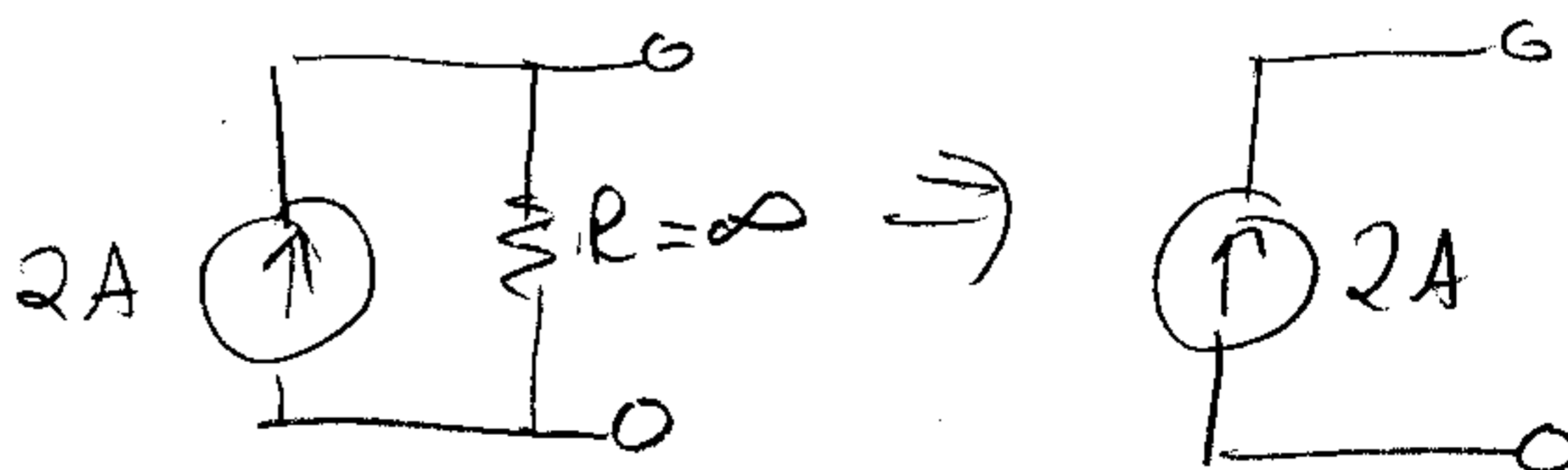


No x-intercept $\Rightarrow V_T$ does not exist

Thevenin equivalent does not exist!

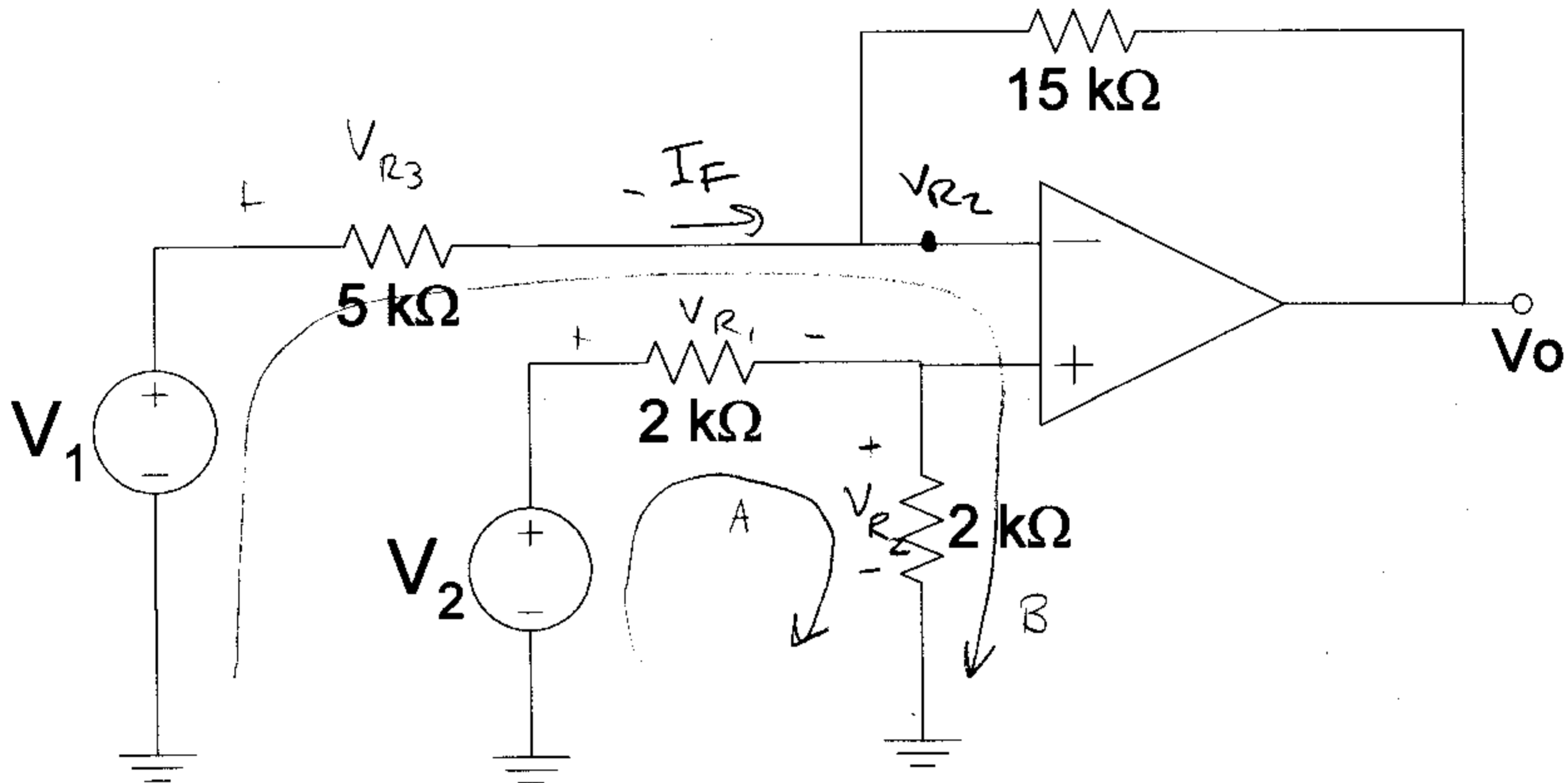Problem 6: 15 Points Possible

For the ideal operational amplifier circuit below, find V_o in terms of V_1 and V_2 . Assume that the operational amplifier is operating linearly (ignore the rails).



KVL on input loops:

A: $-V_2 + V_{R1} + V_{R2} = 0$

but since same resistance and same current (no current into op-amp input),

$-V_2 + 2V_{R2} = 0$

$V_{R2} = V_2/2$

B: $-V_1 + V_{R3} + V_{R2} = 0$

$V_{R3} = V_1 - V_{R2} = V_1 - V_2/2$

Feedback current:

$I_F = \frac{V_{R3}}{5k} = \frac{V_1}{5k} - \frac{V_2}{10k}$

KVL on output loop:

$-V_o - 15kI_F + V_{R2} = 0$

$V_o = V_{R2} - 15kI_F$

$= \frac{V_2}{2} - 15k \left(\frac{V_1}{5k} - \frac{V_2}{10k} \right)$

$= \frac{V_2}{2} - 3V_1 + 1.5V_2$


$= \boxed{2V_2 - 3V_1}$

Name: Solutions**Problem 7:** 15 Points Possible

Design an operational amplifier circuit that has an output voltage $V_O = 3V_2 - 5V_1$. The input voltage sources V_1 and V_2 cannot be detached from ground, and each have their negative terminals at ground. Assume that your amplifier is operating linearly.

You will lose 5 points if you use more than one differential amplifier. If you are desperate, the instructor will "sell" you a hint for points.

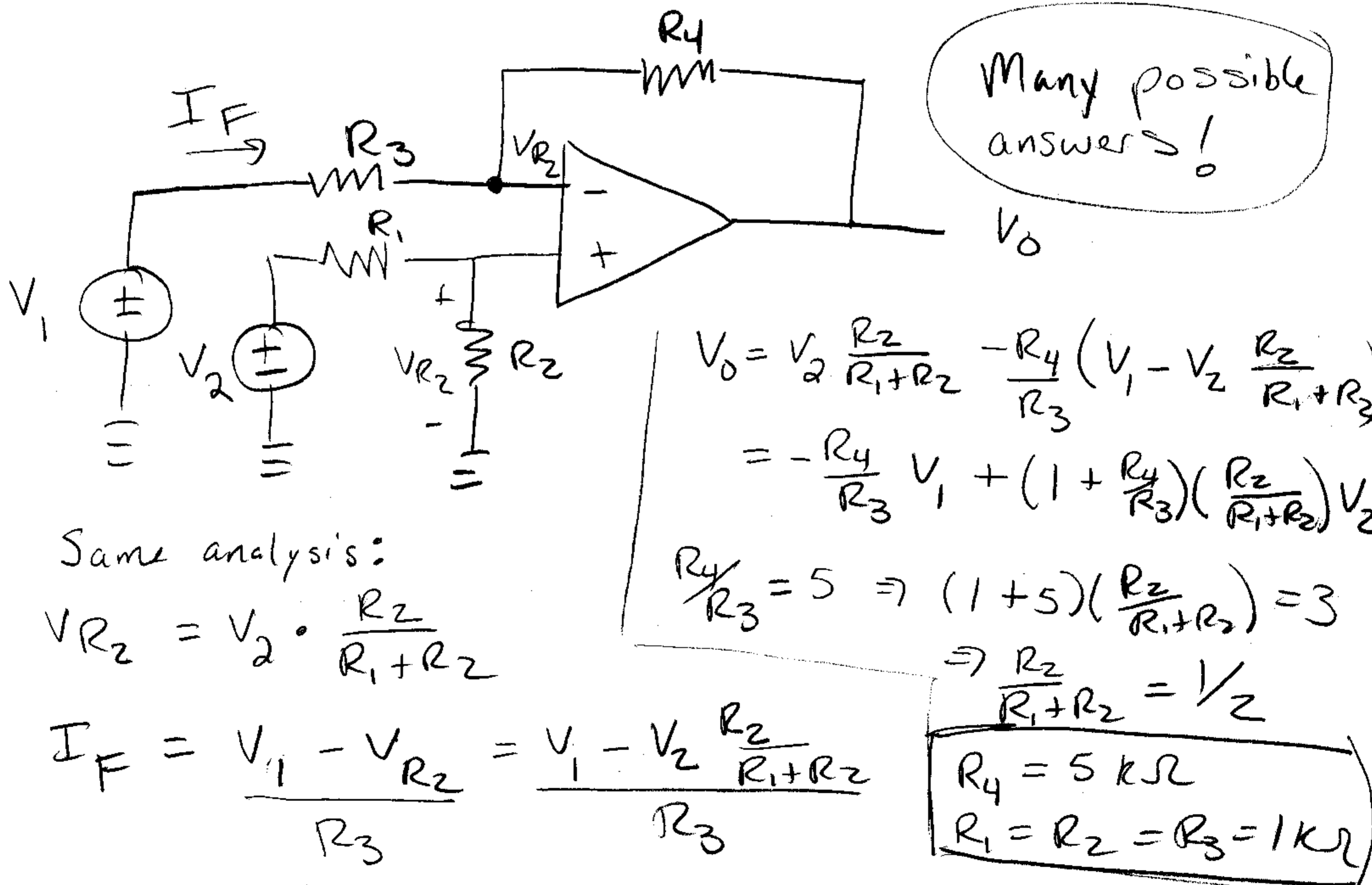$3V_2 - 5V_1$ has same form as Problem 6
(V_2 on non-inverting, V_1 on inverting terminal)
Use same circuit, change values:



Same analysis:


$$V_{R_2} = V_2 \cdot \frac{R_2}{R_1 + R_2}$$

$$I_F = \frac{V_1 - V_{R_2}}{R_3} = \frac{V_1 - V_2 \frac{R_2}{R_1 + R_2}}{R_3}$$

$$-V_O - R_4 I_F + V_{R_2} = 0 \Rightarrow V_O = V_{R_2} - R_4 I_F \quad \uparrow$$

Problem 8: 5 Points Possible

Suppose that we want to "clean up" a logic signal by transforming input voltages over 2.5 V (the threshold voltage) to 5 V (logic 1) as output and voltages under 2.5 V to logic 0. Design a differential amplifier circuit that will perform this function. You may use one ideal differential amplifier; $R_i = \infty$, $R_o = 0 \Omega$ and gain $A = \infty$. You must specify the rail voltages for this amplifier.

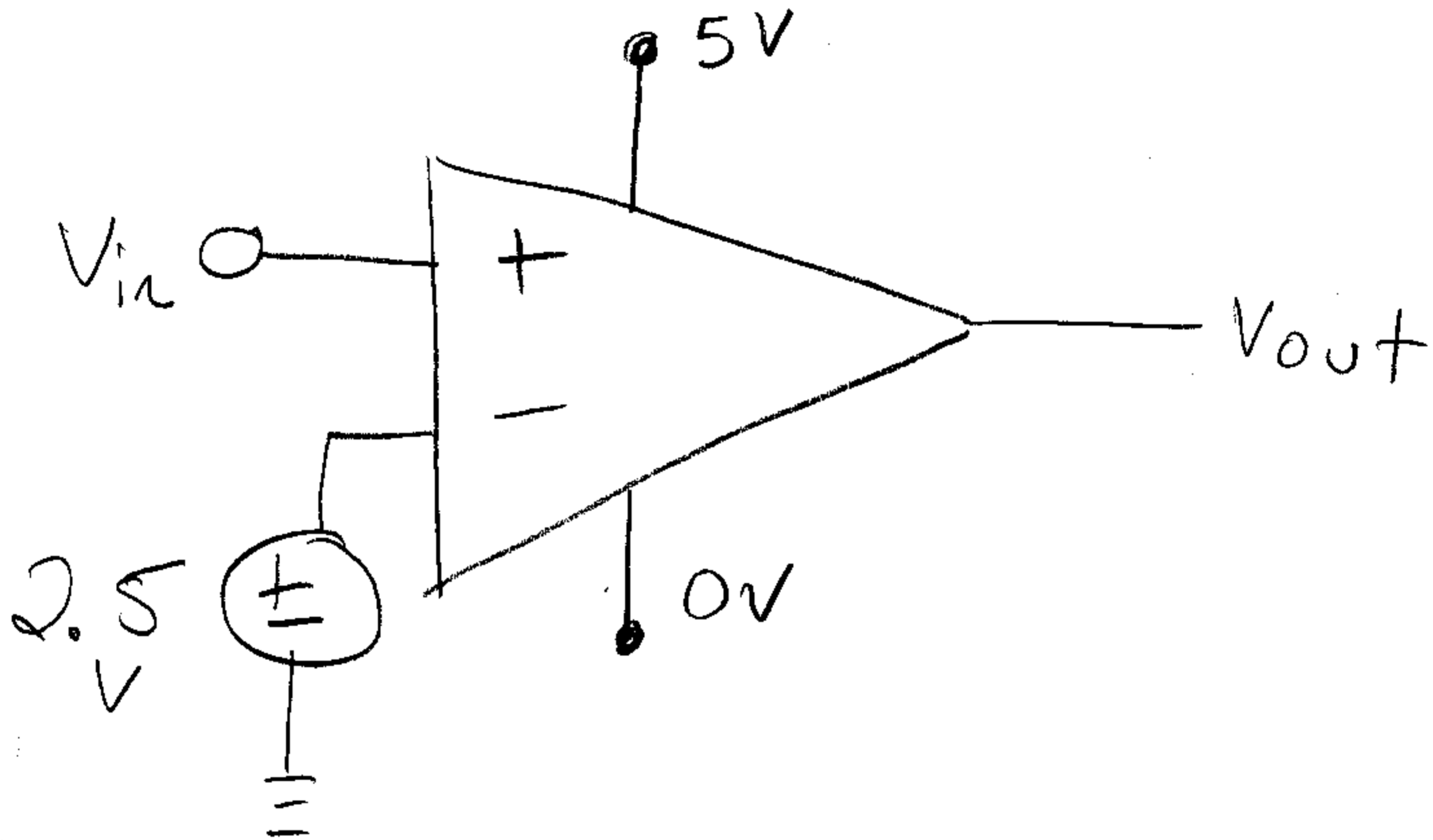

Problem 9: 15 Points Possible

Now suppose that your differential amplifier circuit from Problem 8 has a finite gain $A = 10,000$. For the input $v_i(t)$ defined below, determine the propagation delay t_p , where $t_p =$ time output reaches 50% of final value - time input reaches 50% of final value.

$$v_i(t) = \begin{cases} 0 & \text{for } t < 0 \\ t & \text{for } 0 \leq t \leq 5 \\ 5 & \text{for } t > 5 \end{cases} \quad \begin{array}{l} t \text{ in seconds, } v_i \text{ in volts} \end{array}$$

time input reaches 50% of f.v. is

$$\text{time } v_i(t) = 2.5 \text{ V}$$

$$t = 2.5 \text{ s (from above definition)}$$

During transition, V_{out} has equation

$$\begin{aligned} V_{out}(t) &= A(V_p - V_n) = 10^4 (v_i(t) - 2.5 \text{ V}) \\ &= 10^4 v_i(t) - 2.5 \cdot 10^4 \end{aligned}$$

$$\text{Want } V_{out}(t) = 2.5$$

$$2.5 = 10^4 v_i(t) - 2.5 \cdot 10^4$$

$$10^4 v_i(t) = 2.5 + 2.5 \cdot 10^4$$


$$v_i(t) = 2.5 + 2.5 \cdot 10^{-4}$$

$$\text{this occurs when } t = 2.5 + 2.5 \cdot 10^{-4}$$

$$\text{difference in times: } 2.5 + 2.5 \cdot 10^{-4} - 2.5 = \boxed{250 \mu\text{s}}$$

Problem 10: 10 Points Possible

Find the time constant for the RC circuit below. DO NOT INCLUDE || symbol in final answer; write the full mathematical expression.

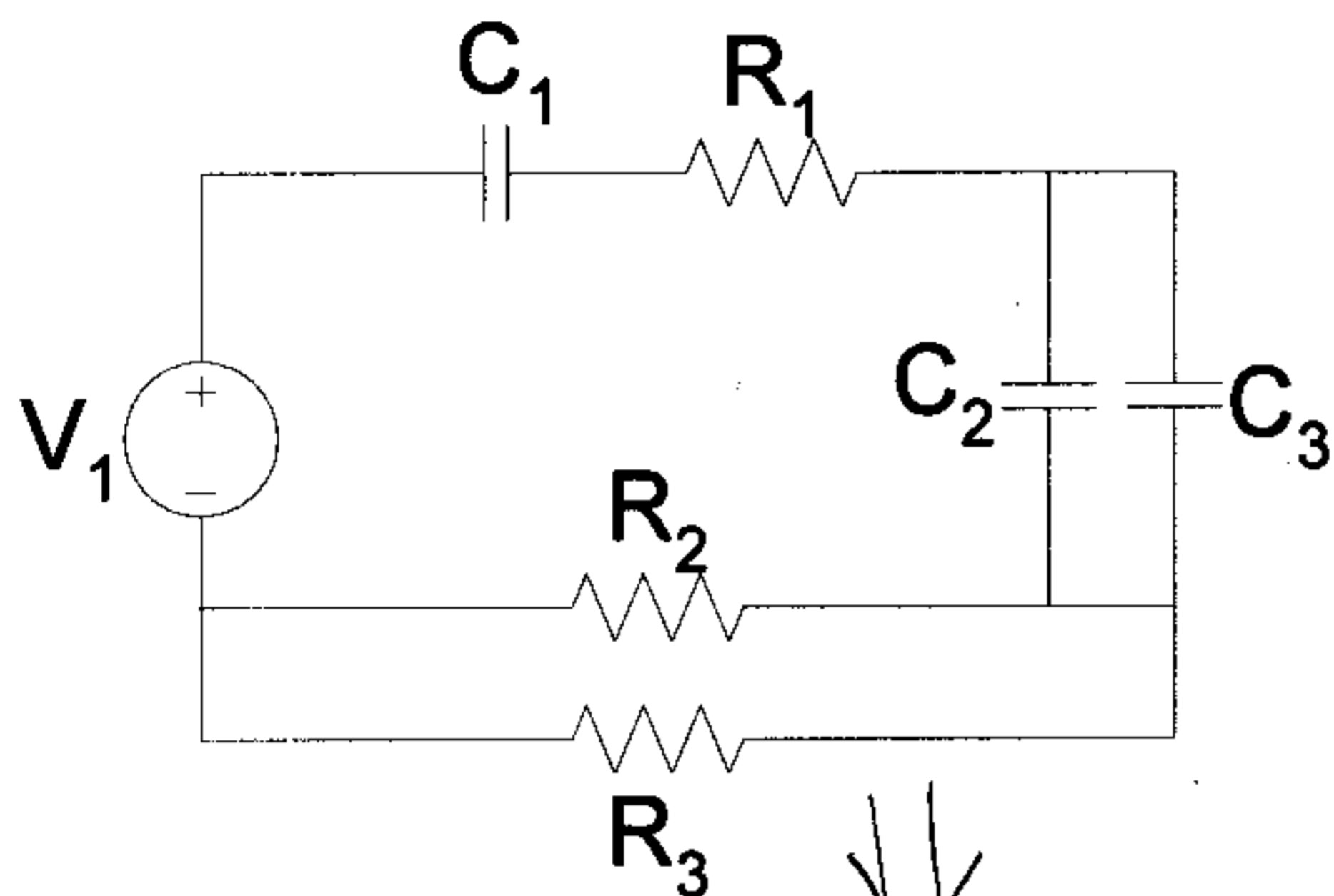

$$\begin{aligned} \tau &= R_{eq} C_{eq} \\ &= \left(R_1 + \frac{R_2 R_3}{R_2 + R_3} \right) \left(\frac{C_1 (C_2 + C_3)}{C_1 + C_2 + C_3} \right) \end{aligned}$$

