

UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering and Computer Sciences

EECS 40
Introduction to Microelectronic Circuits

Fall 2003
Prof. King

FINAL EXAMINATION
December 10, 2003
Time allotted: 2 hours 50 minutes (170 minutes)

NAME: _____, _____
(print) **Last** **First**

Signature: _____ **STUDENT ID#:** _____

1. This is a **CLOSED BOOK** exam. However, you may use 3 sheets of notes and a calculator.
2. **SHOW YOUR WORK or REASONING** on this exam.
(Make your methods clear to the grader.)
3. **Write your answers clearly (legibly) in the spaces (lines, boxes, or plots) provided.**
4. Remember to specify the units on answers whenever appropriate.

SCORE: 1 _____ / 20

2 _____ / 20

3 _____ / 20

4 _____ / 20

5 _____ / 20

6 _____ / 20


7 _____ / 20

8 _____ / 10

Total: _____ / 150

Problem 1: Circuit Analysis and Equivalent Circuits [20 points in total]

a) Consider the following circuit:

 

i) Use a source transformation in order to find i_x . [6 pts]

$$i_x = \underline{\hspace{2cm}}$$


ii) What is the power developed/absorbed by the 5 mA current source? [3 pts]

$$\text{Power} = \underline{\hspace{2cm}}$$

[developed, absorbed]
(circle the correct choice)

Problem 1 (continued)

b) Consider the following circuit:

 


i) Find V_{out} . [6 pts]

$V_{out} =$ _____


ii) Draw the Thevenin Equivalent circuit. [5 pts]

Thevenin Equivalent Circuit:

 

Problem 2: Op Amp Circuit [20 points in total]

 a) The following is the circuit model for an op amp circuit operating in its linear region:




Typically, R_{in} is very large ($\sim 1 \text{ M}\Omega$), A is very large ($> 10^4$), and R_{out} is very small ($< 100 \Omega$).

What type of feedback is used in an op amp circuit, in order to ensure that the op amp will operate in its linear region? Illustrate (with a simple diagram) how this is achieved. [5 pts]

Problem 2 (continued)

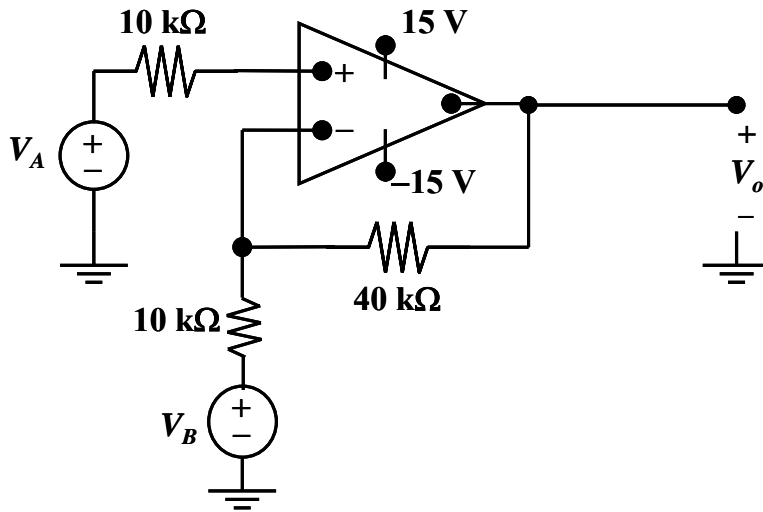
b) Consider the following op amp circuit below. You can assume that the op amp is ideal.



i) Find an expression for V_o , using superposition. [10 pts]


$V_o =$ _____

ii) Suppose V_A is fixed at 1 Volt. Plot V_o vs. V_B . [5 pts]

 

 Problem 3: First-Order Circuits [20 points in total]

In the circuit below, the switch is open for all $t < 0$. The switch is closed at $t = 0$, and then it is opened again at $t = 10$ ms.




i) Write an equation for $v_c(t)$, for $0 \leq t \leq 10$ ms. [8 pts]

$0 \leq t \leq 10$ ms: $v_c(t) =$ _____

ii) Write an equation for $v_c(t)$, for $t > 10$ ms. [8 pts]


$t > 10$ ms: $v_c(t) =$ _____

iii) Sketch $v_c(t)$ for $t > 0$ [4 pts]

 

Problem 4: pn junctions; diodes [20 points in total]

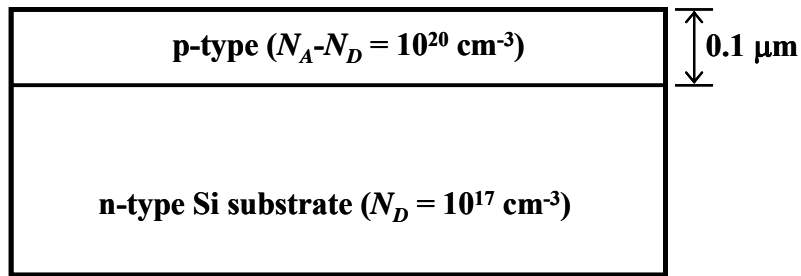- a) Consider a pn junction formed in the surface of an n-type silicon wafer maintained at $T = 300\text{K}$. The p and n regions are uniformly doped, as indicated in the figure below:



Schematic cross-sectional view of pn junction

In the p-type region, the electron mobility is $100 \text{ cm}^2/\text{V}\cdot\text{s}$ and the hole mobility = $50 \text{ cm}^2/\text{V}\cdot\text{s}$


- i) Estimate the sheet resistance of the p-type region. [6 pts]
(Use the following values of constants: $q = 1.6 \times 10^{-19} \text{ C}$, $n_i = 10^{10} \text{ cm}^{-3}$)

Sheet resistance = _____


- ii) Suppose the p-type region serves as the drain region of a p-channel MOSFET in a CMOS inverter, and that the n-type substrate is therefore biased at the power-supply voltage V_{DD} . How will the pn-junction capacitance change as the PMOSFET is turned on (so that the drain bias is changed from 0 V to V_{DD})? Explain briefly. [4 pts]

Problem 4 (continued)

 
b) Consider the diode circuit below. Assume the diode is a perfect rectifier.



i) Plot v_{out} vs. v_{in} . [5 pts]

 


ii) Sketch v_{out} for the given $v_{in}(t)$, using the same axes. [5 pts]

 

Problem 5: MOSFET [20 points in total]

a) Consider an NMOSFET with parameters $W = 1 \mu\text{m}$, $L = 0.1 \mu\text{m}$, $k_n' = 10^{-3} \text{ A/V}^2$, $V_T = 0.5\text{V}$, biased at $V_{GS} = V_{DD} = 1 \text{ V}$. The areal gate capacitance $C_{ox} = 3 \times 10^{-6} \text{ F/cm}^2$.

 i) Accurately sketch the I_D vs. V_{DS} characteristic in the range $0 \leq V_{DS} \leq 1 \text{ V}$, neglecting velocity saturation and channel-length modulation. Indicate the numerical values for the saturation voltage (V_{DSAT}) and current (I_{DSAT}). [6 pts]



ii) Estimate the effective resistance of this MOSFET (for digital circuit applications). (Again, assume that velocity saturation and channel-length modulation can be neglected. [3 pts]

iii) On the same plot in part (i) above, accurately sketch and label the I_D vs. V_{DS} characteristic, taking into account that the electron velocity in the MOSFET channel saturates at 10^7 cm/s . [5 pts]

Problem 5 (continued)

- b) High drive current (I_{DSAT}) is desirable for reduced equivalent resistance, to achieve smaller propagation delay to allow higher-speed circuit operation. Indicate in the table below how you would adjust various MOSFET parameters so as to increase I_{DSAT} . Briefly describe the tradeoff or disadvantage involved, if any, for each. (For example, the answer for gate length L is given.) [6 pts]

| MOSFET Parameter | To increase I_{DSAT}, parameter must be | Associated tradeoff or disadvantage |
|-------------------------|---|--|
| Gate length L | decreased | Subthreshold leakage current increases, so that static power dissipation increases |
| Threshold voltage V_T | | |
| Channel width W | | |

Problem 6: Logic Circuits [20 points in total]

a) Given the following truth table for the logic function **F**:

| A | B | F |
|----------|----------|----------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

i) Write a simple logic expression for **F**. [2 pts]


F = _____

ii) Implement the function **F**, using only 2-input NAND gates. [5 pts]

Logic circuit for F:







Problem 6 (continued)

 b) Consider the S-R flip-flop circuit below:




The output C is initially equal to 0, and the output D is initially equal to 1.

For the given S and R timing diagrams below, draw the timing diagrams (for $t > 0$) for A, B, C, and D on the plots provided. [13 pts]

      

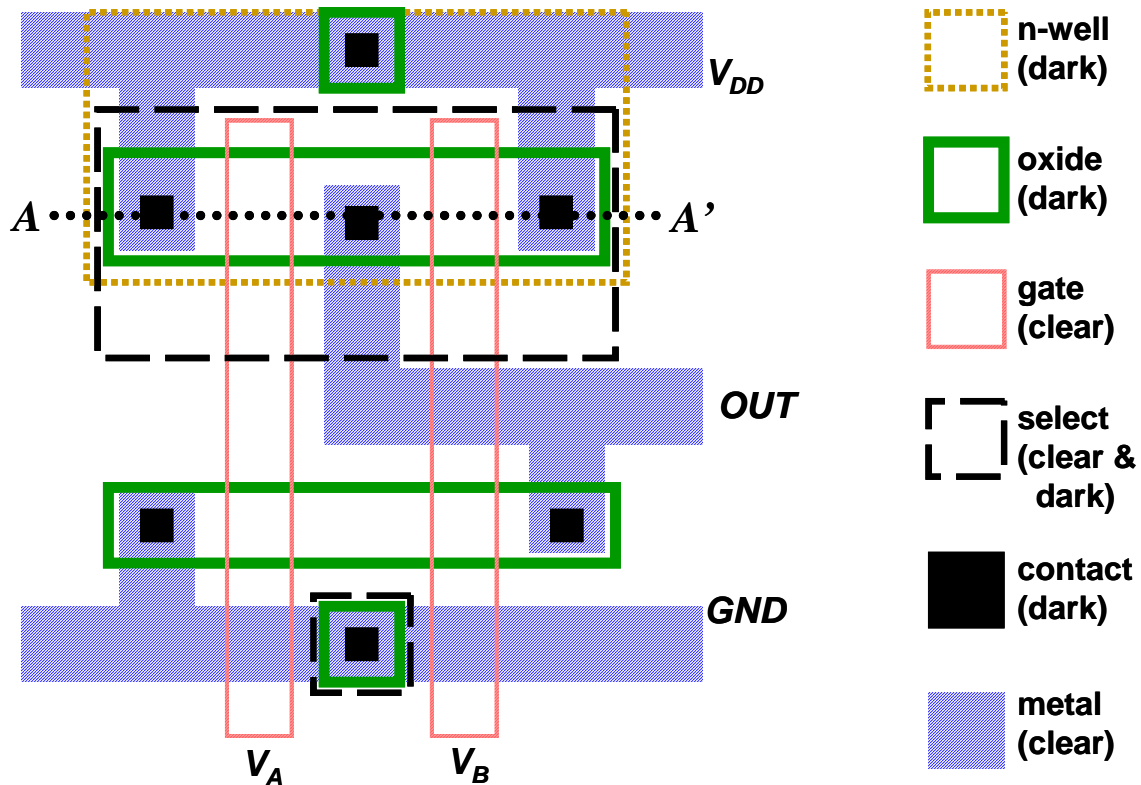Problem 7: CMOS Technology [20 points in total]

The layout of a CMOS logic gate is shown below:




The following fabrication process (starting with a p-type Si wafer) is used:

1. Thermally grow 700 nm of SiO_2 .
2. Pattern the SiO_2 using the n-well mask.
3. Implant phosphorus and perform a high-temperature, long anneal to “drive in” the well to a depth of 1 μm .
4. Remove the SiO_2 (using a highly selective wet etch process which does not etch Si).
5. Grow 0.5 μm of SiO_2 (“field oxide”).
6. Pattern the SiO_2 using the oxide mask.
7. Thermally grow 10 nm of SiO_2 (“gate oxide”) in the bare regions of the Si.
8. Deposit 200 nm of poly-Si (by CVD).
9. Pattern the poly-Si using the gate mask.
10. Use clear-field select mask to pattern photoresist; implant phosphorus. This will form the n+ source and drain junctions for the n-channel MOSFETs.
11. Use dark-field select mask to pattern photoresist; implant boron. This will form the p+ source and drain junctions for the p-channel MOSFETs.
12. Thermally anneal the wafer in order to activate the implanted dopants. The final source/drain junction depth is 100 nm.
13. Deposit 0.5 μm of SiO_2 (“passivation oxide”).
14. Pattern the deposited SiO_2 using the contact mask.
15. Deposit 0.5 μm of aluminum.
16. Pattern the aluminum using the metal mask.


Problem 7 (continued)

 a) Draw cross-section A-A' in the space provided. Identify all layers clearly. [10 pts]



Cross-section A-A'

 b) Draw the circuit schematic, labeling V_{DD} , GND , V_A , V_B , and OUT . [5 pts]



Circuit Schematic

c) Assuming that $k_n' = 3k_p'$, would you expect this logic gate to have comparable worst-case “pull-up” and “pull-down” propagation delays? (Is $t_{pLH} \cong t_{pHL}$?) Justify your answer. [5 pts]

Problem 8: Technology Scaling (Short-Answer Questions) [10 points in total]

a) Explain how transistor scaling improves both the cost (per function) and performance (circuit operating speed) of CMOS integrated circuits. **[5 pts]**

b) Explain why interconnect delay is becoming more of a concern as CMOS technology advances. **[5 pts]**