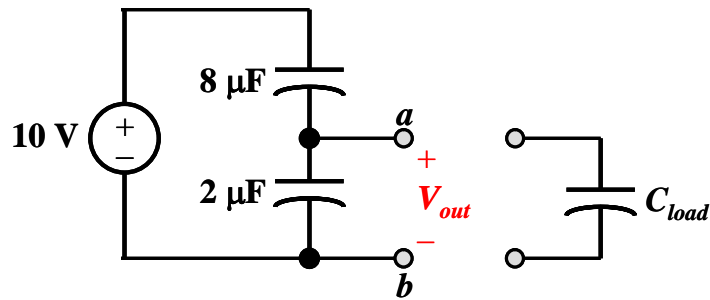


Problem 1: Energy-Storage Elements and 1st-Order Circuits [16 points in total]


a) Consider the capacitive voltage-divider circuit below. Find V_{out} . How will V_{out} change if a small load capacitance $C_{load} < 2 \mu\text{F}$ is connected between terminals a and b ? [4 pts]



$V_{out} =$ _____

V_{out} will [increase, decrease, not change] (circle one) when C_{load} is connected, because

b) Consider the following RC circuit:

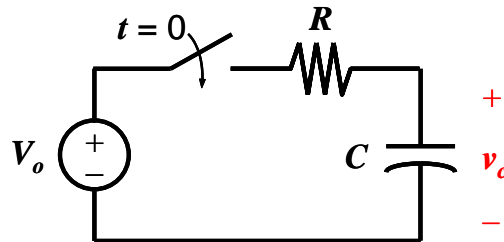


Provide a physical reason why it takes longer for v_c to reach its final value if R is increased. (Why is the characteristic time constant τ proportional to R ?) [2 pts]


v_c will take longer to reach its final value if R is increased because

Problem 1 (continued)

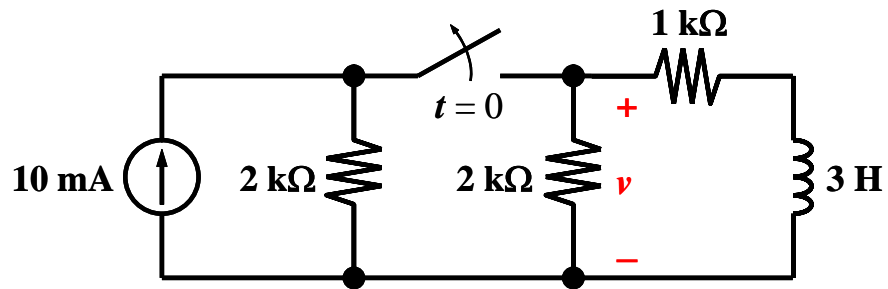- c) Assume that the circuit below is operating in steady state with the switch open for $t < 0$. Find and accurately sketch $v(t)$ for all t . [10 pts]



For $t < 0$: $v(t) =$ _____. For $t > 0$: $v(t) =$ _____

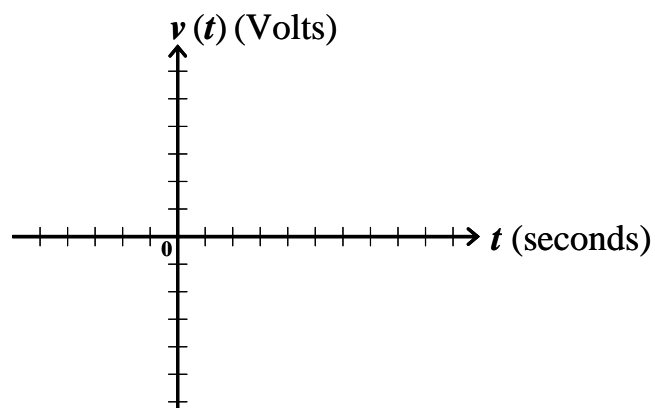

Problem 2: Semiconductor Materials and Devices [17 points in total]

- a) Consider a Si sample maintained at $T = 300\text{K}$, uniformly doped with Arsenic atoms to a concentration $3 \times 10^{16} \text{ cm}^{-3}$. The electron mobility = $1000 \text{ cm}^2/\text{V}\cdot\text{s}$; hole mobility = $400 \text{ cm}^2/\text{V}\cdot\text{s}$.
- i) Estimate the resistivity of this sample. (Use $q = 1.6 \times 10^{-19} \text{ C}$ in your calculation.) [4 pts]

resistivity = _____

- ii) How will the resistivity of this sample change if it were to be doped additionally with $3 \times 10^{16} \text{ cm}^{-3}$ Phosphorus atoms? [3 pts]


The resistivity will [increase, decrease, not change] (circle one)
by a factor that is [greater than, less than, equal to] (circle one) 2 when phosphorus is added because

- b) Explain (using 1 or 2 sentences) why a pn junction has capacitance. [2 pts]

A pn junction has capacitance because

Problem 2 (continued)

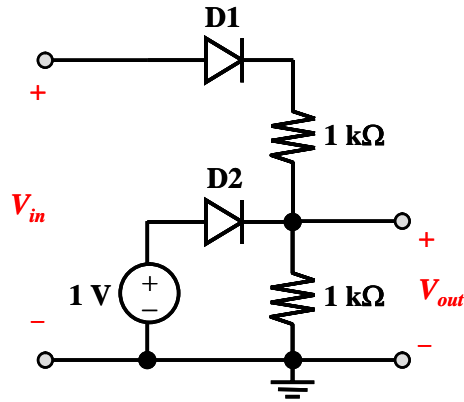c) Assume the diodes in the circuit below can be modeled as perfect rectifiers.




i) For what values of V_{in} is D1 on? Explain your reasoning. [3 pts]

D1 is on for V_{in} _____ because

ii) For what values of V_{in} is D2 on? Explain your reasoning. [2 pts]


D2 is on for V_{in} _____ because

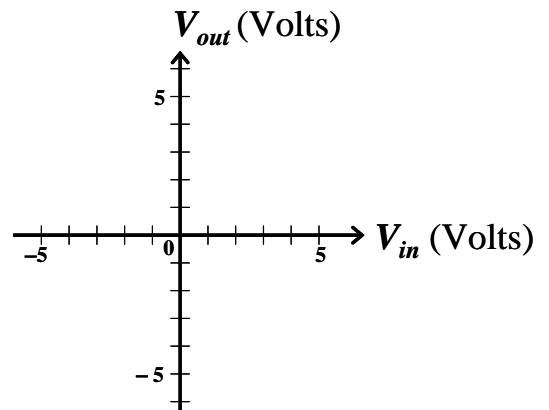iii) Accurately plot V_{out} vs. V_{in} on the axes provided. [3 pts]




Problem 3 (continued)

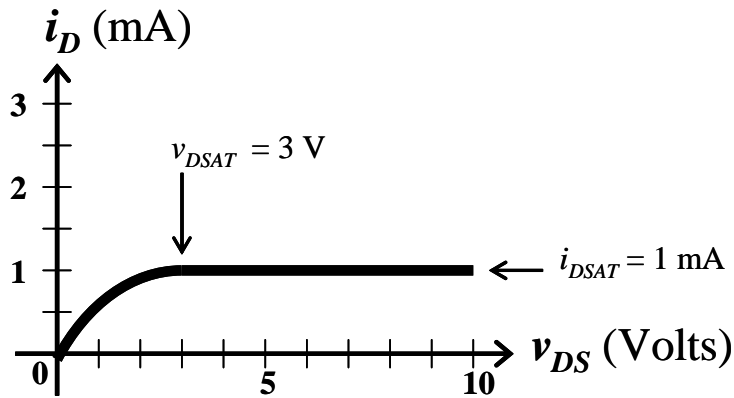b) Below to the left is the i_D vs. v_{DS} characteristic for a long n-channel MOSFET with $V_T = 1$ V.



What is V_{GS} ? [2 pts]

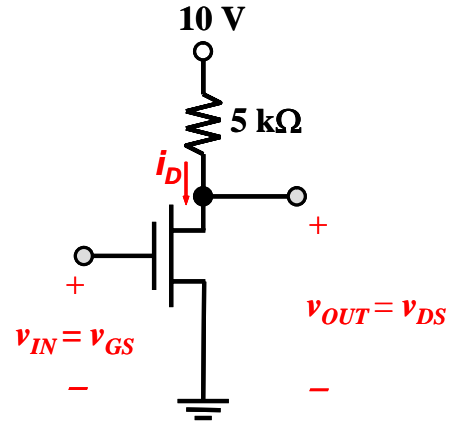

$V_{GS} = \underline{\hspace{2cm}}$

c) Suppose the MOSFET in part (b) is used in the amplifier circuit shown above to the right.

i) Draw the load line on the MOSFET i_D - v_{DS} plot (above to the left). [3 pts]

ii) In what region is the MOSFET operating? [2 pts]

The MOSFET is operating in the [linear, saturation, cutoff] (circle one) region because

iii) What is the incremental change in the output voltage (*i.e.* v_{out}) for a -1 mV change in the input voltage (*i.e.* $v_{gs} = -1$ mV)? [4 pts]

$v_{out} = \underline{\hspace{2cm}}$