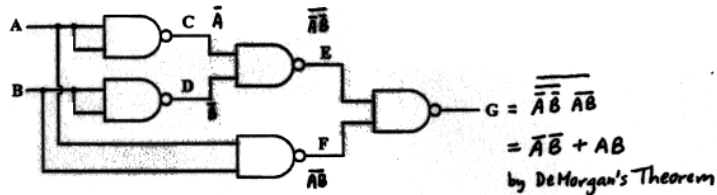


Problem 1: Logic Gates and Timing Diagrams [25 points]

Consider the following digital logic circuit:



a) Fill out the truth table for the logic function G. [8 pts]

A	B	G
0	0	1
0	1	0
1	0	0
1	1	1

b) Write a simple logical expression for the function G. [5 pts]


$$G = \overline{AB} + AB$$

c) How many unit gate delays are there between the inputs (A and B) and the output (G)? [2 pts]
(In other words, how many unit gate delays must you wait, after changing A and/or B, before you can trust the value of G to be valid?)


The longest path between the input variables and the output variable is 3 logic gates. Therefore, we need to wait for a period of 3 unit gate delays after an input variable is changed, before we can trust the value of G to be valid.

3 unit gate delays

Problem 1 (continued)

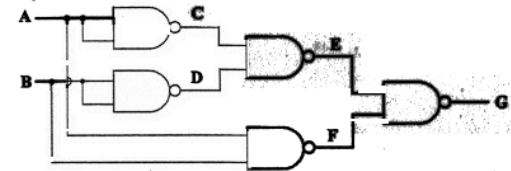

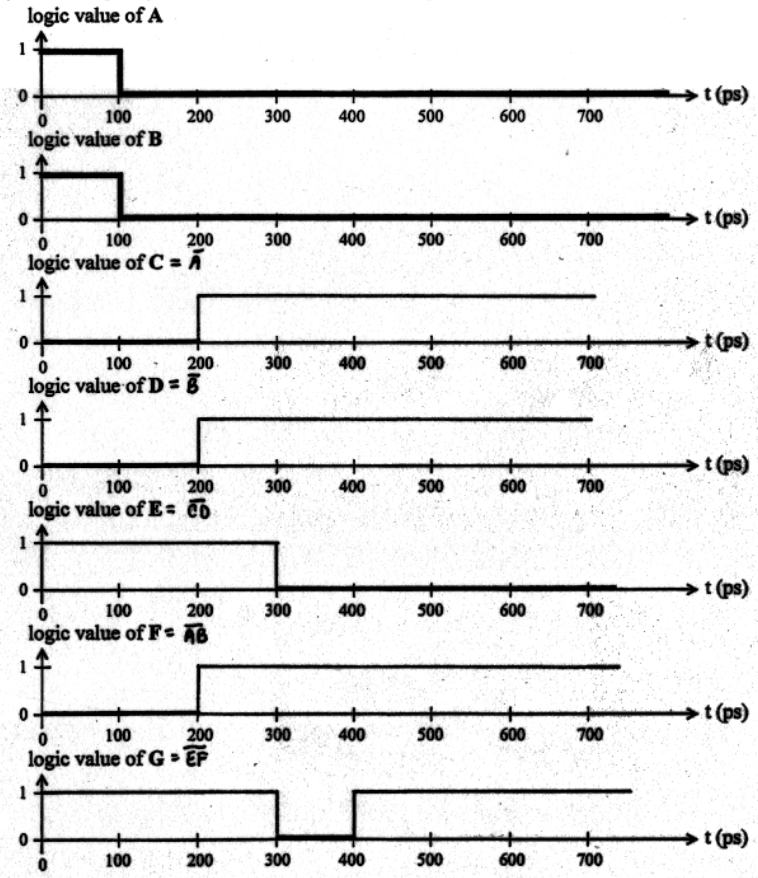d) Assume each logic gate has a unit gate delay $\tau = 100$ ps. Draw the timing diagrams for $t=0$ to $t=700$ ps, for the given logic input values A and B. [10 pts]



Truth tables:


C	D	E
0	0	1
0	1	1
1	0	1
1	1	0

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

E	F	G
0	0	1
0	1	1
1	0	1
1	1	0


Problem 2: Resistive Circuits [30 points]

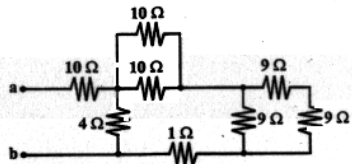a) Find the equivalent resistance R_{ab} for the following circuit. [6 pts]






$R_{ab} = 13 \Omega$

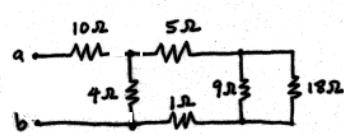9Ω resistors in series → 18Ω resistor
10Ω resistors in parallel → 5Ω resistor



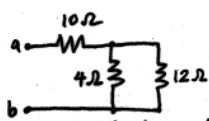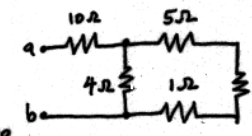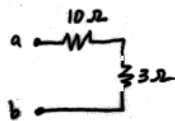9Ω resistor in parallel with 18Ω resistor → $\frac{9 \cdot 18}{9+18} = 6\Omega$ resistor





5Ω, 6Ω, 1Ω resistors in series → 12Ω resistor

$(\frac{4 \cdot 12}{4+12} = 3)$

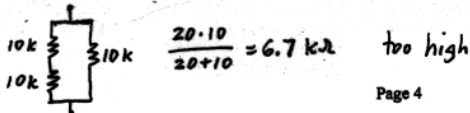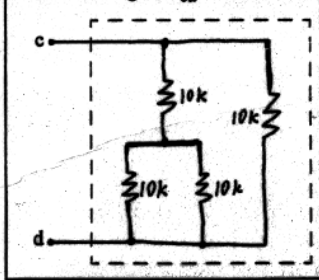b) Suppose you need a 6 kΩ resistor for your Tutebot project, but your TA gives you only a supply of 10 kΩ resistors. Being a clever Cal student, how would you connect several 10 kΩ resistors together, to achieve a 6 kΩ resistance? [7 pts]

- To achieve an equivalent resistance lower than the individual resistors, we should connect resistors in parallel.
- But the parallel combination of 2 10kΩ resistors is 5kΩ — too low!
⇒ need to increase the resistance of one of the parallel branches
- Try parallel combination of a 10kΩ resistor and two 10kΩ resistors in series:

Circuit diagram of 10-kΩ resistors connected to give $R_{cd} = 6 \text{ k}\Omega$:




$\frac{20 \cdot 10}{20+10} = 6.7 \text{ k}\Omega$ too high

Try increasing the resistance of one parallel branch by only 5kΩ (10kΩ // 10kΩ) instead of 10kΩ
 $\frac{15 \cdot 10}{15+10} = 6 \text{ k}\Omega$!

Problem 2 (continued)

c) Consider the following circuit:

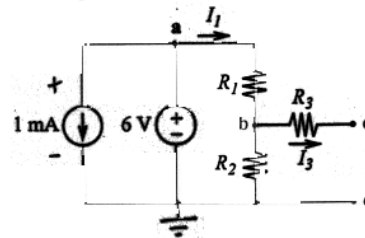

$R_1 = 1 \text{ k}\Omega$
 $R_2 = 2 \text{ k}\Omega$
 $R_3 = 2 \text{ k}\Omega$

d) Find V_{cd} [3 pts]

$V_{cd} = 4 \text{ V}$

$I_3 = 0$ since terminal c is not connected

Thus the current flowing through R_1 equals the current flowing through R_2 , i.e. we have a voltage divider. ⇒ $V_{bd} = \frac{R_2}{R_1+R_2} (6)$
Since there is no voltage drop across R_3 (because $I_3 = 0$), $V_c = V_b = \frac{2}{1+2} (6) = 4 \text{ V}$
⇒ $V_{cd} = V_{bd} = 2 \text{ V}$

ii) Find the power developed/absorbed by the current source, P_I . [3 pts]

The voltage across the current source is established by the voltage source and is equal to 6V.

$P_I = IV = (1 \text{ mA})(6 \text{ V}) = 6 \text{ mW}$

Since positive current is entering the positive terminal of the current source, it is absorbing power.

$P_I = 6 \text{ mW}$
[developed, absorbed] (circle correct choice)

iii) Indicate in the table below (by checking the appropriate boxes) how various circuit parameters would change if the terminals c and d were to be shorted together. Justify your answers. [6 pts]

Parameter	Value will:			Brief Explanation/Justification
	increase	decrease	not change	
V_{bd}		✓		The resistance between b and d decreases; by the voltage-divider formula, V_{bd} decreases
I_1	✓			Total resistance between a and d decreases; V_{ad} remains 6V; $I_1 = \frac{V_{ad}}{R_{ad}}$
Power developed by voltage source	✓			Since I_1 increases, the current supplied by the voltage source increases.

iv) What is the value of I_3 when the terminals c and d are shorted together? [5 pts]

Equivalent resistance between terminals a and d is

$R_1 + R_2 // R_3 = 1 + \frac{2 \cdot 2}{2+2} = 2 \text{ k}\Omega$

⇒ $I_1 = \frac{6 \text{ V}}{2 \text{ k}\Omega} = 3 \text{ mA}$


Using current-divider formula,

$I_3 = \frac{2}{2+2} (3 \text{ mA}) = 1.5 \text{ mA}$

$I_3 = 1.5 \text{ mA}$

Problem 3: Nodal Analysis [20 points]

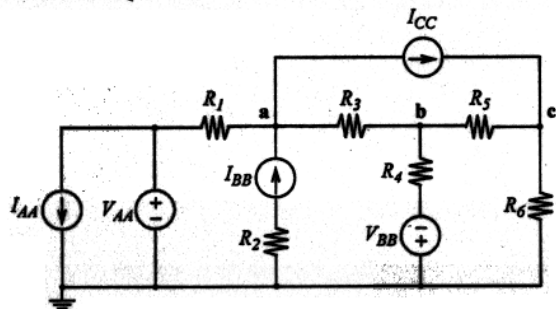- a) In the circuit below, the independent source values and resistances are known. Use the nodal analysis technique to write 3 equations sufficient to solve for V_a , V_b , and V_c . To receive credit, you must write your answer in the box below. [10 pts]
DO NOT SOLVE THE EQUATIONS!



Apply Kirchoff's Current Law to nodes a, b, c:
(Sum of currents entering a node = 0)

$$(a) \frac{V_{AA} - V_a}{R_1} + I_{BB} - I_{CC} + \frac{V_b - V_a}{R_3} = 0$$

$$(b) \frac{V_a - V_b}{R_3} + \frac{-V_{BB} - V_b}{R_4} + \frac{V_c - V_b}{R_5} = 0$$

$$(c) I_{CC} + \frac{V_b - V_c}{R_5} + \frac{-V_c}{R_6} = 0$$

} 3 independent equations for 3 unknowns (V_a, V_b, V_c)
⇒ can solve to find unknowns

Write the nodal equations here:


$$\frac{V_{AA} - V_a}{R_1} + I_{BB} - I_{CC} + \frac{V_b - V_a}{R_3} = 0$$

$$\frac{V_a - V_b}{R_3} - \frac{V_{BB} + V_b}{R_4} + \frac{V_c - V_b}{R_5} = 0$$

$$I_{CC} + \frac{V_b - V_c}{R_5} - \frac{V_c}{R_6} = 0$$

Problem 3 (continued)

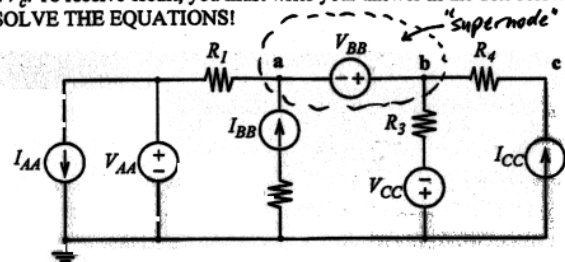- b) Similarly to part (a), use the nodal analysis technique to write 3 equations sufficient to solve for V_a , V_b , and V_c . To receive credit, you must write your answer in the box below. [10 pts]
DO NOT SOLVE THE EQUATIONS!



Current flowing through the voltage source V_{BB} cannot be expressed as a function of the node voltages V_a and V_b
⇒ use the "supernode" approach.

Applying Kirchoff's Current Law to the supernode and node c:

$$\text{supernode: } \frac{V_{AA} - V_a}{R_1} + I_{BB} + \frac{-V_{CC} - V_b}{R_3} + I_{CC} = 0$$

$$\text{node c: } \frac{V_b - V_c}{R_4} + I_{CC} = 0$$

Need one more equation in order to be able to solve for the 3 unknowns:

$$V_b - V_a = V_{BB}$$

Write the nodal equations here:


$$\frac{V_{AA} - V_a}{R_1} + I_{BB} - \frac{V_{CC} + V_b}{R_3} + I_{CC} = 0$$

$$\frac{V_b - V_c}{R_4} + I_{CC} = 0$$

$$V_b - V_a = V_{BB}$$

Problem 4: Thevenin and Norton Equivalent Circuits [25 points]

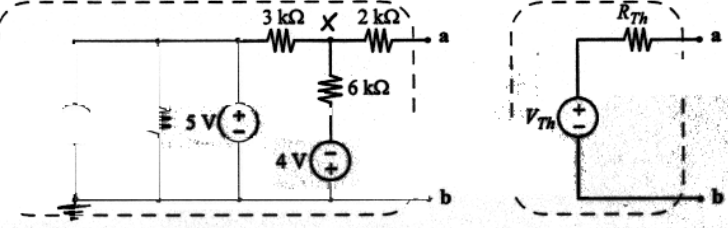a) Find the Thevenin Equivalent Circuit for the following circuit. [10 pts]




The open-circuit voltage, V_{oc} , is equal to V_{ab} , which is equal to V_{xb} since no current is flowing through the $2k\Omega$ resistor. Applying KCL to node x (defining node b as the reference node)

$$V_{Th} = 2 \text{ V}$$


$$R_{Th} = 4 \text{ k}\Omega$$

$$\rightarrow \frac{5 - V_x}{3} + \frac{-4 - V_x}{6} = 0 \Rightarrow 6 = 3V_x \Rightarrow V_x = 2 \text{ V} \therefore V_{oc} = V_{Th} = 2 \text{ V}$$

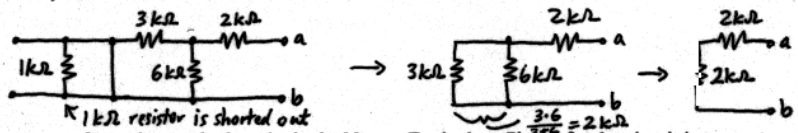To find R_{Th} , set all the independent sources to zero:



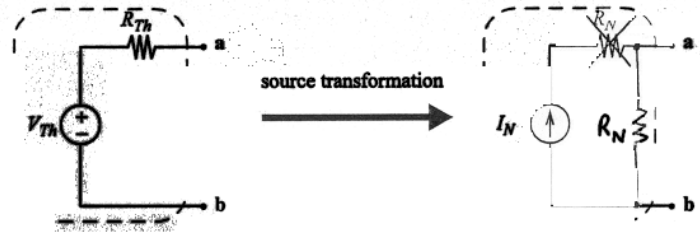b) Use the source transformation method to obtain the Norton Equivalent Circuit for the circuit in part (a). [5 pts]



$$R_N = R_{Th} = 4 \text{ k}\Omega$$



$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{2 \text{ V}}{4 \text{ k}\Omega} = 0.5 \text{ mA}$$

$$I_N = 0.5 \text{ mA}$$

$$R_N = 4 \text{ k}\Omega$$

Problem 4 (continued)

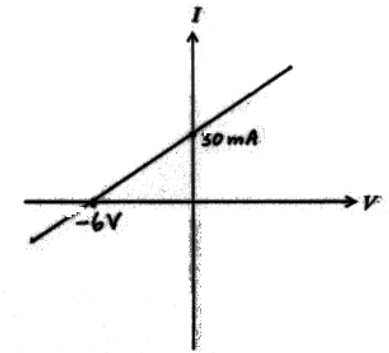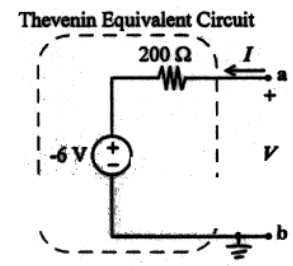
c) The Thevenin Equivalent Circuit for a certain linear circuit is given below. Plot the current (I) versus the output voltage (V) for the circuit, labelling the y-intercept and x-intercept. [5 pts]



When $I = 0$, $V = -6 \text{ V}$

When $V = 0$ (i.e. terminals a and b shorted together), $I = \frac{0 - (-6 \text{ V})}{200} = 30 \text{ mA}$

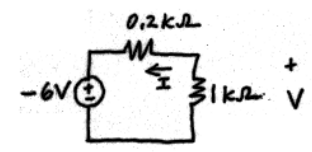d) The circuit in part (c) is connected to a $1 \text{ k}\Omega$ load resistor (placed between the terminals a and b). Find the power absorbed in the load resistor, P_{lk} . [5 pts]



$$P_{lk} = 25 \text{ mW}$$

Using voltage-divider formula, $V = \frac{1000}{1000 + 200} (-6) = -5 \text{ V}$

$$P = IV = \left(\frac{V}{R}\right)V = \frac{V^2}{R} = \frac{(-5)^2}{1000} = 25 \text{ mW}$$