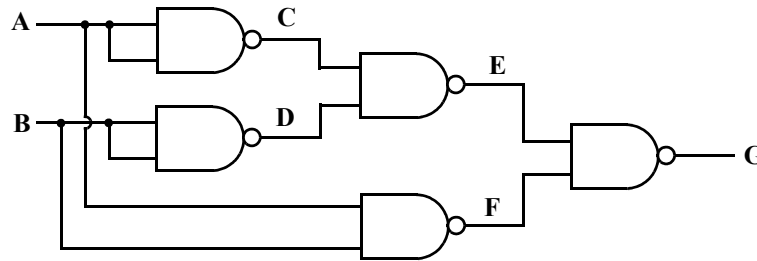


Problem 1: Logic Gates and Timing Diagrams [25 points]

Consider the following digital logic circuit:



a) Fill out the truth table for the logic function G. [8 pts]


A	B	G
0	0	
0	1	
1	0	
1	1	

b) Write a simple logical expression for the function G. [5 pts]

G = _____


c) How many unit gate delays are there between the inputs (A and B) and the output (G)? [2 pts]
 (In other words, how many unit gate delays must you wait, after changing A and/or B, before you can trust the value of G to be valid?)

_____ unit gate delays

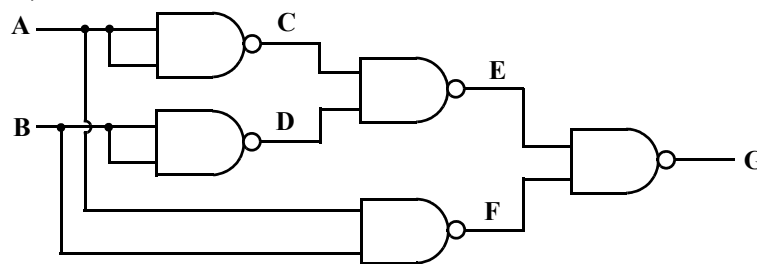Problem 1 (continued)


d) Assume each logic gate has a unit gate delay $\tau = 100$ ps.

Draw the timing diagrams for $t=0$ to $t=700$ ps, for the given logic input values A and B. [10 pts]

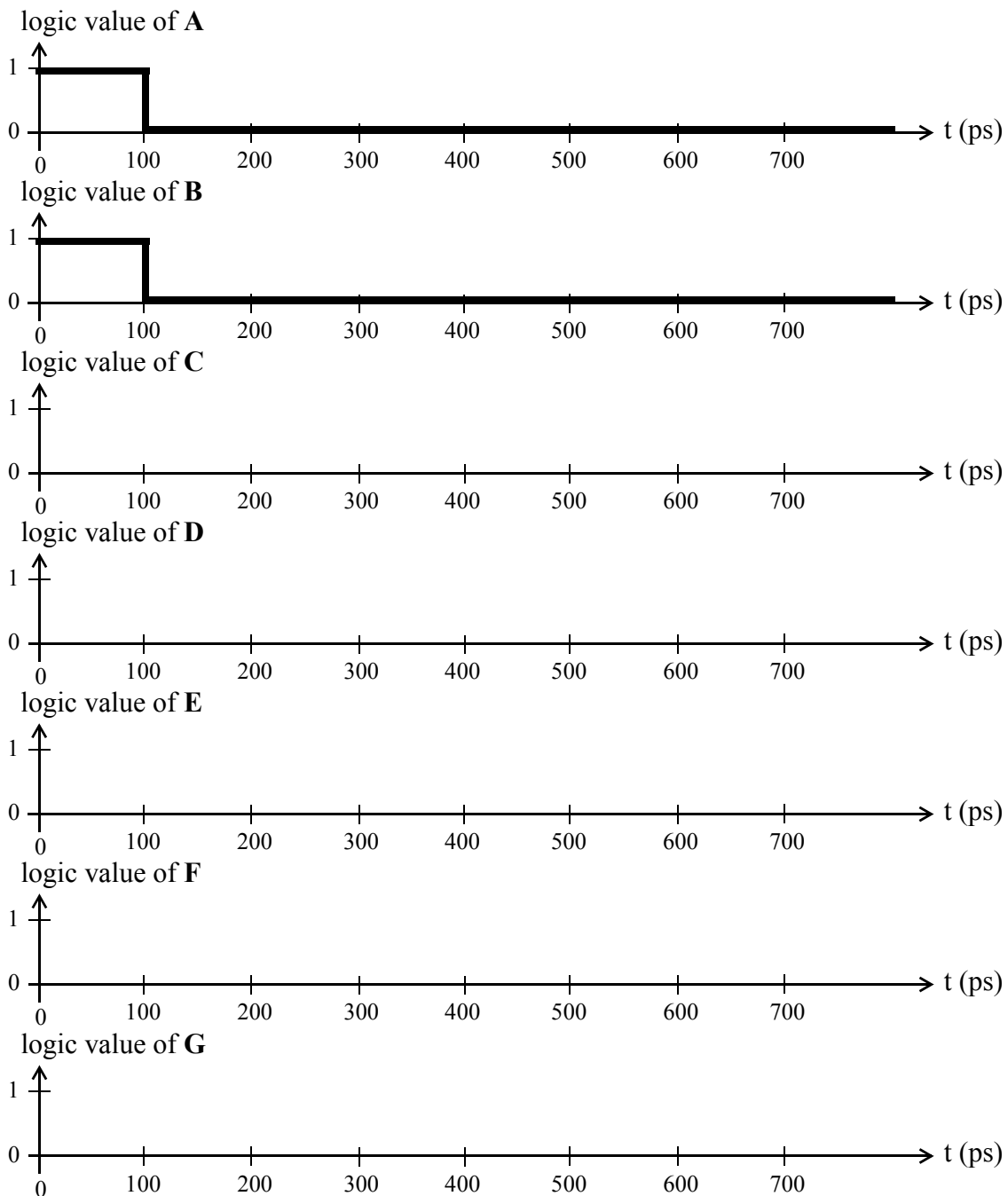

Problem 2: Resistive Circuits [30 points]

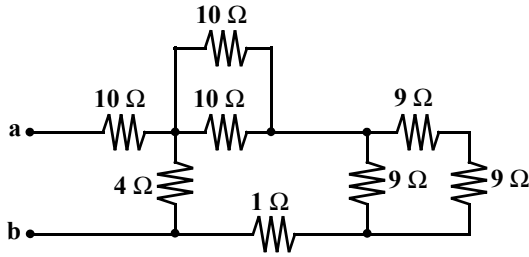
a) Find the equivalent resistance R_{ab} for the following circuit. [6 pts]



$R_{ab} = \underline{\hspace{2cm}} \Omega$
--

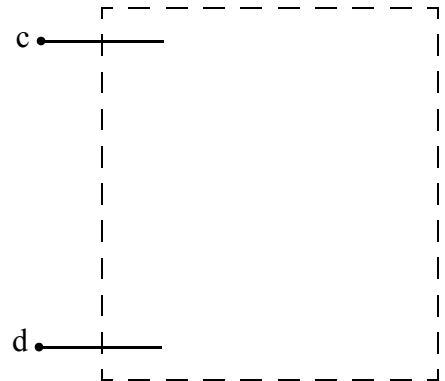
b) Suppose you need a **6 kΩ** resistor for your Tutebot project, but your TA gives you only a supply of 10 kΩ resistors. Being a clever Cal student, how would you connect several 10 kΩ resistors together, to achieve a 6 kΩ resistance? [7 pts]

Circuit diagram of 10-kΩ resistors connected to give $R_{cd} = 6 \text{ k}\Omega$:



Problem 2 (continued)

c) Consider the following circuit:

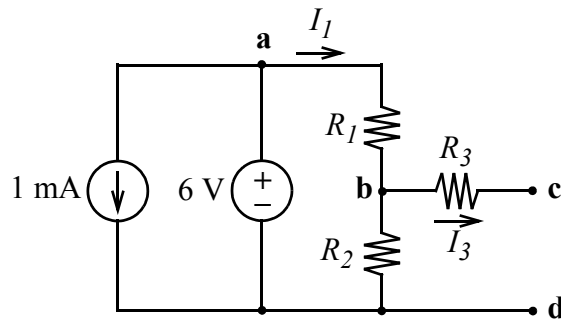

$R_1 = 1 \text{ k}\Omega$
 $R_2 = 2 \text{ k}\Omega$
 $R_3 = 2 \text{ k}\Omega$

i) Find V_{cd} . [3 pts]

$V_{cd} = \text{_____ V}$

ii) Find the power developed/absorbed by the current source, P_I . [3 pts]

$P_I = \text{_____ W}$ [developed, absorbed] (circle correct choice)

iii) Indicate in the table below (by checking the appropriate boxes) how various circuit parameters would change if the terminals **c** and **d** were to be shorted together. Justify your answers. [6 pts]

Parameter	Value will:			Brief Explanation/Justification
	increase	decrease	not change	
V_{bd}	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	
I_1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	
Power developed by voltage source	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	

iv) What is the value of I_3 when the terminals **c** and **d** are shorted together? [5 pts]

$I_3 = \text{_____ A}$


Problem 3: Nodal Analysis [20 points]

a) In the circuit below, the independent source values and resistances are known.

Use the nodal analysis technique to write 3 equations sufficient to solve for V_a , V_b , and V_c .

To receive credit, you must write your answer in the box below. **[10 pts]**

DO NOT SOLVE THE EQUATIONS!

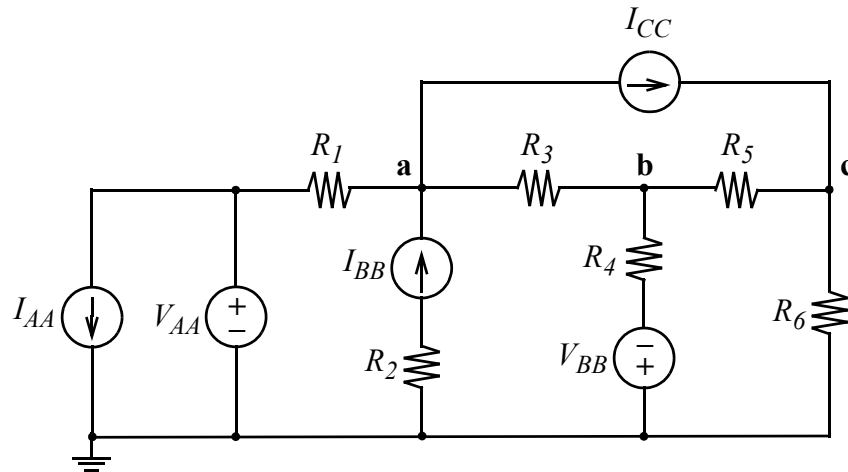


Write the nodal equations here:

<hr style="border: 0; border-top: 1px solid black; margin-bottom: 10px;"/> <hr style="border: 0; border-top: 1px solid black; margin-bottom: 10px;"/> <hr style="border: 0; border-top: 1px solid black; margin-bottom: 10px;"/> <hr style="border: 0; border-top: 1px solid black;"/>
--

Problem 3 (continued)


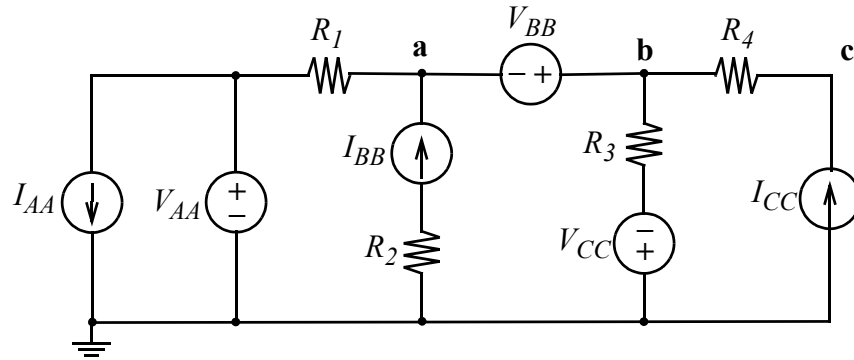
- b) Similarly to part (a), use the nodal analysis technique to write 3 equations sufficient to solve for V_a , V_b , and V_c . To receive credit, you must write your answer in the box below. **[10 pts]**
DO NOT SOLVE THE EQUATIONS!



Write the nodal equations here:


Problem 4: Thevenin and Norton Equivalent Circuits [25 points]

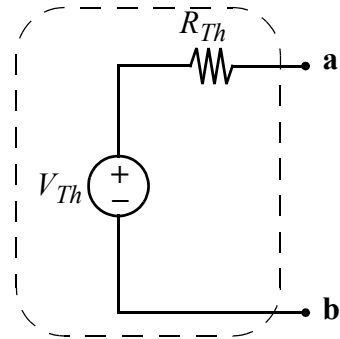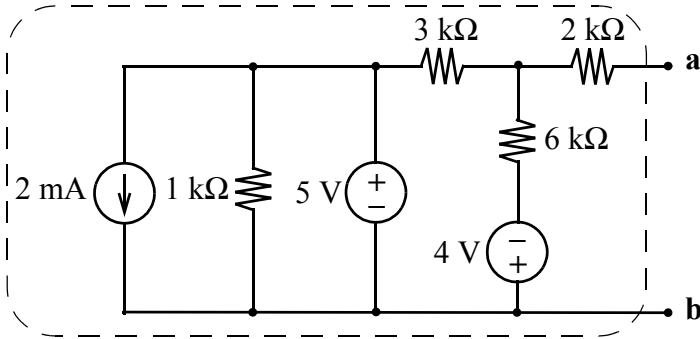a) Find the Thevenin Equivalent Circuit for the following circuit. [10 pts]




$V_{Th} =$ _____ V
$R_{Th} =$ _____ Ω

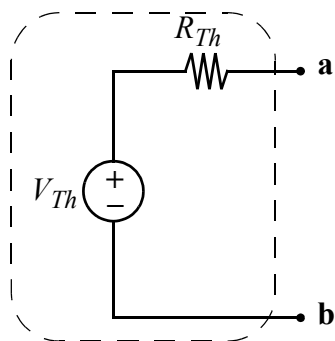b) Use the source transformation method to obtain the Norton Equivalent Circuit for the circuit in part (a). [5 pts]




source transformation

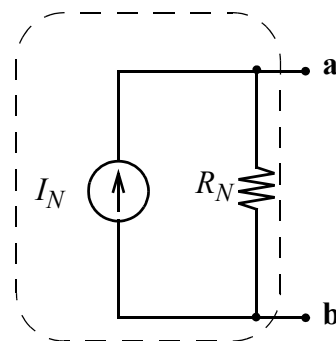

$I_N =$ _____ A
$R_N =$ _____ Ω

Problem 4 (continued)

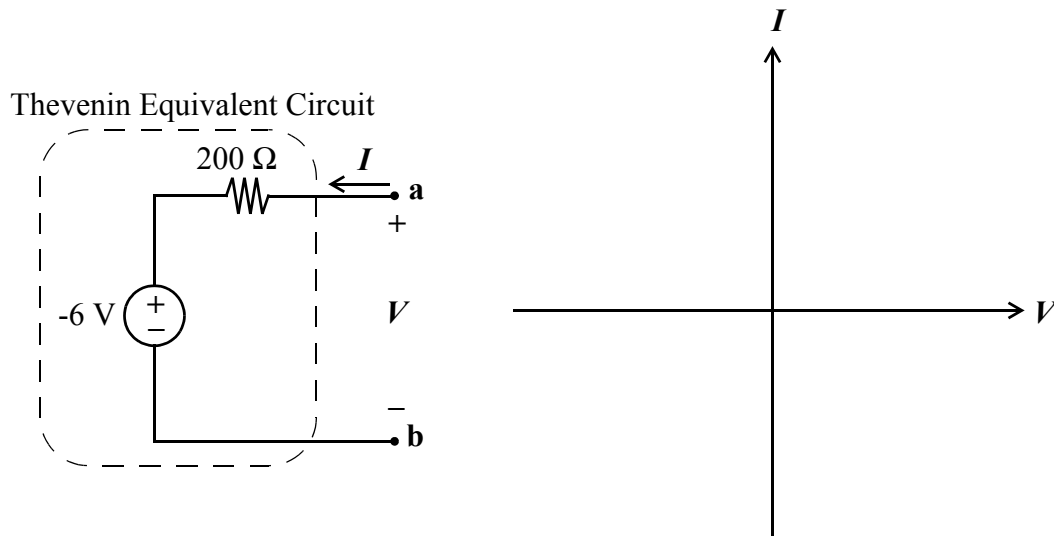- c) The Thevenin Equivalent Circuit for a certain linear circuit is given below. Plot the current (I) versus the output voltage (V) for the circuit, **labelling the y-intercept and x-intercept.** [5 pts]



- d) The circuit in part (c) is connected to a $1\text{ k}\Omega$ load resistor (placed between the terminals **a** and **b**). Find the power absorbed in the load resistor, P_{1k} . [5 pts]

$P_{1k} = \underline{\hspace{2cm}} \text{ W}$

