

UNIVERSITY OF CALIFORNIA, BERKELEY
College of Engineering
Department of Electrical Engineering and Computer Sciences

EECS 40
Introduction to Microelectronic Devices

Spring 2000
Prof. King

MIDTERM EXAMINATION #2

April 6, 2000

Time allotted: 80 minutes

NAME: _____
(print) Last First Signature

STUDENT ID#: _____

1. This is a **CLOSED BOOK EXAM**. However, you may use 2 pages of notes and a calculator.
2. Show your work on this exam.
MAKE YOUR METHODS CLEAR TO THE GRADER.
3. **Write your answers clearly in the spaces (lines, boxes or plots) provided.**
Numerical answers must be accurate to within 10% unless otherwise noted.
4. Remember to specify the units on answers whenever appropriate.
5. **Do not unstaple the pages of this exam.**

SCORE: 1 _____ / 20

 2 _____ / 30

 3 _____ / 25

 4 _____ / 25

Total: _____ / 100


Physical Constants

<u>Description</u>	<u>Symbol</u>	<u>Value</u>
Electronic charge	q	$1.602 \times 10^{-19} \text{ C}$
Permittivity of vacuum	ϵ_0	$8.854 \times 10^{-14} \text{ F/cm}$
Boltzmann's constant	k	$8.62 \times 10^{-5} \text{ eV/K}$
Thermal voltage at 300K	kT/q	0.026 V

Properties of Silicon at 300K

<u>Description</u>	<u>Symbol</u>	<u>Value</u>
Thermal velocity	v_{th}	10^7 cm/s
Relative permittivity	ϵ_r	11.7
Intrinsic carrier density	n_i	$1.45 \times 10^{10} \text{ cm}^{-3}$

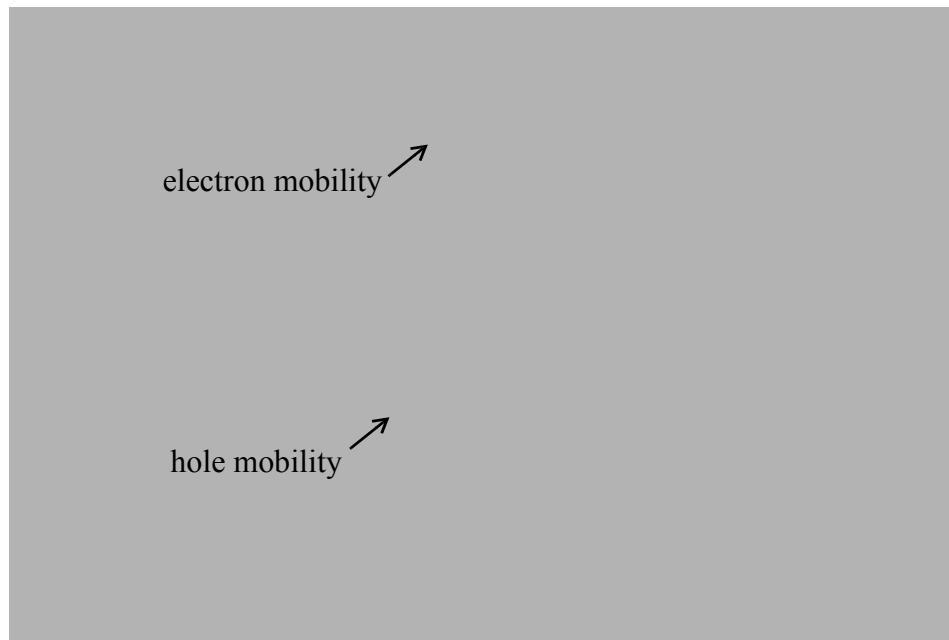Electron and Hole Mobilities in Silicon at 300K



Conversion Factors

$$1 \text{ eV} = 1.602 \times 10^{-19} \text{ J}$$

$$1 \text{ } \mu\text{m} = 10^{-4} \text{ cm} = 10^{-6} \text{ m}$$

$$\text{Farad} = \text{Coulomb} / \text{Volt}$$


$$\text{Henry} = \text{Volt} / (\text{Ampere/second})$$

$$\text{Watt} = \text{Volt} \times \text{Ampere}$$

$$\text{Joule} = \text{Watt} \times \text{second}$$

Problem 1 Circuits with Dependent Sources [20 points]


a) Find V_o . [4 pts]

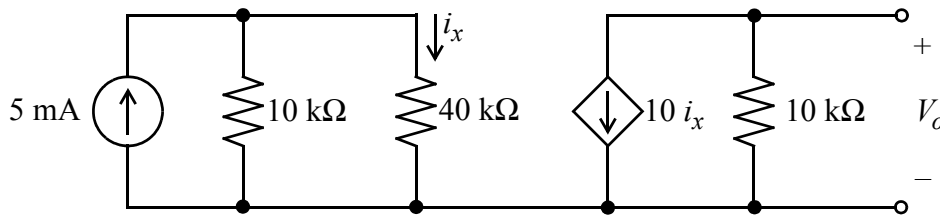

$V_o = \underline{\hspace{2cm}} \text{ V}$

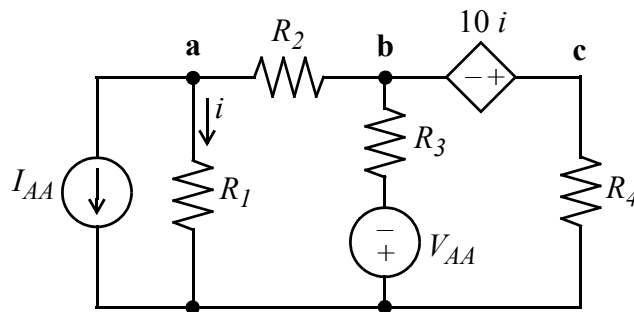b) In the circuit below, the independent source values and resistances are known.


Use the **nodal analysis technique** to write **3 equations sufficient to solve for V_a , V_b , and V_c** .
 To receive credit, you must write your answer in the box below. [6 pts]
DO NOT SOLVE THE EQUATIONS!



Write the nodal equations here:

Problem 1 (continued)

c) Consider the following circuit:

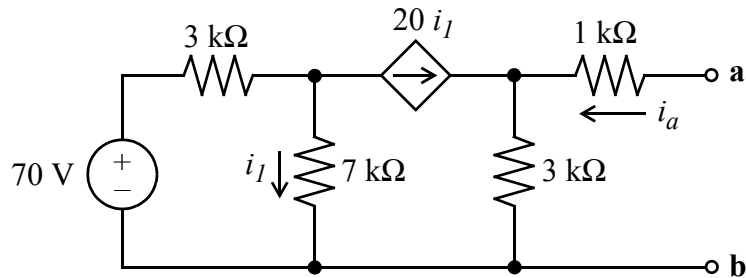
i) Find the voltage V_{ab} . [5 pts]

$V_{ab} = \underline{\hspace{2cm}} \text{ V}$

ii) What is the current i_a when the terminals **a** and **b** are shorted together? [3 pts]


$i_a = \underline{\hspace{2cm}} \text{ A}$
--

iii) Draw the Thevenin Equivalent Circuit. [2 pts]

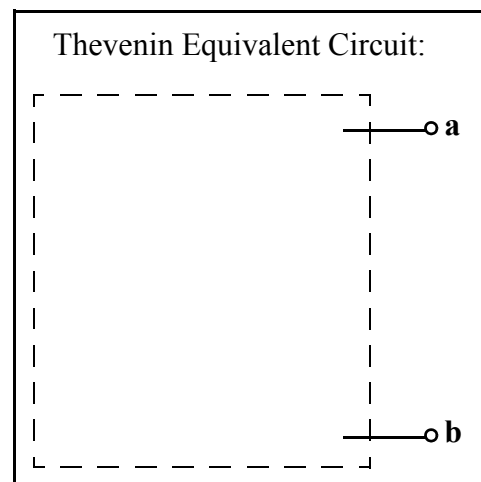

Problem 2: Transient Response [30 points]

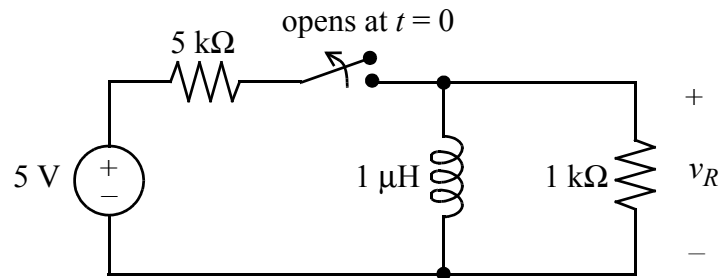a) In the circuit below, the switch has been in the closed position for a long time.




i) Find the value of v_R just after the switch opens ($t = 0^+$). [3 pts]

$v_R(0^+) = \underline{\hspace{2cm}} \text{ V}$

ii) How much energy is dissipated in the 1 kΩ resistor after the switch is opened? [2 pts]

Energy dissipated = $\underline{\hspace{2cm}}$ J
--

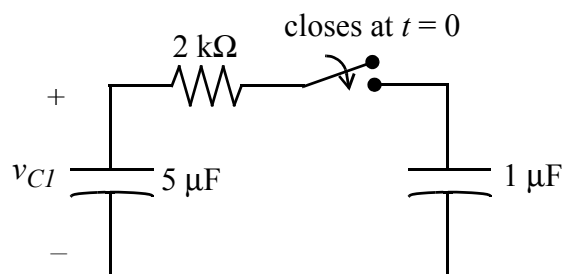
b) In the circuit below, the 5 μF capacitor is initially charged to 5 V ($v_{CI}(0^-) = 5 \text{ V}$). (The 1 μF capacitor is initially uncharged.) The switch is then closed at time $t = 0$. What is the final value of v_{CI} ? [5 pts]



Final value of $v_{CI} = \underline{\hspace{2cm}} \text{ V}$
--

Problem 2 (continued)

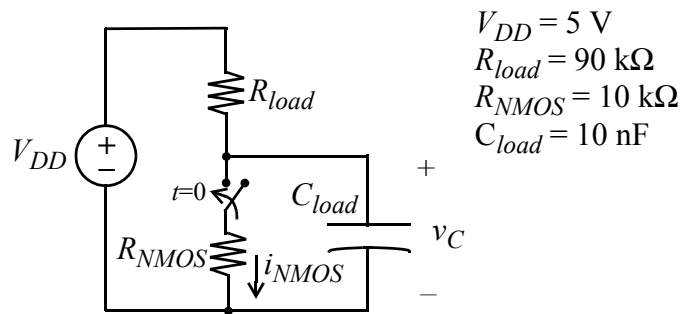c) The following is a circuit model for an NMOS inverter, in which the transistor is turned on at time $t = 0$:



i) What is the value of v_C at $t = 0^-$? [3 pts]

$v_C(0^-) = \underline{\hspace{2cm}} \text{ V}$


ii) What is the value of i_{NMOS} at $t = 0^+$? [3 pts]

$i_{NMOS}(0^+) = \underline{\hspace{2cm}} \text{ A}$

iii) What is the final value of v_C ? [3 pts]

final value of $v_C = \underline{\hspace{2cm}} \text{ V}$

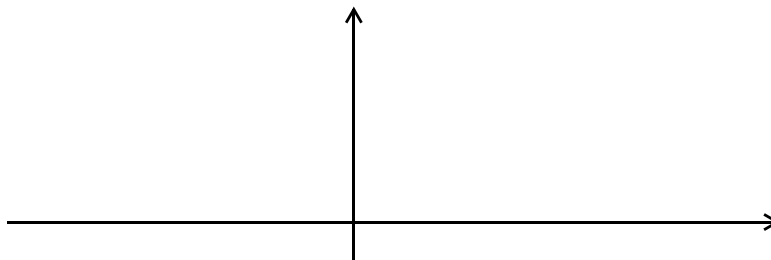iv) Neatly sketch the graph of i_{NMOS} for all t , labelling the axes. [5 pts]




v) Write an equation for i_{NMOS} as a function of time, for $t > 0$. [6 pts]

Equation for i_{NMOS} : $\underline{\hspace{10cm}}$

Problem 3: Op-Amp Circuits [25 points]

Assume the op-amps in this problem are ideal.

a) Consider the following circuit:

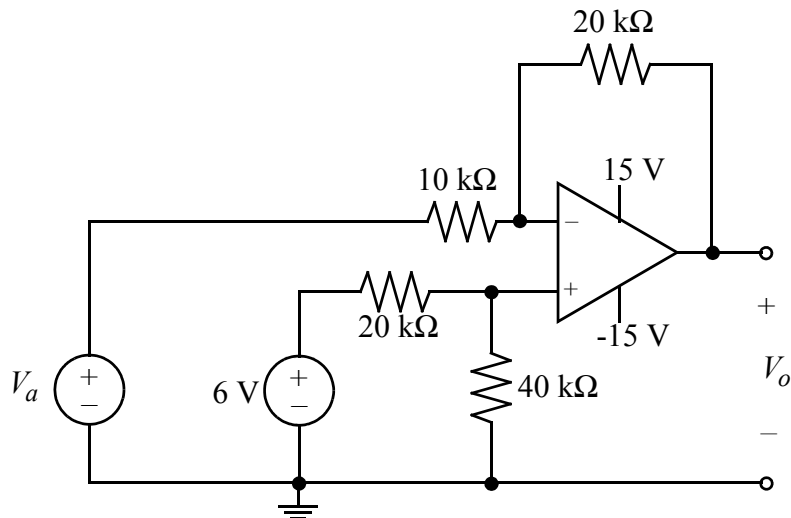

i) Find an expression for V_o as a function of V_a . [6 pts]

Expression for V_o : _____

ii) Find V_o for $V_a = 2$ V. [3 pts]


$V_o =$ _____ V

iii) For what values of V_a will the op-amp be saturated? [6 pts]

Values of V_a for which the op-amp will be saturated: _____

Problem 3 (continued)

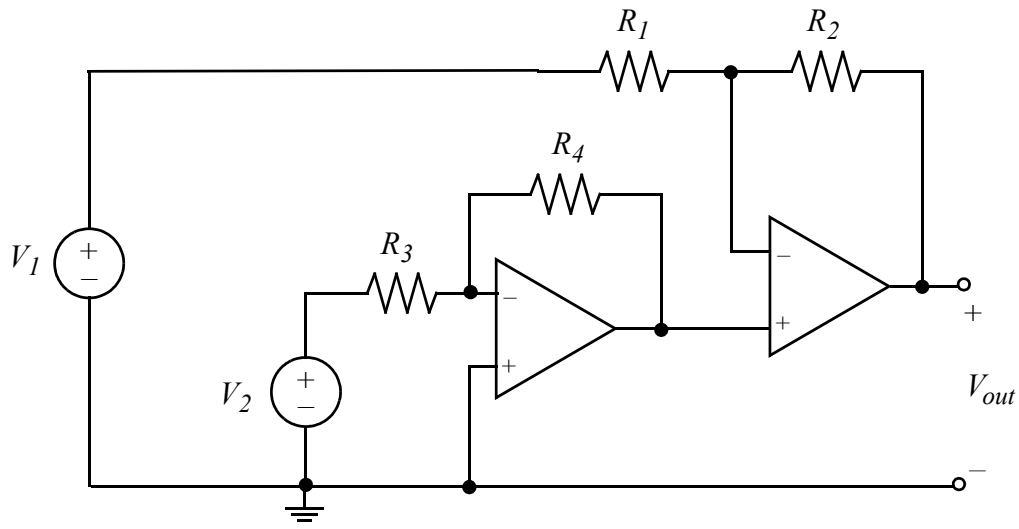b) In the following circuit, the op-amps are operating linearly.




Find V_{out} in terms of V_1 , V_2 , R_1 , R_2 , R_3 , R_4 . [10 pts]
 (Hint: The superposition method might be helpful here.)

$V_{out} = \underline{\hspace{10cm}}$

Problem 4: Semiconductor properties; p-n diodes [25 points]

- a) Consider a silicon sample maintained at 300K under equilibrium conditions, uniformly doped with $1 \times 10^{16} \text{ cm}^{-3}$ phosphorus atoms. The surface region of the sample is **additionally** doped uniformly with $5 \times 10^{16} \text{ cm}^{-3}$ boron atoms, to a depth of $1 \mu\text{m}$, as shown in the figure below.

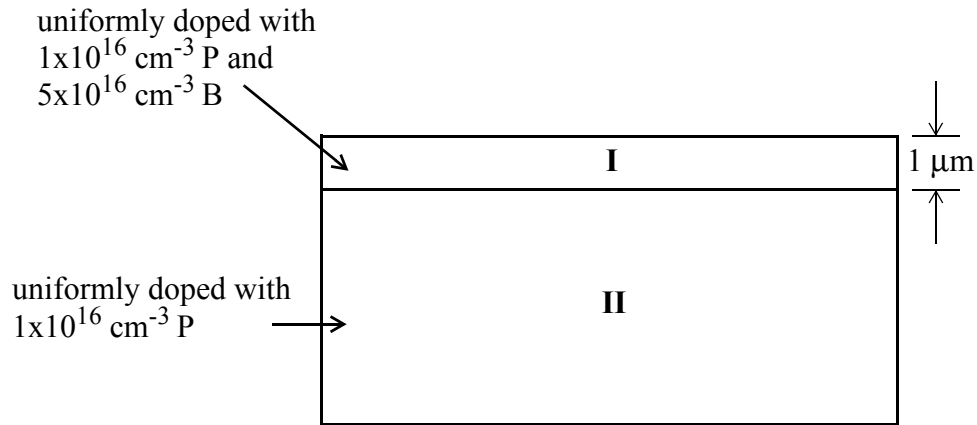**Schematic cross-sectional view of silicon sample**

- i) In the figure above, indicate the type of the regions (I and II) by labelling them as “n” or “p” type. [2 pts]
- ii) What are the electron and hole concentrations in Region I? [5 pts]

$n =$ _____ cm^{-3} $p =$ _____ cm^{-3}
--

- iii) What is the sheet resistance of Region I? [5 pts]

$R_s =$ _____ Ω/square

- iv) Suppose any voltage between 0 V and 5 V can be applied to Region I. What fixed voltage (“bias”) would you apply to Region II, to guarantee that no current would ever flow between Region I and Region II? **Briefly explain your answer.** [3 pts]

Region II bias voltage = _____ V

Problem 4 (continued)



- b) If a diode is operated only within a small range of forward-bias voltages, its behavior can be accurately modelled by a resistor, whose value is dependent on the bias voltage. Derive an expression for the diode “small-signal” resistance:

$$R_{diode} = \left(\frac{\partial I}{\partial V} \right)^{-1}$$

in terms of the saturation current I_s , the bias voltage V , and the absolute temperature T . [5 pts]

$R_{diode} = \underline{\hspace{10cm}}$

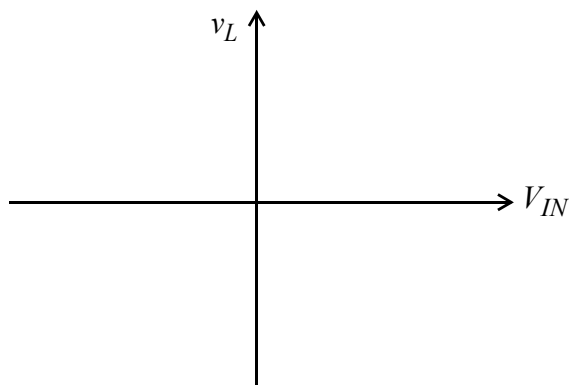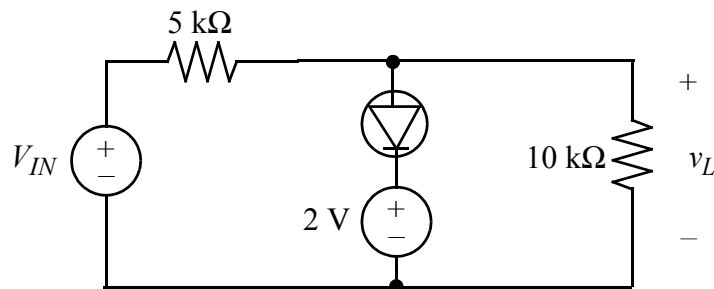- c) Plot v_L vs. V_{IN} for $-10 \text{ V} < V_{IN} < 10 \text{ V}$ on the axes provided, for the circuit below. Note that the diode is a perfect rectifier. **Label the axes.** [5 pts]



UNIVERSITY OF CALIFORNIA, BERKELEY
College of Engineering
Department of Electrical Engineering and Computer Sciences

EECS 40
Introduction to Microelectronic Devices

Spring 2000
Prof. King

MIDTERM EXAMINATION #2

April 6, 2000

Time allotted: 80 minutes

NAME: _____
(print) Last First Signature

STUDENT ID#: _____

1. This is a **CLOSED BOOK EXAM**. However, you may use 2 pages of notes and a calculator.
2. Show your work on this exam.
MAKE YOUR METHODS CLEAR TO THE GRADER.
3. **Write your answers clearly in the spaces (lines, boxes or plots) provided.**
Numerical answers must be accurate to within 10% unless otherwise noted.
4. Remember to specify the units on answers whenever appropriate.
5. **Do not unstaple the pages of this exam.**

SCORE: 1 _____ / 20

 2 _____ / 30

 3 _____ / 25

 4 _____ / 25

Total: _____ / 100


Physical Constants

<u>Description</u>	<u>Symbol</u>	<u>Value</u>
Electronic charge	q	$1.602 \times 10^{-19} \text{ C}$
Permittivity of vacuum	ϵ_0	$8.854 \times 10^{-14} \text{ F/cm}$
Boltzmann's constant	k	$8.62 \times 10^{-5} \text{ eV/K}$
Thermal voltage at 300K	kT/q	0.026 V

Properties of Silicon at 300K

<u>Description</u>	<u>Symbol</u>	<u>Value</u>
Thermal velocity	v_{th}	10^7 cm/s
Relative permittivity	ϵ_r	11.7
Intrinsic carrier density	n_i	$1.45 \times 10^{10} \text{ cm}^{-3}$

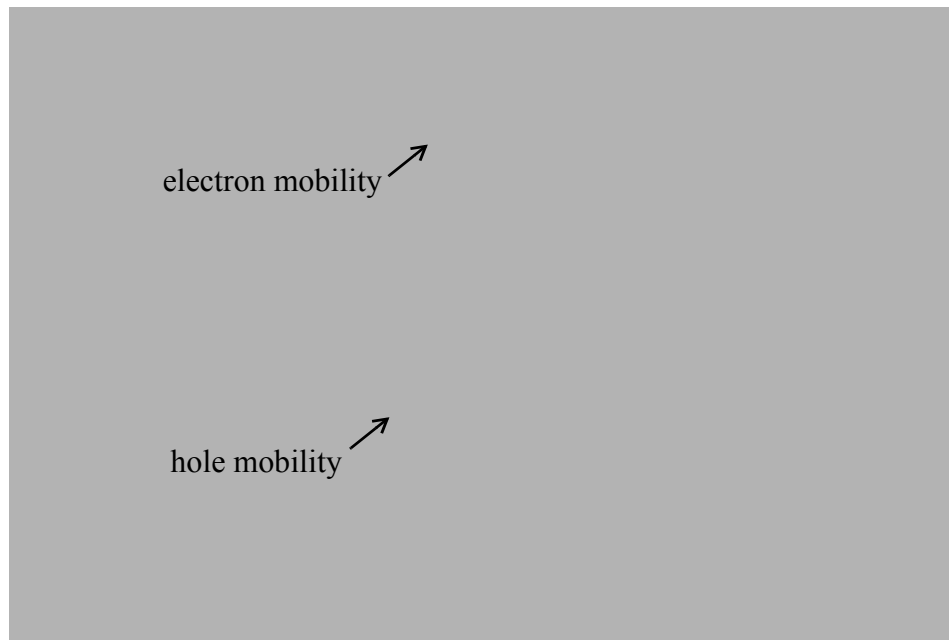Electron and Hole Mobilities in Silicon at 300K



Conversion Factors

$$1 \text{ eV} = 1.602 \times 10^{-19} \text{ J}$$

$$1 \text{ } \mu\text{m} = 10^{-4} \text{ cm} = 10^{-6} \text{ m}$$

$$\text{Farad} = \text{Coulomb} / \text{Volt}$$


$$\text{Henry} = \text{Volt} / (\text{Ampere/second})$$

$$\text{Watt} = \text{Volt} \times \text{Ampere}$$

$$\text{Joule} = \text{Watt} \times \text{second}$$

Problem 1 Circuits with Dependent Sources [20 points]


a) Find V_o . [4 pts]

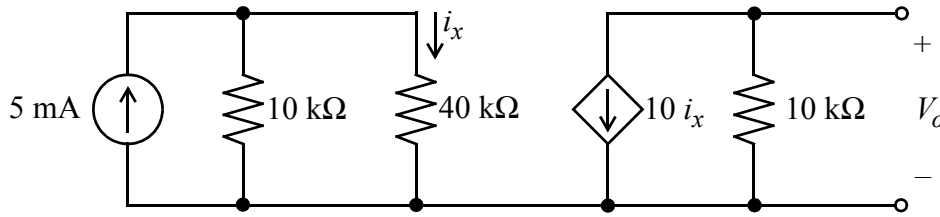

$V_o = \underline{\hspace{2cm}} \text{ V}$

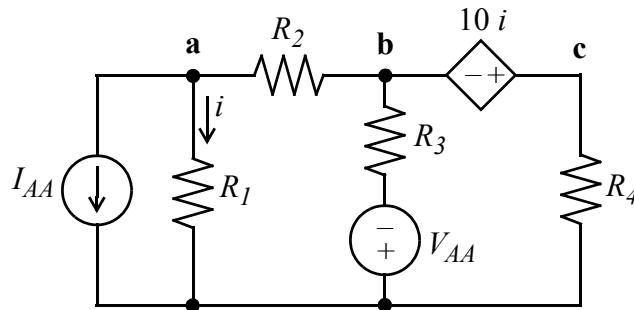b) In the circuit below, the independent source values and resistances are known.


Use the **nodal analysis technique** to write **3 equations sufficient to solve for V_a , V_b , and V_c** .
 To receive credit, you must write your answer in the box below. [6 pts]
DO NOT SOLVE THE EQUATIONS!



Write the nodal equations here:

Problem 1 (continued)

c) Consider the following circuit:

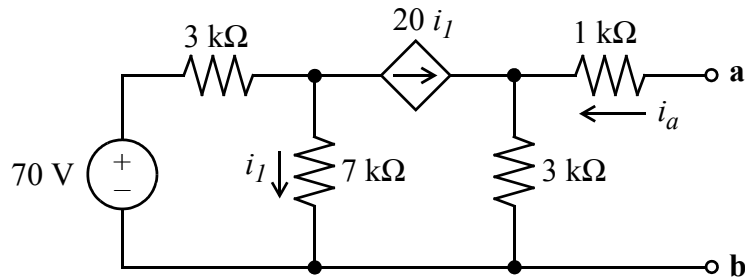


i) Find the voltage V_{ab} . [5 pts]

$V_{ab} = \underline{\hspace{2cm}} \text{ V}$

ii) What is the current i_a when the terminals **a** and **b** are shorted together? [3 pts]


$i_a = \underline{\hspace{2cm}} \text{ A}$
--

iii) Draw the Thevenin Equivalent Circuit. [2 pts]

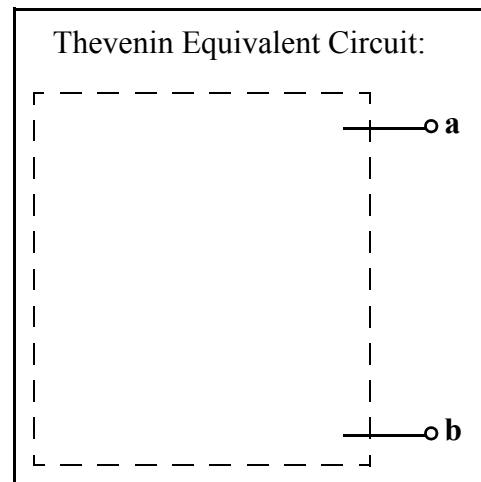

Problem 2: Transient Response [30 points]

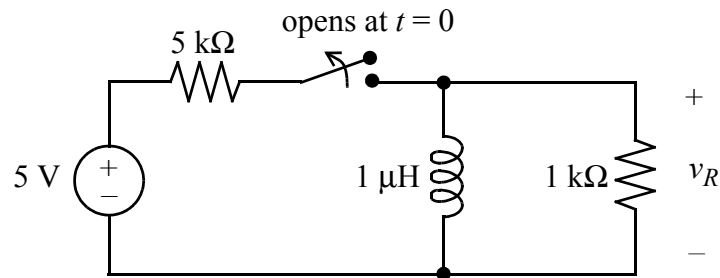a) In the circuit below, the switch has been in the closed position for a long time.




i) Find the value of v_R just after the switch opens ($t = 0^+$). [3 pts]

$v_R(0^+) = \underline{\hspace{2cm}} \text{ V}$

ii) How much energy is dissipated in the $1 \text{ k}\Omega$ resistor after the switch is opened? [2 pts]

Energy dissipated = $\underline{\hspace{2cm}}$ J
--

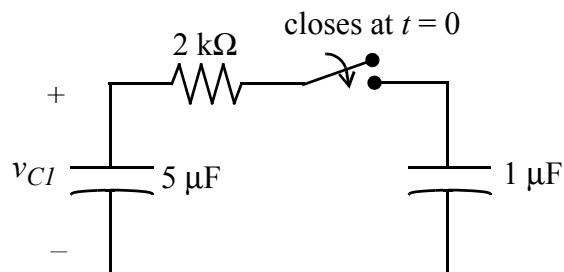
b) In the circuit below, the $5 \mu\text{F}$ capacitor is initially charged to 5 V ($v_{CI}(0^-) = 5 \text{ V}$). (The $1 \mu\text{F}$ capacitor is initially uncharged.) The switch is then closed at time $t = 0$. What is the final value of v_{CI} ? [5 pts]



Final value of $v_{CI} = \underline{\hspace{2cm}} \text{ V}$
--

Problem 2 (continued)

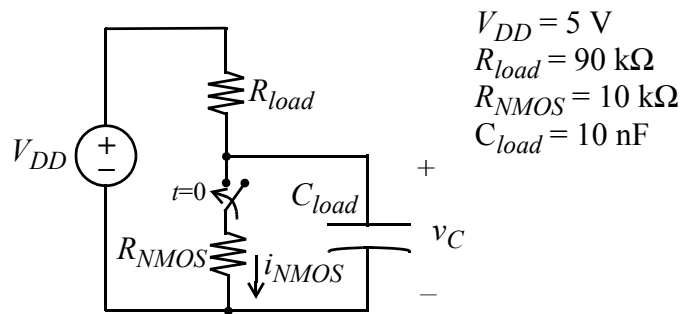c) The following is a circuit model for an NMOS inverter, in which the transistor is turned on at time $t = 0$:



i) What is the value of v_C at $t = 0^-$? [3 pts]

$v_C(0^-) = \underline{\hspace{2cm}} \text{ V}$


ii) What is the value of i_{NMOS} at $t = 0^+$? [3 pts]

$i_{NMOS}(0^+) = \underline{\hspace{2cm}} \text{ A}$

iii) What is the final value of v_C ? [3 pts]

final value of $v_C = \underline{\hspace{2cm}} \text{ V}$

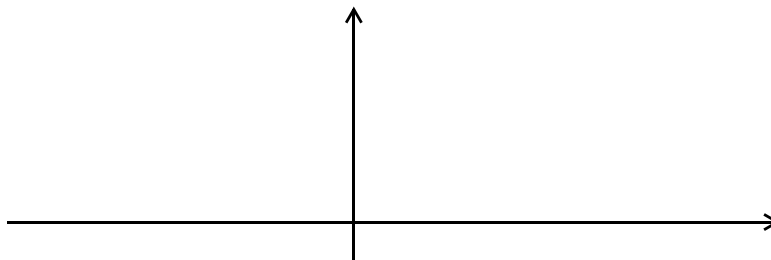iv) Neatly sketch the graph of i_{NMOS} for all t , labelling the axes. [5 pts]




v) Write an equation for i_{NMOS} as a function of time, for $t > 0$. [6 pts]

Equation for i_{NMOS} : $\underline{\hspace{10cm}}$

Problem 3: Op-Amp Circuits [25 points]

Assume the op-amps in this problem are ideal.

a) Consider the following circuit:

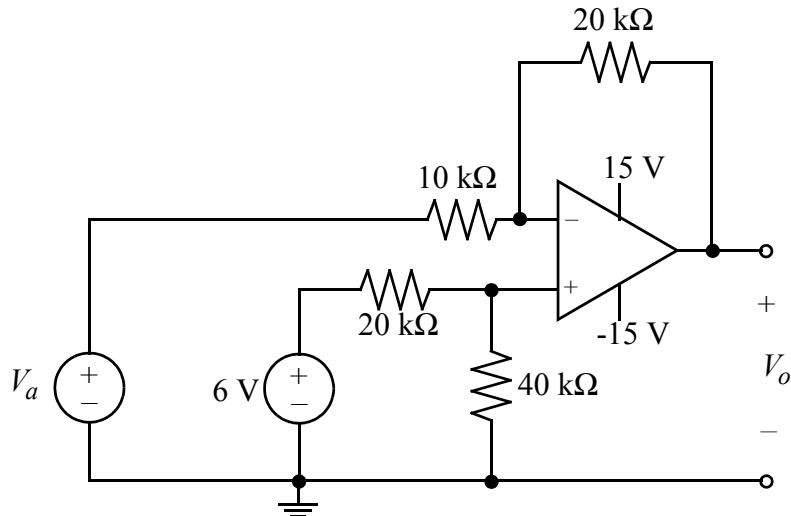

i) Find an expression for V_o as a function of V_a . [6 pts]

Expression for V_o : _____

ii) Find V_o for $V_a = 2$ V. [3 pts]


$V_o =$ _____ V

iii) For what values of V_a will the op-amp be saturated? [6 pts]

Values of V_a for which the op-amp will be saturated: _____

Problem 3 (continued)

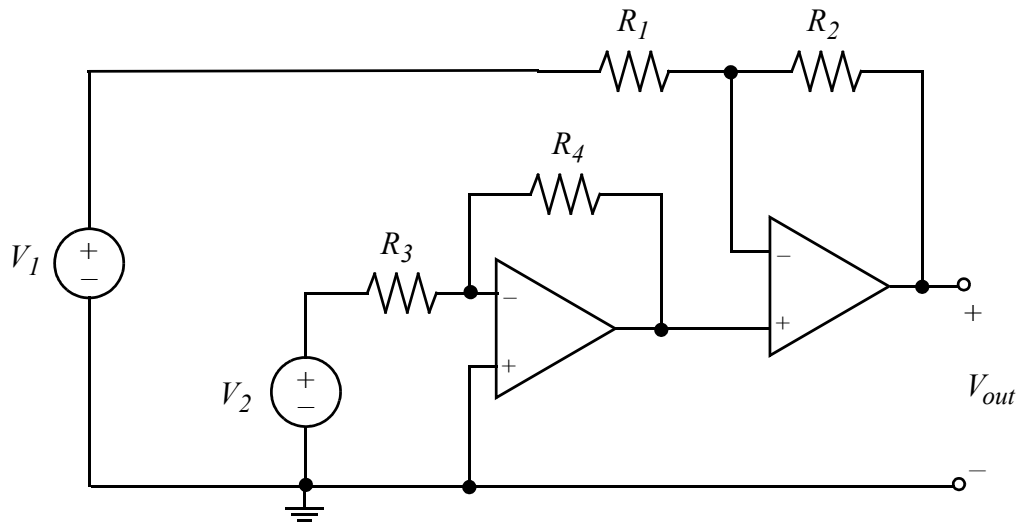b) In the following circuit, the op-amps are operating linearly.




Find V_{out} in terms of V_1 , V_2 , R_1 , R_2 , R_3 , R_4 . [10 pts]
 (Hint: The superposition method might be helpful here.)

$V_{out} = \underline{\hspace{10cm}}$

Problem 4: Semiconductor properties; p-n diodes [25 points]

- a) Consider a silicon sample maintained at 300K under equilibrium conditions, uniformly doped with $1 \times 10^{16} \text{ cm}^{-3}$ phosphorus atoms. The surface region of the sample is **additionally** doped uniformly with $5 \times 10^{16} \text{ cm}^{-3}$ boron atoms, to a depth of $1 \mu\text{m}$, as shown in the figure below.

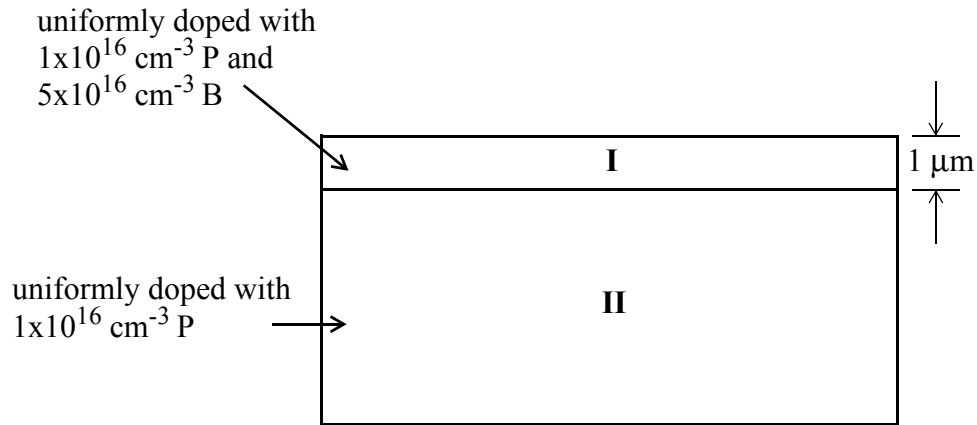**Schematic cross-sectional view of silicon sample**

- i) In the figure above, indicate the type of the regions (I and II) by labelling them as “n” or “p” type. [2 pts]
- ii) What are the electron and hole concentrations in Region I? [5 pts]

$n =$ _____ cm^{-3} $p =$ _____ cm^{-3}
--

- iii) What is the sheet resistance of Region I? [5 pts]

$R_s =$ _____ Ω/square

- iv) Suppose any voltage between 0 V and 5 V can be applied to Region I. What fixed voltage (“bias”) would you apply to Region II, to guarantee that no current would ever flow between Region I and Region II? **Briefly explain your answer.** [3 pts]

Region II bias voltage = _____ V

Problem 4 (continued)

- b) If a diode is operated only within a small range of forward-bias voltages, its behavior can be accurately modelled by a resistor, whose value is dependent on the bias voltage. Derive an expression for the diode “small-signal” resistance:

$$R_{diode} = \left(\frac{\partial I}{\partial V} \right)^{-1}$$

in terms of the saturation current I_s , the bias voltage V , and the absolute temperature T . [5 pts]

$R_{diode} = \underline{\hspace{10cm}}$

- c) Plot v_L vs. V_{IN} for $-10 \text{ V} < V_{IN} < 10 \text{ V}$ on the axes provided, for the circuit below. Note that the diode is a perfect rectifier. **Label the axes.** [5 pts]

