

Name Solutions + Grading

EE 40

Midterm 3

April 24, 2003

**PLEASE WRITE YOUR NAME ON EACH ATTACHED PAGE**

**PLEASE SHOW YOUR WORK TO RECEIVE PARTIAL CREDIT**

**PLEASE DO NOT LEAVE UNTIL EXAM PERIOD IS OVER**

Problem 1: 15 Points Possible \_\_\_\_\_

Problem 2: 20 Points Possible \_\_\_\_\_

Problem 3: 15 Points Possible \_\_\_\_\_

Problem 4: 20 Points Possible \_\_\_\_\_

Problem 5: 20 Points Possible \_\_\_\_\_

Problem 6: 10 Points Possible \_\_\_\_\_


TOTAL: 100 Points Possible \_\_\_\_\_

Name Solutions

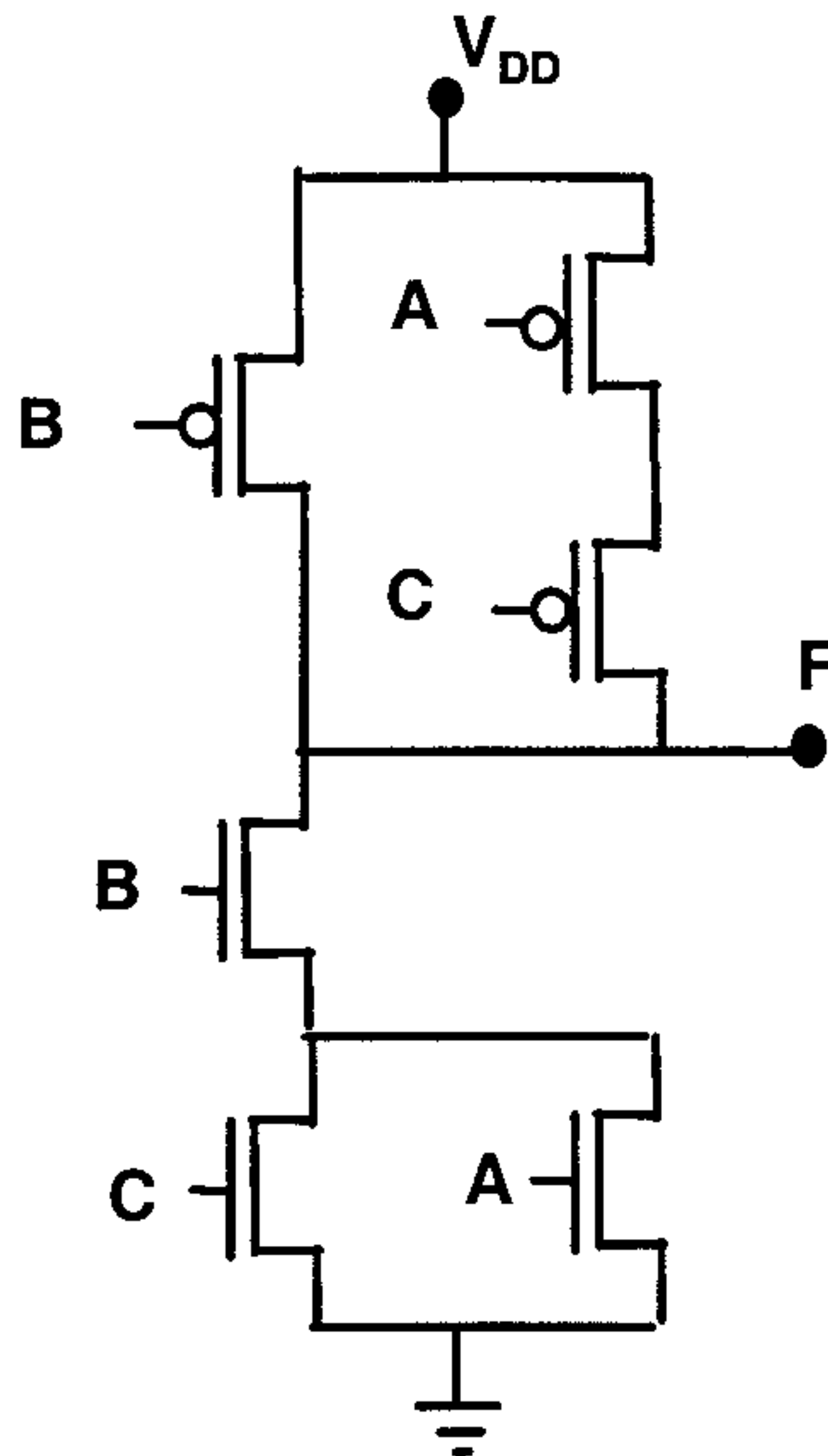**Problem 1:** 15 Points Possible

Determine whether the circuit below performs a logical operation. If it does, give the Boolean function it computes. If not, give a set of inputs that results in an invalid output.

For your convenience, 8 copies of this circuit are given on the next page. Assume that all PMOS transistors have source terminal on top, and all NMOS transistors have source terminal on the bottom.



From looking at PMOS half:  $F = V_{DD}$  if  
B conducts OR (A conducts AND C conducts)

$$F = \overline{B} + \overline{A} \overline{C}$$

From looking at NMOS half:  $F = 0$  if  
B conducts AND (A conducts OR C conducts)


$$\overline{F} = B(A + C)$$

These agree by De Morgan's law; it is a logic circuit.

Name Solutions

Problem 1 Workspace

Do switches for each ABC combo

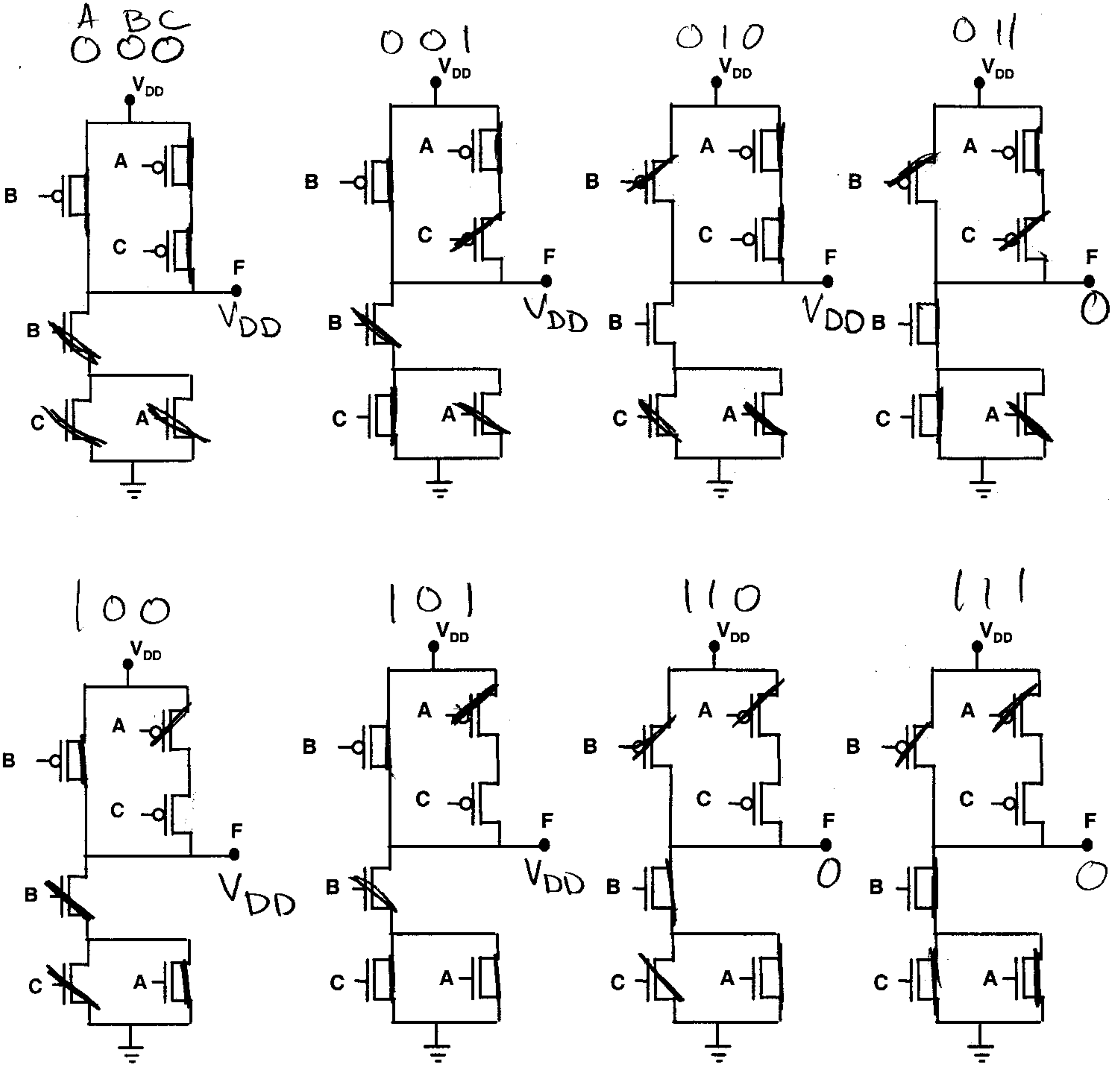


$$F = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C$$

(Equivalent to previous results)

Name Solutions

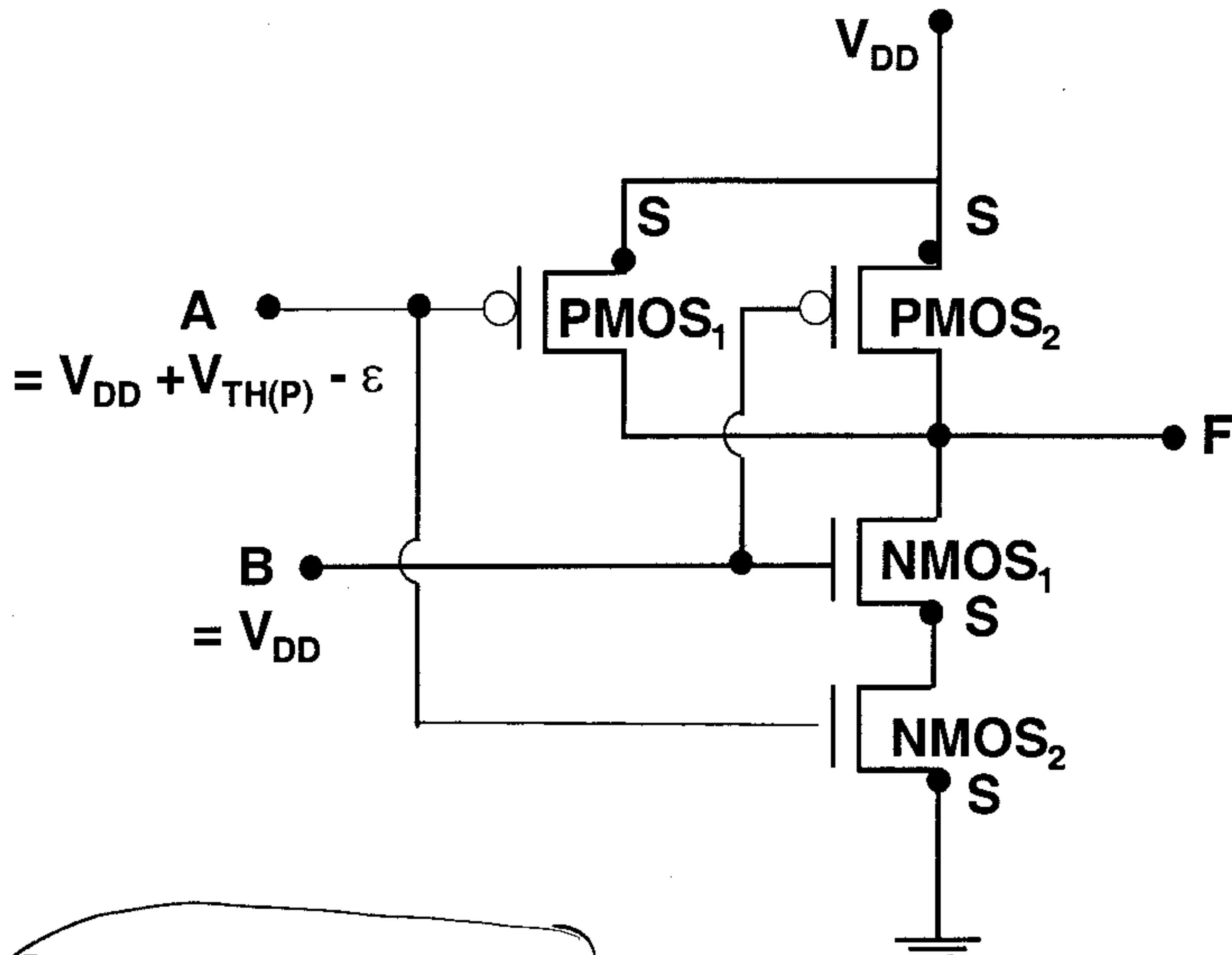**Problem 2:** 20 Points Possible

For the CMOS logic circuit below, determine the most probable mode of operation for each transistor. Assume that  $\epsilon$  is a very small positive number, and  $V_{DD}$  is much larger in magnitude than either  $V_{TH}$ .



$PMOS_2$  cutoff ( $V_{GSP2} = V_{DD} - V_{DD} = 0V$ )  
 $PMOS_1$  barely on ( $V_{GSP1} = V_{DD} + V_{THP} - \epsilon - V_{DD} = V_{THP} - \epsilon$ )  
 $I_D$  shared by  $PMOS_1$ ,  $NMOS_1$ ,  $NMOS_2$  is small  
 $V_{GSN2} = V_{DD} + V_{THP} - \epsilon$  for  $NMOS_2$  is not small and is positive, since  $V_{DD}$  is much larger in magnitude than  $V_{THP}$  or  $\epsilon$  (by assumption).  
 $NMOS_2$  fully on with small  $I_D \Rightarrow NMOS_2$  triode  
 $NMOS_2$  therefore also has small  $V_{DSN2}$ ,  
 so  $V_{GSN1} = V_{DD} - V_{DSN2}$ , the gate-source voltage for  $NMOS_1$ , is not small.  $NMOS_1$  fully on, small  $I_D \Rightarrow NMOS_1$  triode

Name Solutions

Problem 2 Workspace

NMOS<sub>1</sub> therefore has small  $V_{DSN_1}$ .

$$V_{DD} = \underbrace{V_{DSN_1}}_{\text{small}} + \underbrace{V_{DSN_2}}_{\text{small}} - V_{DSP_1}$$

$\Rightarrow V_{DSP_1}$  negative with large magnitude

$V_{DSP_1}$  with small magnitude  $\downarrow$   $V_{DSP_1}$  with large magnitude

$\Rightarrow$  PMOS<sub>1</sub> saturation

Name Solutions

**Problem 3:** 15 Points Possible

Consider the inverter at right, which turns on an LED when the output voltage is high.


I have put a resistor in series with the LED to limit the current so the LED doesn't burn.

But, the LED needs a current of at least 20 mA to light up.

I want the LED to light up for an input voltage as high as 0.8 V.

Will the LED light up for an input of 0.8 V?

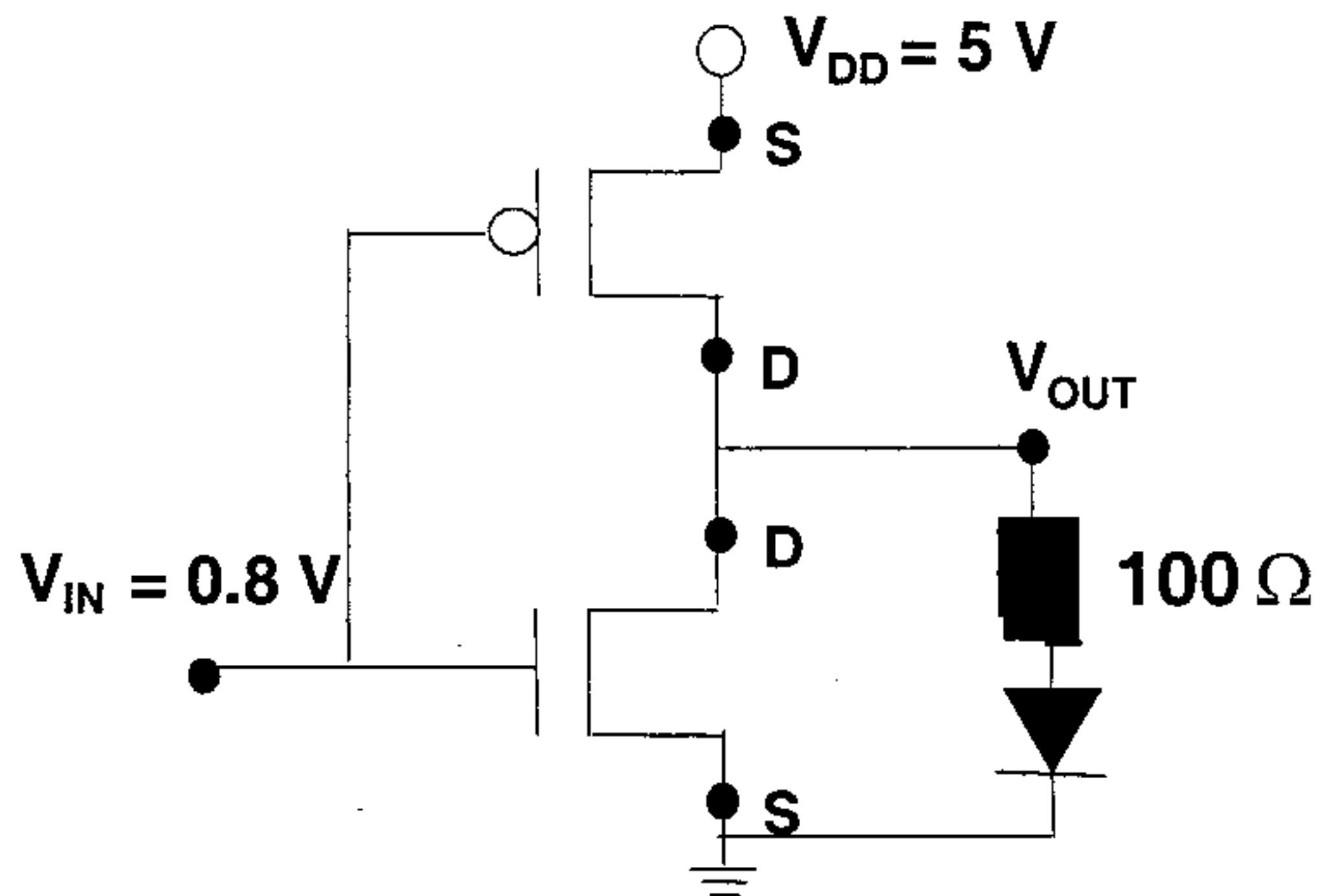$W/L \mu C_{ox} = 100 \text{ mA/V}^2$  for both transistors,  
 $V_{TH(N)} = -V_{TH(P)} = 1 \text{ V}$ ,  
 $\lambda = 0 \text{ V}^{-1}$  for both transistors,  
 $V_F = 2 \text{ V}$  for the LED (use large-signal model).



NMOS cutoff ( $V_{GSN} = V_{IN} = 0.8 \text{ V}$ )  $\Rightarrow I_{DN} = 0 \text{ A}$

PMOS triode (will show PMOS sat. is wrong)

$$\textcircled{1} \quad I_{DP} = -100 \text{ mA/V}^2 \left( \underbrace{0.8 \text{ V} - 5 \text{ V} - (-1 \text{ V} - \frac{V_{DSP}}{2})}_{V_{GSP}} \right) V_{DSP}$$

By KVL,  $V_{DSP} = V_{OUT} - V_{DD} = V_{OUT} - 5$

By KCL,  $I_{DP} = -\frac{V_{OUT} - V_F}{100} = -\frac{V_{OUT} - 2 \text{ V}}{100}$

Put  $\textcircled{3}$  and  $\textcircled{2}$  into  $\textcircled{1}$  and solve for  $V_{out}$ :

$$V_{out} = \{ -1.51 \text{ V}, 4.91 \text{ V} \}$$

↑ impossible!      ↑ keep.

$V_{DSP} = -0.09 \text{ V}$  OK for triode mode.

$$I_{diode} = \frac{V_{out} - 2 \text{ V}}{100 \Omega} = 29.1 \text{ mA}$$

LED  
Lights up!

## Solutions

If guessed saturation for PMOS,

$$I_{Dp} = -\frac{1}{2} \cdot 100 \text{ mA} (0.8 \text{ V} - 5 \text{ V} - -1 \text{ V})^2$$
$$= -512 \text{ mA}$$

$$V_{Dsp} = V_{out} - V_{DD} = -100 I_{Dp} + 2 \text{ V} - 5 \text{ V}$$
$$= 48.2 \text{ V} \quad \text{whoa!}$$

impossible.

Name Solutions

**Problem 4:** 20 Points Possible


Consider the CMOS inverter at right, with

$W/L \mu C_{OX} = 1 \text{ mA/V}^2$  for both transistors,

$V_{TH(N)} = -V_{TH(P)} = 1 \text{ V}$ ,

$\lambda = 0.01 \text{ V}^{-1}$  for both transistors.

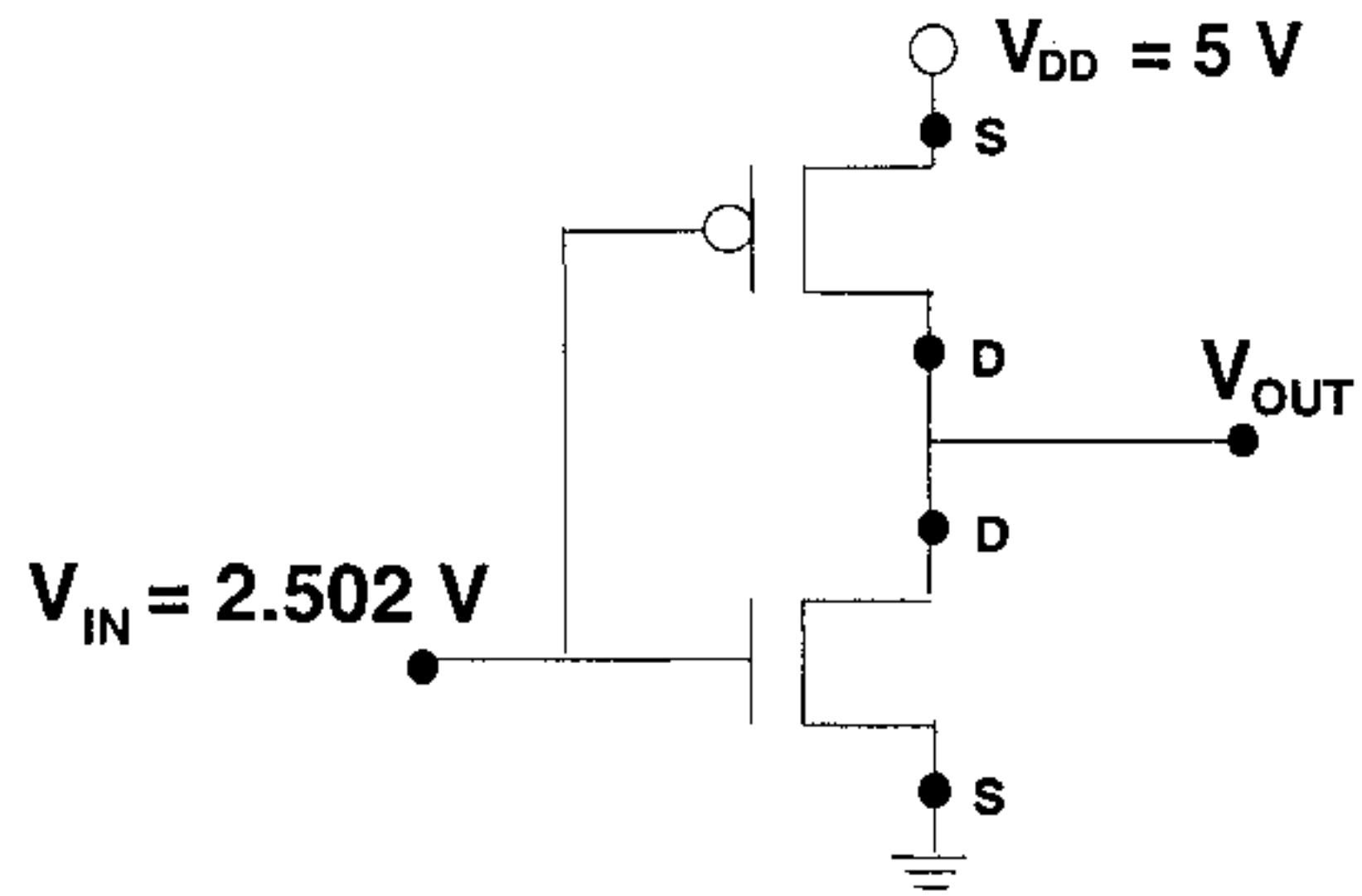$\rightarrow$  negative for PMOS  
For this inverter,  $V_M = 2.5 \text{ V}$ .



a) Find  $V_{OUT}$  for  $V_{IN} = 2.502 \text{ V}$ . Hint for guessing modes: Notice that  $V_{IN}$  is close to  $V_M$ .

b) Find the slope of the  $V_{OUT}$  vs.  $V_{IN}$  curve in this region, given by

$$\frac{\Delta V_{OUT}}{\Delta V_{IN}} = \frac{V_{OUT}(\text{for } V_{IN} = 2.502 \text{ V}) - V_M}{2.502 \text{ V} - V_M}$$

Since we have unloaded inverter with  $V_{in}$  close to  $V_M$ , assume "region C" with both transistors in saturation.

$$I_{DN} = \frac{1}{2} \cdot 1 \text{ mA/V}^2 (2.502 \text{ V} - 1 \text{ V})^2 (1 + 0.01 V_{DSN})$$

$$I_{DP} = -\frac{1}{2} \cdot 1 \text{ mA/V}^2 (2.502 \text{ V} - 5 \text{ V} - (-1 \text{ V}))^2 (1 - 0.01 V_{DSP})$$

KVL:  $V_{DSP} = V_{DSN} - V_{DD} = V_{DSN} - 5 \text{ V}$

KCL:  $I_{DP} + I_{DN} = 0 \Rightarrow I_{DN} = -I_{DP}$

Solve the above to get  $V_{DSN} = \boxed{V_{OUT} = 2.23 \text{ V}}$


$$\frac{\Delta V_{OUT}}{\Delta V_{IN}} = \frac{2.23 \text{ V} - 2.5 \text{ V}}{2.502 \text{ V} - 2.5 \text{ V}} = -135$$




Name Solutions

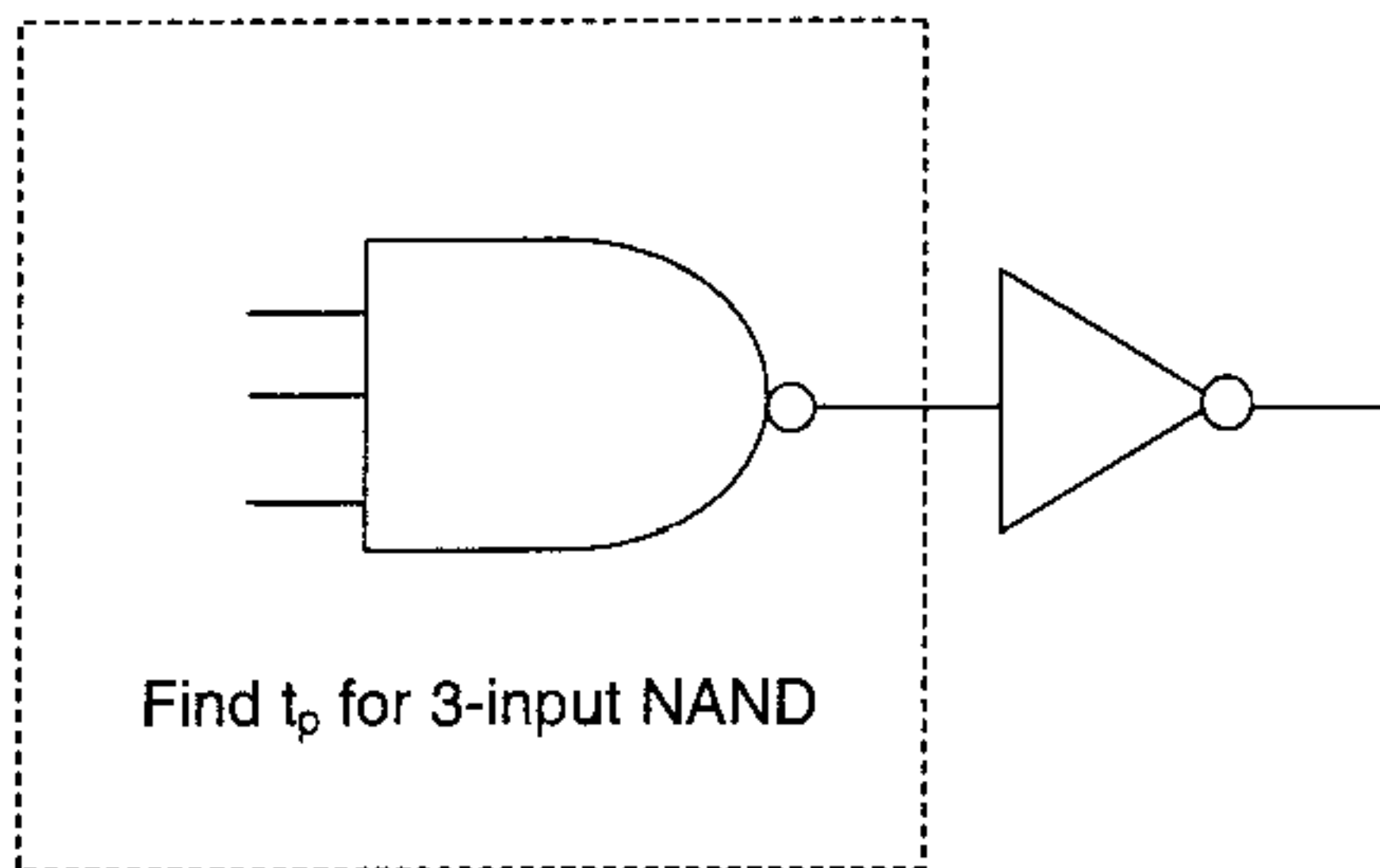**Problem 5:** 20 Points Possible

Find the propagation delay for this 3-input NAND gate with inverter load,



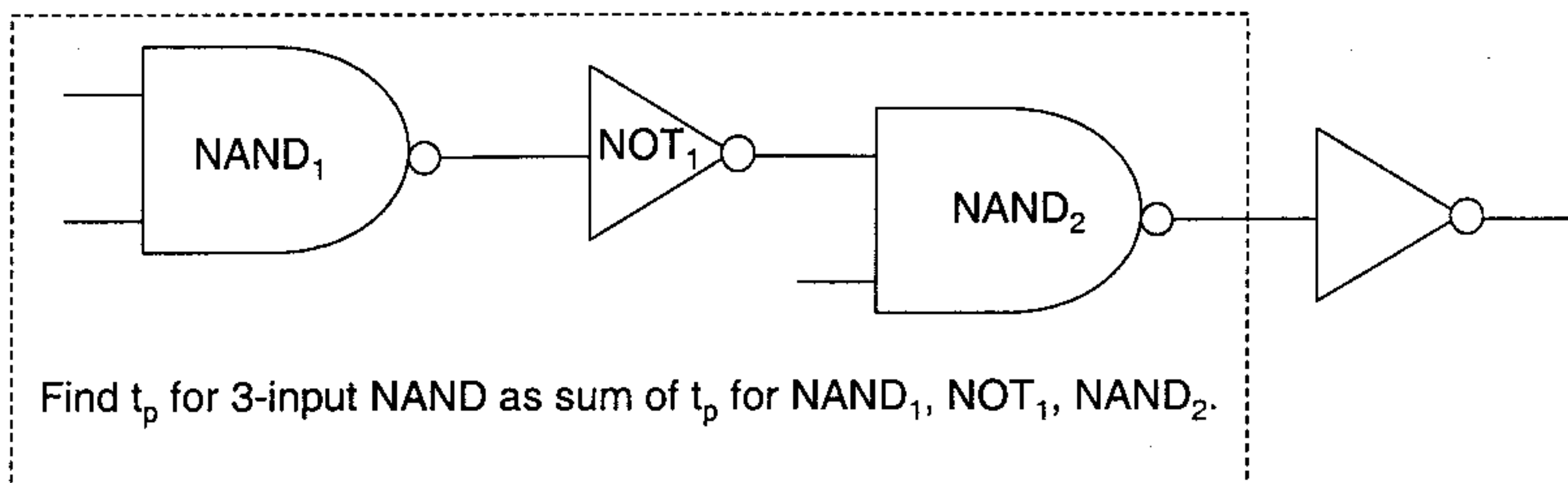
where the 3-input NAND is implemented using two 2-input NAND gates and an inverter:




Compute the propagation delay  $t_p$  for the 3-input NAND as the sum of the worst-case propagation delays of the individual gates inside.

Use  $R_N = 1 \text{ k}\Omega$ ,  $R_P = 2 \text{ k}\Omega$ , and  $C_G = 10 \text{ fF}$  per transistor. Ignore interconnect capacitance.

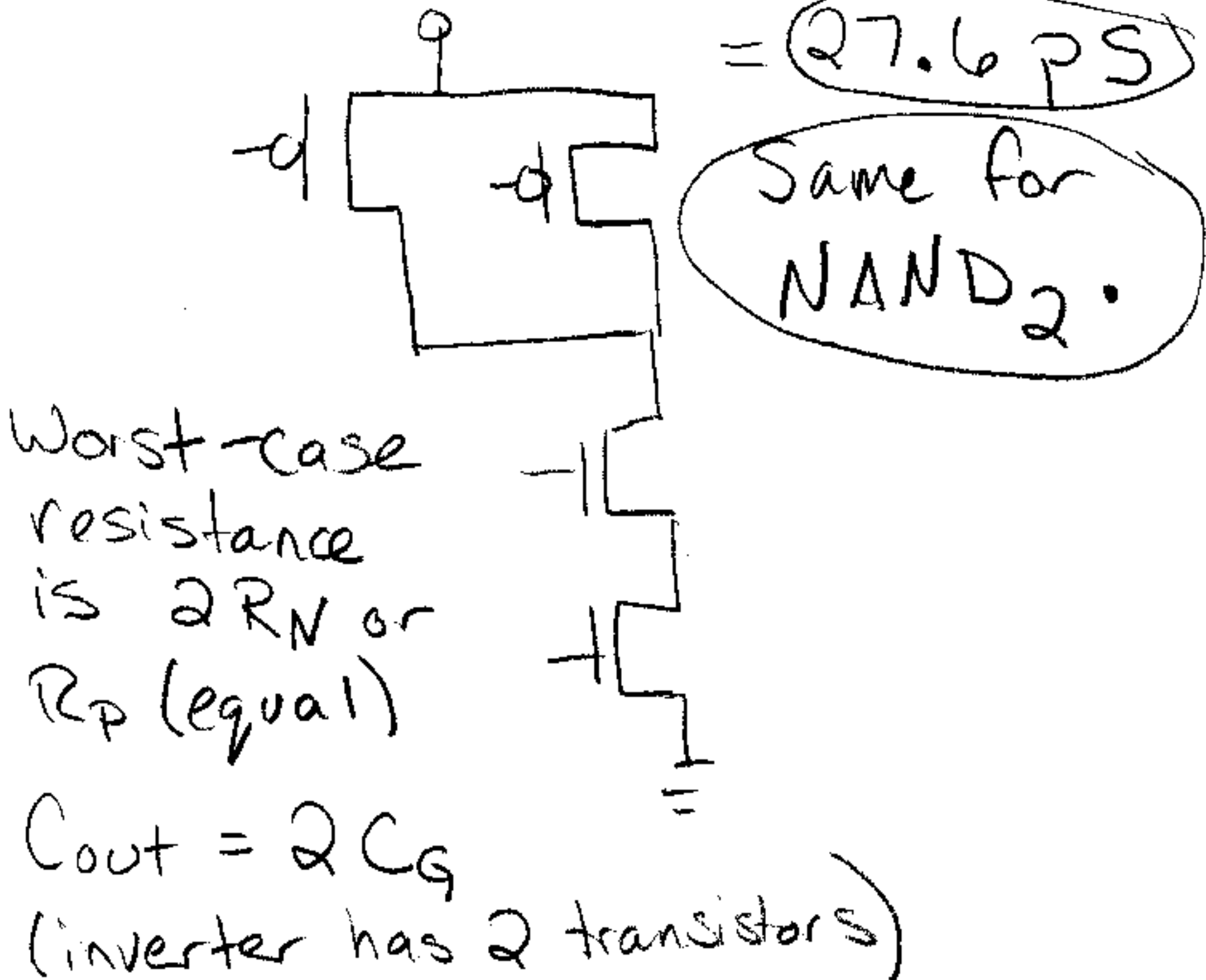NAND<sub>1</sub>:  $t_p = 0.69 R_P (2C_G)$   
 $= 27.6 \text{ pS}$



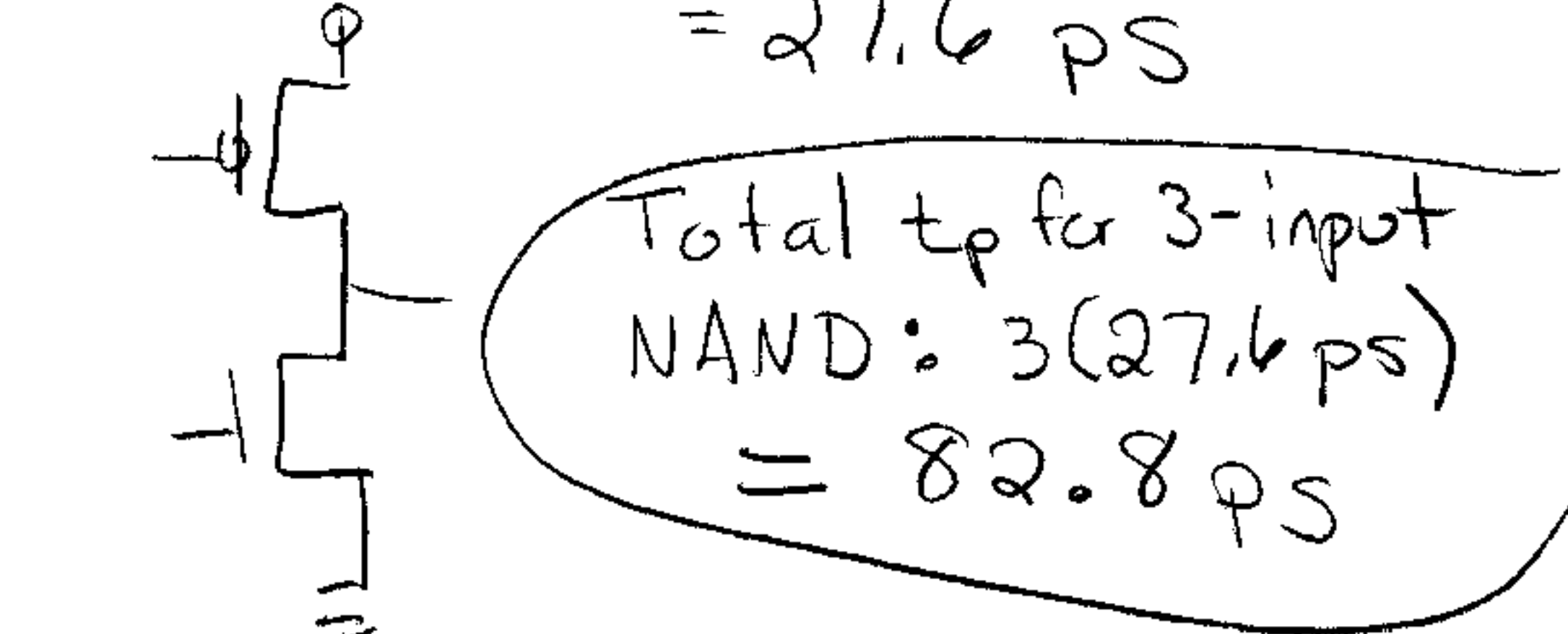NOT<sub>1</sub>:  $t_p = 0.69 R_P (2C_G)$   
 $= 27.6 \text{ pS}$



Worst-case resistance is  $R_P$ .  
 $C_{out} = 2C_G$   
 (output goes to one input of NAND:  
 2 of the 4 transistors)

Name Solutions

**Problem 6:** 10 Points Possible


Design a circuit, using only NMOS and PMOS transistors (and a power supply), that performs the 3-input NAND function with **shorter** worst-case propagation delay than the implementation given in Problem 5, when a single inverter is attached as the output load.

Assume that your transistors have the same characteristics as those in Problem 5:

Use  $R_N = 1 \text{ k}\Omega$ ,  $R_P = 2 \text{ k}\Omega$ , and  $C_G = 10 \text{ fF}$  per transistor. Ignore interconnect capacitance.

Provide your design and its worst-case propagation delay with single inverter output load.

Popular solution:

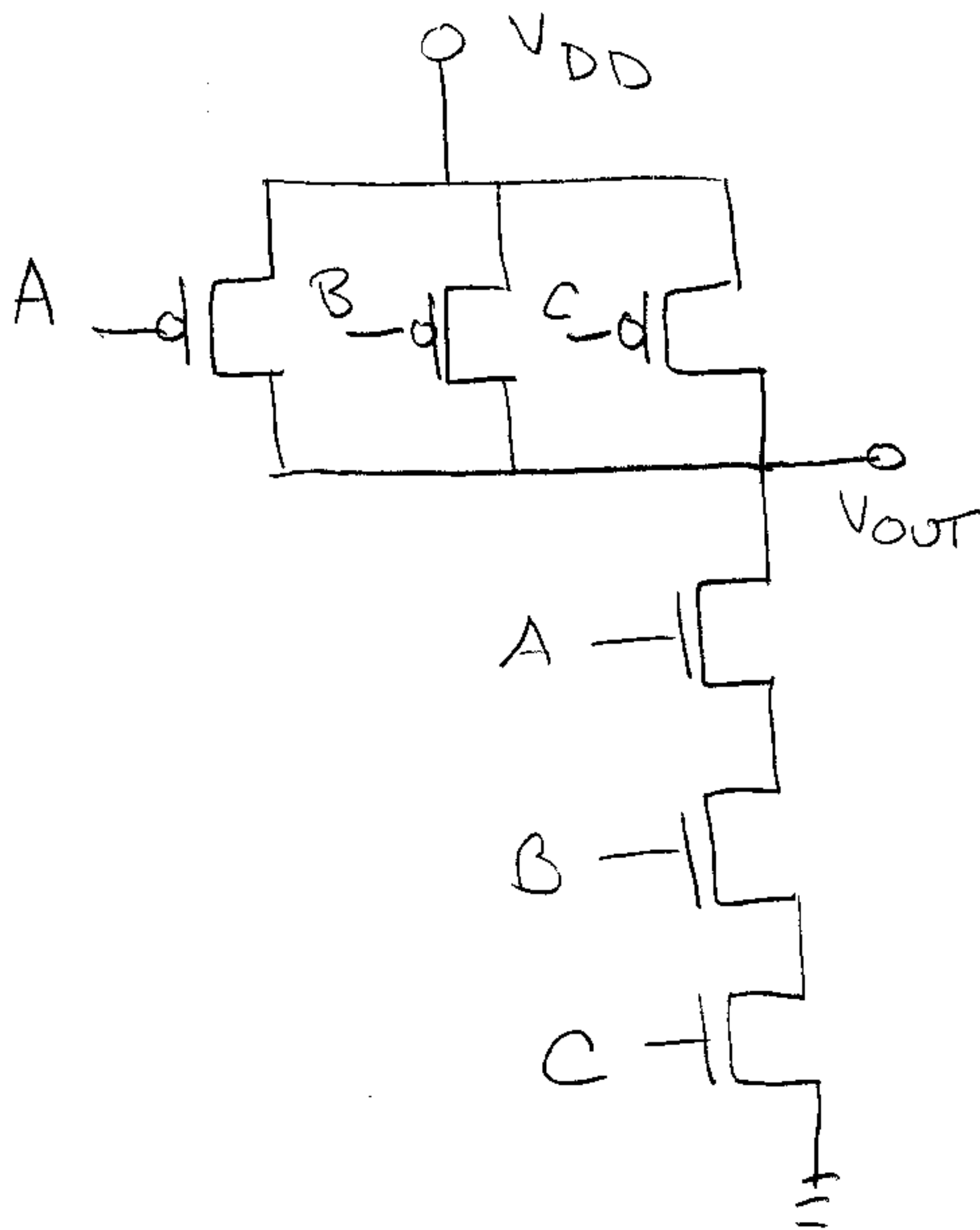


Worst-case resistance:  
 $3R_N$  (pull-down)  
If attached to inverter,  
 $C_{OUT} = 2C_G$   
 $t_p = 0.69(3R_N)(2C_G)$   
 $= 41.4 \text{ ps}$   
(half the delay of  
the Problem 5 analysis)

Name Grading

 **Problem 1:** 15 Points Possible

Determine whether the circuit below performs a logical operation. If it does, give the Boolean function it computes. If not, give a set of inputs that results in an invalid output.

For your convenience, 8 copies of this circuit are given on the next page. Assume that all PMOS transistors have source terminal on top, and all NMOS transistors have source terminal on the bottom.




15 points for  
correct function  
(any form)

-5 for various major errors  
(De Morgan applied wrong, things  
inverted or and/or ed where they shouldn't  
be, etc).

Name Grading

**Problem 1 Workspace**

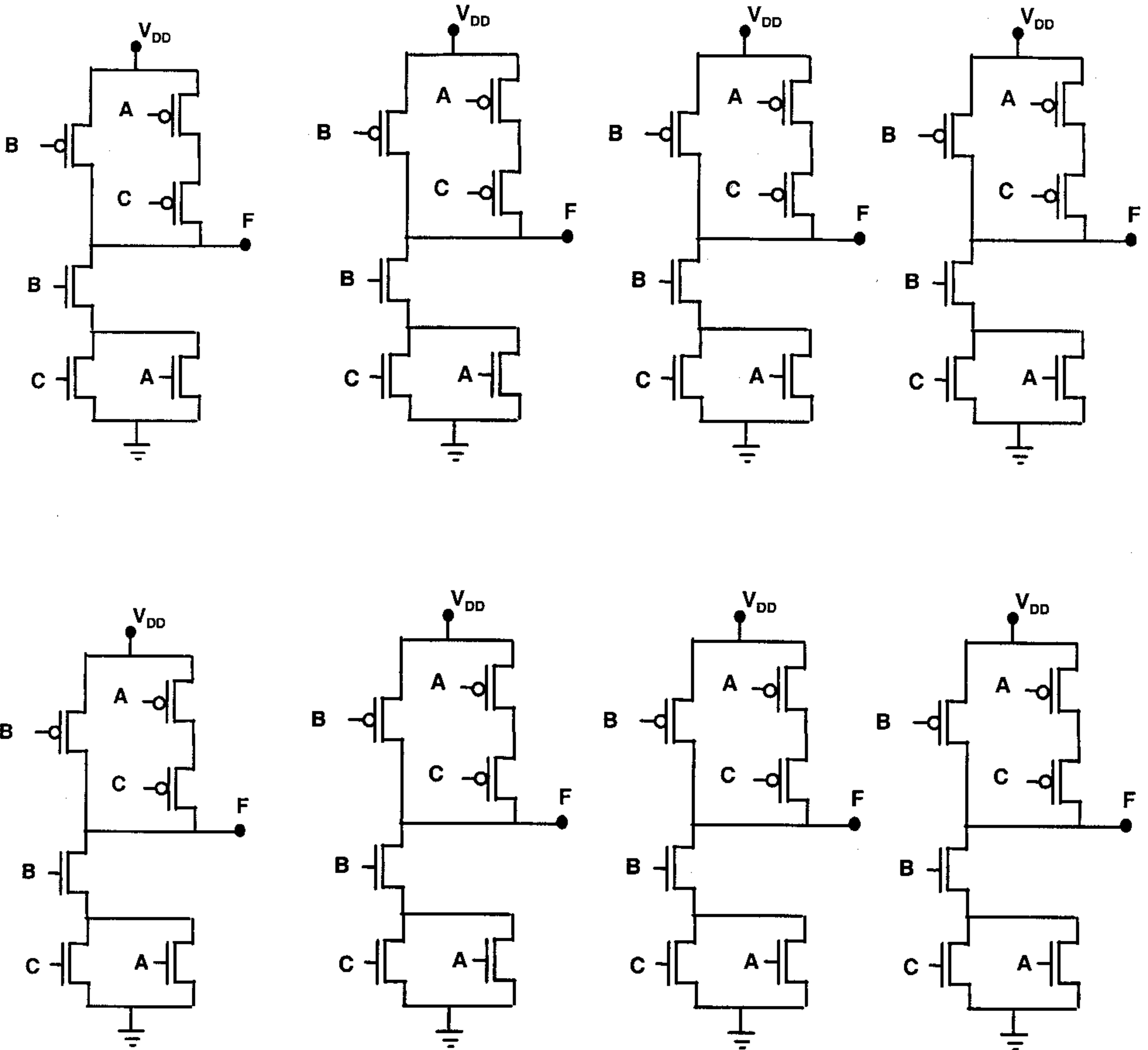


1.5 points for each correct output, all or nothing

3 points for corresponding Boolean function  
(award 1.5 points if it has a very small error)

Name Grading

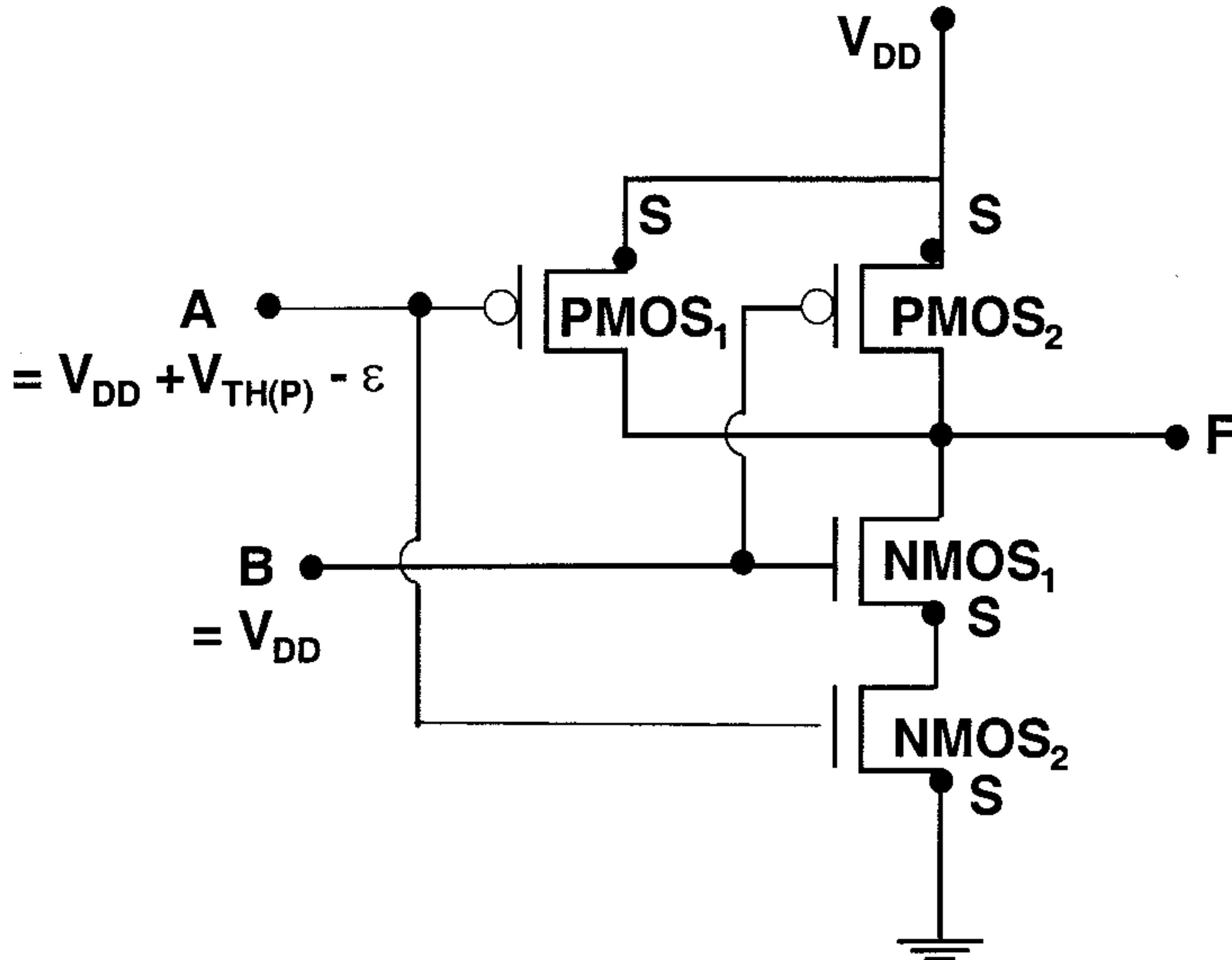**Problem 2:** 20 Points Possible

For the CMOS logic circuit below, determine the most probable mode of operation for each transistor. Assume that  $\epsilon$  is a very small positive number, and  $V_{DD}$  is much larger in magnitude than either  $V_{TH}$ .



5 points for each transistor

Mostly all-or-nothing, but if complete & correct information about a transistor is provided and the mode is accidentally recorded wrong, subtract only 2 points.

Also, if mode is wrong, but would be correct given the previous wrong assumptions/conclusions, do not subtract points.

Name Grading

**Problem 3:** 15 Points Possible

Consider the inverter at right, which turns on an LED when the output voltage is high.


I have put a resistor in series with the LED to limit the current so the LED doesn't burn.

But, the LED needs a current of at least 20 mA to light up.

I want the LED to light up for an input voltage as high as 0.8 V.

Will the LED light up for an input of 0.8 V?

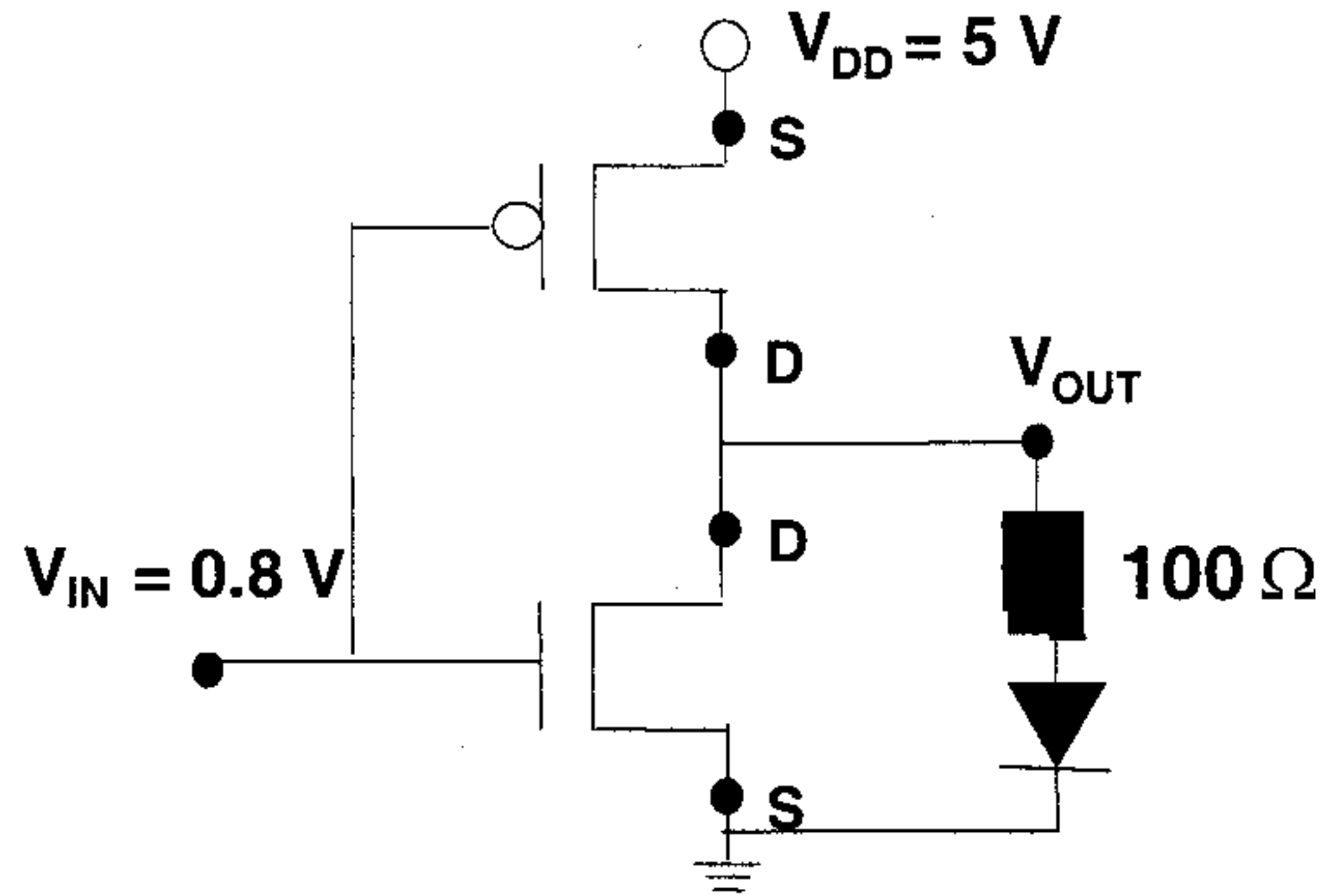$W/L \mu C_{ox} = 100 \text{ mA/V}^2$  for both transistors,  
 $V_{TH(N)} = -V_{TH(P)} = 1 \text{ V}$ ,  
 $\lambda = 0 \text{ V}^{-1}$  for both transistors,  
 $V_F = 2 \text{ V}$  for the LED (use large-signal model).



Grading based on reasoning as well as yes/no answer.

-2 if math error      -3 for minor error

-7 if answer is just "yes" or based on saturation mode

Other errors graded accordingly.

-4 for various major errors,

-6 if assumed  $I_{D_p} = -2.0 \text{ mA}$

Name Grading

**Problem 4:** 20 Points Possible


Consider the CMOS inverter at right, with

$W/L \mu C_{OX} = 1 \text{ mA/V}^2$  for both transistors,

$V_{TH(N)} = -V_{TH(P)} = 1 \text{ V}$ ,

$\lambda = 0.01 \text{ V}^{-1}$  for both transistors.

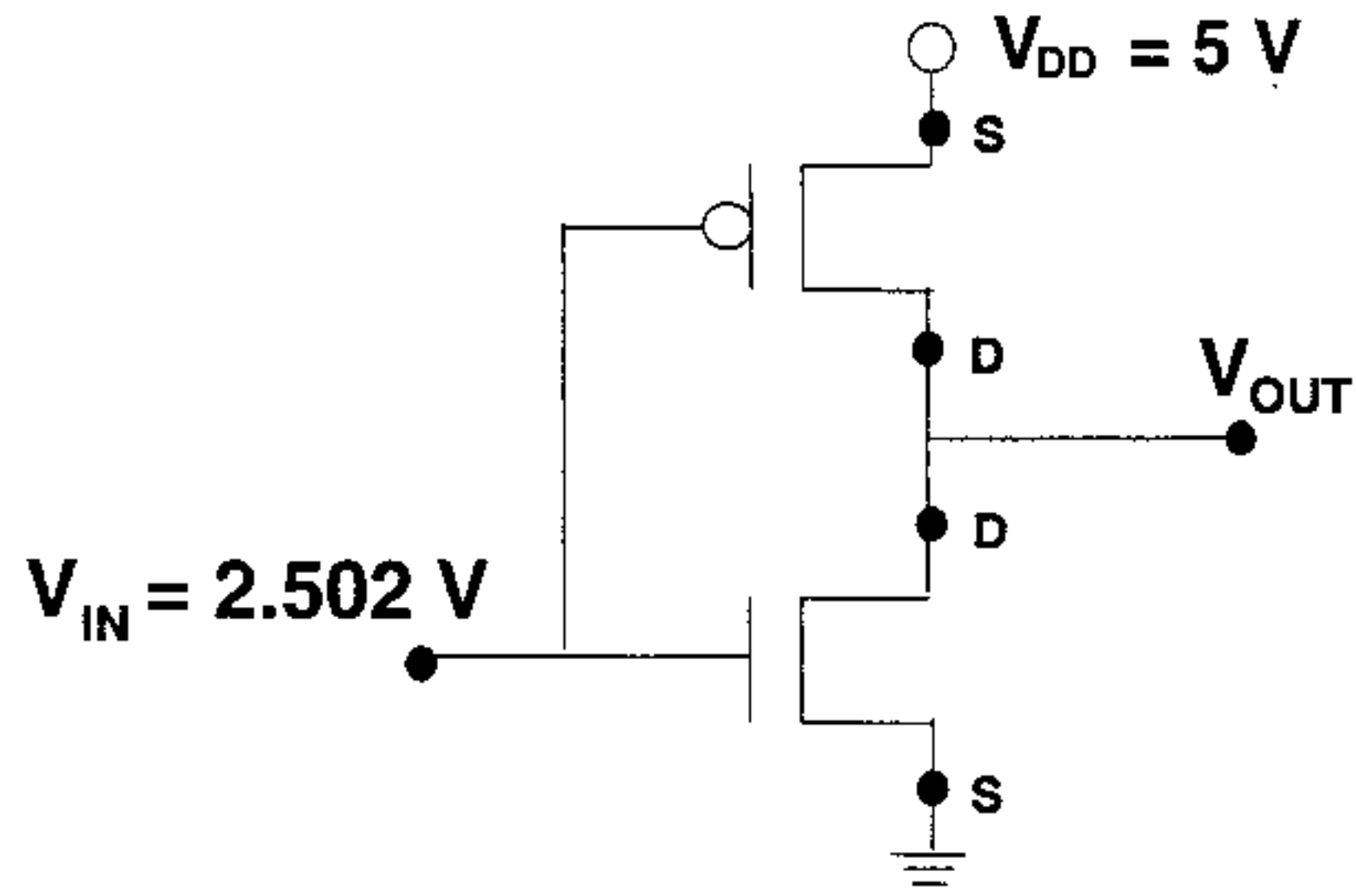For this inverter,  $V_M = 2.5 \text{ V}$ .



a) Find  $V_{OUT}$  for  $V_{IN} = 2.502 \text{ V}$ . Hint for guessing modes: Notice that  $V_{IN}$  is close to  $V_M$ .

b) Find the slope of the  $V_{OUT}$  vs.  $V_{IN}$  curve in this region, given by

$$\frac{\Delta V_{OUT}}{\Delta V_{IN}} = \frac{V_{OUT}(\text{for } V_{IN} = 2.502 \text{ V}) - V_M}{2.502 \text{ V} - V_M}$$

a) 5 points for correct modes  
5 points for correctly written equations  
5 points for solution


b) 5 points for correct computation

Possibility of -2 for math errors or  
-3 to -4 for other relatively minor errors.


Name Grading

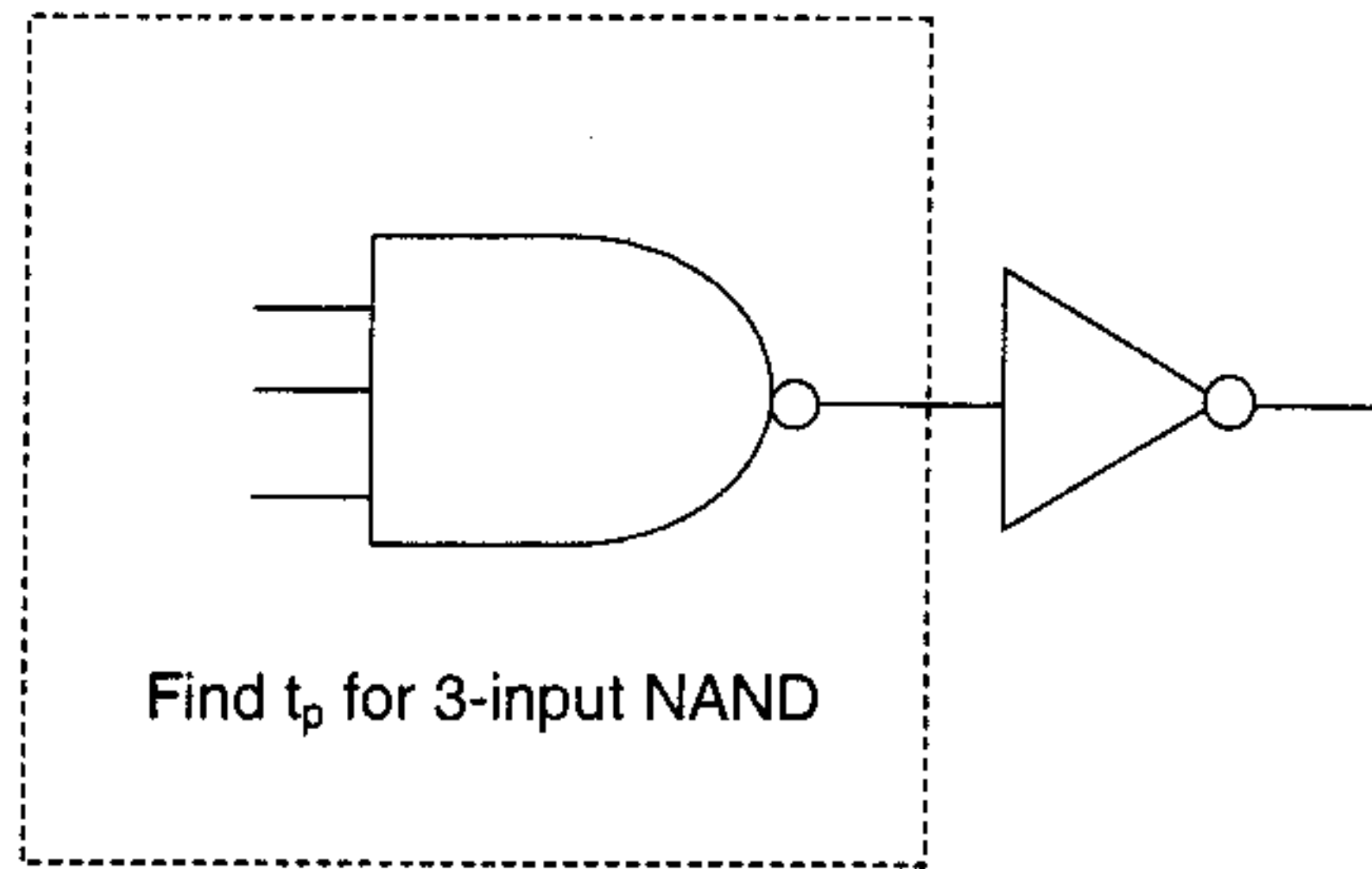**Problem 5:** 20 Points Possible

Find the propagation delay for this 3-input NAND gate with inverter load,



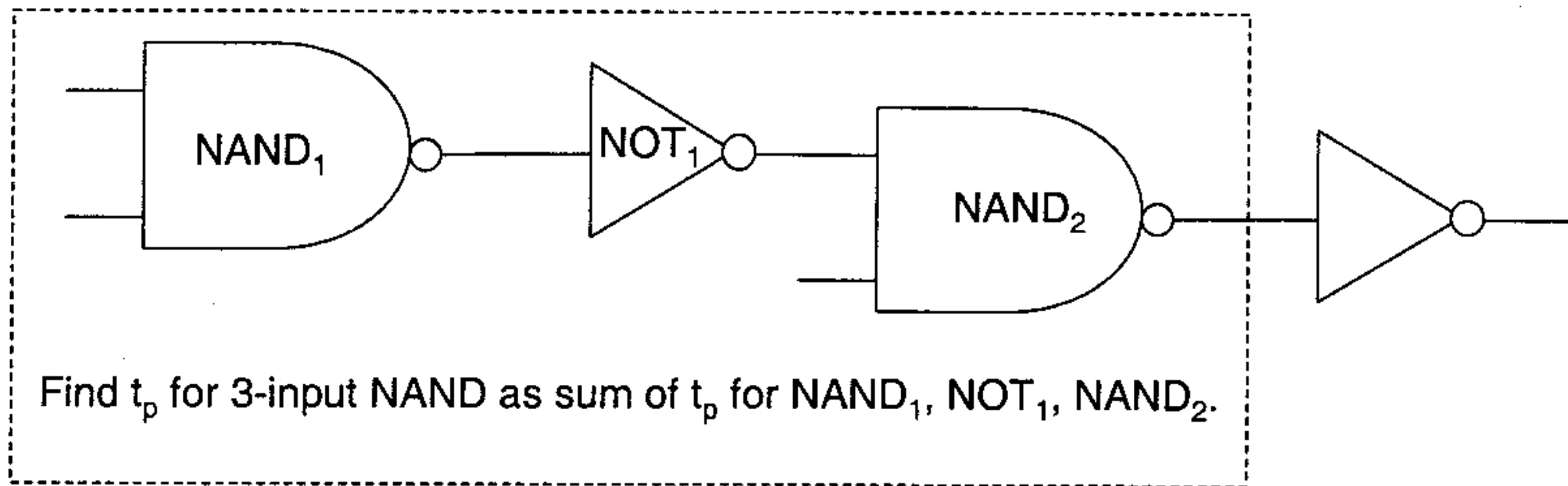where the 3-input NAND is implemented using two 2-input NAND gates and an inverter:



Compute the propagation delay  $t_p$  for the 3-input NAND as the sum of the worst-case propagation delays of the individual gates inside.

Use  $R_N = 1 \text{ k}\Omega$ ,  $R_P = 2 \text{ k}\Omega$ , and  $C_G = 10 \text{ fF}$  per transistor. Ignore interconnect capacitance.

- 4 for wrong worst-case resistance

- 4 for wrong output capacitance

Don't double-count same mistake

(i.e., only -4 for wrong resistance for NAND<sub>1</sub> & NAND<sub>2</sub>)

- 2 for math error (incl. powers of 10 error)



Name Grading

**Problem 6:** 10 Points Possible

Design a circuit, using only NMOS and PMOS transistors (and a power supply), that performs the 3-input NAND function with **shorter** worst-case propagation delay than the implementation given in Problem 5, when a single inverter is attached as the output load.

Assume that your transistors have the same characteristics as those in Problem 5:

Use  $R_N = 1 \text{ k}\Omega$ ,  $R_P = 2 \text{ k}\Omega$ , and  $C_G = 10 \text{ fF}$  per transistor. Ignore interconnect capacitance.

Provide your design and its worst-case propagation delay with single inverter output load.

If design does 3-input NAND but is not correctly proven to have shorter  $t_p$ ,  
- 9 points.

Otherwise,

If design only has very small error, -3 points.

If propagation delay calculated incorrectly,  
-4 points.