

1.

a) (5 points)

A silicon sample is uniformly doped with Boron to a concentration of $10^{16} \text{ atoms/cm}^3$. Determine the resistivity of the sample at room temperature.

Use electron mobility = $\mu_n = 1000 \text{ cm}^2/\text{v-s}$, hole mobility = $\mu_p = 400 \text{ cm}^2/\text{v-s}$,


$q = 1.6 \cdot 10^{-19} \text{ C}$ and $n_i = 10^{10}$ at room temperature.

b) (5 points)

The same sample is then to be counter doped to a depth of $5 \mu\text{m}$ with Arsenic atoms to create a resistor technology with resistance of $100 \Omega/\square$.

Determine the required Arsenic doping density.


2.

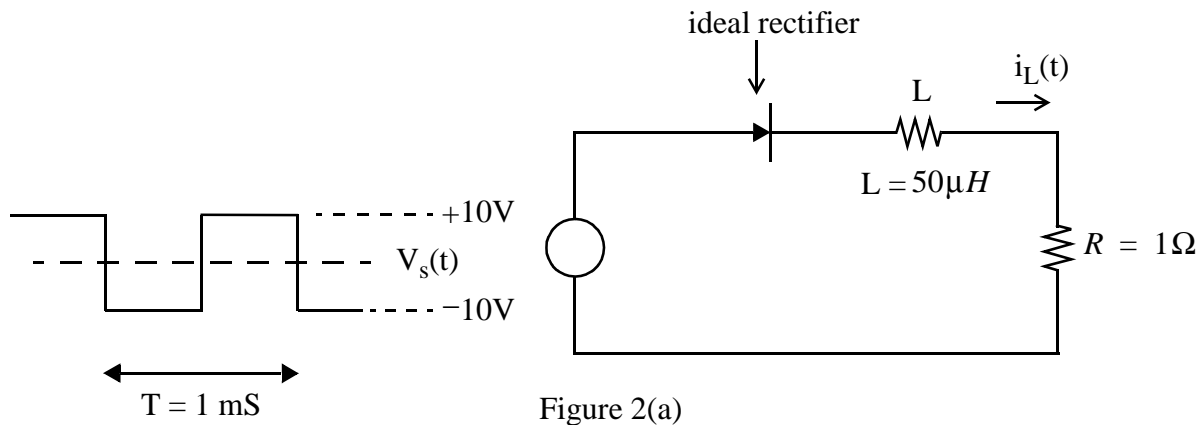

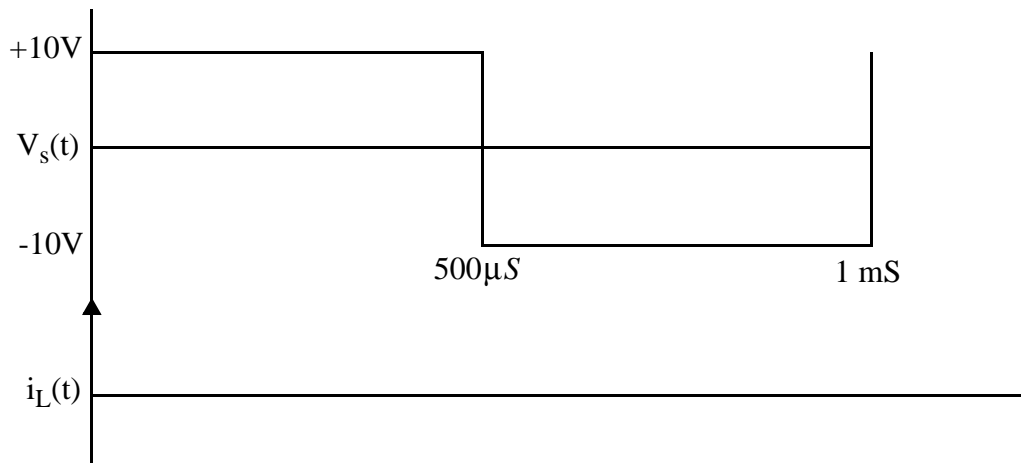a) (10 points)

The diode in Figure 2(a) is ideal. The waveform $V_s(t)$ is a balanced square wave with amplitude of 10 V and period of 1mS. Take $L = 50\mu H$ and $R = 1\Omega$.

The circuit operates in a periodic steady state. Sketch and carefully dimension one period of the $i_L(t)$ waveform on the axes below. Make reasonable approximations.



b) (10 points)

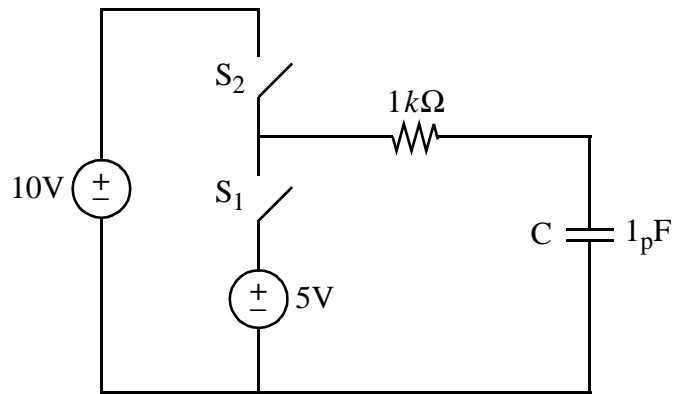


Figure 2(b)

In the circuit of Figure 2(b), switch S_1 is initially closed and the circuit is in equilibrium. Switch S_1 is then opened and switch S_2 is closed for a sufficiently long time so that the circuit can be considered to be in equilibrium. How much energy is dissipated in the $1k\Omega$ resistor during the transient?

Hint: Think in terms of net charge and energy flow. Detailed transient analysis is **NOT** needed.

3.

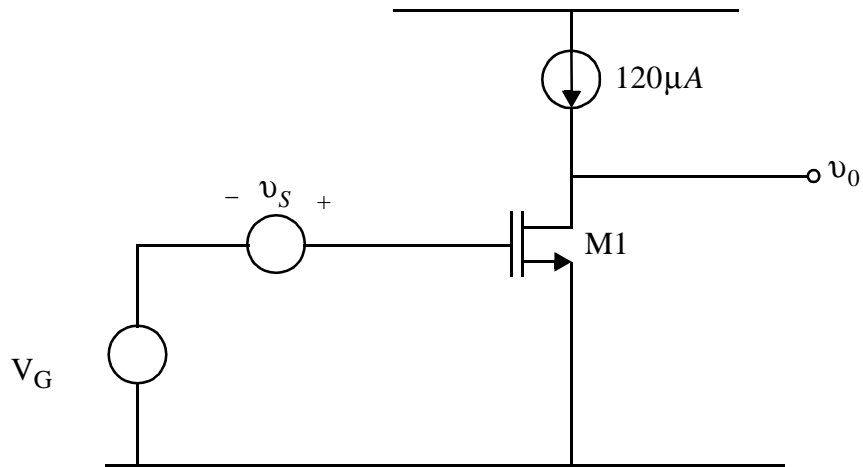


Figure 3

$$\lambda = 0.1 \text{ V}^{-1}$$

$$V_T = 0.5 \text{ V}$$

$$k' = 100 \mu\text{A}/\text{V}^2$$

$$\frac{W}{L} = 2$$

Mosfet M1 in Figure 3 is modeled by $i_D = \frac{1}{2}k' \frac{W}{L} (v_{GS} - V_T)^2 (1 + \lambda v_{DS})$ in saturation with parameters listed in Figure 3.

a) (5 points)

Determine the requires bias voltage V_G so that M1 is biased in saturation with $V_{DS} = 2\text{V}$. Take $v_S = 0$ for this calculation.

b) (10 points)

Draw the small signal model for this circuit. Compute the parameters of this small signal model.

c) (5 points)

Determine the small signal gain $A_v = \frac{v_0}{v_S}$.