UNIVERSITY OF CALIFORNIA AT BERKELEY EECS Department

EECS 40, Summer 2005 Instructor: Octavian Florescu Homework #1

Due Monday, 6/27/05 at 6PM in HW Box (2nd floor lounge)
Total Points:

Note: Be sure to put (1) your name and (2) discussion section number on your homework. You will get the graded homework back in your discussion session.

Current and voltage

Problem 1: Problem 1.8 in the textbook

Power and energy

Problem 2: Problem 1.14 in the textbook

Kirchhoff's Current And Voltage Law

Problem 3: Problem 1.28 in the textbook Problem 4: Problem 1.34 in the textbook

Introduction to Circuits

Problem 5: Problem 1.50 in the textbook Problem 6: Problem 1.52 in the textbook Problem 7: Problem 1.53 in the textbook Problem 8: Problem 1.58 in the textbook