


HW1 Solution

① P 1.8 text book

(a) $i(t) = 10 \sin(200\pi t)$

$$\omega = 200\pi = \frac{2\pi}{T}$$

$$T = 10 \text{ ms}$$

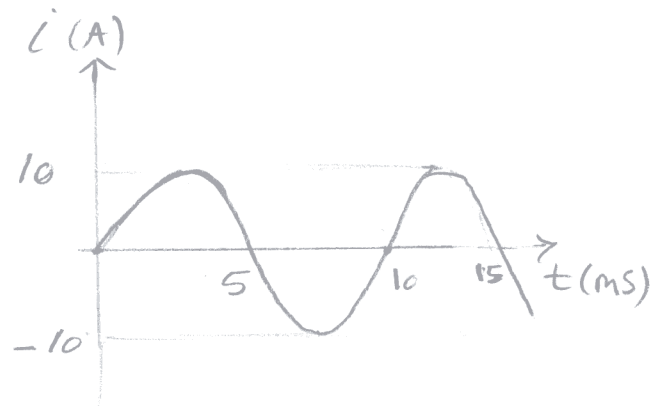

$$(b) Q = \int_{t_1=0}^{t_2=0.005} i(t) dt = 10 \int_{t=0}^{t=5 \text{ ms}} \sin(200\pi t) dt$$

$$Q = \frac{10}{200\pi} \cos(200\pi t) \Big|_0^{0.005} \Rightarrow \boxed{Q = 0.0318 \text{ C}}$$

$$(c) Q = \int_{t_1=0}^{t_2=0.01} i(t) dt = 10 \int_0^{0.01} \sin(200\pi t) dt \Rightarrow \boxed{Q = 0 \text{ C}}$$

② P 1.14 text book


(a) $P = -V_a i_a = -20 \text{ W}$ Energy is being supplied by the element

(b) $P = V_b i_b = 50 \text{ W}$ Energy is being absorbed by the element

(c) $P = -V_c i_c = 40 \text{ W}$ Energy is being absorbed by the element

HW1 Solution

③ P1.28 text book

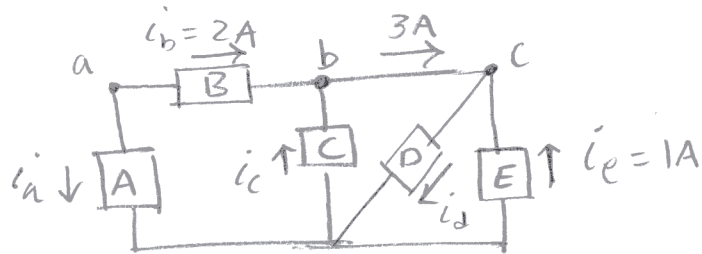


$$\text{KCL @ node a: } i_a = -i_b \Rightarrow \boxed{i_a = -2A}$$

$$\text{KCL @ node b: } -2A - i_c + 3A = 0 \Rightarrow \boxed{i_c = 1A}$$

$$\text{KCL @ node c: } -3A + i_d - i_e = 0 \Rightarrow \boxed{i_d = 4A}$$

Elements A and B are connected in series.

④ P1.34 text book

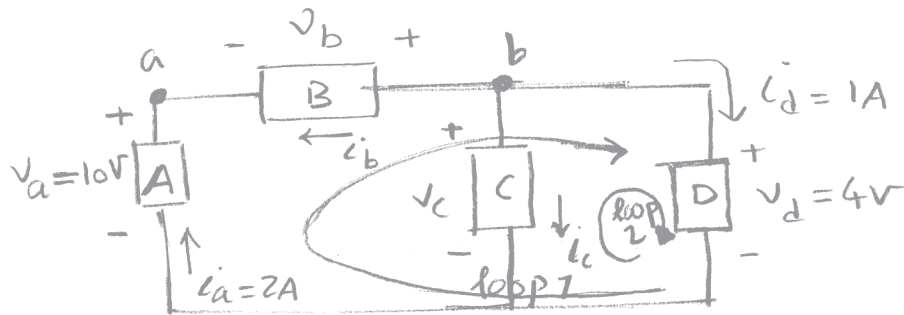

KCL @ node a: $i_b = -i_a \Rightarrow \boxed{i_b = -2A}$

KCL @ node b: $i_b + i_c + i_d = 0 \Rightarrow i_c = -(i_d + i_b)$

$i_c = -(1A + (-2A))$

$\boxed{i_c = 1A}$

KVL for loop 1 (ABDA): $-v_a - v_b + v_d = 0$

$v_b = -v_a + v_d \Rightarrow \boxed{v_b = -6V}$

KVL for loop 2 (CDC): $-v_c + v_d = 0 \Rightarrow \boxed{v_c = v_d = 4V}$

Power calculation:

$P_A = -i_a v_a = -20W$

$P_B = i_b v_b = 12W$


$P_C = i_c v_c = 4W$

$P_D = i_d v_d = 4W$

$P_A + P_B + P_C + P_D = 0$

\therefore Power is conserved

⑤ P 1.50 textbook

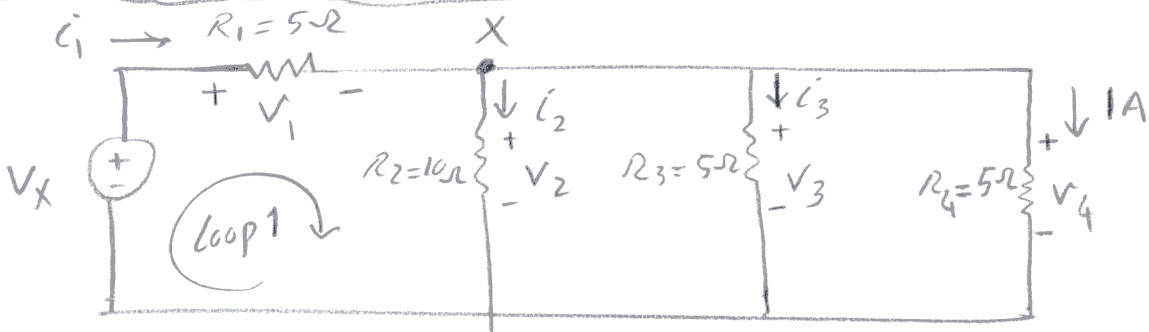

Ohm's Law for R_4 : $V_4 = R_4 \cdot (1A) \Rightarrow \boxed{V_4 = 5V}$

Notice that R_2 , R_3 and R_4 are connected in parallel. Therefore, $\boxed{V_2 = V_3 = V_4 = 5V}$

Ohm's Law for R_3 : $i_3 = \frac{V_3}{R_3} = \frac{5V}{5\Omega} = 1A$

Ohm's Law for R_2 : $i_2 = \frac{V_2}{R_2} = 0.5A$

KCL at X: $-i_1 + i_2 + i_3 + 1A = 0 \Rightarrow i_1 = i_2 + i_3 + 1A$
 $i_1 = 2.5A$

Ohm's Law for R_1 : $V_1 = R_1 i_1 = 12.5V$


KVL for Loop 1: $-V_x + V_1 + V_2 = 0$

$V_x = V_1 + V_2 = 12.5V + 5V$

$\Rightarrow \boxed{V_x = 17.5V}$

HW1 solution

⑥ P1.52 text book

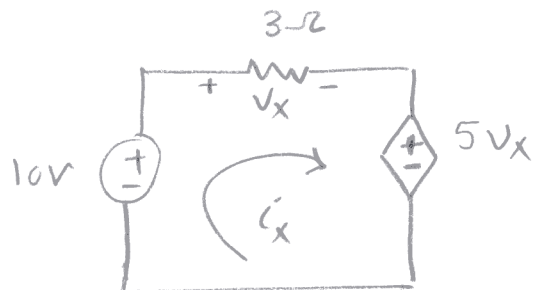

$$(a) \quad -10 + V_x + 5V_x = 0$$

$$6V_x = 10 \Rightarrow \boxed{V_x = \frac{10}{6} \text{ V} \approx 1.67 \text{ V}}$$

$$(b) \quad i_x = \frac{V_x}{R} = \frac{(10/6) \text{ V}}{3 \Omega} \Rightarrow \boxed{i_x = \frac{10}{18} \text{ A} \approx 0.56 \text{ A}}$$

$$P_{\text{Independent source}} = (-i_x)(10 \text{ V}) = -\frac{100}{18} \text{ W} \quad \text{delivered}$$

$$P_R = V_x i_x = \left(\frac{10}{6} \text{ V}\right) \left(\frac{10}{18} \text{ A}\right) = \frac{100}{108} \text{ W} \quad \text{absorbed}$$


$$P_{\text{dependent source}} = (i_x)(5V_x) = \left(\frac{10}{18} \text{ A}\right) \left(\frac{50}{6} \text{ V}\right) \\ = \frac{500}{108} \text{ W} \quad \text{absorbed}$$

$$P_{\text{total}} = \left(-\frac{100}{18} \text{ W}\right) + \left(\frac{100}{108} \text{ W}\right) + \left(\frac{500}{108} \text{ W}\right) = 0$$

\Rightarrow Power is conserved

HW1 Solution

⑦ P 1.53 text book

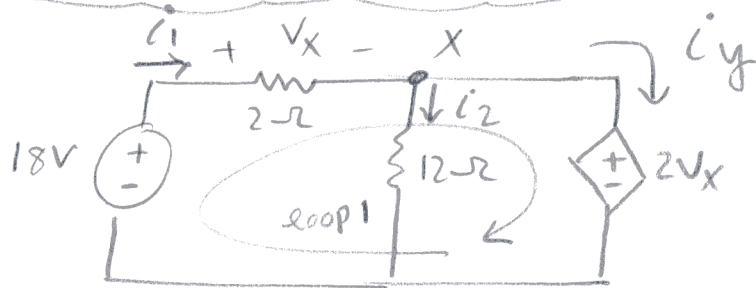

$$\text{KVL loop 1: } -18 + V_x + 2V_x = 0 \Rightarrow 3V_x = 18 \Rightarrow \boxed{V_x = 6\text{V}}$$


$$i_1 = \frac{V_x}{2\Omega} = 3\text{A}$$

$$i_2 = \frac{2V_x}{12\Omega} = 1\text{A}$$

$$\text{KCL at node X: } -i_1 + i_2 + i_y = 0$$

$$i_y = i_1 - i_2 \Rightarrow \boxed{i_y = 2\text{A}}$$

⑧ P 1.58 text book

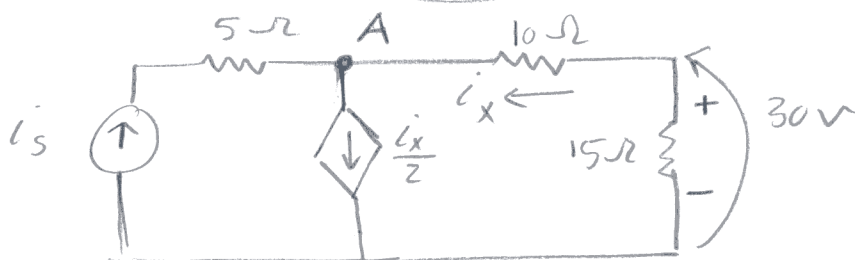

$$i_x = \frac{-30\text{V}}{15\Omega} = -2\text{A}$$

$$\text{KCL @ node A: } -i_s + \frac{i_x}{2} - i_x = 0 \Rightarrow i_s = -\frac{i_x}{2}$$

$$\boxed{i_s = 1\text{A}}$$

Type of sources: