

UNIVERSITY OF CALIFORNIA AT BERKELEY  
EECS Department


EECS 40, Summer 2005  
Octavian Florescu  
Homework #3

Due Tuesday, 7/12 at 6PM in HW Box (2<sup>nd</sup> floor lounge)  
Total Points:


First Order Circuits

Problem 1

 - a) Consider the capacitive voltage-divider circuit below. Find  $V_{out}$ . How will  $V_{out}$  change if a small load capacitance  $C_{Load} < 2 \mu\text{F}$  is connected between terminals a and b?




- b) Consider the following RC circuit

 

Provide a physical reason why it takes longer for  $V_c$  to reach its final value if  $R$  is increased. (Why is the characteristic time constant proportional to  $R$ )

- c) Assume that the circuit below is operating in steady state with the switch open for  $t < 0$ . Find and accurately sketch  $v(t)$  for all  $t$ .

 

**Problem 2:** P4.20 in the textbook.

**Problem 3:** P4.26 in the textbook

**Problem 4:** P4.33 in the textbook

**Problem 5:** P4.35 in the textbook

**Second Order Circuits:**

**Problem 6:** P4.48 in the textbook

**Complex Impedances:**

**Problem 7:** P5.41 from the textbook

**Problem 8:** P5.42 from the textbook

**Problem 9:** P5.43 from the textbook

**Problem 10:** P5.44 from the textbook