


EECS 40
Summer 05

HW3 Solution

①

$$a) V_{out} = \frac{8\text{MF}}{8\text{MF} + 2\text{MF}} (10\text{V}) = \boxed{8\text{V}}$$

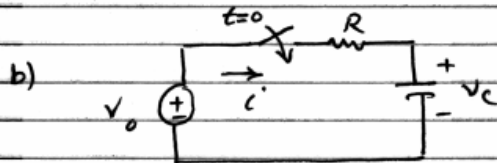V_{out} will decrease because the capacitance between terminals a and b will increase.






$$i = \frac{v_o - v_c}{R} = C \frac{dv_c}{dt}$$

The current flowing through R (to charge C) will decrease, hence it will take longer to deliver the charge $Q = Cv_o$

①


problem 1 continued

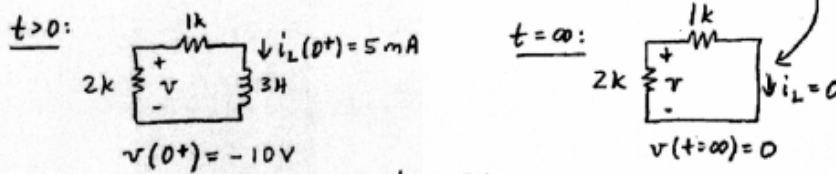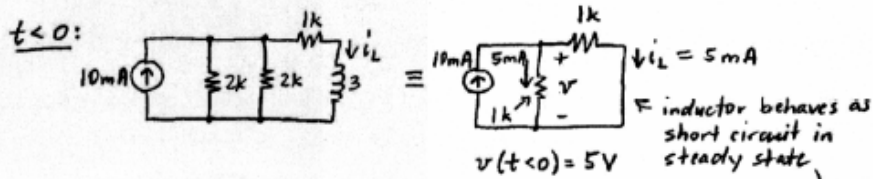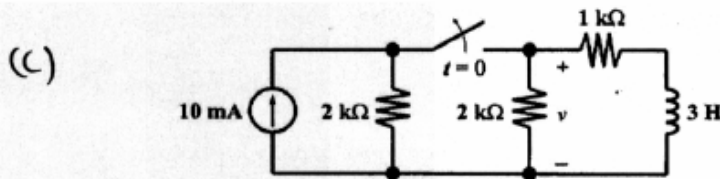

$$\tau = \frac{L}{R} = \frac{3H}{2k\Omega + 1k\Omega} = 1ms$$

$$v = 0 + [-10 - 0]e^{-t/1ms} = -10e^{-1000t}$$

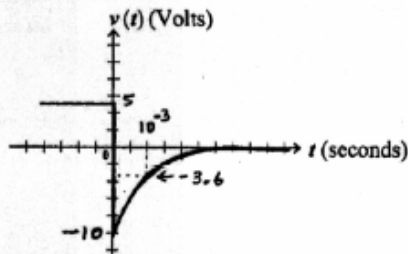For $t < 0$: $v(t) = 5V$. For $t > 0$: $v(t) = -10e^{-1000t}$



② p 4.20

$t < 0$ $V_R(t) = 0$
 $V_C(t) = \frac{10k\Omega}{(20k\Omega + 10k\Omega)} \cdot 30V = 10V$

$t > 0$ $V_R(t) = Ri = V_C(t)$

~~$Ri = V_C(t)$~~
 $\Rightarrow RC \frac{dV_C(t)}{dt} = -V_C(t)$


$\Rightarrow \frac{dV_C(t)}{dt} + \frac{1}{RC} V_C(t) = 0$

$V_C(t) = K_1 e^{-\frac{t}{\tau}} + K_2$

$\begin{cases} V_C(0^-) = V_C(0^+) = 10V \\ V_C(\infty) = 0 \end{cases} \Rightarrow \begin{cases} K_1 = 10V \\ K_2 = 0 \end{cases}$

$V_C(t) = V_R(t) = 10 e^{-\frac{t}{\tau}} \quad \tau = RC = 2S$

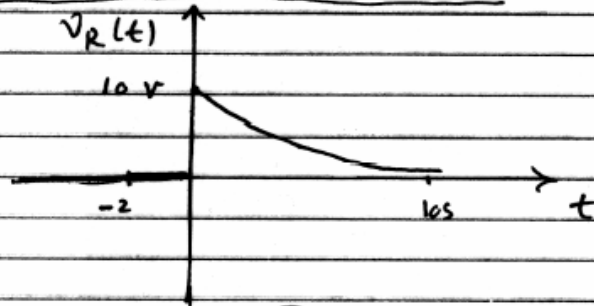$\therefore V_R(t) = \begin{cases} 0V & t < 0 \\ 10 e^{-\frac{t}{2}} V & t > 0 \end{cases}$



③

③ P. 4.26


$$t < 0 \quad i(t) = \frac{100V}{25\Omega + 75\Omega} = 1A$$

$t < 0$

$$i(t) = K_1 e^{-\frac{t}{\tau}} + K_2 \quad \frac{1}{\tau} = \frac{R}{L} = \frac{25\Omega}{2H} = 12.5S$$

$$\textcircled{1} \quad \begin{cases} i(0^-) = i(0^+) = 1A \Rightarrow K_1 + K_2 = 1 \end{cases}$$

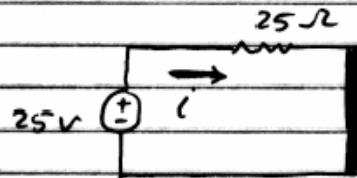
$$\textcircled{2} \quad \begin{cases} i(\infty) = \frac{100V}{25\Omega} = 4A \end{cases}$$



note that the Inductor becomes a short circuit in steady state, when $t \rightarrow \infty$.

$$\therefore \textcircled{1}, \textcircled{2} \Rightarrow \begin{cases} K_2 = 4 \\ K_1 = -3 \end{cases}$$
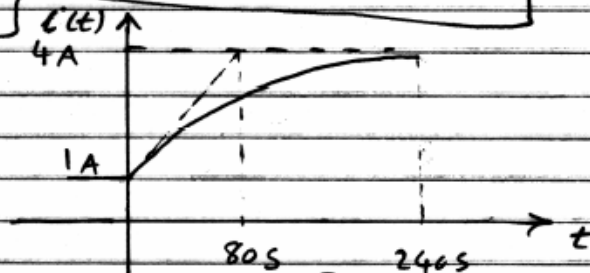
$$i(t) = \begin{cases} 1A & \text{for } t < 0 \\ -3e^{-12.5t} + 4 & \text{for } t \geq 0 \end{cases} A$$



④

④ P 4.33

$$\text{KVL: } \frac{V_c(t) - v(t)}{R} + C \frac{dV_c(t)}{dt} = 0$$

Rearranging this equation and substituting $v(t) = t$, we have

$$RC \frac{dV_c(t)}{dt} + V_c(t) = t \text{ for } t > 0 \quad (1)$$

$$V_{cp}(t) = A + Bt \quad (2)$$

Substituting equation 2 into equation 1:

$$RCB + A + Bt = t$$

$$\Rightarrow B = 1$$

$$A = -RC$$

$$\Rightarrow V_{cp}(t) = -RC + t$$

The complementary solution to the homogeneous equation is of the form:

$$V_{cc}(t) = K_1 e^{-\frac{t}{RC}}$$

Thus the complete solution is

$$V_c(t) = V_{cp}(t) + V_{cc}(t) = -RC + t + K_1 e^{-\frac{t}{RC}}$$


⑤

problem ④ continued

The solution must meet the given initial condition

$$V_c(0) = 0 = -RC + K_1 \Rightarrow K_1 = RC$$

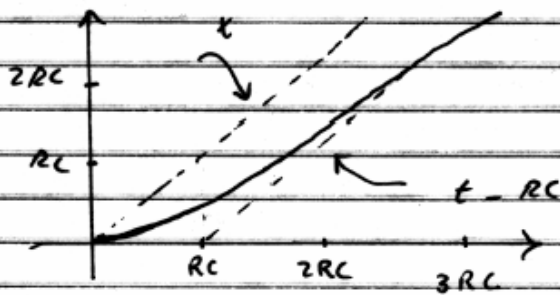
$$V_c(t) = V_{fp}(t) + V_{fc}(t) = -RC + t + RC e^{-\frac{t}{RC}}$$



⑥

⑤ p 4.35

$$R = 10 \Omega$$
$$L = 1 \text{ H}$$

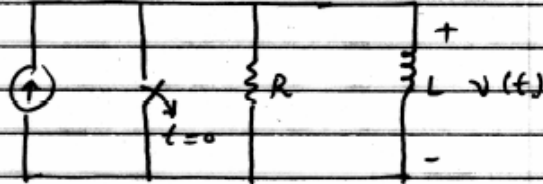

$$\text{KCL: } \frac{v(t)}{R} + \frac{1}{L} \int v(t) dt = 5 \cos(10t)$$

$$\frac{1}{R} \frac{dv(t)}{dt} + \frac{1}{L} v(t) = -50 \sin(10t)$$

$$v(t) + \frac{L}{R} \frac{dv(t)}{dt} = -50L \sin(10t) \quad (1)$$

We know $v(t) = v_p(t) + v_c(t)$

where $v_p(t)$ is the particular solution
and $v_c(t)$ is the complementary
solution to the differential equation.

$$v_p(t) = A \cos(10t) + B \sin(10t) \quad (2)$$

We substitute (2) into equation (1):

$$A \cos(10t) + B \sin(10t) + \frac{L}{R} (-10A \sin(10t) + 10B \cos(10t))$$
$$= -50L \sin(10t)$$

$$\Rightarrow \left[A + (10B) \left(\frac{L}{R} \right) \right] \cos(10t) + \left[B - (10A) \left(\frac{L}{R} \right) \right] = -50L \sin$$

$$\Rightarrow \begin{cases} A + (10B) \left(\frac{L}{R} \right) = 0 \\ B - (10A) \left(\frac{L}{R} \right) = -50L \end{cases} \xrightarrow{\frac{L}{R} = 10} \begin{cases} A + B = 0 \\ B - A = -50 \end{cases}$$

⑦

⑤ continued

$$\begin{array}{l} A = 25 \\ B = -25 \end{array}$$

$$\Rightarrow v_p(t) = 25 \cos(10t) - 25 \sin(10t)$$

$$v_c(t) = K e^{-\frac{t}{\tau}} \quad \tau = \frac{L}{R} = 0.15$$

$$\therefore v(t) = v_p(t) + v_c(t)$$

$$v(t) = K e^{-\frac{t}{\tau}} + 25 \cos(10t) - 25 \sin(10t) \quad (3)$$

Because the current in the inductor is zero at $t = 0^+$, the 5A supplied by the source must flow through the 10Ω resistor and we have $v(0^+) = 50$. substituting this into the general solution, equation (3), we get $K_1 = 25$

Thus

$$v(t) = 25 e^{-\frac{t}{\tau}} + 25 \cos(10t) - 25 \sin(10t) \quad t \geq 0$$
$$\tau = 0.15$$

⑧

⑥ p4. 48

$$(a) \quad \alpha = \frac{1}{2RC} = 20 \times 10^6$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10 \times 10^6 \frac{1}{s}$$

$$\zeta = \frac{\alpha}{\omega_0} = 2$$

Thus we have an overdamped circuit

(b) writing a current equation at $t=0^+$, we have

$$\frac{V(0^+)}{R} + i_L(0^+) + C V'(0^+) = 1$$

substituting $V(0^+) = 0$ and $i_L(0^+) = 0$, yields

$$V'(0^+) = \frac{1}{C} = 10^9 \frac{V}{s}$$

(c)

under steady-state conditions, the inductance acts as a short circuit. Therefore, the particular solution for $v(t)$ is:

$$V_p(t) = 0$$

$$\text{note: } v(t) = V_c(t) + V_p(t)$$

we know that $V_c(t)$ is a multiple of e^{-st} , so $V_c(t) = 0$ for $t \rightarrow \infty$

~~Therefore~~

⑨

We know $v(t) = 0$ when $t \rightarrow \infty$. Thus

$$V_p(t) = 0$$

$$(d) \quad s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -2.679 \times 10^6$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -37.32 \times 10^6$$

The complementary solution is

$$V_c(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

Since the particular solution is zero
the complete solution is

$$V(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

$$v(0^+) = 0 \quad \text{and} \quad v'(0^+) = 10^9 \text{ V}$$

Thus we have:

$$v(0^+) = 0 = K_1 + K_2$$

$$v'(0^+) = 10^9 = s_1 K_1 + s_2 K_2$$

$$\Rightarrow K_1 = 28.87$$

$$K_2 = -28.87$$

$$v(t) = 28.87 e^{s_1 t} - 28.87 e^{s_2 t}$$

⑦ p5.41

$$I_s = 10 \angle 0^\circ \text{ mA}$$

$$V = I_s \frac{1}{1/R + 1/j\omega L + j\omega C} = 10^{-2} \frac{1}{1/1000 - j0.005 + j0.005}$$

$$V = 10 \angle 0^\circ \text{ V}$$

$$I_R = \frac{V}{R} = 10 \angle 0^\circ \text{ mA}$$

$$I_L = \frac{V}{j\omega L} = 50 \angle -90^\circ \text{ mA}$$

$$I_C = V(j\omega C) = 50 \angle 90^\circ \text{ mA}$$

The peak value of $i_L(t)$ is five times larger than the source current! This is possible because current in the capacitance balances the current in the inductance.

⑧ p 5.42

$$V_1 = 100 \angle -90^\circ = -j100$$


$$V_2 = 100 \angle 30^\circ$$

$$I = \frac{V_1 - V_2}{R + j\omega L} = \frac{-j100 - (86.60 + j150)}{100 + j50}$$

$$I = \frac{-86.60 - j150}{100 + j50} = 1.549 \angle -146.6^\circ \text{ A}$$

$$V_R = 100 I = 154.9 \angle -146.6^\circ \text{ V}$$
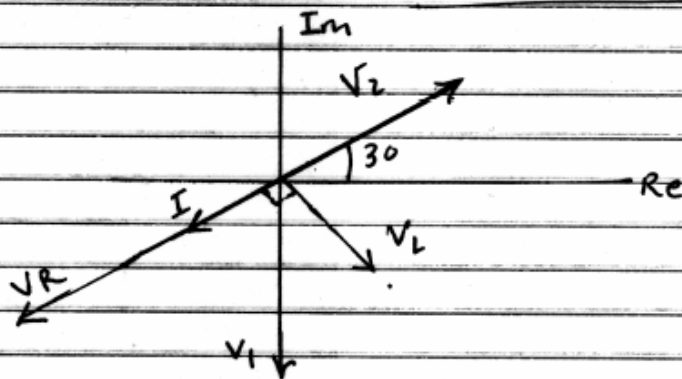
$$V_L = j50 I = 77.45 \angle -56.6^\circ$$



I lags V_1 by 56.6°

I lags V_L by 90.0°

② P.5.43

$$Z_{total} = j\omega L + \frac{1}{\frac{1}{R} + j\omega C}$$

$$= j100 + \frac{1}{0.01 + j0.01}$$

$$= \frac{j100 + 50 - j50}{1}$$

$$= 50 + j50 = 70.71 \angle 45^\circ$$


$$I = \frac{100 \angle 0^\circ}{Z_{total}} = 1.414 \angle -45^\circ$$

$$I_R = I \frac{Z_C}{R + Z_C} = (1.414 \angle -45^\circ) \times \frac{-j100}{100 - j100}$$

$$I_R = 1 \angle -90^\circ$$

$$I_C = I \frac{R}{R + Z_C} = (1.414 \angle -45^\circ) \times \frac{100}{100 - j100}$$

$$I_C = 1 \angle 0^\circ$$

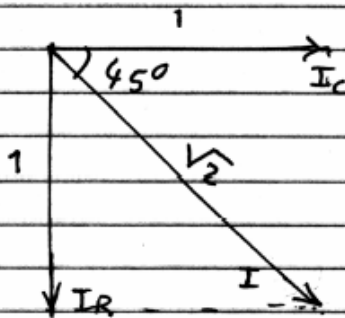

13

⑩ P. 5.44

writing KCL equations at nodes 1 and 2
we obtain

$$\frac{V_1}{10} + \frac{V_1 - V_2}{5 + j15} = 1 \angle 0^\circ$$

$$\frac{V_2}{-j10} + \frac{V_2 - V_1}{5 + j15} = 1 \angle 30^\circ$$

Solving these equations, we obtain

$$V_1 = 6.735 \angle -38.54^\circ$$

$$V_2 = 16.25 \angle -55.52^\circ$$