

## Announcements

- HW #2 due on Tuesday at 6pm in Cory.
- Midterm #1 on 7/12 12:00-1:30. Location TBD.

## Lecture #6


### OUTLINE

- Chap 5
  - Phasors
  - Complex Impedances

### Reading

Chap 5.1-5.4

## Complex Numbers

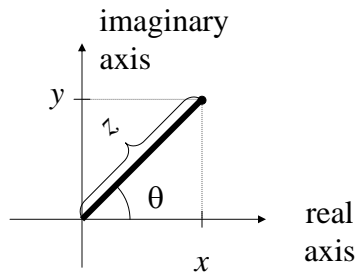

- $x$  is the real part
- $y$  is the imaginary part
- $z$  is the magnitude
- $\theta$  is the phase

## More Complex Numbers

- Polar Coordinates:  $\mathbf{A} = z \angle \theta$
- Rectangular Coordinates:  $\mathbf{A} = x + jy$

$$x = z \cos \theta$$

$$y = z \sin \theta$$

$$z = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1} \frac{y}{x}$$

## Summary of Phasors

- Phasor (frequency domain) is a complex number:

$$\mathbf{X} = z \angle \theta = x + jy$$

- Sinusoid is a time function:

$$x(t) = z \cos(\omega t + \theta)$$

## Examples

Find the time domain representations of

$$\mathbf{X} = -1 + j2$$

$$\mathbf{V} = 104V - j60V$$

$$\mathbf{A} = -1mA - j3mA$$

## Arithmetic With Complex Numbers

- To compute phasor voltages and currents, we need to be able to perform computation with complex numbers.
  - Addition
  - Subtraction
  - Multiplication
  - Division

## Addition


- Addition is most easily performed in rectangular coordinates:

$$\mathbf{A} = x + jy$$

$$\mathbf{B} = z + jw$$

$$\mathbf{A} + \mathbf{B} = (x + z) + j(y + w)$$

## Addition

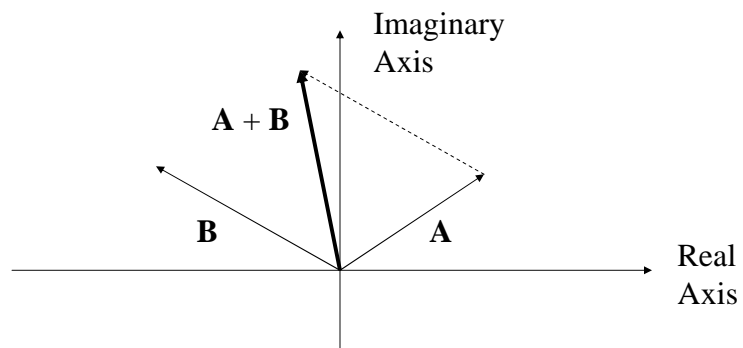

## Subtraction


- Subtraction is most easily performed in rectangular coordinates:

$$\mathbf{A} = x + jy$$

$$\mathbf{B} = z + jw$$

$$\mathbf{A} - \mathbf{B} = (x - z) + j(y - w)$$

## Subtraction

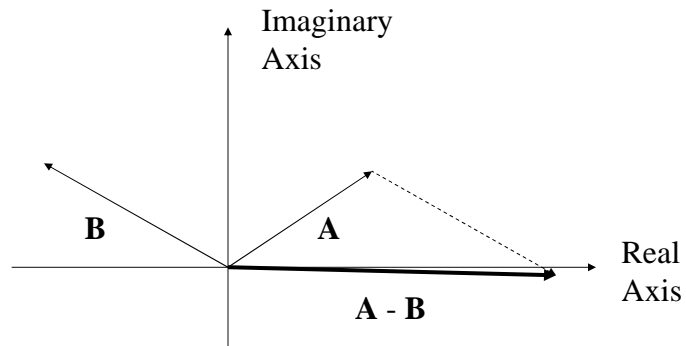

## Multiplication


- Multiplication is most easily performed in polar coordinates:

$$\mathbf{A} = A_M \angle \theta$$

$$\mathbf{B} = B_M \angle \phi$$

$$\mathbf{A} \times \mathbf{B} = (A_M \times B_M) \angle (\theta + \phi)$$

## Multiplication

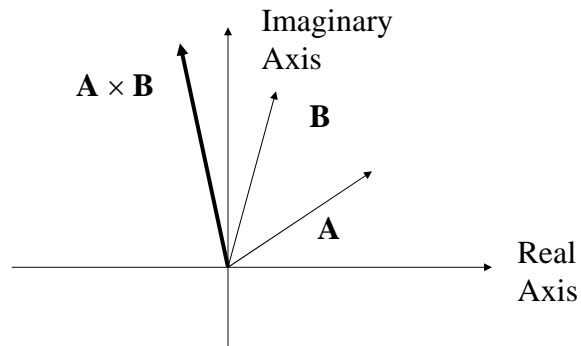

## Division


- Division is most easily performed in polar coordinates:

$$\mathbf{A} = A_M \angle \theta$$

$$\mathbf{B} = B_M \angle \phi$$

$$\mathbf{A} / \mathbf{B} = (A_M / B_M) \angle (\theta - \phi)$$

## Division

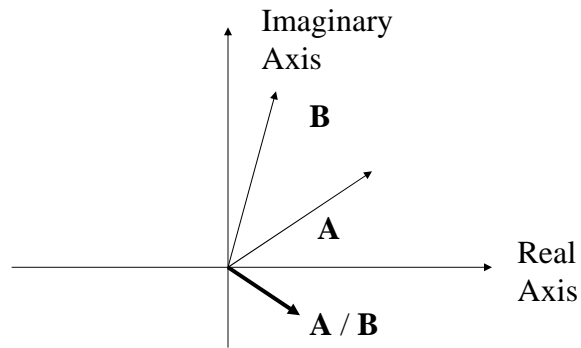

## Complex Exponentials

- We represent a real-valued sinusoid as the real part of a complex exponential.
- Complex exponentials provide the link between time functions and phasors.
- Complex exponentials make solving for AC steady state an algebraic problem.



## Complex Exponentials

- A complex number  $A = z \angle \theta$  can be represented as

$$A = z \angle \theta = z e^{j\theta} = z \cos \theta + j z \sin \theta$$

- A complex exponential is

$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$

- What do you get when you multiply  $A$  and  $e^{j\omega t}$  and find the real part?

## Complex Exponentials

$$A e^{j\omega t} = z e^{j\theta} e^{j\omega t} = z e^{j(\omega t + \theta)}$$

$$z e^{j(\omega t + \theta)} = z \cos (\omega t + \theta) + j z \sin (\omega t + \theta)$$

$$\text{Re}[A e^{j\omega t}] = z \cos (\omega t + \theta)$$

## Sinusoids, Complex Exponentials, and Phasors

- Sinusoid:

$$z \cos(\omega t + \theta)$$

- Complex exponential:

$$Ae^{j\omega t} = z e^{j(\omega t + \theta)}$$


- Phasor:

$$\mathbf{V} = z \angle \theta$$

## Phasor Relationships for Circuit Elements

- Phasors allow us to express current-voltage relationships for inductors and capacitors much like we express the current-voltage relationship for a resistor.
- A complex exponential is the mathematical tool needed to obtain this relationship.

## I-V Relationship for a Capacitor

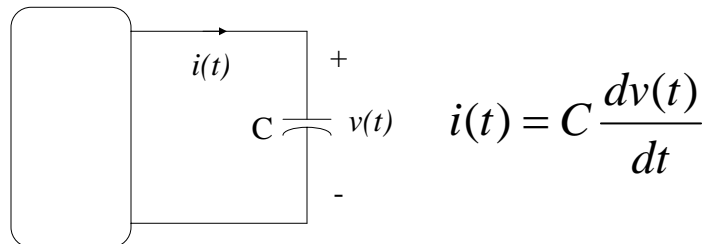

Suppose that  $v(t)$  is a sinusoid:

$$v(t) = V_M e^{j(\omega t + \theta)}$$

Find  $i(t)$ .

## Computing the Current

$$i(t) = C \frac{dv(t)}{dt} = C \frac{dV_M e^{j\omega t + j\theta}}{dt}$$

$$i(t) = j\omega C V_M e^{j\omega t + j\theta} = j\omega C v(t)$$

## Phasor Relationship

- Represent  $v(t)$  and  $i(t)$  as phasors:

$$\mathbf{V} = V_M \angle \theta$$

$$\mathbf{I} = j\omega C \mathbf{V}$$

- The derivative in the relationship between  $v(t)$  and  $i(t)$  becomes a multiplication by  $j\omega$  in the relationship between  $\mathbf{V}$  and  $\mathbf{I}$ .


## Example

$$v(t) = 120V \cos(377t + 30^\circ)$$

$$C = 2\mu\text{F}$$

- What is  $\mathbf{V}$ ?
- What is  $\mathbf{I}$ ?
- What is  $i(t)$ ?

## I-V Relationship for an Inductor

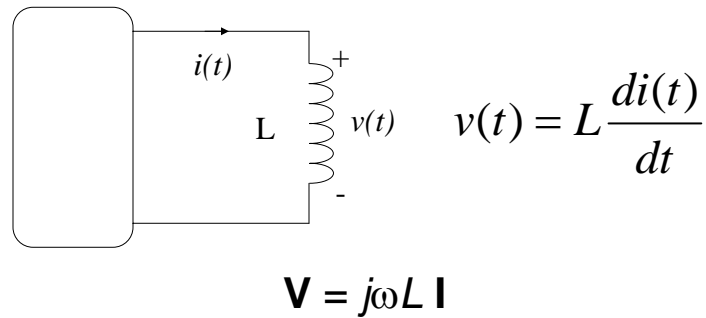

## Example

$$i(t) = 1\mu\text{A} \cos(2\pi 9.15 \cdot 10^7 t + 30^\circ)$$

$$L = 1\mu\text{H}$$

- What is  $\mathbf{I}$ ?
- What is  $\mathbf{V}$ ?
- What is  $v(t)$ ?

### Resistor I-V relationship

$v_R = i_R R$  .....  $\mathbf{V}_R = \mathbf{I}_R R$  where  $R$  is the resistance in ohms,  
 $\mathbf{V}_R$  = phasor voltage,  $\mathbf{I}_R$  = phasor current  
(boldface indicates complex quantity)

### Capacitor I-V relationship

$i_C = C dv_C/dt$  ..... Phasor current  $\mathbf{I}_C$  = phasor voltage  $\mathbf{V}_C /$   
capacitive impedance  $\mathbf{Z}_C \rightarrow \mathbf{I}_C = \mathbf{V}_C / \mathbf{Z}_C$   
where  $\mathbf{Z}_C = 1/j\omega C$ ,  $j = (-1)^{1/2}$  and boldface  
indicates complex quantity

### Inductor I-V relationship

$v_L = L di_L/dt$  ..... Phasor voltage  $\mathbf{V}_L$  = phasor current  $\mathbf{I}_L /$   
inductive impedance  $\mathbf{Z}_L \rightarrow \mathbf{V}_L = \mathbf{I}_L \mathbf{Z}_L$   
where  $\mathbf{Z}_L = j\omega L$ ,  $j = (-1)^{1/2}$  and boldface  
indicates complex quantity

## Phasor Diagrams

- A phasor diagram is just a graph of several phasors on the complex plane (using real and imaginary axes).
- A phasor diagram helps to visualize the relationships between currents and voltages.

## Impedance

- AC steady-state analysis using phasors allows us to express the relationship between current and voltage using a formula that looks like Ohm's law:


$$\mathbf{V} = \mathbf{I} \mathbf{Z}$$

- $\mathbf{Z}$  is called *impedance*.

## Some Thoughts on Impedance

- Impedance depends on the frequency  $\omega$ .
- Impedance is (often) a complex number.
- Impedance allows us to use the same solution techniques for AC steady state as we use for DC steady state.

## Example: Single Loop Circuit

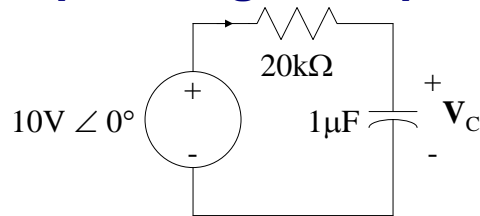

$$\omega = 377$$

Find  $V_C$


How do we find  $V_C$ ?

First compute impedances for resistor and capacitor:

$$Z_R = 20\text{k}\Omega = 20\text{k}\Omega \angle 0^\circ$$

$$Z_C = 1/j(377 \text{ } 1\mu\text{F}) = 2.65\text{k}\Omega \angle -90^\circ$$

## Impedance Example

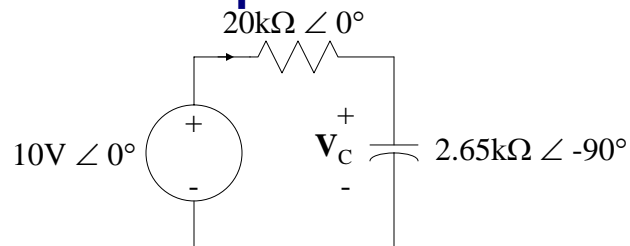


Now use the voltage divider to find  $V_C$ :

$$V_C = 10\text{V} \angle 0^\circ \left( \frac{2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right)$$

$$V_C = 1.31\text{V} \angle -82.4^\circ$$




## What happens when $\omega$ changes?

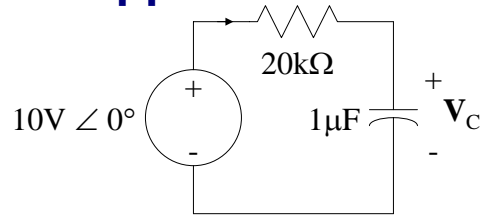


$\omega = 10$   
Find  $V_C$

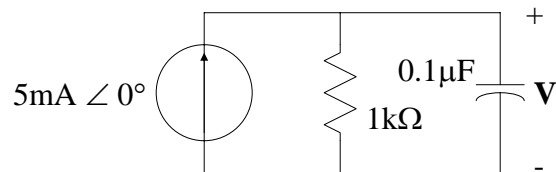
## Low Pass Filter: A Single Node-pair Circuit



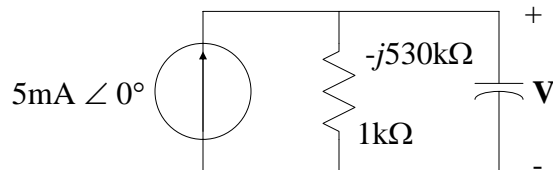Find  $v(t)$  for  $\omega = 2\pi \cdot 3000$



## Find the Equivalent Impedance

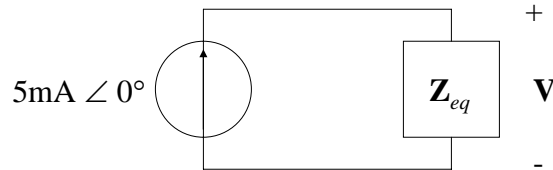

$$\mathbf{Z}_{eq} = \frac{1000(-j530)}{1000 - j530} = \frac{10^3 \angle 0^\circ \times 530 \angle -90^\circ}{1132 \angle -27.9^\circ}$$


$$\mathbf{Z}_{eq} = 468.2\Omega \angle -62.1^\circ$$

$$\mathbf{V} = \mathbf{I}\mathbf{Z}_{eq} = 5\text{mA} \angle 0^\circ \times 468.2\Omega \angle -62.1^\circ$$


$$\mathbf{V} = 2.34\text{V} \angle -62.1^\circ$$

$$v(t) = 2.34\text{V} \cos(2\pi 3000t - 62.1^\circ)$$


## Change the Frequency

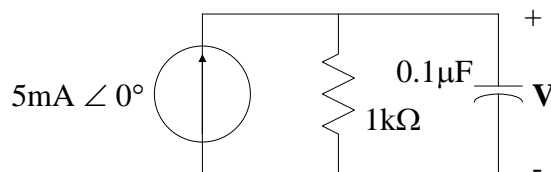

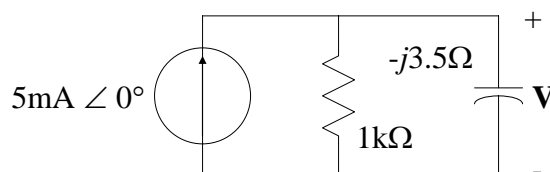Find  $v(t)$  for  $\omega = 2\pi 455000$



## Find an Equivalent Impedance

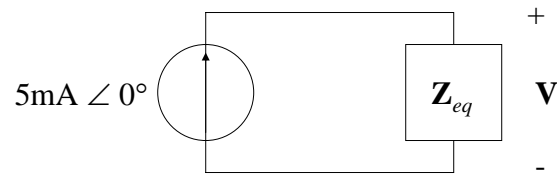

$$\mathbf{Z}_{eq} = \frac{1000(-j3.5)}{1000 - j3.5} = \frac{10^3 \angle 0^\circ \times 3.5 \angle -90^\circ}{1000 \angle -0.2^\circ}$$

$$\mathbf{Z}_{eq} = 3.5\Omega \angle -89.8^\circ$$

$$\mathbf{V} = \mathbf{I}\mathbf{Z}_{eq} = 5\text{mA} \angle 0^\circ \times 3.5\Omega \angle -89.8^\circ$$

$$\mathbf{V} = 17.5\text{mV} \angle -89.8^\circ$$

$$v(t) = 17.5\text{mV} \cos(2\pi 455000t - 89.8^\circ)$$