

Announcements

- Midterm #1
 - Tuesday July 12, 11:30 am – 1pm in 145 Dwinelle
 - Non-programmable calculators allowed
 - 1 double-sided cheat sheet allowed. Must be hand made
 - Material up to and including lecture 7

- Midterm Review Session
 - Monday July 11, 5 – 8pm in 277 Cory

- Attend only your second lab slot next week

Review

- Phasors
 - Source vs. Impedence representation

- First Order Circuits
 - Initial and Final conditions

- Second Order Circuits
 - Solution

Lecture #8

OUTLINE

- Decibels
- Transfer function
- First-order lowpass filter
- Cascade connection and Logarithmic frequency scales
- Bode Plots

Reading

- Chap 6-6.5

Bel and Decibel (dB)

- A **bel** (symbol **B**) is a unit of measure of ratios of power levels, i.e. relative power levels.
 - The name was coined in the early 20th century in honor of Alexander Graham Bell, a telecommunications pioneer.
 - The bel is a logarithmic measure. The number of bels for a given ratio of power levels is calculated by taking the logarithm, to the base 10, of the ratio.
 - one bel corresponds to a ratio of 10:1.
 - $B = \log_{10}(P_1/P_2)$ where P_1 and P_2 are power levels.
- The bel is too large for everyday use, so the **decibel (dB)**, equal to 0.1B, is more commonly used.
 - $1\text{dB} = 10 \log_{10}(P_1/P_2)$
- dB are used to measure
 - Electric power, Gain or loss of amplifiers, Insertion loss of filters.

Logarithmic Measure for Power

- To express a power in terms of decibels, one starts by choosing a reference power, $P_{\text{reference}}$, and writing

$$\text{Power } P \text{ in decibels} = 10 \log_{10}(P/P_{\text{reference}})$$

- Exercise:

- Express a power of 50 mW in decibels relative to 1 watt.
- $P \text{ (dB)} = 10 \log_{10}(50 \times 10^{-3}) = -13 \text{ dB}$

- Exercise:

- Express a power of 50 mW in decibels relative to 1 mW.
- $P \text{ (dB)} = 10 \log_{10}(50) = 17 \text{ dB}$.

- dBm to express **absolute** values of power relative to a milliwatt.

- $\text{dBm} = 10 \log_{10}(\text{power in milliwatts} / 1 \text{ milliwatt})$
- $100 \text{ mW} = 20 \text{ dBm}$
- $10 \text{ mW} = 10 \text{ dBm}$

Aside About Resonant Circuits

- When dealing with resonant circuits it is convenient to refer to the frequency difference between points at which the power from the circuit is half that at the peak of resonance.
- Such frequencies are known as “half-power frequencies”, and the power output there referred to the peak power (at the resonant frequency) is
- $10 \log_{10}(P_{\text{half-power}}/P_{\text{resonance}}) = 10 \log_{10}(1/2) = -3 \text{ dB}$.

Logarithmic Measures for Voltage or Current

From the expression for power ratios in decibels, we can readily derive the corresponding expressions for voltage or current ratios.

Suppose that the voltage V (or current I) appears across (or flows in) a resistor whose resistance is R . The corresponding power dissipated, P , is V^2/R (or I^2R). We can similarly relate the reference voltage or current to the reference power, as

$$P_{\text{reference}} = (V_{\text{reference}})^2/R \text{ or } P_{\text{reference}} = (I_{\text{reference}})^2R.$$

Hence,

$$\begin{aligned} \text{Voltage, } V \text{ in decibels} &= 20\log_{10}(V/V_{\text{reference}}) \\ \text{Current, } I, \text{ in decibels} &= 20\log_{10}(I/I_{\text{reference}}) \end{aligned}$$


Note that the voltage and current expressions are just like the power expression except that they have **20 as the multiplier instead of **10** because power is proportional to the square of the voltage or current.**

Exercise: How many decibels larger is the voltage of a 9-volt transistor battery than that of a 1.5-volt AA battery? Let $V_{\text{reference}} = 1.5$. The ratio in decibels is

$$20 \log_{10}(9/1.5) = 20 \log_{10}(6) = 16 \text{ dB.}$$

Transfer Function

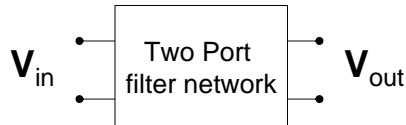- Transfer function is a function of frequency
 - Complex quantity
 - Both magnitude and phase are function of frequency




$$\mathbf{H}(f) = \frac{\mathbf{V}_{out}}{\mathbf{V}_{in}} = \frac{V_{out}}{V_{in}} \angle (\theta_{out} - \theta_{in})$$

$$\mathbf{H}(\mathbf{f}) = H(f) \angle \theta$$

Filters

- Circuit designed to retain a certain frequency range and discard others
 - Low-pass*: pass low frequencies and reject high frequencies
 - High-pass*: pass high frequencies and reject low frequencies
 - Band-pass*: pass some particular range of frequencies, reject other frequencies outside that band
 - Notch*: reject a range of frequencies and pass all other frequencies

Common Filter Transfer Function vs. Freq

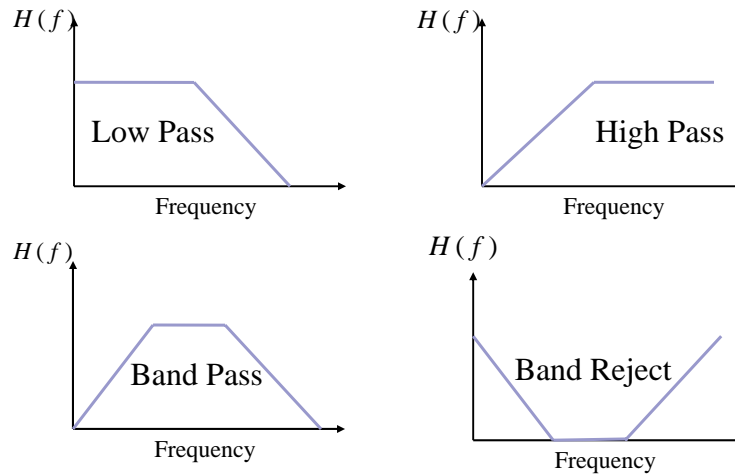

EE40 Summer 2005: Lecture 8

Instructor: Octavian Florescu

11

First-Order Lowpass Filter

$$\mathbf{H}(\mathbf{f}) = \frac{\mathbf{V}_C}{\mathbf{V}} = \frac{1/(j\omega C)}{1/(j\omega C) + R} = \frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1}(\omega RC)$$


$$\text{Let } \omega_B = \frac{1}{RC} \text{ and } f_B = \frac{1}{2\pi RC}$$

$$\mathbf{H}(\mathbf{f}) = H(f) \angle \theta$$

$$H(f) = \frac{1}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}, \theta = -\tan^{-1}\left(\frac{f}{f_B}\right)$$

$$H(f_B) = \frac{1}{\sqrt{2}} = 2^{-1/2}$$
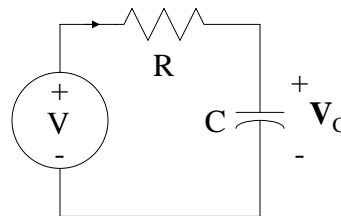
$$20 \log_{10} \frac{H(f_B)}{H(0)} = 20 \left(-\frac{1}{2}\right) \log_{10} 2 = -3 \text{ dB}$$



EE40 Summer 2005: Lecture 8

Instructor: Octavian Florescu

12


First-Order Highpass Filter

$$\mathbf{H}(f) = \frac{\mathbf{V}_R}{\mathbf{V}} = \frac{R}{1/(j\omega C) + R} = \frac{j\omega RC}{1 + j\omega RC} = \frac{(\omega RC)}{\sqrt{1 + (\omega RC)^2}} \angle \left[\frac{\pi}{2} - \tan^{-1}(\omega RC) \right]$$

$$H(f) = \frac{\left(\frac{f}{f_B}\right)}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}, \theta = \frac{\pi}{2} - \tan^{-1}\left(\frac{f}{f_B}\right)$$

$$H(f_B) = \frac{1}{\sqrt{2}} = 2^{-1/2}$$
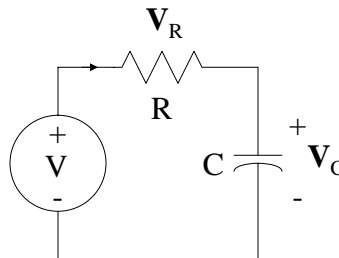
$$20 \log_{10} \frac{H(f_B)}{H(0)} = 20 \left(-\frac{1}{2}\right) \log_{10} 2 = -3 \text{ dB}$$




First-Order Lowpass Filter

$$\mathbf{H}(f) = \frac{\mathbf{V}_R}{\mathbf{V}} = \frac{1}{\frac{j\omega L}{R} + 1} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \angle -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

Let $\omega_B = \frac{R}{L}$ and $f_B = \frac{R}{2\pi L}$

$$\mathbf{H}(f) = H(f) \angle \theta$$
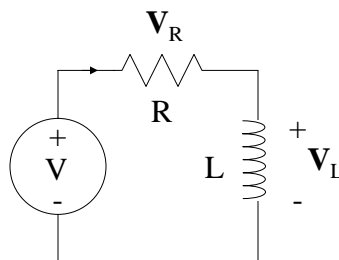
$$H(f) = \frac{1}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}, \theta = -\tan^{-1}\left(\frac{f}{f_B}\right)$$




First-Order Highpass Filter

$$\mathbf{H}(f) = \frac{\mathbf{V}_L}{\mathbf{V}} = \frac{\frac{j\omega L}{R}}{\frac{j\omega L}{R} + 1} = \frac{\frac{\omega L}{R}}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \angle \left[\frac{\pi}{2} - \tan^{-1}\left(\frac{\omega L}{R}\right) \right]$$


Let $\omega_B = \frac{R}{L}$ and $f_B = \frac{R}{2\pi L}$

$$\mathbf{H}(f) = H(f) \angle \theta$$
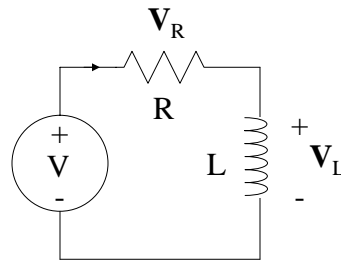
$$H(f) = \frac{\left(\frac{f}{f_B}\right)}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}, \theta = \frac{\pi}{2} - \tan^{-1}\left(\frac{f}{f_B}\right)$$




First-Order Filter Circuits

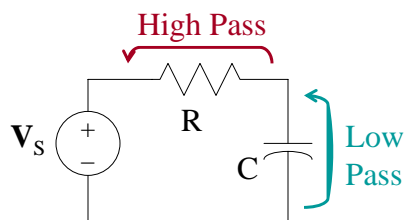

$$\mathbf{H}_R = R / (R + 1/j\omega C)$$
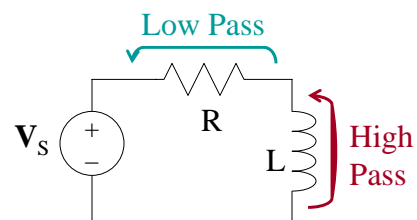
$$\mathbf{H}_C = (1/j\omega C) / (R + 1/j\omega C)$$



$$\mathbf{H}_R = R / (R + j\omega L)$$

$$\mathbf{H}_L = j\omega L / (R + j\omega L)$$

Gain or Loss Expressed in Decibels

The gain produced by an amplifier or the loss of a filter is often specified in decibels.

The input voltage (current, or power) is taken as the reference value of voltage (current, or power) in the decibel defining expression:

$$\begin{aligned}\text{Voltage gain in dB} &= 20 \log_{10}(V_{\text{output}}/V_{\text{input}}) \\ \text{Current gain in dB} &= 20 \log_{10}(I_{\text{output}}/I_{\text{input}}) \\ \text{Power gain in dB} &= 10 \log_{10}(P_{\text{output}}/P_{\text{input}})\end{aligned}$$

Example: The voltage gain of an amplifier whose input is 0.2 mV and whose output is 0.5 V is

$$20 \log_{10}(0.5/0.2 \times 10^{-3}) = 68 \text{ dB.}$$

Change of Voltage or Current with a Change of Frequency

One may wish to specify the change of a quantity such as the output voltage of a filter when the frequency changes by a factor of 2 (an octave) or 10 (a decade).

For example, a single-stage RC low-pass filter has at frequencies above $\omega = 1/RC$ an output that changes at the rate -20dB per decade.

Bode Plot


- Plot of magnitude of transfer function vs. frequency
 - Both x and y scale are in log scale
 - Y scale in dB
- Log Frequency Scale
 - Decade → Ratio of higher to lower frequency = 10
 - Octave → Ratio of higher to lower frequency = 2

High-frequency asymptote of Lowpass filter

The high frequency asymptote of magnitude Bode plot assumes -20dB/decade slope

As $f \rightarrow \infty$
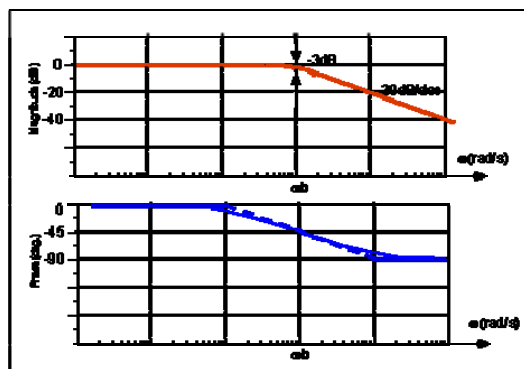
$$H(f) = \left(\frac{f}{f_B}\right)^{-1}$$
$$20 \log_{10} \frac{H(10f_B)}{H(f_B)} = -20dB$$



Low-frequency asymptote of Highpass filter


As $f \rightarrow 0$

$$H(f) = \frac{\left(\frac{f}{f_B}\right)}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}} \xrightarrow{f \rightarrow \infty} \left(\frac{f}{f_B}\right)$$

$$20 \log_{10} \frac{H(f_B)}{H(0.1f_B)} = 20 \text{dB}$$

The low frequency asymptote of magnitude Bode plot assumes 20dB/decade slope

Second-Order Filter Circuits

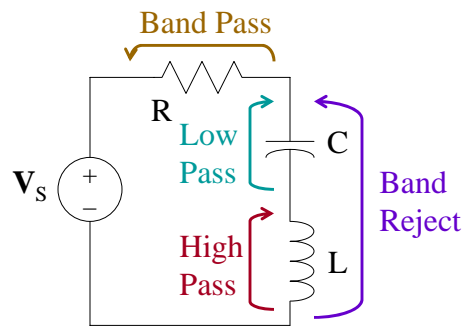

$$\mathbf{Z} = R + 1/j\omega C + j\omega L$$

$$\mathbf{H}_{BP} = R / \mathbf{Z}$$

$$\mathbf{H}_{LP} = (1/j\omega C) / \mathbf{Z}$$

$$\mathbf{H}_{HP} = j\omega L / \mathbf{Z}$$

$$\mathbf{H}_{BR} = \mathbf{H}_{LP} + \mathbf{H}_{HP}$$