

Lecture #11

OUTLINE


- The pn Junction Diode
- -- Uses: Rectification, parts of transistors, light-emitting diodes and lasers, solar cells, electrically variable capacitor (varactor diode), voltage reference (zener diode)
 - Depletion region & junction capacitance
 - I - V characteristic
 - Circuit applications and analysis

Reference Reading


- Hambley, Chapter 10.1 to 10.4
- Howe and Sodini, Chapter 2, Chapter 3.3-3.6

The pn Junction Diode

Schematic diagram

 


Circuit symbol

 


Physical structure: (an example)

 For simplicity, assume that the doping profile changes abruptly at the junction.



Depletion Region

 - When the junction is first formed, mobile carriers *diffuse* across the junction (due to the concentration gradients)
 - Holes diffuse from the **p side** to the n side, leaving behind **negatively charged immobile acceptor ions**
 - Electrons diffuse from the **n side** to the p side, leaving behind **positively charged immobile donor ions**





→ A region depleted of mobile carriers is formed at the junction.

- The space charge due to immobile ions in the depletion region establishes an electric field that opposes carrier diffusion.


Charge Density Distribution

  Charge is stored in the depletion region.




Doping

 
- Typical doping densities:
 $10^{16} \sim 10^{19} \text{ cm}^{-3}$
- Atomic density for Si: $5 \times 10^{22} \text{ atoms/cm}^3$
- 10^{18} cm^{-3} is 1 in 50,000
 - two persons in entire Berkeley wearing a green hat
- P-n junction effect is like



 Electric Field and Built-In Potential ϕ_0



electric field (V/cm)

 


No net current flows across the junction when the externally applied voltage is 0 V.


$$\phi_0 = \frac{kT}{q} \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

$$\frac{kT}{q} \ln(10) = 60 \text{ mV for } T = 300\text{K}$$

potential (V)

 

Effect of Applied Voltage

 

- The quasi-neutral p and n regions have low resistivity, whereas the depletion region has high resistivity. Thus, when an external voltage V_D is applied across the diode, almost all of this voltage is dropped across the depletion region. (Think of a voltage divider circuit.)
- If $V_D > 0$ (**forward bias**), the potential barrier to carrier diffusion is reduced by the applied voltage.
- If $V_D < 0$ (**reverse bias**), the potential barrier to carrier diffusion is increased by the applied voltage.


EE40 Summer 2005: Lecture 10

Instructor: Octavian Florescu


7

Forward Bias

 - As V_D increases, the potential barrier to carrier diffusion across the junction decreases*, and current increases exponentially.



 The carriers that diffuse across the junction become minority carriers in the quasi-neutral regions; they then recombine with majority carriers, "dying out" with distance.



* Hence, the width of the depletion region decreases.



EE40 Summer 2005: Lecture 10

Instructor: Octavian Florescu

8

Reverse Bias

- As $|V_D|$ increases, the potential barrier to carrier diffusion across the junction increases*; thus, no carriers diffuse across the junction.

  


* Hence, the width of the depletion region increases.

I-V Characteristic

Exponential diode equation: $I_D = I_S (e^{qV_D/kT} - 1)$
 
$$\frac{kT}{q} = 0.026 \text{ Volts for } T = 300\text{K}$$



I_S is the diode **saturation current**

- function of n_i^2 , A_D , N_A , N_D , length of quasi-neutral regions
- typical range of values: 10^{-14} to 10^{-17} A/ μm^2

Note that $e^{0.6/0.026} = 10^{10}$ and $e^{0.72/0.026} = 10^{12}$

$\rightarrow I_D$ is in the mA range for V_D in the range 0.6 to 0.7 V, typically.

Depletion Region Width W_j

- The width of the depletion region is a function of the bias voltage, and is dependent on N_A and N_D :


$$W_j = \sqrt{\frac{2\epsilon_{Si}}{q} \left(\frac{N_A + N_D}{N_A N_D} \right) (\phi_0 - V_D)}$$

- If one side is much more heavily doped than the other (which is commonly the case), then this can be simplified:

$$W_j \cong \sqrt{\frac{2\epsilon_{Si}}{qN} (\phi_0 - V_D)} \quad \epsilon_{Si} = 10^{-12} \text{ F/cm}$$

where N is the doping concentration on the more lightly doped side

Junction Capacitance

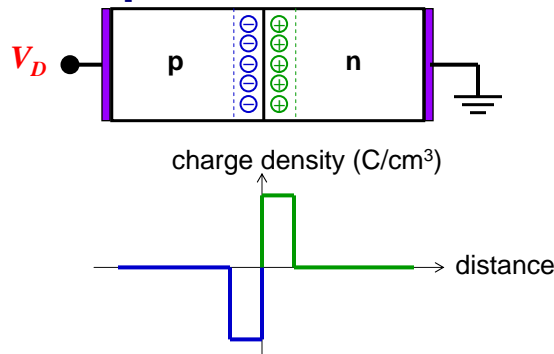

- The charge stored in the depletion region changes with applied voltage. This is modeled as junction capacitance


$$C_j = \frac{A_D \epsilon_{Si}}{W_j}$$

Summary: *pn*-Junction Diode Electrostatics

- A depletion region (in which n and p are each much smaller than the net dopant concentration) is formed at the junction between p- and n-type regions
 - A built-in potential barrier (voltage drop) exists across the depletion region, opposing carrier diffusion (due to a concentration gradient) across the junction:
$$\phi_0 = \frac{kT}{q} \ln \left(\frac{N_A N_D}{n_i^2} \right)$$
 - At equilibrium ($V_D=0$), no net current flows across the junction
 - Width of depletion region $W_j \cong \sqrt{\frac{2\epsilon_{Si}}{qN} (\phi_0 - V_D)}$
 - decreases with increasing forward bias (p-type region biased at higher potential than n-type region)
 - increases with increasing reverse bias (n-type region biased at higher potential than p-type region)
 - Charge stored in depletion region \rightarrow capacitance $C_j = \frac{A_D \epsilon_{Si}}{W_j}$


Summary: *pn*-Junction Diode *I-V*

- Under forward bias, the potential barrier is reduced, so that carriers flow (by diffusion) across the junction
 - Current increases exponentially with increasing forward bias
 - The carriers become minority carriers once they cross the junction; as they diffuse in the quasi-neutral regions, they recombine with majority carriers (supplied by the metal contacts)
 - “injection” of minority carriers
- Under reverse bias, the potential barrier is increased, so that negligible carriers flow across the junction
 - If a minority carrier enters the depletion region (by thermal generation or diffusion from the quasi-neutral regions), it will be swept across the junction by the built-in electric field
 - “collection” of minority carriers \rightarrow reverse current

 


pn-Junction Reverse Breakdown

 - As the reverse bias voltage increases, the peak electric field in the depletion region increases. When the electric field exceeds a critical value ($E_{crit} \cong 2 \times 10^5$ V/cm), the reverse current shows a dramatic increase:




Zener Diode

 A **Zener diode** is designed to operate in the breakdown mode.




Example:

 

Circuit Analysis with a Nonlinear Element

Since the pn junction is a nonlinear circuit element, its presence complicates circuit analysis.

 (Node and loop equations become transcendental.)




EE40 Summer 2005: Lecture 10

Instructor: Octavian Florescu

17

Load Line Analysis Method

1. Graph the I - V relationships for the non-linear element and for the rest of the circuit
2. The operating point of the circuit is found from the intersection of these two curves.

 

The I - V characteristic of all of the circuit except the non-linear element is called the load line


EE40 Summer 2005: Lecture 10

Instructor: Octavian Florescu


18

Ideal Diode Model of pn Diode


Circuit symbol

 

I-V characteristic

 


Switch model

 


- An ideal diode passes current only in one direction.
 - An **ideal diode** has the following properties:
 - when $I_D > 0$, $V_D = 0$
 - when $V_D < 0$, $I_D = 0$
- } Diode behaves like a switch:
- closed in forward bias mode
 - open in reverse bias mode

Large-Signal Diode Model


Circuit symbol

 

I-V characteristic

 

Switch model

 

For a Si pn diode, $V_{Don} \cong 0.7 \text{ V}$

- RULE 1: When $I_D > 0$, $V_D = V_{Don}$
- RULE 2: When $V_D < V_{Don}$, $I_D = 0$
- } Diode behaves like a voltage source in series with a switch:
- closed in forward bias mode
 - open in reverse bias mode

How to Analyze Circuits with Diodes


A diode has only two states:

- **forward biased:** $I_D > 0$, $V_D = 0$ V (or 0.7 V)
- **reverse biased:** $I_D = 0$, $V_D < 0$ V (or 0.7 V)

Procedure:

1. Guess the state(s) of the diode(s)
2. Check to see if KCL and KVL are obeyed.
3. If KCL and KVL are not obeyed, refine your guess
4. Repeat steps 1-3 until KCL and KVL are obeyed.


Example:

 


If $v_s(t) > 0$ V, diode is forward biased
(else KVL is disobeyed – try it)

If $v_s(t) < 0$ V, diode is reverse biased
(else KVL is disobeyed – try it)

 
Application Example #1 (ideal diode model)



“rectified” version of
input waveform:

 

 Application Example #2 (ideal diode model)



EE40 Summer 2005: Lecture 10

Instructor: Octavian Florescu


23

Diode Logic

- Diodes can be used to perform logic functions:


AND gate

 output voltage is high only if
both A and B are high



OR gate

 output voltage is high if
either (or both) A and B are high



Inputs **A** and **B** vary between 0 Volts ("low") and V_{CC} ("high")
Between what voltage levels does **C** vary?

EE40 Summer 2005: Lecture 10

Instructor: Octavian Florescu

24