

Announcements

- Midterm 2 this Thursday 11:30 to 1pm
 - 145 Dwinelle
 - Lectures 8-13, HW #4,5 (no small signal model)
 - Review Session this Wednesday 5-8pm in Cory 277

Lecture #14

OUTLINE

- Load Line and Small signal analyses of:
 - Common source amplifier
 - Source follower
 - Common gate amplifier


Reference Reading

- Hambley: Chapter 12.1-12.5

MOSFET Circuit

- First look at DC case to find Q point
 - Use load line technique
 - All capacitors are open circuit
 - From Q-point, get g_m and r_d for small signal AC model
- AC Small signal analysis
 - DC source is AC ground (because there is no AC signal variation).
 - All capacitors are short circuit (unless otherwise specified).

Common Source Amplifier

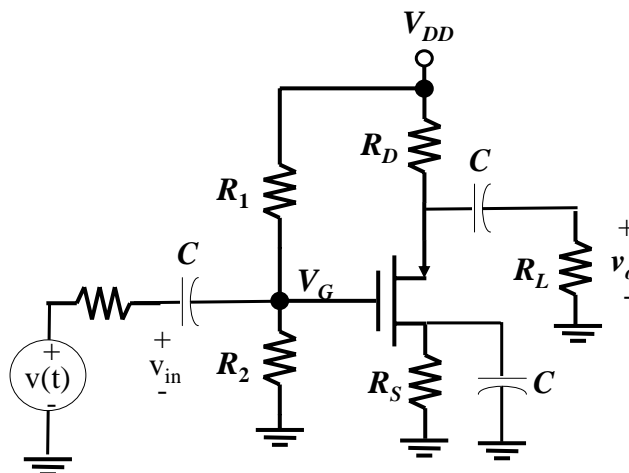


Step 1: find Q point

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{DD} = I_D (R_D + R_S) + V_{DS}$$

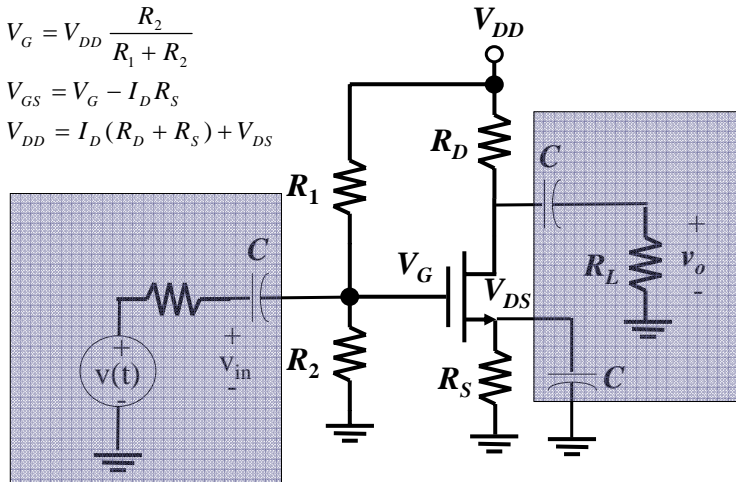

Load line:

From load lines, we get $I_D \rightarrow$ and hence g_m and r_d

Small Signal Model:

$$v_g = v_{in}, v_s = 0 \rightarrow v_{gs} = v_{in}$$

$$v_o = \frac{R_L R_D}{R_L + R_D} (-g_m v_{gs})$$

$$A_v = \frac{v_o}{v_{in}} = -g_m \frac{R_L R_D}{R_L + R_D}$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{R_1 R_2}{R_1 + R_2}$$

For output impedance R_{out} :


1. Turn off all independent sources.

2. Take away load impedance R_L

$$v_{in} = 0, v_{gs} = 0, g_m v_{gs} = 0$$

$$R_{out} = \frac{r_d R_D}{r_d + R_D}$$

Source Follower

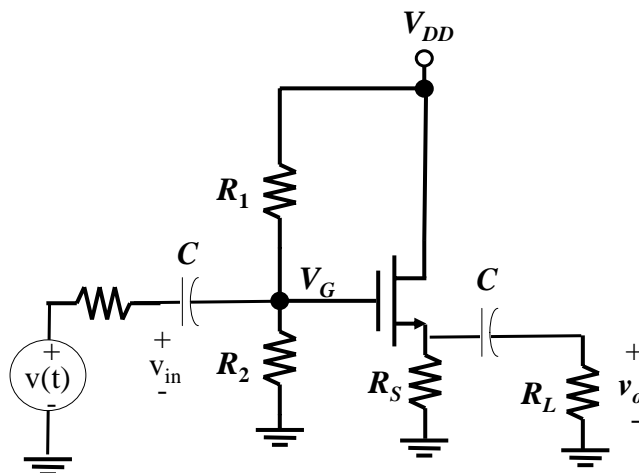


Step 1: find Q point

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{DD} = I_D R_S + V_{DS}$$

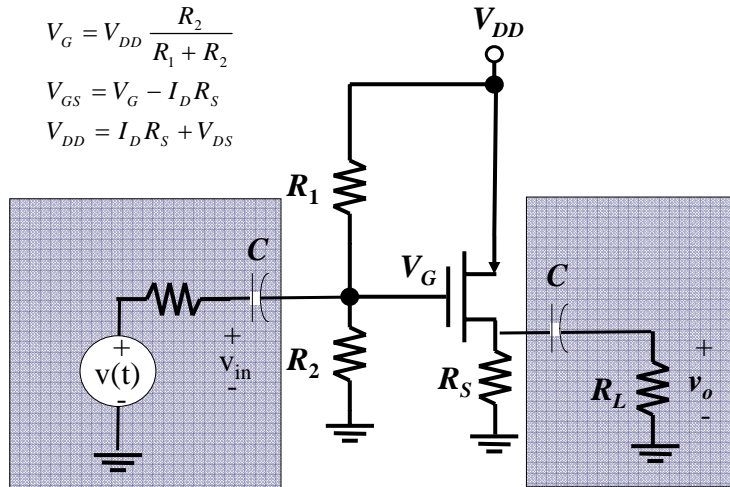

Load line:

From load lines, we get $I_D \rightarrow$ and hence g_m and r_d

Small Signal Model:

$$R_L' = \frac{1}{r_d^{-1} + R_S^{-1} + R_L^{-1}}$$

$$v_{gs} = v_{in} - v_o$$

$$v_o = g_m v_{gs} R_L'$$

$$v_{in} = v_{gs} (1 + g_m R_L')$$

$$A_v = \frac{v_o}{v_{in}} = \frac{g_m R_L'}{1 + g_m R_L'}$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{R_1 R_2}{R_1 + R_2}$$

For output impedance R_{out} :

1. Turn off all independent sources.

2. Take away R_L


3. Add V_x and find i_x

$$v_x = v_s, v_g = 0, v_{gs} = -v_x$$

$$R_s' = \frac{r_d R_s}{r_d + R_s}, i_x = \frac{v_x}{R_s'} - g_m (-v_x) = v_x (R_s'^{-1} + g_m)$$


$$R_{out} = \frac{1}{g_m + r_d^{-1} + R_s'^{-1}}$$

Common Gate Amplifier

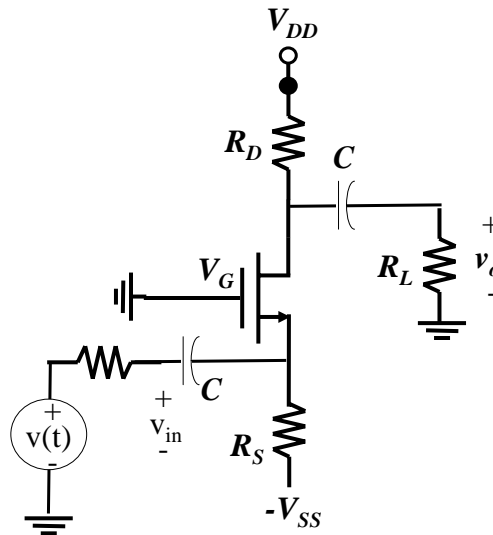

Step 1: find Q point
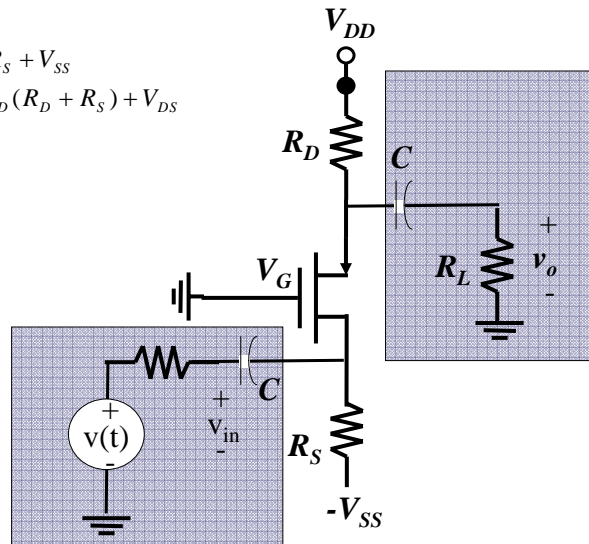
$$V_{GS} = 0 - I_D R_S + V_{SS}$$
$$V_{DD} + V_{SS} = I_D (R_D + R_S) + V_{DS}$$



Load line

The only difference in all three circuits are the intercepts at the axes.

Again from load lines, we get $I_D \rightarrow$ and hence g_m and r_d

Small Signal Model:

$$R_L' = \frac{1}{R_L^{-1} + R_D^{-1}}$$

$$v_{gs} = -v_{in}$$

$$v_o = -g_m v_{gs} R_L'$$

$$A_v = \frac{v_o}{v_{in}} = g_m R_L'$$

$$i_{in} = -(g_m v_{gs} + \frac{v_{gs}}{R_s})$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{1}{g_m + R_s^{-1}}$$

For output impedance R_{out} :

1. Turn off all independent sources.
2. Take away R_L
3. Add V_x and find i_x

$$R' = \frac{R R_s}{R + R_s}$$

$$i_x = \frac{v_x}{R_D} + g_m v_{gs} = v_x (R_s^{-1} + g_m)$$

$$v_{gs} = -g_m v_{gs} R', \text{ but } g_m R' \neq 1 \therefore v_{gs} = 0$$

$$R_{out} = R_D$$

Review on Bode Plots

- Transfer function = $H(f) = V_{out}/V_{in}$
- It is a complex number and typically a function of frequency.

$$\mathbf{H}(f) = \frac{\mathbf{V}_{out}}{\mathbf{V}_{in}} = \frac{V_{out}}{V_{in}} \angle (\theta_{out} - \theta_{in})$$

$$\mathbf{H}(f) = |\mathbf{H}(f)| \angle \theta(f)$$

$|\mathbf{H}(f)|$ is the magnitude

$\theta(f)$ is the phase

Both are functions of frequency f .

Review on Bode Plots

$$\mathbf{H}(f) = \mathbf{H}_1(f) \cdot \mathbf{H}_2(f)$$


$$|\mathbf{H}(f)| = |\mathbf{H}_1(f)| \cdot |\mathbf{H}_2(f)|$$

$$\theta(f) = \theta_1(f) + \theta_2(f)$$

$$Y = 20 \log |\mathbf{H}(f)| = 20 \log |\mathbf{H}_1(f)| + 20 \log |\mathbf{H}_2(f)|$$

- Bode plots include magnitude vs. plot and phase vs. frequency plots
 - Magnitude plots are log-log (dB vs. log Hz) \rightarrow Y vs. log f
 - Phase are linear-log (angle in degrees or radians vs. log frequency)
- Factor of 10 increase in frequency = 1 decade
- Factor of 2 increase in frequency = 1 octave
- If $H(f)$ can be factored into $H_1(f)$ and $H_2(f)$, it will be easier to plot bode plots for each and then sum them up.

Example: Second Order Circuit

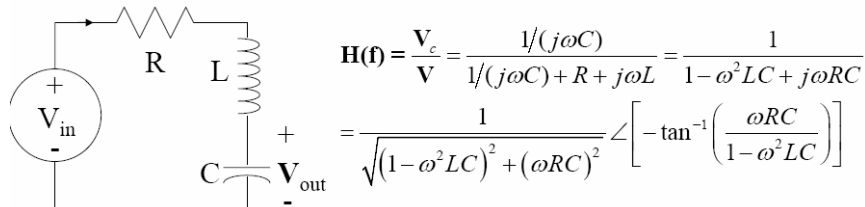

In plotting the magnitude Bode plot, we should evaluate the extreme cases: $\omega=0$ and infinity

In addition, we should examine $0+$ (small positive), and the frequency at which $|\mathbf{H}(f)|$ is maximum or minimum.

Examine $|\mathbf{H}(f)|$, we can easily see that max occurs at $\omega_0 = \left(\frac{1}{\sqrt{LC}}\right)$

$$\max |\mathbf{H}(f)| = \left(\frac{1}{\omega_0 RC}\right) = \frac{\sqrt{LC}}{RC}$$

Recall in Lec. 9 when we talked about 2nd order circuit, we had a resonance frequency, which is exactly $\omega_0 = \left(\frac{1}{\sqrt{LC}}\right)$

Magnitude Response

$$|\mathbf{H}(f)| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

$$\omega = 0, |\mathbf{H}(f)| = 1, Y = 20 \log(1) = 0 \text{ dB}$$

$0 < \omega < \omega_0, \omega^2 LC < 1$, as ω increases, $|\mathbf{H}(f)|$ decreases.

$$\text{At } \omega = \omega_0, 1 - \omega^2 LC = 0, |\mathbf{H}(f)| = \frac{\sqrt{L}}{R\sqrt{C}} = \frac{1}{2\zeta}$$

$$Y = 20 \log \frac{1}{2\zeta} = 20 \left[\log \frac{1}{2} + \log \frac{1}{\zeta} \right]$$

Recall, $\zeta = 1 \rightarrow$ critically damped, $Y(\omega_0) = -3 \text{ dB}$

$\zeta > 1 \rightarrow$ over damped, $Y(\omega_0) < -3 \text{ dB}$


$\zeta < 1 \rightarrow$ under damped, $Y(\omega_0) > -3 \text{ dB}$

$\zeta < 0.5 \rightarrow$ under damped, $Y(\omega_0) > 0 \text{ dB}$

For $\omega \gg \omega_0$, As ω increases, $|\mathbf{H}(f)| \sim \frac{\omega_0^2}{\omega^2}$

Y reduces by 40dB per 10x increase in ω , i.e.

slope in bode magnitude plot = -40dB/dec

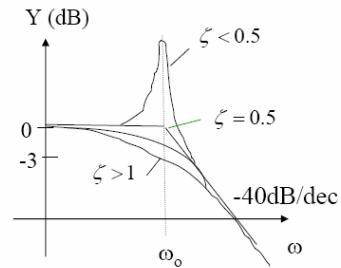

Phase Response

$$\omega = 0, |\mathbf{H}(f)| = 1, \theta = 0$$

$$\omega = 0+, |\mathbf{H}(f)| = 1, \theta = \text{negative small value}$$

As ω increases, θ becomes more negative.

$$\text{at } \omega = \omega_0, 1 - \omega^2 LC = 0, \theta = \frac{\pi}{2} \text{ or } -\frac{\pi}{2}$$

$$\text{at } \omega = \omega_0 - \delta, 1 - \omega^2 LC > 0, \theta \rightarrow -\frac{\pi}{2}$$

$$\text{at } \omega = \omega_0 + \delta, 1 - \omega^2 LC < 0, \theta \rightarrow \frac{\pi}{2}$$

For $\omega \gg \omega_0$, As ω increases, θ is positive but decreases.

as $\omega \rightarrow \infty, \theta \rightarrow 0^\circ$

