

$$\tilde{V}_L = \tilde{V}_s \left(\frac{500}{1000 + \frac{1}{j10^{-3}}} \right) = \tilde{V}_s \left(\frac{500}{1000(1-j)} \right) = 0.25(1+j)\tilde{V}_s$$

$$\tilde{I}_L = \boxed{2.5\sqrt{2}e^{j\pi/4}}$$

$$\tilde{I}_L = \frac{\tilde{V}_s}{1000(1-j)} = 0.005(1+j) = \boxed{5 \times 10^{-3}\sqrt{2}e^{j\pi/4}}$$

ii) $P(t) = V(t) I(t)$

$$= 2.5\sqrt{2} \cos(1000t + \pi/4) * 0.005\sqrt{2} \cos(1000t + \pi/4)$$

$$P(t) = 0.025 \cos^2(1000t + \pi/4)$$

iii) Method 1 RMS

$$V_{RMS} = \frac{2.5\sqrt{2}}{\sqrt{2}} = 2.5, I_{RMS} = \frac{0.005\sqrt{2}}{\sqrt{2}} = 0.005$$

$$P_{avg} = V_{RMS} I_{RMS} = 0.0125W = \boxed{12.5mW}$$

Method 2 Integration


$$P_{avg} = \frac{\int_0^T 0.025 \cos^2(1000t) dt}{T}, T = \frac{1}{1000}$$

$$= 25 \int_0^{\frac{1}{1000}} \frac{1}{2} + \frac{1}{2} \cos(2000t) dt$$

$$= 25 \int_0^{\frac{1}{1000}} \frac{1}{2} dt = 25 \left(\frac{1}{2} \times \frac{1}{1000} \right) = \boxed{12.5mW}$$

iv) $P_{avg} = \frac{1}{2} |V||I| \cos\theta, \theta = \frac{\pi}{4} - \frac{\pi}{4} = 0$
 $= \frac{1}{2} (2.5\sqrt{2})(5 \times 10^{-3}\sqrt{2}) = \boxed{12.5mW}$

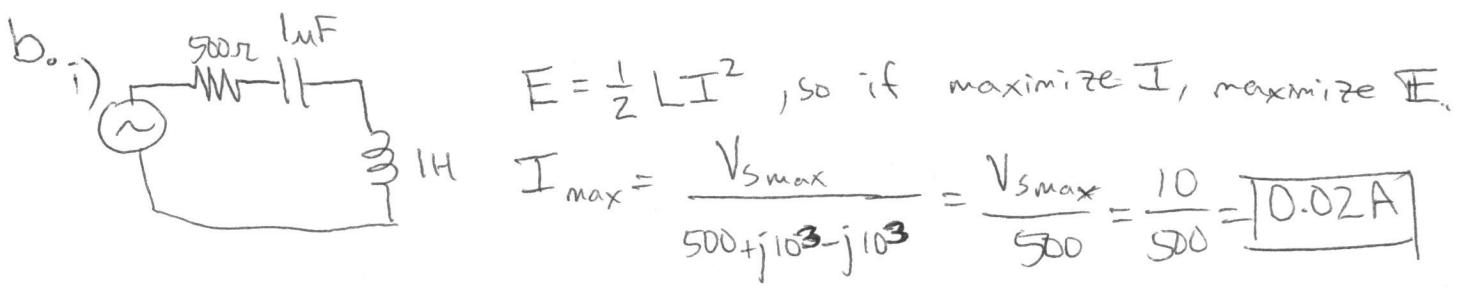v) $P_{avg} = \frac{1}{2} \operatorname{Re}(\tilde{V}\tilde{I}^*) = \frac{1}{2} \operatorname{Re}(2.5\sqrt{2}e^{j\pi/4} * 5 \times 10^{-3}\sqrt{2}e^{-j\pi/4})$
 $= \frac{1}{2} \operatorname{Re}(25 \times 10^{-3}) = \boxed{12.5mW}$



ii) $P_{\text{Avg}} = \frac{1}{2} |V| |I| \cos \theta$, $\theta = \frac{\pi}{2}$ across an inductor

$$= \frac{1}{2} |V| |I| \cos \frac{\pi}{2} = \boxed{0W}$$

iii) $P_{\text{reactive}} = \frac{1}{2} \text{Im}(VI^*) = \frac{1}{2} |\tilde{V}| |\tilde{I}|$

$$V = \tilde{V}_s \frac{j\omega L}{500} = j\tilde{V}_s \times 2 = \boxed{j20V}$$

$$I = \frac{V}{j\omega L} = \frac{j20}{j10^3} = \boxed{0.02A}$$

$$P_{\text{reactive}} = \frac{1}{2} \text{Im}(-j0.4) = \boxed{0.2W}$$

iv) $P_{\text{avg}} = \frac{1}{2} |V_R| |I| = \frac{1}{2} (10)(0.02) = \boxed{0.1W}$

$$V_R = IR = (0.02)(500) = 10V$$

C. To draw max average power, want to cancel (resonate out) reactive components and match resistive ones.

So, $Z_L = Z_s^* = (500 - 1000j)^* = 500 + 1000j$

$$P_{\text{Avg}} = \frac{1}{2} (5V)(0.01A) = \boxed{25mW}$$

d. To maximize power with a purely resistive load

want $|Z_s| = R_L$

$$|Z_s| = |500 - j1000| = \sqrt{500^2 + 1000^2} = \boxed{1118 \Omega}$$

$$P_L = \frac{1}{2} |I| |V|$$


$$\begin{aligned}\tilde{V} &= \tilde{V}_s \frac{1118}{1618 + j10^3} = \frac{\tilde{V}_s (1118)(1618 + j10^3)}{1618^2 + 10^6} \\ &= \tilde{V}_s \frac{1.8 \times 10^6 - j1.1 \times 10^6}{3.6 \times 10^6} = 10(0.5 - j0.3)\end{aligned}$$

$$|V| = \boxed{5.8V}$$

$$I = \frac{V}{1118} \Rightarrow |I| = \frac{|V|}{1118} \Rightarrow P_L = \frac{1}{2} \frac{|V|^2}{1118} = \boxed{15 \text{ mW}}$$

e. To maximize power delivered by a fixed voltage source need to minimize resistance (impedance), or maximize current. So, inductor from port b, that resonates out capacitor is the correct choice. (1H)

2. a.

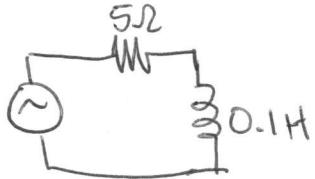

$$Z_L = j \times 377 \times 0.1 = j37.7$$

$$\tilde{V} = V_s = 110V$$

$$\tilde{I} = \frac{\tilde{V}}{Z} = \frac{110}{5 + j37.7} = \frac{550 - j4147}{1446.29} = 0.38 - j2.87$$

$$\tilde{I}^* = 0.38 + j2.87$$

$$\Rightarrow P_{\text{Avg}} = \frac{1}{2} \operatorname{Re}(110(0.38 + j2.87)) = \frac{1}{2} (110 \times 0.38) = 20.9W$$

$$P_{\text{Reactive}} = \frac{1}{2} \operatorname{Im}(110(0.38 + j2.87)) = \frac{1}{2} (110 \times 2.87) = 157.85W$$

b. $\tilde{I}^* = 100 \times (0.38 + j2.87) = [38 + j287]$

$$P_{\text{Avg}} = \frac{1}{2} \operatorname{Re}(110 \times (38 + j287)) = [2090W]$$

$$P_{\text{Reactive}} = \frac{1}{2} \operatorname{Im}(110 \times (38 + j287)) = [15785W]$$

c. i) Choose capacitance with.

$$Z_C = -j \frac{37.7}{100} = \frac{1}{j377 \times C}$$

$$C = \frac{100}{377 \times 37.7} = [7mF]$$


ii)

$$Z_{\text{motor}} = 5/100 \Omega$$

$$\tilde{I} = \frac{110}{5/100} = 2200A$$

$$\Rightarrow P_{\text{Avg}} = \frac{1}{2} \tilde{V} \tilde{I} = \frac{1}{2} \times 110 \times 2200 = [121kW]$$

3.a.

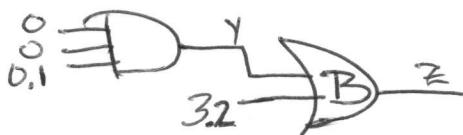

Y should output a "low" so, $0V \leq Y \leq 0.5V$

B has 1 input low, 1 input high so, Z should output a high, or $4.5V \leq Z \leq 5V$

b.



Y is unchanged, so $0 \leq Y \leq 0.5$

B has one input low, one input undefined, so the output of B is undefined, or

$$0V \leq Z \leq 5V$$

c.



A has three inputs high, so


$$4.5V \leq Y \leq 5V$$

If B has one high input and one low input, the output should be a high, so

$$4.5V \leq Z \leq 5V$$

4. If $A=0.9V$, $B=0.9V$, then $V_{O_1}=(-1)(0.9+0.9)=-1.8V$.

a.

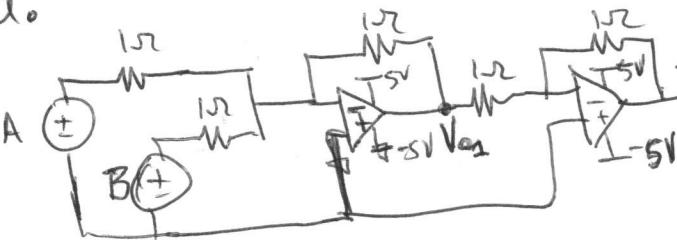

$$\text{Then, } Z = (-1)(-1.8) = 1.8V,$$

which is in the undefined region for our "static discipline",
~~which is~~

- b. Not Graded

5.

a.

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$\begin{aligned} Z &= \overline{A + \bar{A}B + BC} \\ &= \overline{A + B(\bar{A} + C)} \end{aligned}$$

b. The pull-up resistor gives us a path to V_{DD} so that if the PDN network is off, the output will be pulled high. If the resistor were made comparable to the on resistance of a transistor, then when one transistor is on, $V_{out} = V_{DD} \left(\frac{R_{on}}{R_{pull} + R_{on}} \right) \approx \frac{V_{DD}}{2}$ which is not a valid high or low output.

c.

A	B	C	Z
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$Z = \overline{ABC}$

This is NAND3 !

b. a. Does not meet static discipline if


$$V_o = 1 = 5 \left(\frac{R_{on} * N}{R_{on} + N + R} \right) = \frac{N}{5} R_{on} + \frac{R}{5} = R_{on} * N$$

$$\frac{R_{on}}{5} + \frac{R}{5} * \frac{1}{N} = R_{on}$$

$$\frac{4}{5} R_{on} = \frac{R}{5N} \quad \frac{R}{R_{on}} = N = \frac{100}{4} = N = \boxed{25}$$

b. If all inputs are on, then the resistance from Z to ground = $\frac{R_{on}}{n}$ so the current is maximized, and power is $\frac{V_{DD}^2}{R + \frac{R_{on}}{n}}$ which goes to $\frac{V_{DD}^2}{R}$ as $n \rightarrow \infty$.

$$7. Z = \overline{A + B + CD}$$

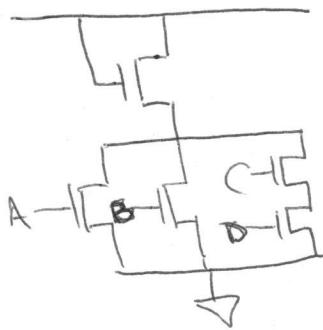

$$V_L = V_{DD} \left(\frac{R_{P, \text{on}, \text{largest}}}{R_{P, \text{on}} + R_{N, \text{on}, \text{largest}}} \right)$$


$$\frac{V_L}{V_{DD}} = \frac{R_{N, \text{on}}}{R_{P, \text{on}} + R_{N, \text{on}}}$$

$$\frac{V_L}{V_{DD}} = \frac{2 \frac{1}{W_{CN}}}{2 \frac{1}{W_{CN}} + \frac{1}{W_{N_{\text{diode-comm}}}}}$$


$$2 \frac{1}{W_{CN}} \left(1 - \frac{V_L}{V_{DD}} \right) = \frac{V_L}{V_{DD}} \frac{1}{W_{N_{\text{diode-comm}}}}$$

$$\frac{W_{N_{\text{diode-comm}}}}{W_{CN}} = \frac{V_L}{2V_{DD}} \left(\frac{1}{1 - \frac{V_L}{V_{DD}}} \right)$$

8. i. a. $A+B \Rightarrow$

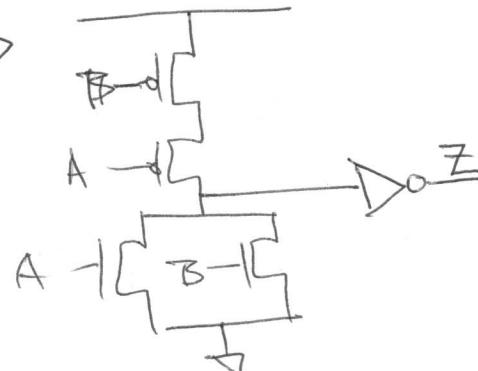


ii. $\overline{A+B}$

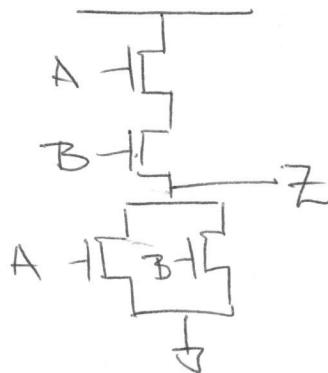


Typically for digital ckts, we set V_L to the minimum value always

Note:

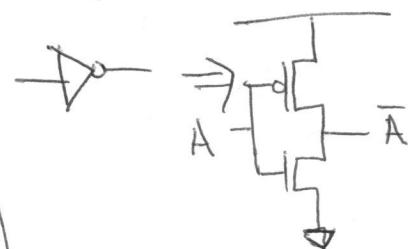


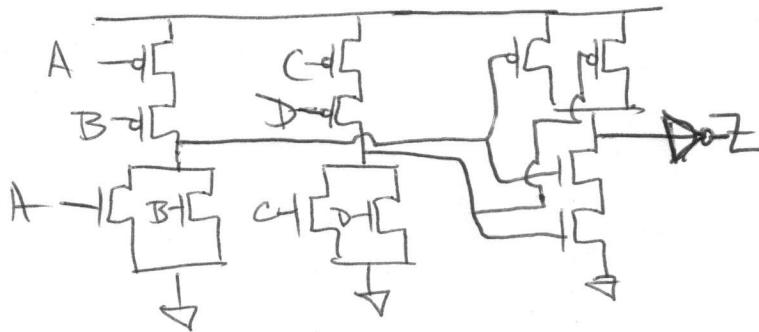iii. $(A+B)(C+D) \Rightarrow AC + AD + BC + BD \Rightarrow A(C+D) + B(C+D)$



iv. Same as iii, but no inverter. $(\overline{A+B})(C+D)$

v. $\overline{A+B} + CD$

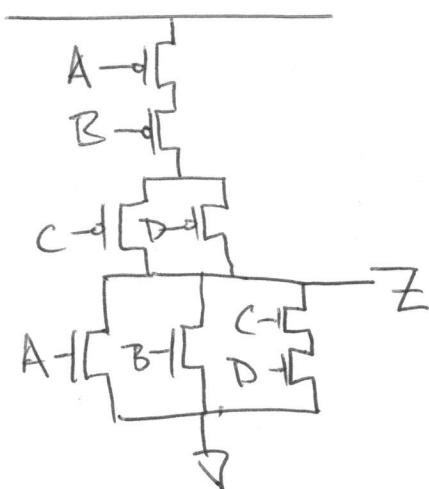

b. No, with static CMOS, in steady-state the output will always be either V_{DD} or GND, and this is not affected by the on resistance.

9.a. CMOS does not have static power dissipation (i.e. 0W)

b. As was shown in HW4, prob. 7, $E_{diss} = \frac{1}{2}CV_{DD}^2$
so, $E_{diss} = \frac{1}{2}(30 \times 10^{-9})(5)^2 = 375 \text{nJ}$

10. CMOS

Advantages

- No static power consumption
- Very narrow ~~forbidden~~ region (large noise margins)
- Output will always go to V_{DD} or GND

Disadvantages

- Possibly considered slower than NMOS (not part of this class)

NMOS only

Advantages

- Possibly faster than CMOS


Disadvantages

- Static power in low output
- possibly wide forbidden region
- output cannot reach GND

II. 9. First define rise and fall time.

t_{rise} is time for output beginning at 0V to reach V_H . t_{fall} is time from V_D to V_L .

Ckt for rise time

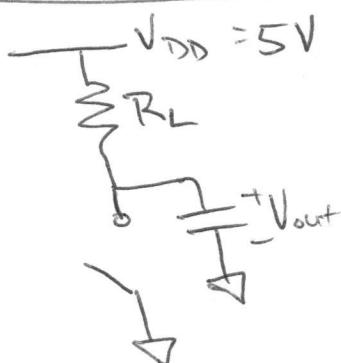

so, solve differential equation
(intuitive method)


$$V_{out}(t) = V_{DD} \left(1 - e^{-t/(R_L C_{GS})}\right)$$

When $V_{out} = 3V$ have reached t_{rise} .

$$3 = 5 \left(1 - e^{-t/10^{-5}}\right)$$

$$10^{-5} \ln \left(\frac{5}{3}\right) = t_{rise} = 5.1 \mu s$$

Ckt for fall time

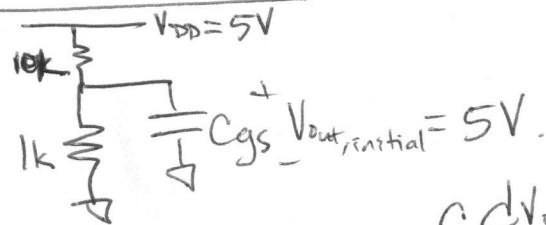

$$C \frac{dV_{out}}{dt} + \frac{V_{out}}{1k} = \frac{V_{DD} - V_{out}}{10k}$$

$$\frac{dV_{out}}{dt} = \frac{V_{DD}}{(C)10k} - \frac{1.0V_{out}}{(C)1k}$$

$$V_{out}(t) = \left(V_{DD} - V_{DD} \left(\frac{1}{11}\right)\right) e^{-t/(10^6 \cdot 1)} + V_{DD} \left(\frac{1}{11}\right)$$

$$1 = \left(5 - \frac{5}{11}\right) e^{-t/(10^6 \cdot 1)} + \frac{5}{11}$$

$$-\ln \left(\frac{\left(\frac{6}{11}\right)}{\left(\frac{50}{11}\right)}\right) = t \left(\frac{1.1}{10^6}\right)$$

$$t = 1.9 \mu s$$

(not
for a
grade)

iii. Propagation delay is usually defined as the amount of time for the output to reach $\frac{V_{DD}}{2}$ after the input reaches $\frac{V_{DD}}{2}$. We usually say NMOS/PMOS switch at $\frac{V_{DD}}{2}$ for a simplistic model.

This means we have two propagation delays t_{PHL} & t_{PLH}

output high to low output low to high

actually $\max\{t_{rise}, t_{fall}\}$

The books definition would say $t_p = t_{rise} = 15.1 \mu s$
 Most digital designers instead say
 $t_p = t_{5\%}$ s.t. $V_{out} = \frac{V_{DD}}{2}$ in a transition, so

$$t_{PHL} \Rightarrow 2.5 = \left(5 - \frac{5}{11}\right) e^{-t/(10^6)} + \frac{5}{11}$$

$$\Rightarrow \boxed{t_{PLH} = 0.02 \mu s} \quad \boxed{t_{PHL} = 0.7 \mu s}$$

$$t_{PLH} \Rightarrow 2.5 = 5(1 - e^{-t/10^5})$$

$$\ln(2)10^5 = \boxed{t_{PLH} = 6.93 \mu s}$$

These are all valid answers

12.

$$\frac{j\omega}{1+j\omega} = \frac{j\frac{\omega}{\omega_c}}{1+j\frac{\omega}{\omega_c}} \text{ with } \omega_c = 1 \frac{\text{rad}}{\text{sec}} \text{ SO, HPF.}$$

