
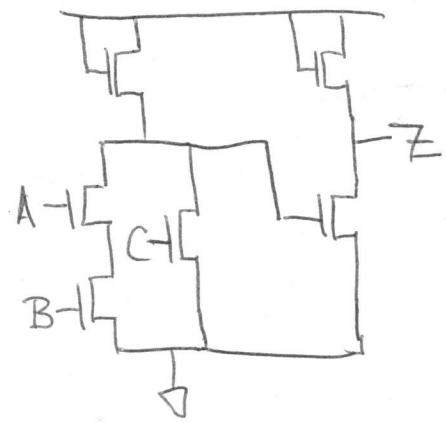


1. (3 pts)


a. $\overline{AB} + C$, NMOS only

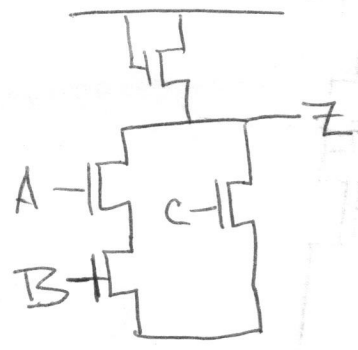


b. $\overline{AB} + C$, NMOS only



c. $\overline{AB} + C$ in CMOS

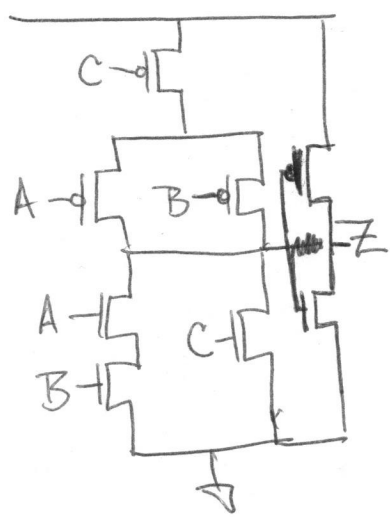

d. $\overline{AB} + C$ in CMOS

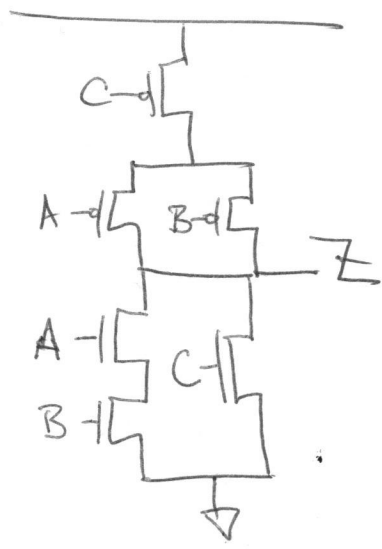

2. (3 pts)

a. Want path through $A \neq B$ to be used as compared to path through C because of higher resistance so longer RC, so longer fall times.

So, inputs that meet this requirement

	①	②
A	0 → 1	1
B	1	0 → 1
C	0	0

b. Use intuitive method

$$V_{out}(t) = 4.5 e^{-t/RC}$$

$$2.5 = 4.5 e^{-t/(2R_{on}C)}$$

$$\Rightarrow -\ln \frac{2.5}{4.5} = \frac{t}{2R_{on}C}$$

$$t_{fall} = -2R_{on}C \ln \left(\frac{2.5}{4.5} \right)$$

~~$$t_{fall} = 2R_{on}C \ln \left(1 + \frac{2.5}{4.5} \right)$$~~

c. Due to symmetry in the PMOS network, all low \rightarrow high transitions will give the same rise time. if both A & B PMOS are on

so,

	①	②	③
A	0	0	1 \rightarrow 0
B	0	1 \rightarrow 0	0
C	1 \rightarrow 0	0	0

d.

$$V_{out}(t) = 0.5 + 4.5(1 - e^{-t/RC})$$

$$2.5 = 0.5 + 4.5(1 - e^{-t/3/2 R_{on} C_L})$$

$$t_{rise} = -\frac{3}{2} R_{on} C_L \ln\left(1 - \frac{2}{4.5}\right)$$

3. a. (5 pts)

i)



Z is falling

Use intuitive method for RC decay from 3V

$$V_{cgs}(t) = 3e^{-t/1 \times 10^{-9}}, \quad 0 \leq t \leq 1 \text{ ns}$$

ii)

$$V_{cgs}(1 \text{ ns}) = 3e^{-1 \times 10^{-9} / 1 \times 10^{-9}} = 3e^{-1} = \boxed{1.104 \text{ V}}$$

iii)

$$1.5 = 3e^{-t/1 \times 10^{-9}} \Rightarrow t = (\ln(2))(1 \times 10^{-9}) = \boxed{0.69 \text{ ns}}$$


iv)

$$P(t) = I_R(t) V(t) = \frac{V(t)^2}{R} = \boxed{9 \times 10^{-3} e^{-2t \times 10^9} \text{ W}}$$

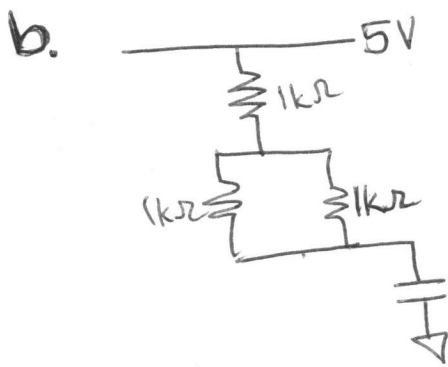v) If you believe $E_{cap} = \frac{1}{2} CV^2$, then $E_{diss} = E_{cap, initial} - E_{cap, final}$

$$E_{diss} = \frac{1}{2} C V_{initial}^2 - \frac{1}{2} C V_{final}^2 = \frac{1}{2} C (V_i^2 - V_f^2)$$

$$= \frac{1}{2} \times 10^{-12} (3^2 - 1.5^2) = \boxed{3.375 \text{ pJ}}$$



i) $V_{cgs}(1ns)$ will be the same as for part a since the voltage across a capacitor doesn't change instantaneously.

$$\boxed{V_{cgs}(1ns) = 1.104V}$$

ii)

$$\boxed{V_{cgs}(t) = 1.104 + (5 - 1.104)(1 - e^{-t/1.5 \times 10^{-9}})}, \quad 1 \times 10^{-9} < t < 2 \times 10^{-9}$$

iii) Question should have read "how high does V_{cgs} ..."

$$V_{cgs}(1 \times 10^{-9}) = 1.104 + (3.896)(1 - e^{-\frac{1}{1.5}}) = \boxed{3V}$$

iv) (Your answer should actually be shorter than 1ns!)

$$2.5 = 1.104 + 3.896(1 - e^{-t/1.5 \times 10^{-9}})$$

$$-\ln\left(1 - \frac{(2.5 - 1.104)}{3.896}\right) \times 1.5 \times 10^{-9} = \boxed{t = 0.665ns}$$

v)

$$P(t) = V_R(t) I_R(t) = \frac{V_R(t)^2}{R}$$

where $R = \frac{3}{2} R_{on} = 1.5k\Omega$

$$\boxed{P(t) = \frac{(V_s - V_{cgs}(t))^2}{1.5 \times 10^3}}$$

or at least no like is implied by the problem

vi) You actually don't need to integrate for this one either. To do this, you need to understand & trust the method of HW 4, prob. 7.

~~$$E = \int_0^t i_c(t) (V_{DD} - V_c(t)) dt$$~~

$$E = \int_0^t i_c(t) (V_{DD} - V_c(t)) dt$$

$$= \int_0^t (V_{DD} - V_c(t)) c \frac{dV_c(t)}{dt} dt = \int_{V_i}^{V_f} (cV_{DD} - cV_c(t)) dV_c(t) \Rightarrow \text{next pg.}$$

$$= C V_{DD} (V_f - V_i) - \frac{1}{2} C (V_f^2 - V_i^2)$$

$$= 10^{-12} \times 5 (3 - 1.104) - \frac{1}{2} \times 10^{-12} (3^2 - (1.104)^2)$$


I_n	t_{rise}	$E_{diss} = 5.6 \text{ pJ}$
I_n	t_{low}	$E_{diss} = 4.46 \text{ pJ}$

$$c. P_{avg} = \frac{E_{cycle}}{T} = \frac{(5.6 + 3.375) \times 10^{-12}}{2 \times 10^{-9}} = 4.49 \times 10^{-3} \text{ W}$$

d. No, since both energies will rise or fall with the squares of V_f, V_i .

$$e. C V_{DD}^2 f \quad (\text{or } C V_{DD}^2 \frac{1}{T})$$

4. (3 pts)

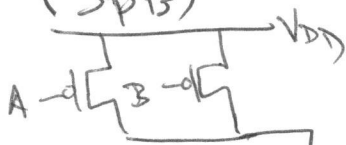

$$a. \tau_{dischg} = 2 R_{on} C_L = 5 \times 10^{-9}$$

$$R_{on} = \frac{5 \times 10^{-9}}{2 \times 10^{-12}} = \frac{5}{2} \times 10^3 = 2.5 \text{ k}\Omega$$


b. For N inputs,

$$\tau_{dischg} = N R_{on} C_L = 2.5 \times 10^{-9} N$$

c. For charging, worst case R is just R_{on} , so $\tau = 2.5 \times 10^{-9} \text{ s}$

$$\text{For best case, } R = \frac{R_{on}}{N} \Rightarrow \tau = \frac{2.5 \times 10^{-9}}{N}$$

5. (3pts)

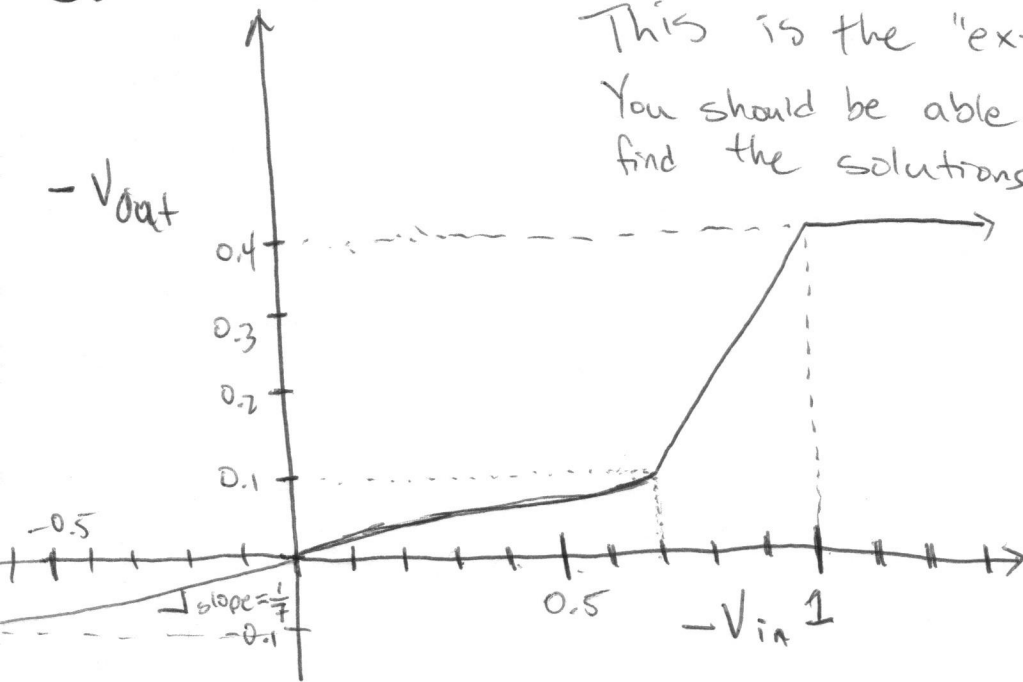


This is the "expert" solution.
You should be able to use this to find the solutions to the other solutions.

~~to a. ... with positive slope~~

6. (not graded) This is actually not a great model of a diode (or LED), but instead the leads and contact resistance of the diode.

7. (3pts)
7. a. i)

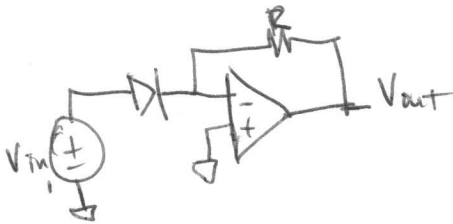

$$I_D = I_S e^{V_{in}/V_T}$$

$$V_{out} = -\frac{I_D}{R} = -\frac{I_S e^{V_{in}/V_T}}{R}$$

ii)




$$V_{out} = V_D = V_T \ln\left(\frac{I_D}{I_S}\right)$$

$$I_D = -\frac{V_{in}}{R}$$

$$V_{out} = V_T \ln\left(\frac{-V_{in}}{R I_S}\right)$$

b.

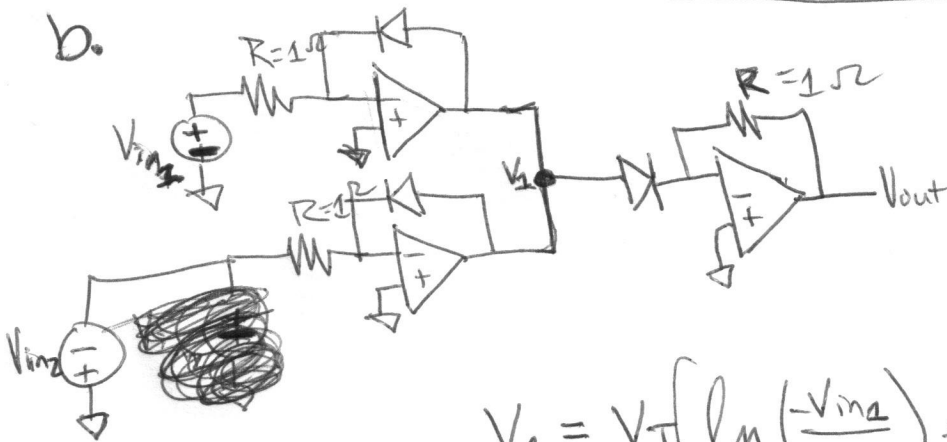

$$V_1 = V_T \left[\ln\left(\frac{-V_{in1}}{R I_S}\right) + \ln\left(\frac{+V_{in2}}{R I_S}\right) \right]$$

$$= V_T \ln\left(\frac{-V_{in1} * V_{in2}}{R I_S}\right)$$



$$V_{out} = -\frac{I_S}{R} e^{V_T \ln\left(\frac{-V_{in1} * V_{in2}}{R I_S}\right)}$$

$$= +\frac{I_S}{R} \left(\frac{+V_{in1} * V_{in2}}{R I_S}\right) = \boxed{V_{in1} * V_{in2}} = V_{out}$$

This ckt will function properly for negative values of V_{in1} , positive values of V_{in2} .

8. (3 pts)

a.

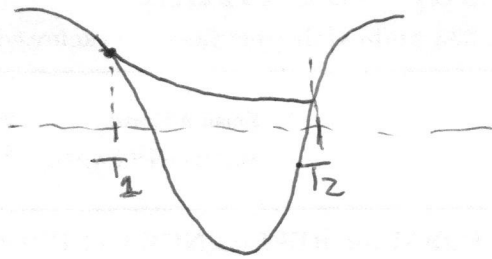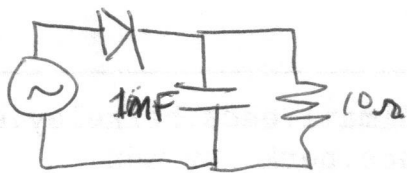

$$V_{out}(T_1) = 10 \cos(2\pi * 60 T_1) \approx 1$$

$$\text{at } T_2, V_{out}(T_1) e^{-t/RC} = \cos(2\pi * 60 (t - T_1))$$

$$\text{so, } e^{-t/RC} = \cos(2\pi * 60 t) * 10$$

~~$$t = RC \ln(\cos(2\pi * 60 t))$$~~

~~Use iteration and guess $t = \frac{1}{20}$~~

~~①~~

→ nonlinear, cannot be solved by algebraic manipulation, so instead use a calculator solver or iteration.

$$T_2 = 0.0132$$

$$V_{out}(T_2) = 10 * e^{-\frac{0.0132}{0.01}} = 2.67 \text{ V}$$

c. For V_{out} to drop no more than 0.1 V want

$$\text{that } V_{out}\left(\frac{1}{60}\right) \approx 9.9 = 10 e^{-\frac{1}{60 RC}}$$

$$\Rightarrow \ln 0.99 = \frac{1}{60 RC}$$

$$\Rightarrow C = \frac{1}{60 \ln(0.99) R} = 0.166 \text{ F}$$