

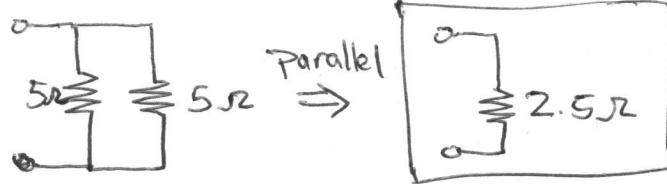


### Ex 2.1


a)

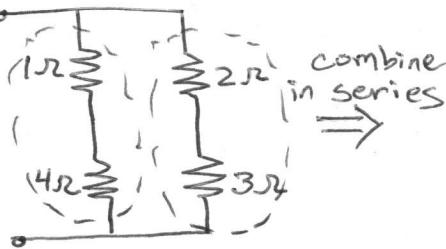


b)

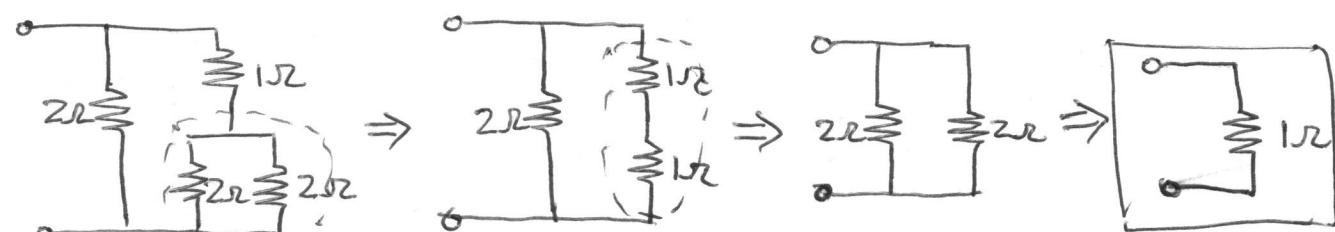


c)

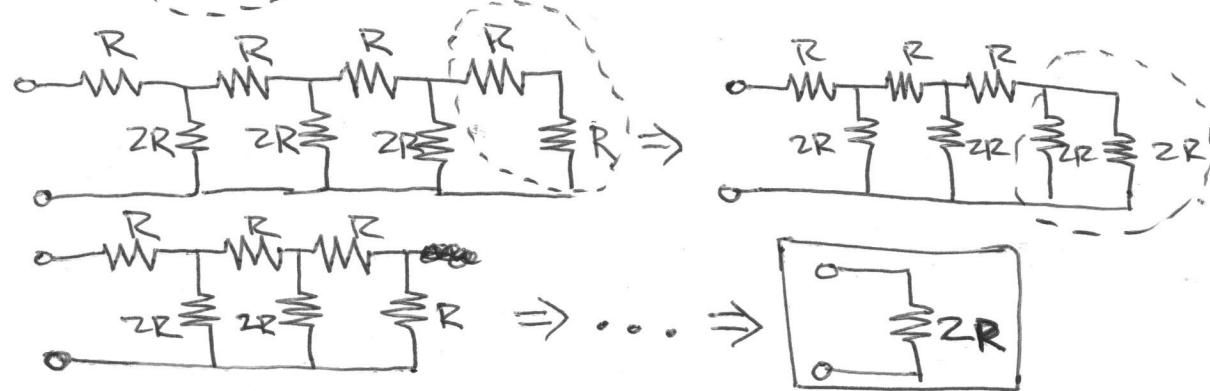

### Prob 2.2

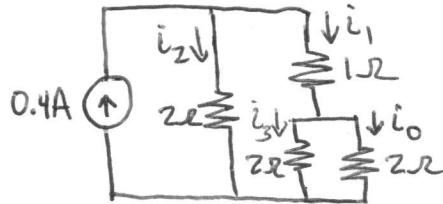

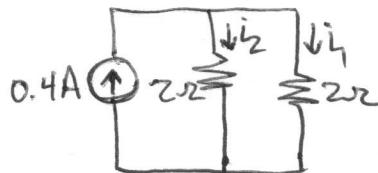
Since the two parallel resistors have the same value, and have the same voltage across them, they have the same current, so  $i_0 = i_3$ .  
By KCL  $i_1 = i_0 + i_3 = 2i_0$ .



Redrawing the circuit, we see  $i_1 = i_2$ , so  $i_1 = \frac{1}{2}(0.4\text{A})$

$$\Rightarrow i_0 = \frac{1}{2}i_1 = 0.1\text{A}$$

$$i_0 = 0.1\text{A}$$

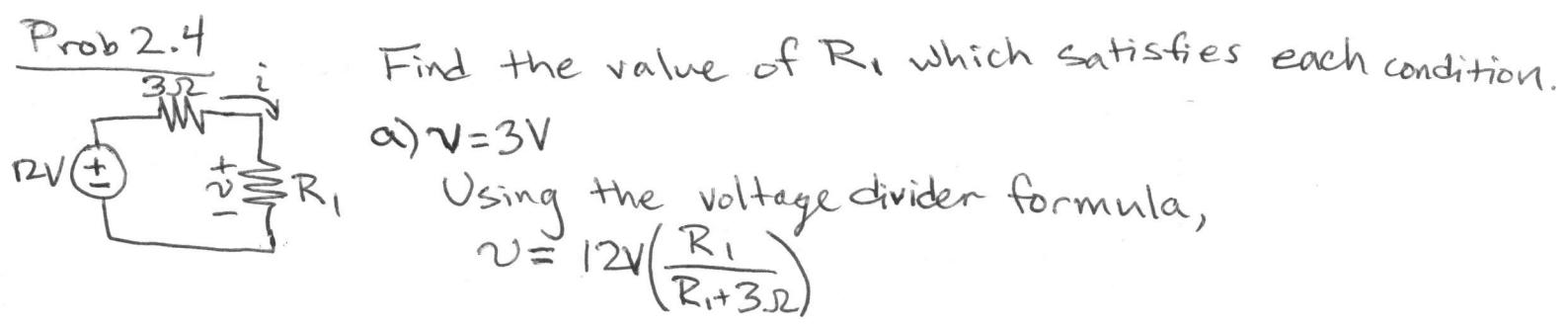

a)  $v = 3V$

Using the voltage divider formula,  
 $v = 12V \left( \frac{R_1}{R_1 + 3\Omega} \right)$

$$3V = \frac{12V R_1}{R_1 + 3\Omega}, \quad \boxed{\frac{9 + 3R_1}{R_1} = 12, \quad R_1 = 1\Omega}$$

b)  $v = 0V$

$$0 = \frac{12R_1}{R_1 + 3\Omega}, \quad 0(R_1 + 3\Omega) = 12R_1, \quad 12R_1 = 0, \quad \boxed{R_1 = 0\Omega}$$

c)  $i = 3A$

Adding the resistances in series and the applying Ohm's law we get:

$$i = \frac{12}{3 + R_1}, \quad 3 = \frac{12}{3 + R_1}, \quad 9 + 3R_1 = 12, \quad \boxed{R_1 = 1\Omega}$$

d)  $P_{R_1} = 12W$


$$P_{R_1} = i^2 R_1 \quad i = \frac{12}{3 + R_1} \quad v = 12 \frac{R_1}{R_1 + 3}, \quad i^2 R_1 = 144 \frac{R_1}{R_1^2 + 6R_1 + 9}$$

$$12 = 144 \frac{R_1}{R_1^2 + 6R_1 + 9}, \quad R_1^2 + 6R_1 + 9 = 12R_1, \quad R_1^2 - 6R_1 + 9 = 0$$

$$(R_1 - 3)^2 = 0 \Rightarrow \boxed{R_1 = 3\Omega}$$

Note: This is the maximum power that can be delivered to  $R_1$ . This fact will be explored at some point this semester.

### Prob 2.6

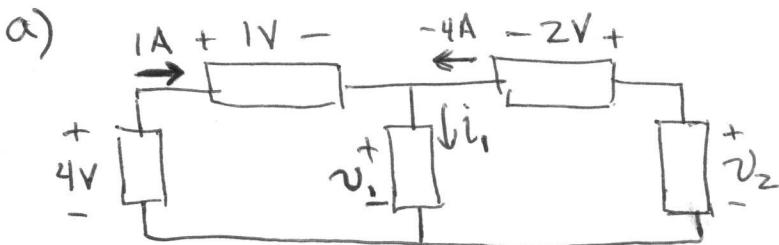

By KVL


$$4V - 1V - v_1 = 0V \Rightarrow \boxed{v_1 = 3V}$$

$$v_1 + (-2V) - v_2 = 0V \Rightarrow \boxed{v_2 = 1V}$$

By KCL

$$1A + (-4A) = i_1 \Rightarrow \boxed{i_1 = -3A}$$

b)

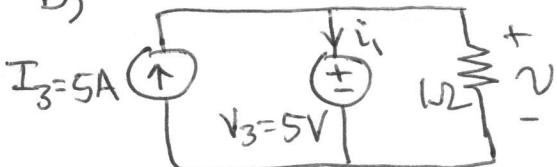

By KVL  $\boxed{V = 5V}$  (the voltage source is in parallel with the resistor, and elements in parallel have the same voltage across their terminals)

Applying Ohm's law to the resistor,  $i_R = \frac{5V}{1\Omega} = 5A$ , and by KCL,  $i_1 + i_R = I_3$ ,  $i_1 = 5A - 5A = \boxed{0A = i_1}$

Prob 2.10



$$V_o = V_i \left( \frac{R_4}{R_3 + R_4} \right) \quad V_1 = V_i \left( \frac{R_2}{R_1 + R_2} \right)$$


$$V_o = V_i \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_2}{R_1 + R_2} \right), \quad V_o = \frac{V_i}{1000}$$

$$1000R_2R_4 = R_1R_3 + R_2R_3 + R_2R_4 + R_1R_4$$

$$999R_2R_4 = R_1R_3 + R_2R_3 + R_1R_4, \text{ let } R_2 = R_3 = R_4 = 1\Omega.$$

Then  $999 = R_1 + 1 + R_1$ ,  $2R_1 = 998$ ,  $\boxed{R_1 = 499\Omega}$ . This problem is very unconstrained. There are ~~a large number of~~ a very large number of solutions and ways of going about this problem.

Prob 2.17

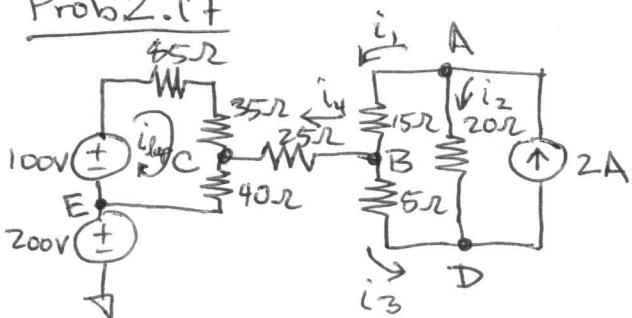

Using node voltage

at node A  
By KCL  $i_1 + i_2 = 2A$ .

Also, by KCL (at node D)

$$2A = i_2 + i_3 \Rightarrow i_1 = i_3.$$

Then applying KCL at node B

$$i_4 + i_3 = i_1 \Rightarrow i_4 = 0A.$$



Since no current is injected from  $i_4$ , the currents in all branches of the loop on the left are equal. By KVL,  
 $100V = i_{loop}(85 + 35 + 40) \Rightarrow i_{loop} = \frac{1}{1.6} A$ .

$$V_{C_{gnd}} = V_E_{gnd} + V_{CE}, \quad V_{E_{gnd}} = 200V \text{ (just a voltage source)}$$

$$V_{CE} = i_{loop}(40\Omega) = 25V$$


$$\text{so, } V_{C_{gnd}} = 200 + 25 = \boxed{225V}$$

### Ex 2.3 d

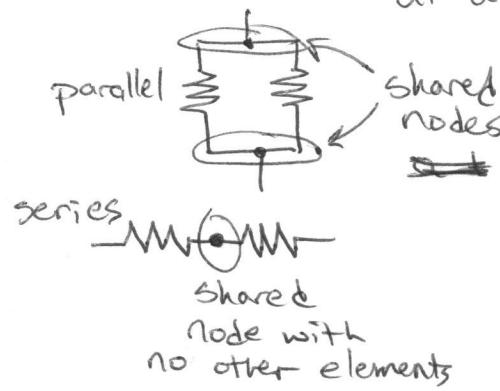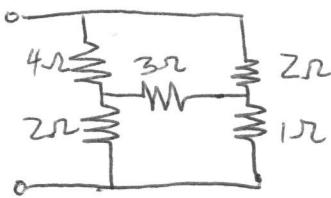

Series and parallel combinations cannot be used to solve this problem because none of the elements are in series/parallel. For two elements to be in parallel, both terminals of both devices must meet at a node (one node per pair of terminals), which does not apply for any of the elements. To be in series, two elements must meet at a node, and no other elements have a terminal at the shared node. Since no element in this network meets either definition, series and parallel combination techniques cannot be used to simplify this circuit.

### Ex 3.1

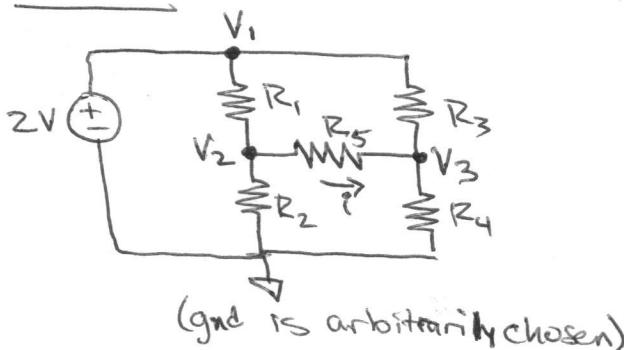

$$\frac{V_1 - V_2}{R_1} = \frac{V_2}{R_2} + \frac{V_3}{R_4} + \frac{V_3 - V_1}{R_3} \Rightarrow V_1 \left( \frac{1}{R_1} + \frac{1}{R_3} \right) = V_2 \left( \frac{1}{R_2} + \frac{1}{R_5} \right) + V_3 \left( \frac{1}{R_4} + \frac{1}{R_5} \right)$$

$$2 \cdot \frac{5}{6} = \frac{3}{4} V_2 + \frac{5}{6} V_3 \Rightarrow V_2 = \frac{45}{36} (2 - V_3)$$

$$= \frac{40}{18} - \frac{20}{18} V_3$$

Substituting into ② we have


$$\frac{V_1}{R_3} + \frac{40}{18} - \frac{20}{18} V_3 = V_3 \left( \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right)$$

$$\frac{52}{18} = V_3 \left( \frac{33+20}{18} \right) \Rightarrow V_3 = \frac{52}{53} V \quad \text{and} \quad V_2 = \boxed{\frac{10}{9} \left( 2 - \frac{52}{53} \right)}$$

$$I = \frac{V_2 - V_3}{R_5} = \frac{60 - 52}{53} = \boxed{\frac{8}{53} A}$$

$$V_2 = \boxed{\frac{60}{53} V}$$

Prob 3.3

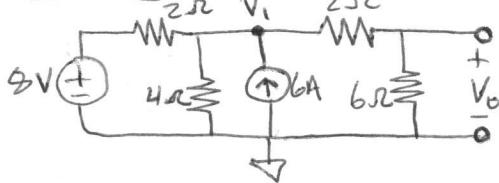

Node voltage eqns

$$\textcircled{1} \quad \frac{V_0}{6} = \frac{V_1 - V_0}{2} \Rightarrow \frac{2}{3}V_0 = \frac{V_1}{2} \Rightarrow V_0 = \frac{3V_1}{4}$$

$$\textcircled{2} \quad \frac{V_1 - V_0}{2} = 6 + \frac{8 - V_1}{2} - \frac{V_1}{4}$$

substituting  $\textcircled{1}$  into  $\textcircled{2}$


$$\frac{V_1}{2} - \frac{3}{8}V_1 = 6 + 4 - \frac{V_1}{2} - \frac{V_1}{4}$$

$$\frac{1}{8}V_1 + \frac{3}{4}V_1 = 10$$

$$\frac{7}{8}V_1 = 10 \Rightarrow V_1 = \frac{80}{7}V \Rightarrow V_0 = \frac{60}{7}V \approx 8.57V$$

Extra Problems

Ex 2.3d

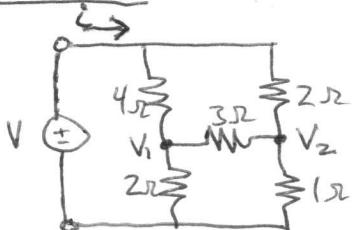

Using the hint given and applying a test voltage  $V$  across the terminals

$$i = \frac{V - V_1}{4\Omega} + \frac{V - V_2}{2\Omega} = \frac{V_1}{2\Omega} + \frac{V_2}{1\Omega}$$

$$3V = 3V_1 + 6V_2, \quad V = V_1 + 2V_2$$


then applying node voltage at  $V_2$ ,

$$\frac{V - V_2}{2\Omega} + \frac{V_1 - V_2}{3\Omega} = \frac{V_2}{1\Omega}$$

$$3V + 2V_1 = 11V_2$$

$$5V = 15V_2 \Rightarrow V_2 = \frac{V}{3}$$

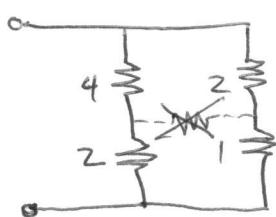
substituting back  
 $= V_1 = V - \frac{2V}{3} = \frac{V}{3}$



This means no current flows through the 3Ω resistor.




### Prob 2.3

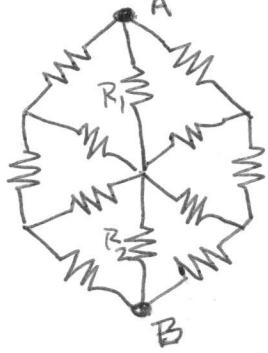

By symmetry and KCL, if a voltage is applied from A to B or B to A, current flow should be the same up to sign. This means the same current will flow in  $R_1$  and  $R_2$ . Also, the two side branches are symmetric so no current flows between them. Hence the problem can be solved as three parallel branches.


① & ③

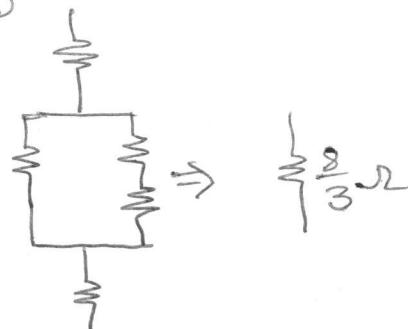

②



combining we have

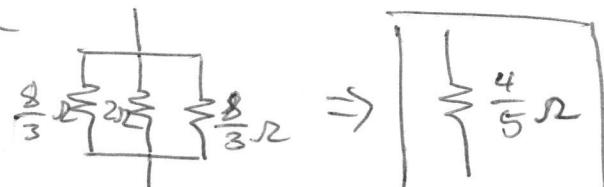

Prob 2.10 I believe the solution given earlier is the simplest

### Prob 3.1

$$R = 1 + \alpha T$$

Start with  $T = \beta P$

$$P = I_o^2 R$$

$$\text{So, } T = \beta I_o^2 R = \beta I_o^2 (1 + \alpha T)$$

$$T(1 - \alpha \beta I_o^2) = \beta I_o^2$$

$$T = \frac{\beta I_o^2}{1 - \alpha \beta I_o^2}$$

solving for when  $1 - \alpha \beta I_o^2 = 0$

$$I_o = \sqrt{\frac{1}{\alpha \beta}} = \sqrt{225} = 15 \text{ A}$$