

Have negative fb, so $V^- = V^+ = 0$


$$i_{in} = \frac{0 - V_1}{R_1}, V_1 = -\frac{i_{in}}{R_1} R_1$$

$$i_1 = \frac{V_1}{R_2}, V_1 = \frac{i_1}{R_2} R_2 \Rightarrow -\frac{i_{in} R_1}{R_2} = i_1$$

$$i_o = -i_{in} + i_1$$

$$i_o = -i_{in} \left(1 + \frac{R_1}{R_2}\right)$$

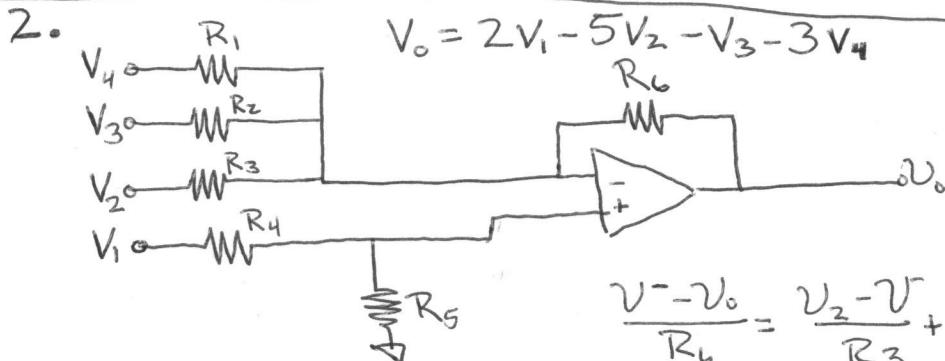This is a current amplifier. The current through R_L (i_o) is independent of the value of R_L .



$$V^+ = V_1 \left(\frac{R_5}{R_4 + R_5} \right) = V^-$$

↑
summing pt.

$$\frac{V^- - V_o}{R_6} = \frac{V_2 - V^+}{R_3} + \frac{V_3 - V^-}{R_2} + \frac{V_4 - V^-}{R_1}$$

$$V_1 \left(\frac{R_5}{R_4 + R_5} \right) - V_o = \frac{V_2}{R_3} - V_1 \frac{R_5}{R_3} \left(\frac{1}{R_4 + R_5} \right) + \frac{V_3}{R_2} - V_1 \frac{R_5}{R_2} \left(\frac{1}{R_4 + R_5} \right) + \frac{V_4}{R_1} - V_1 \frac{R_5}{R_1} \left(\frac{1}{R_4 + R_5} \right)$$

$$V_o = V_1 \left(\frac{R_5}{R_4 + R_5} \right) \left(1 + \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_1} \right) R_6 - V_2 \frac{R_6}{R_3} - V_3 \frac{R_6}{R_2} - V_4 \frac{R_6}{R_1}$$

Let $R_6 = 100\Omega$
 ~~$R_5 = 100\Omega$~~
 ~~$R_4 = 100\Omega$~~

$$V_o = V_1 \left(1 + \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_1} \right) (100) - V_2 \left(\frac{100}{R_3} \right) - V_3 \left(\frac{100}{R_2} \right) - V_4 \left(\frac{100}{R_1} \right)$$


so, $\frac{100}{R_3} = 5, \frac{100}{R_2} = 1, \frac{100}{R_1} = +3$

$$R_3 = 20\Omega, R_2 = 100\Omega, R_1 = 33\Omega$$

$$Z = \left(1 + \frac{1}{20} + \frac{1}{100} + \frac{1}{33} \right) (100) \left(\frac{R_5}{R_4 + R_5} \right)$$

$$Z = (100 + 5 + 1 + 3) \left(\frac{R_5}{R_4 + R_5} \right)$$
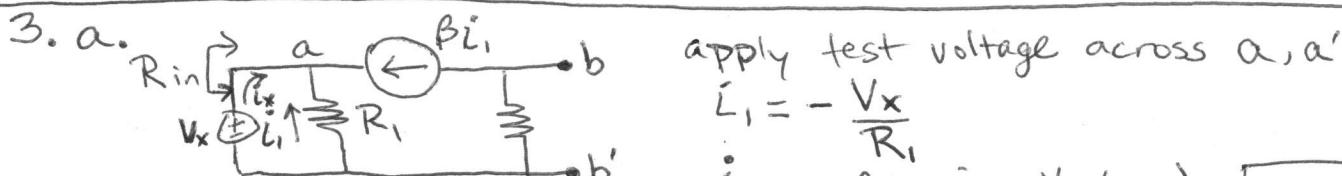
$$\frac{2}{109} = \frac{R_5}{R_4 + R_5} \quad \text{so, } R_5 = 2 \quad R_4 = 107\Omega$$




apply test voltage across a, a'


$$i_1 = -\frac{V_x}{R_1}$$

$$i_x = -\beta i_1 - i_1 = \frac{V_x}{R_1} (1 + \beta) \Rightarrow R_{in} = \frac{R_1}{1 + \beta}$$

b.

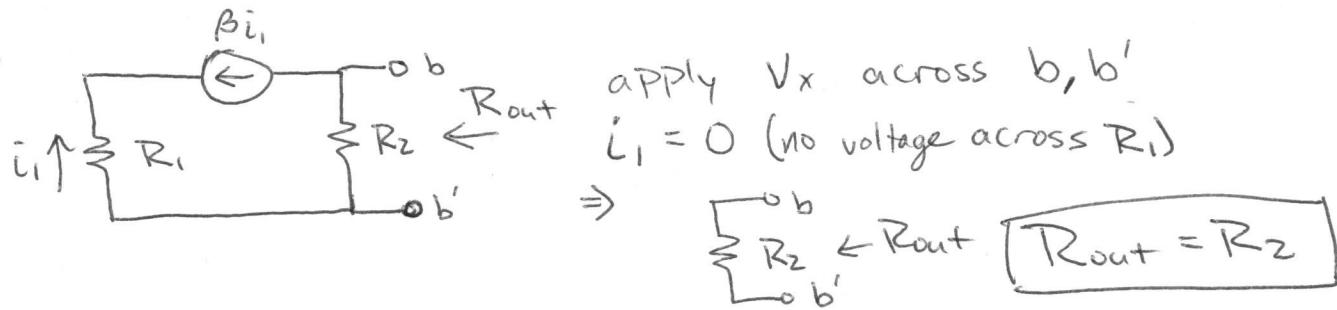

4.

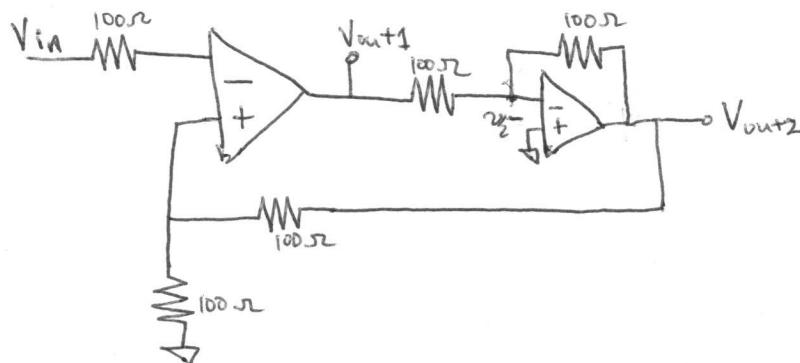

a. $V_{out2} = -A(V_2^-) \Rightarrow V_2^- = -\frac{V_{out2}}{A}$ { $V_1^+ = V_{out2}(\frac{1}{2})$
 $V_{out1} - V_2^- = \frac{V_2^- - V_{out2}}{100}$ $V_{out1} = (\frac{1}{2}V_{out2} - V_{in})A$
 $V_{out2} = -\frac{1}{2}V_{out2}A + V_{in}A$ $V_{out2} = -\frac{1}{1+2/A}(V_{out2}A - V_{in}A)$
 $V_{out2} = -\frac{1}{2}V_{out2}A^2 + V_{in}A^2$ $V_{out2} = \frac{2V_{in}A^2}{4+2A+A^2}$
 $V_{out2}(A+2+\frac{1}{2}A^2) = V_{in}A^2$ $V_{out2} = \frac{2V_{in}A^2}{4+2A+A^2}$

b. $V_1^+ = \frac{1}{2}V_{out2}$, so $V_1^+ = \frac{V_{in}A^2}{4+2A+A^2}$ { $\lim_{A \rightarrow \infty} V_1^+ = V_{in}$ } Summing pt. !

c. The amp connecting V_{out1} to V_{out2} is the typical inverting neg. fb of amp.



d. i) increase ($A(V_1^+ - V_1^-)$)

ii) decrease (now V_2^- went up)

iii) decrease (just a resistive voltage divider connection to V_{out2})

~~III~~

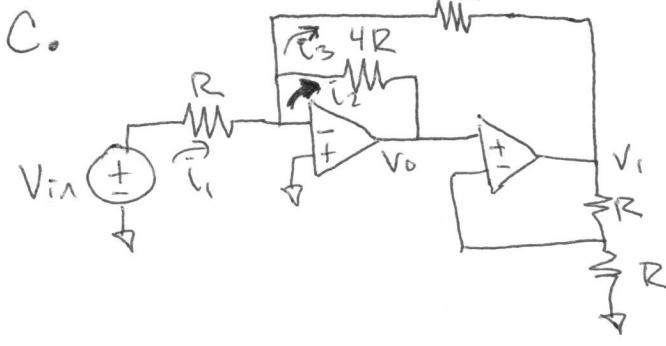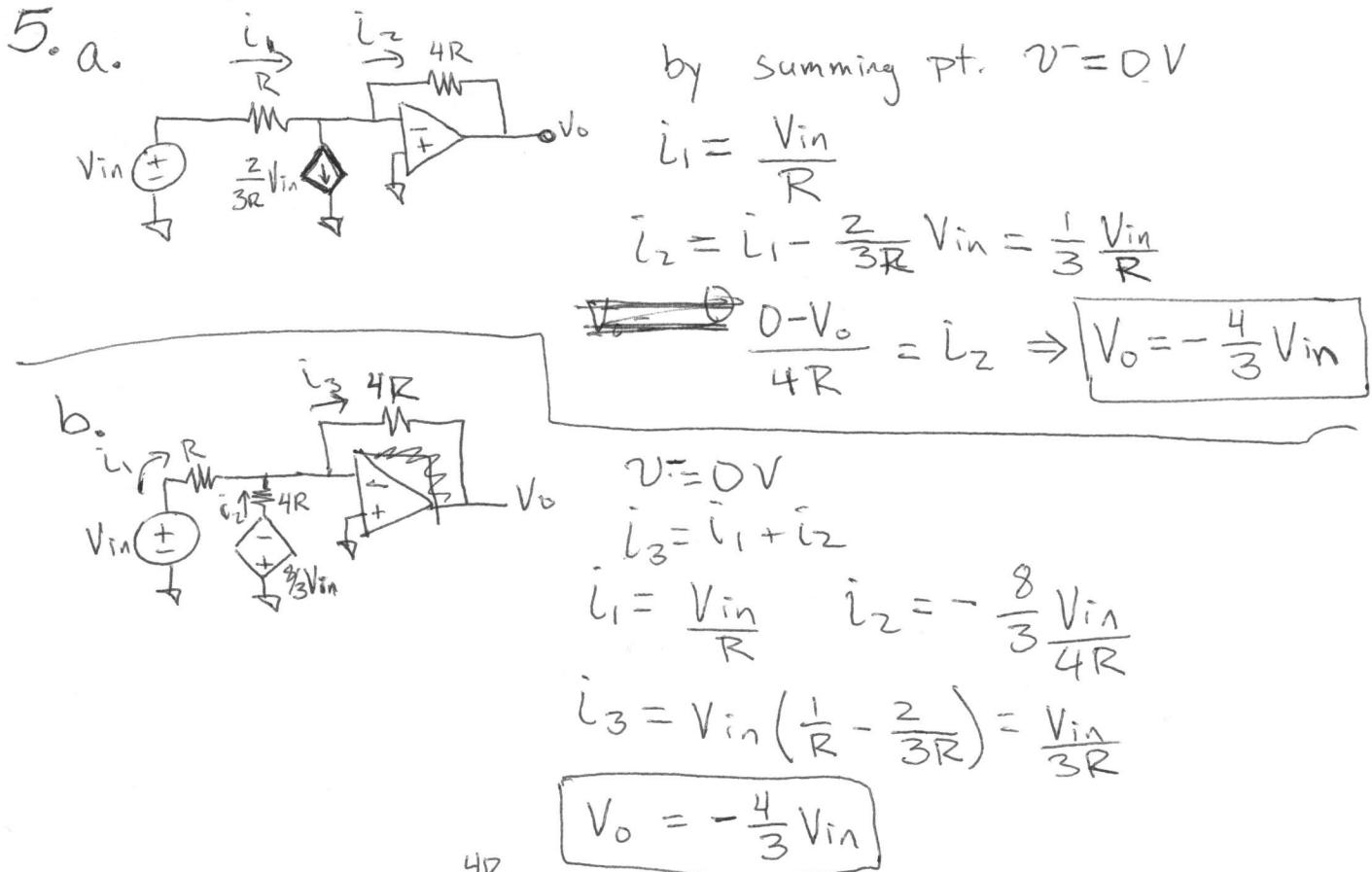e. Of course! As pointed out, b. gives the summing pt. const. Also, c & d are a great intuitive way of showing neg fb. exists.




$$V_1 = \frac{V_o}{2} \quad (\text{basic non-inverting topology})$$


$$V_1^- = 0$$

$$\frac{V_{in}}{R} = \frac{-V_o}{4R} - \frac{V_o}{8R}$$
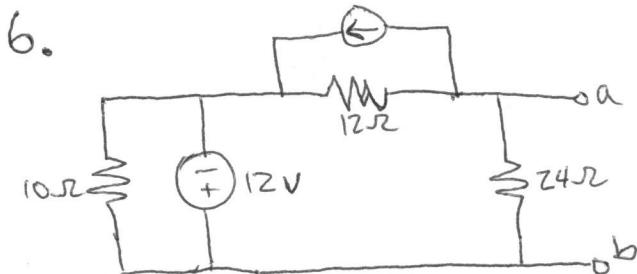
$$V_o = -\frac{8V_{in}}{3} \Rightarrow V_1 = -\frac{4}{3} V_{in}$$



Use superposition (this is one of the most powerful techniques for solving circuits. Along with node voltage there is much you can't solve)
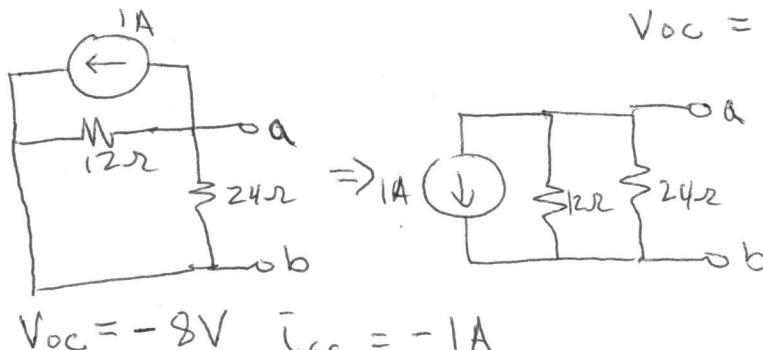
$$V_{oc} = -8V \quad i_{sc} = -1A$$


$$V_{oc,\text{tot}} = -16V$$

$$i_{sc,\text{tot}} = -2A$$

$$\Rightarrow R_{th} = 8\Omega$$

7.

$$I = \frac{V}{k_1} + k_2 \quad \text{when } V = V_{th}, I = 0$$

$$\text{so, } \frac{V_{th}}{k_1} = k_2$$


when $I = +I_N$ (or $I_{th} = I_{sc}$)

$$V = 0$$

$$+I_N = k_2$$

$$\Rightarrow \frac{1}{k_1} = +\frac{I_N}{V_{th}} = +\frac{1}{R_{th}}$$

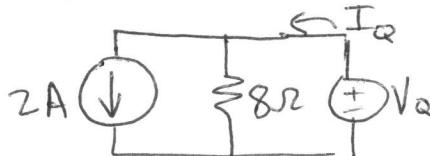8. a. Use Norton equivalent from 6. (If you don't do this, maybe you don't trust Norton/Thevenin. If that's the case you need to convince yourself fast. These will continue to be extremely important in this class and future circuits classes.) Without them you'll waste a lot of time!




$$I_Q(0) = 2A = +I_N$$

$$V_Q(0) = -2(8) = -16V = V_{th}$$

from 7,

$$I_Q = +\frac{V_Q}{8} + 2$$

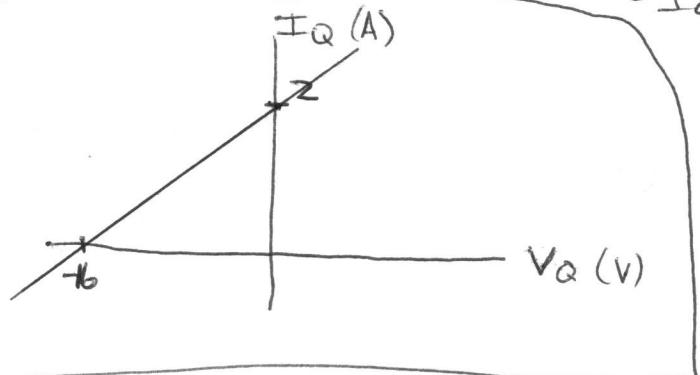

b. Yes, we can see this quickly by finding ~~R_th between a & c~~ which is I_{sc} between a & c using superposition


$$I_{source} \Rightarrow I_{sc} = -1A$$


$$V_{source} \Rightarrow I_{sc} = \frac{12}{24} = \frac{1}{2}A \Rightarrow I_{sc} = \frac{1}{2}A \neq -2A$$

c. $I_N = -I_Q(0) = \frac{V_{th}}{R_{th}} = -2A$

$$R_{th} = 8\Omega$$

$$\Rightarrow V_{th} = -16V$$

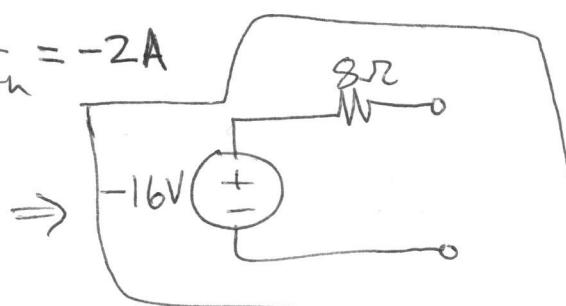

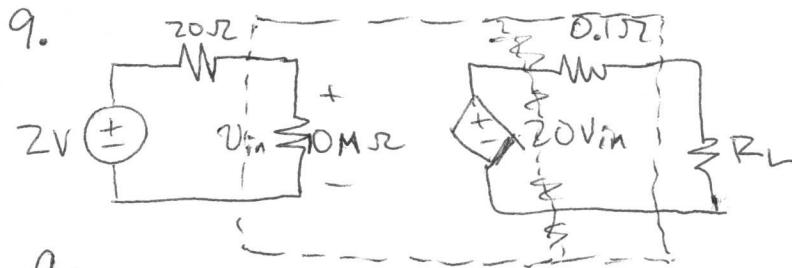

a.

↑ amp is boxed

$$\cancel{P = \frac{V^2}{R}}, V \approx 2V \quad \left(\frac{10M}{20+10M} \approx 1 \right)$$

$$P = \frac{4}{10^7} = \boxed{400nW}$$

b.



$$V_{out} = \left(\frac{R_L}{0.1 + R_L} \right) \cancel{40}$$

$$\frac{20}{40} = \frac{R_L}{0.1 + R_L} \Rightarrow \boxed{R_L = 0.1\Omega}$$

c.

$$P_L = \frac{V_L^2}{R_L} = \frac{V_s^2 \left(\frac{R_L^2}{(R_s + R_L)^2} \right)}{R_L} = \frac{V_s^2 R_L}{R_s^2 + 2R_s R_L + R_L^2}$$

want to minimize denom.

$$R_s^2 + 2R_s R_L + R_L^2 \quad \text{with } R_s > 0, R_L > 0$$

so want to minimize

$$R_s^2 + 2R_s R_L = R_s(R_s + 2R_L), \text{ set } \boxed{R_s = 0}$$