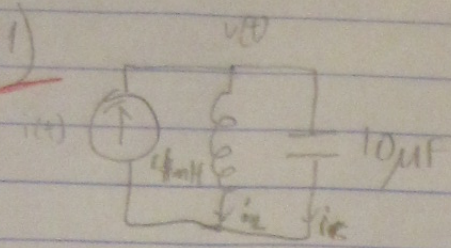


~~20 pts total~~

20 pts total

~~(Normalize to 20 pt grade)~~



$$i_L = 0.1 \cos(5000t) \text{ Amps} \quad \text{- Given}$$

$$v(t) = 4 \text{ mH} \cdot i_L' \\ = -5000 \cdot 0.1 \cdot 4 \text{ m} \cdot \sin(5000t) \\ = -2 \sin(5000t)$$

3 pts

$$i_C(t) = 10 \mu\text{F} \cdot v'(t) = -10 \mu\text{F} \cdot 2 \cdot 5 \text{ k} \cos(5000t) = -100 \mu\text{F} \cdot \cos(5000t) \text{ mV} = -0.1 \cos(5000t) \text{ V}$$

$$i(t) = i_L + i_C = 0 \text{ mA}$$

what this means is that adding a ^{nonzero} current source to a parallel LC circuit can't yield $i_L = 0.1 \cos(5000t)$

$$\text{Total energy is } \frac{1}{2} \cdot (0.1 \text{ A})^2 \cdot 4 \text{ mH} = 0.02 \text{ mJ} = \frac{1}{2} \cdot 10 \mu\text{F} \cdot (2 \text{ V})^2$$

3 pts

a) Position 1: $V_C = 2, i_L = 0$

Short cut

Position 2: Normal LC circuit w/ $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \cdot 0.1}} = 10 \text{ sec}^{-1}$

$$V_C(t) = 2 \cos(10t), \text{ so } i_L(t) = i_C(t) = C \cdot V_C'(t) = -0.2 \sin(10t)$$

Or the long way! $I_C = I_L$

$$\frac{I_C}{C} + L \frac{dI_C}{dt} = 0$$

$$\frac{I_C}{C} + L I_C'' = 0$$


$$I_C'' = -\frac{I_C}{LC} \Rightarrow s^2 = -\frac{1}{LC} \quad s_{1,2} = \pm j\omega_0$$

Use initial condition to find constants...


etc. etc as we did in lecture 11 (July 16th)

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

2 pts

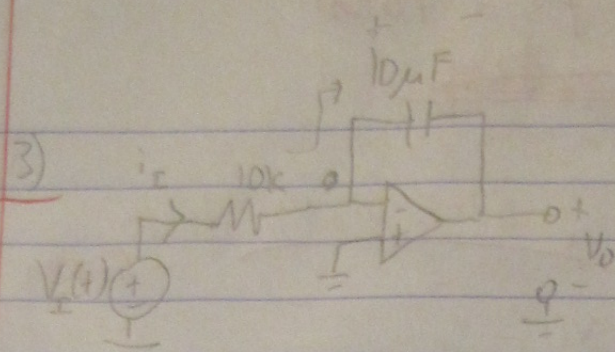
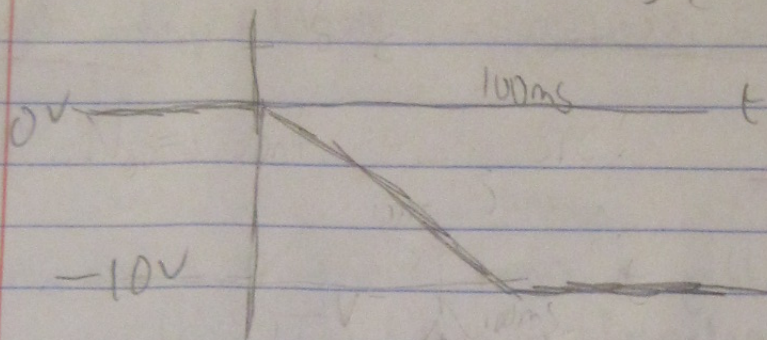
$$I = \frac{V_I(t)}{10k} \quad V_o = -\int \frac{I}{C} = -\int \frac{V_I(t) \cdot dt}{10\mu \cdot 10k} = -10 \int V_I(t) dt$$



1 pt
for ~~all~~
all of
4.

4a) $(8+j7)(5e^{j30})(e^{-j39})(0.3-j0.1)$

$$(10.63 \angle 0.718)(5 \angle 30)(1 \angle -39)(0.3162 \angle -0.3218)$$

$$16.8 \angle 0.2391$$

$$\text{or } 16.8 \angle 13.7^\circ$$

b) $(8.5+j34) \cdot (20e^{-j25})(60) \frac{\cos(10) + j\sin(10)}{(25e^{j20} \cdot 37e^{j23})}$

$$(35.04 \angle 1.32)(20 \angle 0.43)(60 \angle 0) \frac{1 \angle -2.56}{25 \angle 0.349 \cdot 37 \angle 0.4014}$$

$$25 \angle 0.349 \cdot 37 \angle 0.4014$$

$$45 \angle 0.31 \quad \text{or } 45.47 \angle 18^\circ$$

c) $(25 \angle 0.52) \cdot (10 \angle 0.4712)(19.1 \angle -6.748)$
 $2.25 \angle -1.1$

$$2140 \angle 1.35$$

$$\text{or } 2140 \angle 78^\circ$$

Don't
count
off
for no
work.

5) $9(5.83 \angle 1.03)(4 \angle 0.87)(7 \angle -0.349)$

$163.24 \angle 1.55$

$163.26671 \angle 1.534$

$2.7461 + 163.2436$

- Note that with such an extreme angle, rounding errors can be pretty big so full credit if you're within a factor of 5.

Keep this in mind if you're doing some design problem someday

b) $(10 \angle 0.8727) \angle 0.349 = 10 \angle 1.2218$

$3.4195 + 9.3972j$

c) $10 \angle 0.8727 \cdot \omega$
 $10 \angle (\omega + 0.8727)$

$10 \cos(\omega + 0.8727)$

d) $|E| e^{j\theta} e^{j\omega t} = |E| e^{j(\theta + \omega t)}$

Note this is not $|E| \angle \theta$

$|E| \cos(\omega t + \theta)$


$|E| \angle \theta$ is just another way to write $|E| e^{j\theta}$. This has an $e^{j\omega t}$ stuck to it.

2 pts
total

6. Ha question 6

7. Zero-input response is when $V_s = 0$.

1 pt

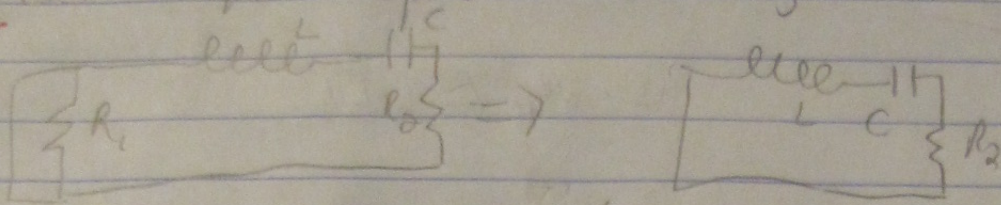

$$\alpha = R/2L = \frac{15}{2 \mu H} = 7.5 \times 10^{-6} \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-14}}} = \frac{1}{10^{-7}} = 10^7$$

$\alpha < \omega_0$, so underdamped

1 pt

8. $i = 5e^{j\omega t}$

These could also be $-5L0$, $5L3\pi$, $-5L-\pi$ etc.

$5L\pi$


$-5+0j$

[NOT $5+0j$]!!!

or 36.990°

b. $\sqrt{13} \cos(20t + 0.588)$

4 pts total

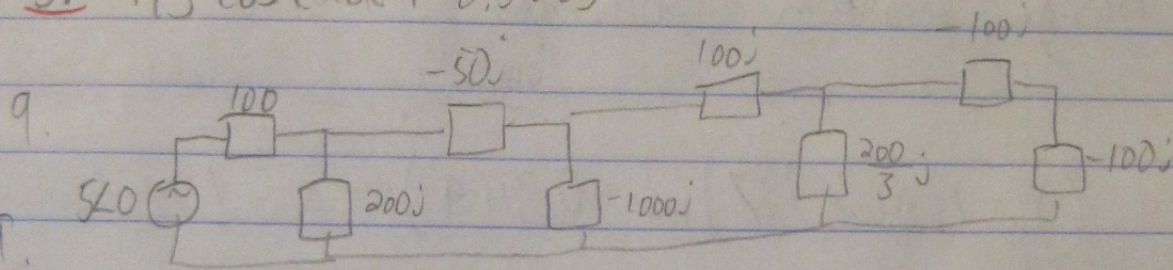

$V_{\text{sing}} \quad Z_C = \frac{1}{j\omega C} = -\frac{j}{100 \cdot C} \quad Z_L = j\omega L = 100jL$

1 pt

b. $Z_{eq} = \left(\left(\left((-100j) + (-100j) \right) \parallel \frac{200}{3}j + 100j \right) \parallel -1000j \right) - 50j \parallel 200j + 100$


$100j$

$(200j \parallel -1000j) = 250j$

$(200j \parallel 200j) = 100j$

$Z_{eq} = 100 + 100j$

(so, for example, Z_{eq} could also be

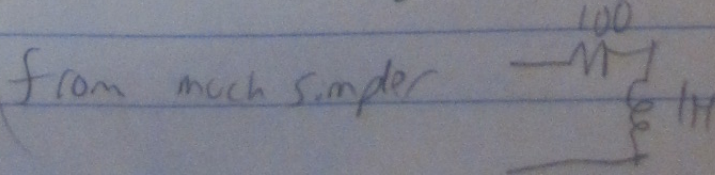

c. $\frac{5 \angle 0}{100 + j100} = \frac{5 \angle 0^\circ}{\sqrt{2} 100 \angle 45^\circ} = \frac{1}{20\sqrt{2}} \angle -45^\circ = \hat{I}$

1/2 pt

d. $i_{s,p}(t) = \frac{1}{20\sqrt{2}} \cos(100t - 45^\circ)$

1/2 pt


e. $i_s(t) = \frac{1}{20\sqrt{2}} \cos(100t - 45^\circ)$

~~scribble~~

0 pts

f) $i_s(t) = \frac{5V}{100\Omega} = 50mA$ since inductors are shorts and caps are open


1/2 pt

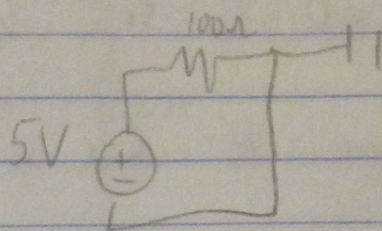

1/2 pt

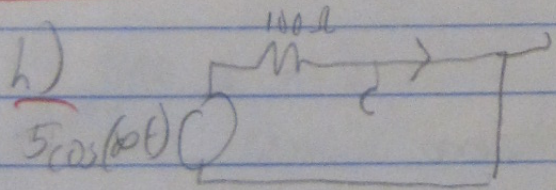g) Z_C goes to zero (short) as $\omega \rightarrow \infty$
 Z_C goes to infinity (open) as $\omega \rightarrow 0$

Z_L goes to infinity (open) as $\omega \rightarrow \infty$
 Z_L goes to zero (short) as $\omega \rightarrow 0$



$$\lim_{\omega \rightarrow \infty} i_s(t) = \frac{5 \cos(\omega t)}{100}$$

Not for a grade

i) Node A: $\frac{V_a - 5 \cos(100t)}{100} + \int \frac{V_a}{2H} + 200\mu F (V_a' - V_b') = 0$

Defining nodes left to right



Node B: $200\mu F (V_b' - V_a') + 10\mu F V_b' + \int \frac{V_b}{1H} - \int \frac{V_c}{1H} = 0$

Node C: $\int \frac{V_c}{1H} - \int \frac{V_b}{1H} + \int \frac{V_d \cdot 3}{2H} + 100\mu F \cdot (V_c' - V_j') = 0$

Node D: $(V_j' - V_c') \cdot 100\mu F + V_j' \cdot 100\mu F = 0$


3 pts.

10 a)

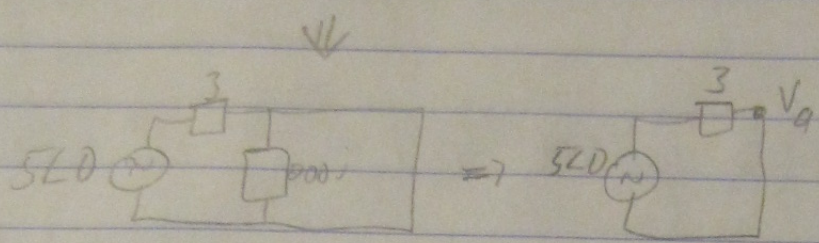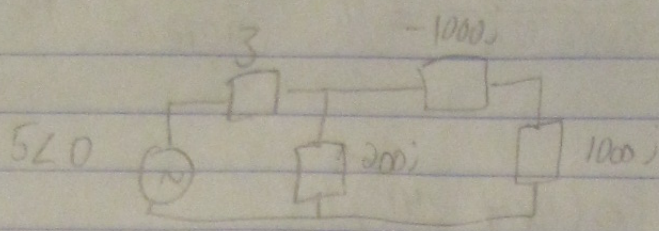

$\hat{V}_a = 0$ so $V_a(t) = 0 \cdot \cos(100t + 0) = 0V$

b. Impedances of Cs and Ls change.

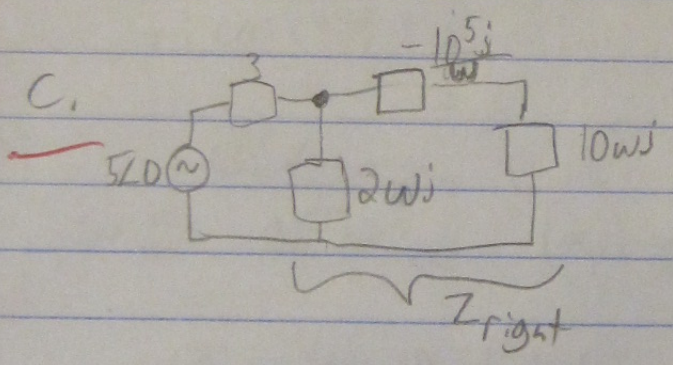

$$\hat{V} = \frac{Z_{right}}{Z_{right} + 3} \cdot 5\angle 0$$

Thus, $\hat{V} = 0$ iff Z_{right} is zero.

$$Z_{right} = \frac{(10\omega j - \frac{10^5 j}{\omega}) \cdot 2\omega j}{(10\omega j - \frac{10^5 j}{\omega} + 2\omega j)}$$

Zero iff numerator is zero or denominator is infinite

Numerator: $(10\omega j - \frac{10^5 j}{\omega}) \cdot 2\omega j = 20\omega^2 j^2 - 2 \cdot 10^5 j^2$
 assuming $\omega \neq 0$ - because I canceled ω/ω
 $\omega^2 = \frac{2 \cdot 10^5}{20} = 10000 \quad \omega = \pm 100$


$$\text{because } 5\cos(-100t) = 5\cos(100t)$$

$\omega = -100$ is the same thing as $\omega = 100$, so I guess that's kind of another ω .

Then checking $\omega = 0$, we have $Z = \frac{0 \cdot \infty}{\infty}$

Could use L'Hôpital's rule, but better way is to abandon phasors since $V(t)$ is no longer AC if $\omega = 0$.

Thus, we just consider:

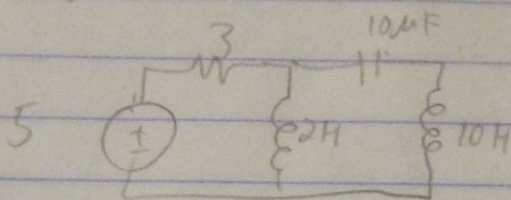

In steady state, $V_a(t) = 0V$

So $\omega = -100$ and $\omega = 0$ give same answer.
↑ but this one is same as $\omega = 100$.

d. It decays to zero. Increasing R makes it hit steady state faster. } - not for a grade

No time to write solutions for extra problems. email me* or come to office hours.

* At first, it seemed bizarre to write a personal message on a piece of paper to be read by other people. Then I remembered that all those suckers before us actually did this as a primary form of communication.