# EE40 Lecture 12 Josh Hug

### 7/21/2010

# **Logistical Things**

- HW6 due Friday at 5PM (also short)
- Midterm next Wednesday 7/28
  - Focus is heavily on HW4, 5, 6, and Labs P1,4, 5
  - Will reuse concepts from HW 1,2,3

# **Filtering**

- For the past couple of lectures, we've discussed using phasors and impedances to solve circuits
- Usually, we've assumed we have some single frequency source, and found the resulting output
- Last time in lecture, we showed that we could apply two different frequencies at one time using superposition
  - Each was scaled and shifted by different amounts

# **Transfer Functions**

- $\hat{V}_{out} = H(j\omega)\hat{V}_{in}$ , e.g.  $\hat{V}_{out} = \frac{1}{1+0.1jw}\hat{V}_{in}$
- Maps system input signal to system output signal
  - Plug an input voltage  $A\cos(\omega t + \phi)$  into  $\hat{V}_I$
  - Get an output voltage  $A|H(j\omega)|\cos(\omega t + \phi + \angle H(j\omega))$ 
    - Output is scaled and shifted in time – Scaling and shifting depend on frequency
    - Frequency is unchanged (linear system)
- Tells you how system will respond to any frequency, a.k.a. frequency response

## **Using a Transfer Function**

• 
$$\hat{V}_{out} = H(j\omega)\hat{V}_{in} = \frac{1}{1+0.1jw}\hat{V}_{in}$$

• Suppose  $v_{in}(t)$  is  $3\cos(10t + \frac{\pi}{2})$ 

$$-\hat{V}_{I} = 3 \angle \frac{\pi}{2} \qquad |H(j10)| = 1/\sqrt{2} \\ \angle H(j10) = -ArcTan[1/1] \\ = -\pi/4 \qquad = -\pi/4$$

• Output phasor  $\hat{V}_{out}$  is just  $\hat{V}_{in} \times H(j10)$ 

$$-\hat{V}_{out} = \frac{3}{\sqrt{2}} \angle \left(\frac{\pi}{2} - \frac{\pi}{4}\right)$$

$$-v_{out}(t) = \frac{3}{\sqrt{2}}\cos(10t + \frac{\pi}{2} - \frac{\pi}{4})$$

# **Using a Transfer Function**

• 
$$\hat{V}_{out} = H(j\omega)\hat{V}_{in} = \frac{1}{1+0.1jw}\hat{V}_{in}$$

• Suppose  $v_i(t)$  is  $3\cos(50t + \frac{\pi}{4})$ 

$$-\hat{V}_{I} = 3 \angle \frac{\pi}{4} \qquad |H(j50)| = 1/\sqrt{26} \\ \angle H(j50) = -ArcTan[5/1] \\ = -1.37$$

• Output phasor  $\hat{V}_C$  is just  $\hat{V}_I \times H(j50)$ 

$$-\hat{V}_{C} = \frac{3}{\sqrt{26}} \angle \left(\frac{\pi}{4} - 1.37\right)$$
$$-\nu_{C}(t) = \frac{3}{\sqrt{26}} \cos(50t + \frac{\pi}{4} - 1.37)$$


# **Transfer Function**

- $\hat{V}_{out} = H(j\omega)\hat{V}_{in} = |H(j\omega)| \angle H(j\omega)\hat{V}_{in}$
- For each frequency, different:
  - Scaling [magnitude]
  - Delay [phase shift]
- It is useful to graphically depict the magnitude and phase of the transfer function


# **Bode Magnitude Plot**

• 
$$\hat{V}_C = \frac{1}{1+0.1jw} \hat{V}_I = H(j\omega)\hat{V}_I$$
  
 $|H(j\omega)| = 1/\sqrt{1+0.01\omega^2}$ 

• Magnitude plot is just a plot of  $|H(j\omega)|$  as a function of  $\omega$ 

 

 
# **Bode Magnitude Plot in Context of Circuit**


 
#### **Bode Phase Plot**


• 
$$\hat{V}_{C} = \frac{1}{1+0.1jw} \hat{V}_{I} = H(j\omega)\hat{V}_{I}$$
  
 $\angle H(j\omega) = -ArcTan[0.1\omega/1]$ 

Phase plot is just a plot of∠H(jω) as a function of ω



10
 
### **Bode Phase Plot in Context of Circuit**




# **Multiple Frequencies**

- Real signals are often a combination of a continuum of many frequencies
  - Radio antenna input
  - Microphone input
- Intuitively:
  - Thunder contains a bunch of low frequency sounds
  - Boiling kettles contains a bunch of high frequency sounds
- There is a mathematically well defined idea of what it means for a signal to "contain many frequencies"

 
# **Time vs. Frequency Domain**

- The Fourier Transform takes a function f(t) and converts it into a function  $\mathcal{F}(\omega)$
- Every signal can be made out of a sum of an infinite number of sinusoids
- Fourier transform tells you how much of each one to include



 
# **Multiple Frequencies**

 The "1" button on a phone is a combination of a 697 Hz tone and a 1209 Hz tone



 
# **Multiple Frequencies**

 Bill and Ted saying the word "bogus" is a more complex set of frequencies



 
# Filtering Example

 If we apply a filter with the frequency response on the right to the signal on the left



# **More complex filtering**

 


Each frequency individually scaled

17

Hug

#### **Phase Effects**

 

EE40 Summer 2010

### **Magnitude and Phase Demo**

• Let's try the ever risky live demo


### **Bode Plots**


- Hopefully I've convinced you that magnitude and phase plots are useful
- Now, the goal will be to draw them straight from the transfer function
- First, some reminders on loglog plots

# Loglog Plots

• On a loglog plot,  $f(x) = Ax^n$  looks like a straight line w/slope n and y-offset A, because:

$$-\log(y) = nlog(x) + \log(A)$$

 

 


EE40 Summer 2010

Hua

 
# **Loglog Plots**

- On a loglog plot,  $f(x) = x^n + k^n$  will: – Be flat for values of  $x^n < k^n$ 
  - Be a straight line of slope n for values of  $x^n > k^n$
  - Have a y-offset of  $1 + k^n$


 
# **Loglog Plots**

- On a loglog plot, f(x) = A(x<sup>n</sup> + k<sup>n</sup>) will:
  Be flat for values of x<sup>n</sup> < k<sup>n</sup>
  - Be a straight line of slope n for values of  $x^n > k^n$
  - Have an y-offset of  $Ak^n$



### **Manual Bode Plots**

• On board, using handout

# **2<sup>nd</sup> Order Filter Example**

Also on board

#### 2<sup>nd</sup> order Bode Plots


- Also on board
- This is where we stopped in class

# **Active filter example**

On board
 
### **Magnitude Plot Units**

 So far, we've been plotting our Bode plots on where 10<sup>0</sup> represents a signal getting through perfectly



#### **Bel and Decibel (dB)**

- A **bel** (symbol **B**) is a unit of measure of ratios of power levels, i.e. relative power levels.
  - $\mathbf{B} = \log_{10}(P_1/P_2)$  where  $P_1$  and  $P_2$  are power levels.
  - The bel is a logarithmic measure
  - Zero bels corresponds to a ratio of 1:1
  - One bel corresponds to a ratio of 10:1
  - Three bels corresponds to a ratio of 1000:1
- The bel is too large for everyday use, so the decibel (dB), equal to 0.1B, is more commonly used.
  - $1 dB = 10 \log_{10}(P_1/P_2)$
  - 0 dB corresponds to a ratio of 1:1
  - 10 dB corresponds to a ratio of 10:1
  - -10 dB corresponds to a ratio of 1:10
- dB are used to measure
  - Electric power, filter magnitude

#### **Logarithmic Measure for Power**

- To express a power in terms of decibels, one starts by choosing a reference power, P<sub>reference</sub>, and writing
   Power P in decibels = 10 log<sub>10</sub>(P/P<sub>reference</sub>)
- Exercise:
  - Express a power of 50 mW in decibels relative to 1 watt.
  - $P (dB) = 10 \log_{10} (50 \times 10^{-3}) = -13 dB$
- Use logarithmic scale to express power ratios varying over a large range

dB: 
$$10 \log \left(\frac{P_1}{P_2}\right) (dB)$$

Note: dB is not a unit for a physical quantity since power ratio is unitless. It is just a notation to remind us we are in the log scale.

#### **Decibels for measuring transfer function magnitude?**


- Decibels provide a measure of relative power
- However, we said they also can be used for transfer functions
- The key is in realizing that  $P \propto V^2 \propto I^2$
- Thus, if a voltage gets reduced by a factor of 100, we'd say the power ratio between the output and in the input would be

$$-10\log_{10}\left(\frac{V_{out}^{2}}{V_{in}^{2}}\right) = 10\log_{10}\left(\left(\frac{V_{out}}{V_{in}}\right)^{2}\right) = 20\log_{10}\left(\frac{V_{out}}{V_{in}}\right)$$

# **Transfer Function in dB**

- Given a transfer function magnitude  $|H(j\omega)|$
- We can convert this transfer function into dB by:
- $|H(j\omega)|_{in \, dB} = 20 \log_{10}(|H(j\omega|))$
- There's not that much to this, but it's common in datasheets

# Example

 

$$|H(j\omega)|_{in\,dB} = 20\log_{10}(|H(j\omega|)$$