
EE40
Lecture 14
Josh Hug

7/26/2010

Logisticals


- Midterm Wednesday
 - Study guide online
 - Study room on Monday
 - Cory 531, 2:00
 - Cooper, Tony, and I will be there 3:00-5:10
 - Study room on Tuesday
 - Cory 521, 2:30 and on
- Completed homeworks that have not been picked up have been moved into the lab cabinet
- If you have custom Project 2 parts, I've emailed you with details about how to pick them up

Lab

- Lab will be open on Tuesday if you want to work on Project 2 or the Booster Lab or something else
 - Not required to start Project 2 tomorrow
- No lab on Wednesday (won't be open)


Power in AC Circuits

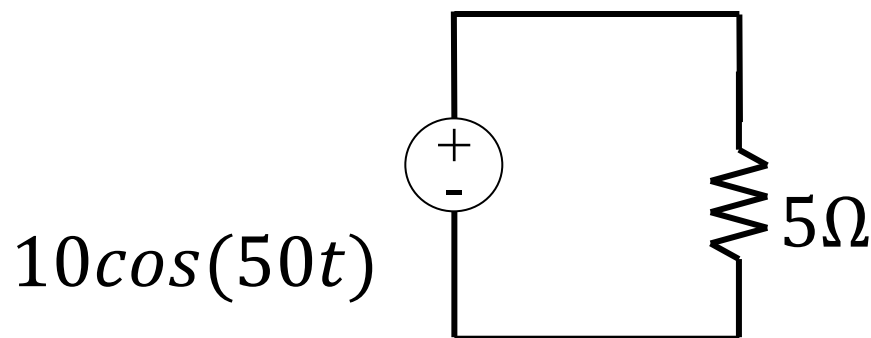- One last thing to discuss for Unit 2 is power in AC circuits
- Let's start by considering the power dissipated in a resistor:




$$\begin{aligned} P(t) &= v(t)i(t) = 10 \cos(50t) \times \frac{10}{5} \cos(50t) \\ &= 20 \cos^2(50t) \end{aligned}$$


Or graphically

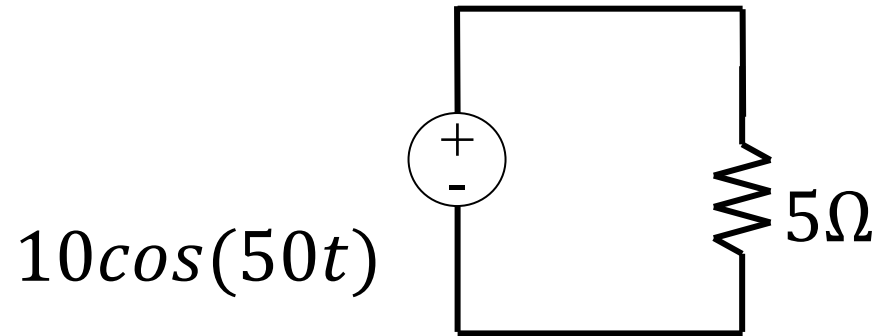

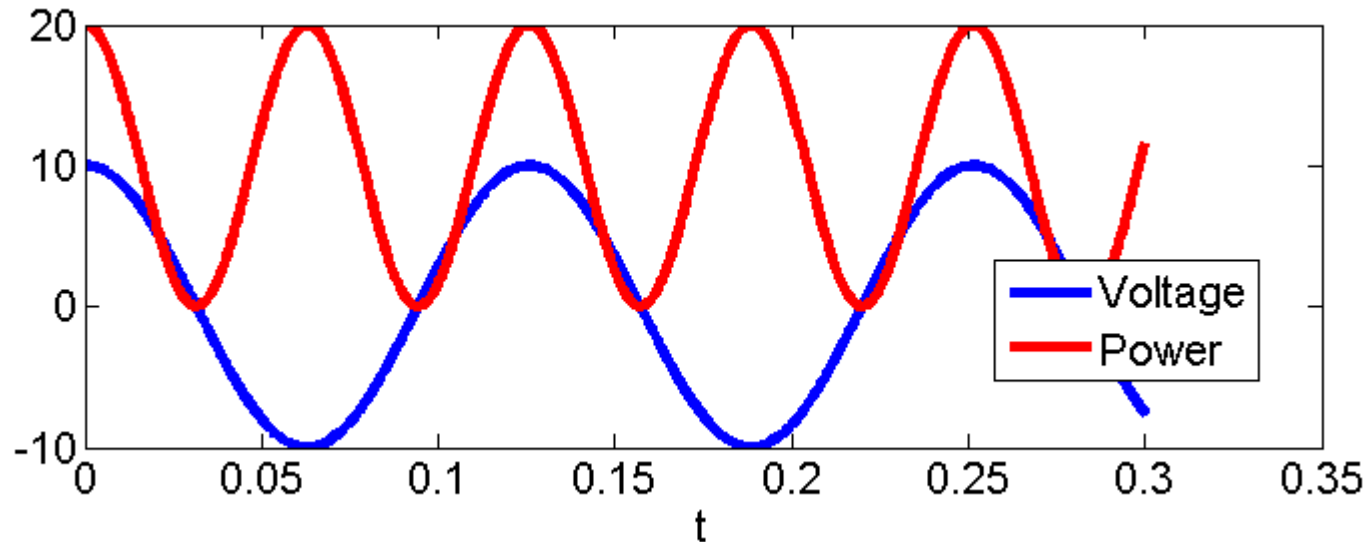
$$P(t) = v(t)i(t) = 10 \cos(50t) \times \frac{10}{5} \cos(50t) \\ = 20 \cos^2(50t)$$




Average Power

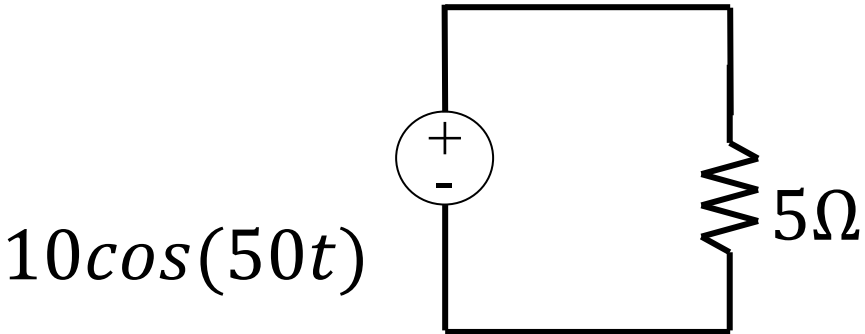

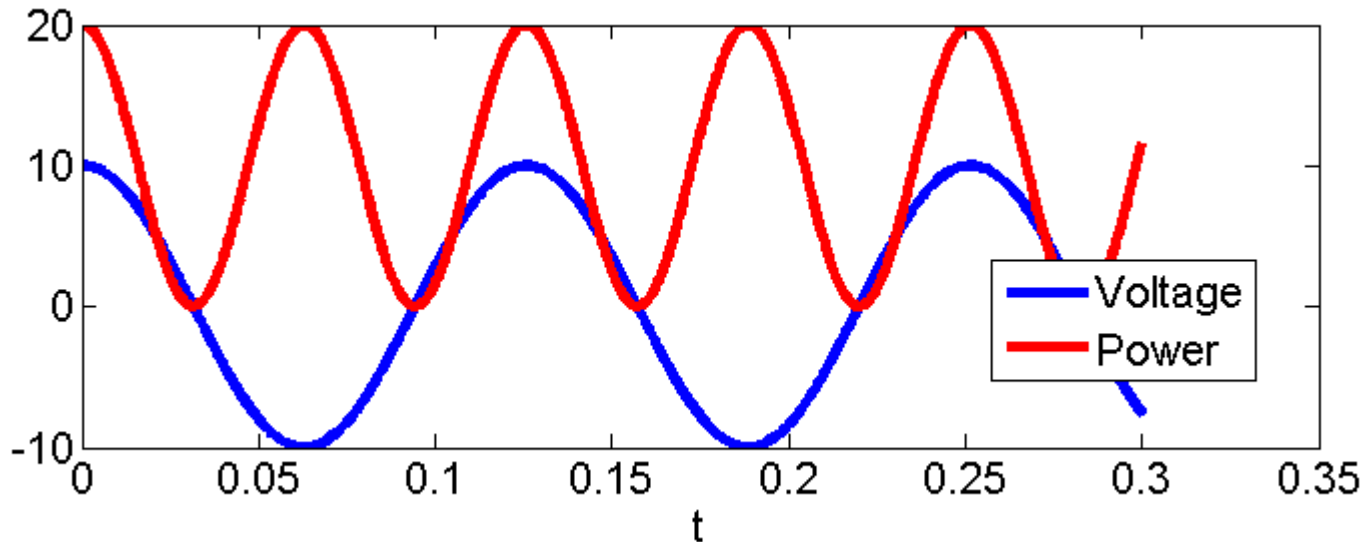Peak Power: 20W
Min Power: 0W
Avg Power: 10W




Capacitor example

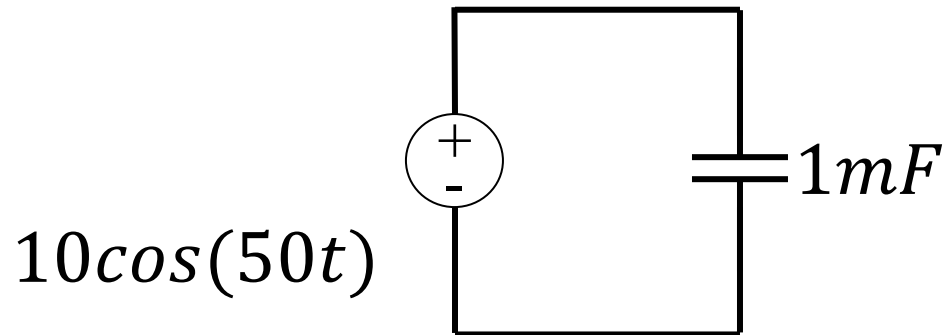

Find $p(t)$


- $i(t) = 10^{-3} \times (-500 \sin(50t)) = -0.5 \sin(50t)$
- $p(t) = -5 \sin(50t) \cos(50t)$

Graphically

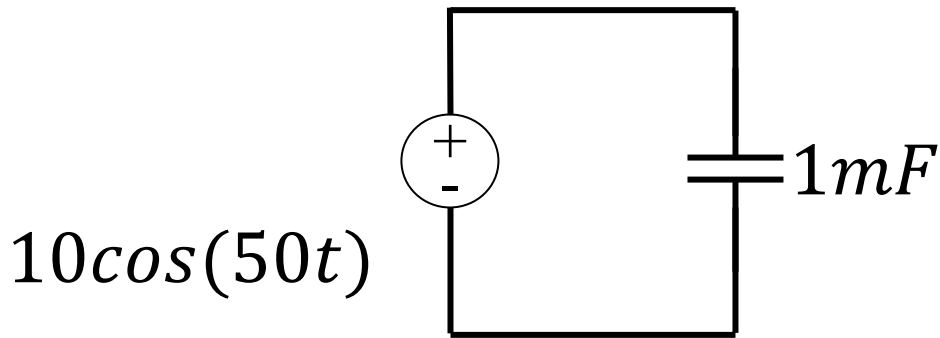


Peak Power: $5/2W$
Min Power: $-5/2W$
Avg Power: $0W$

$$p(t) = -5 \sin(50t) \cos(50t)$$

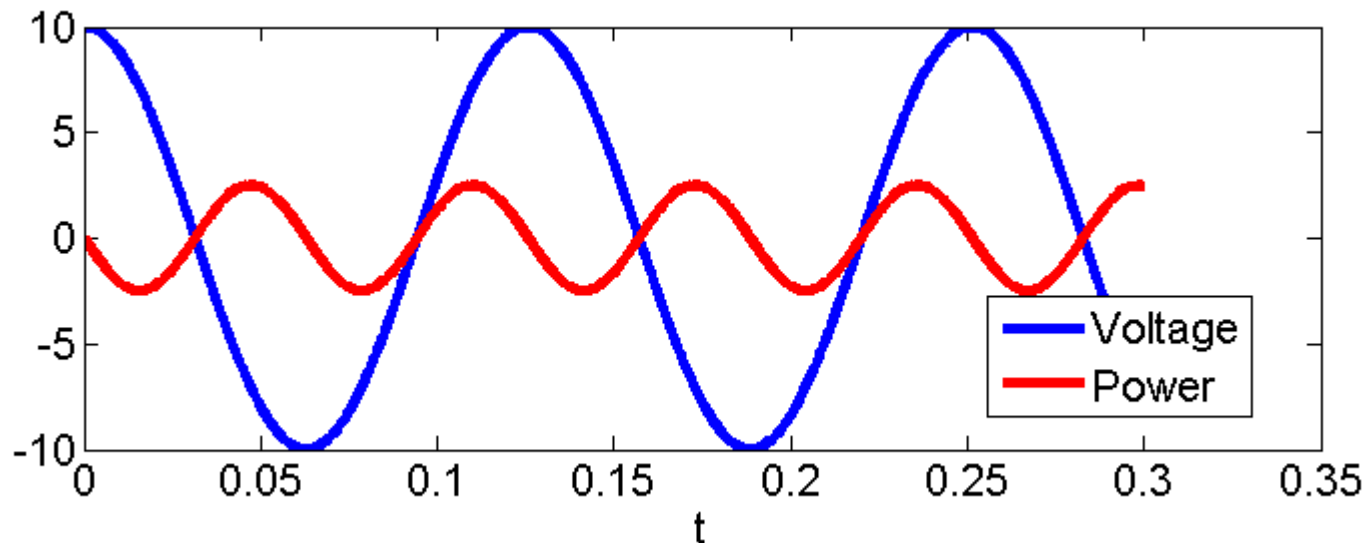


Is there some easier way of calculating power?

- Like maybe with... phasors?

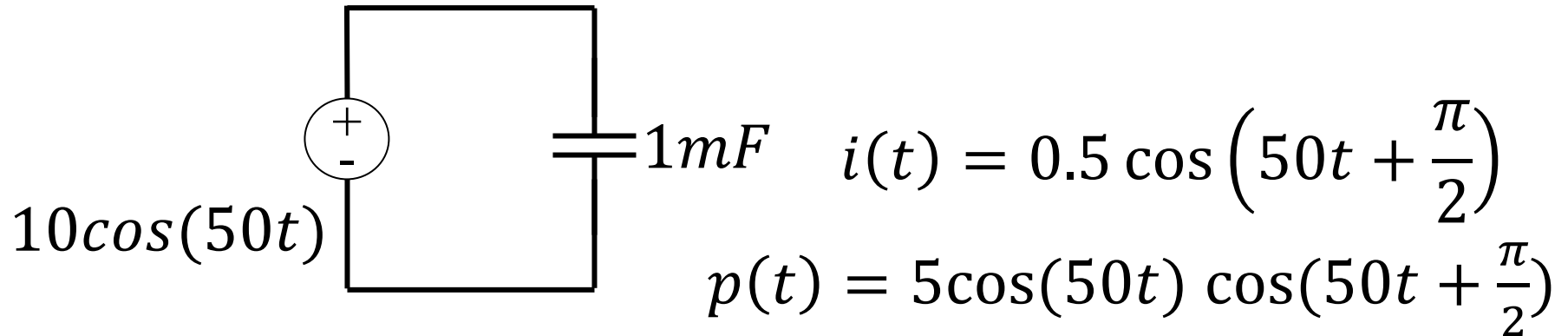


- Phasors are:
 - $\hat{V} = 10\angle 0$
 - $\hat{I} = 0.5\angle \frac{\pi}{2}$
- How about $\hat{P} = \hat{V}\hat{I}$?

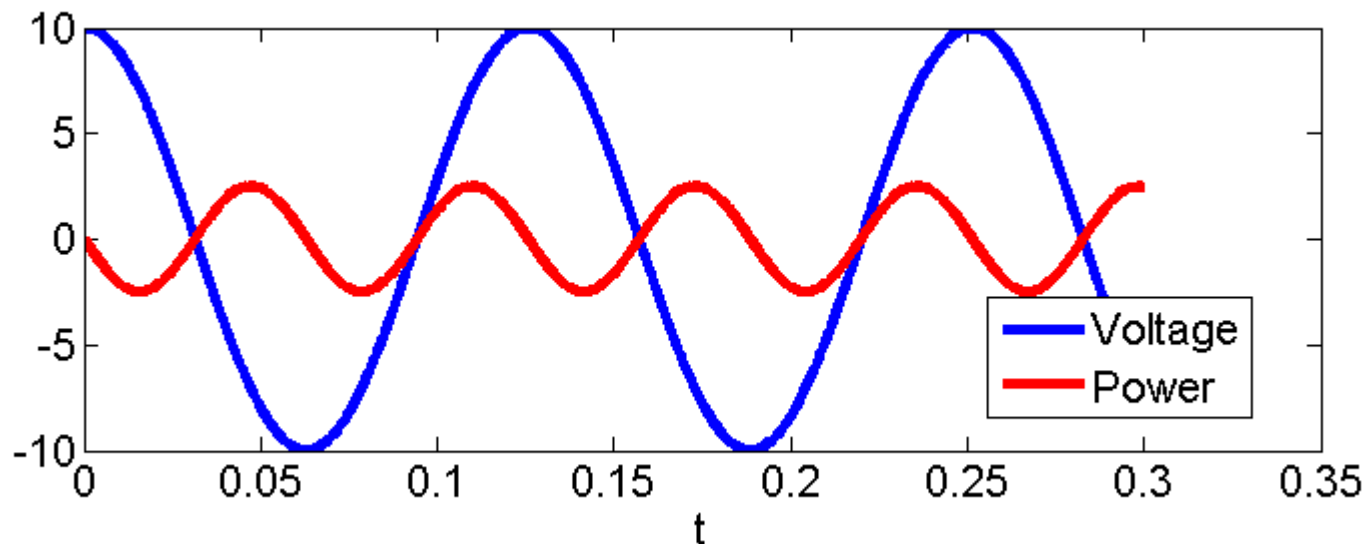Is there some easier way of measuring power?



- Phasors are:
 - $\hat{V} = 10 \angle 0$
 - $\hat{I} = 0.5 \angle \frac{\pi}{2}$
 - Does $\hat{P} = \hat{V} \hat{I}$?
 - $\hat{V} \hat{I} = 5 \angle \frac{\pi}{2}$
- $p(t) = 5 \cos(50t) \cos(50t + \frac{\pi}{2})$
- A. Yes, $\hat{V} \hat{I}$ matches $p(t)$
 - B. No, wrong magnitude
 - C. No, wrong phase
 - D. No, wrong frequency

It gets worse

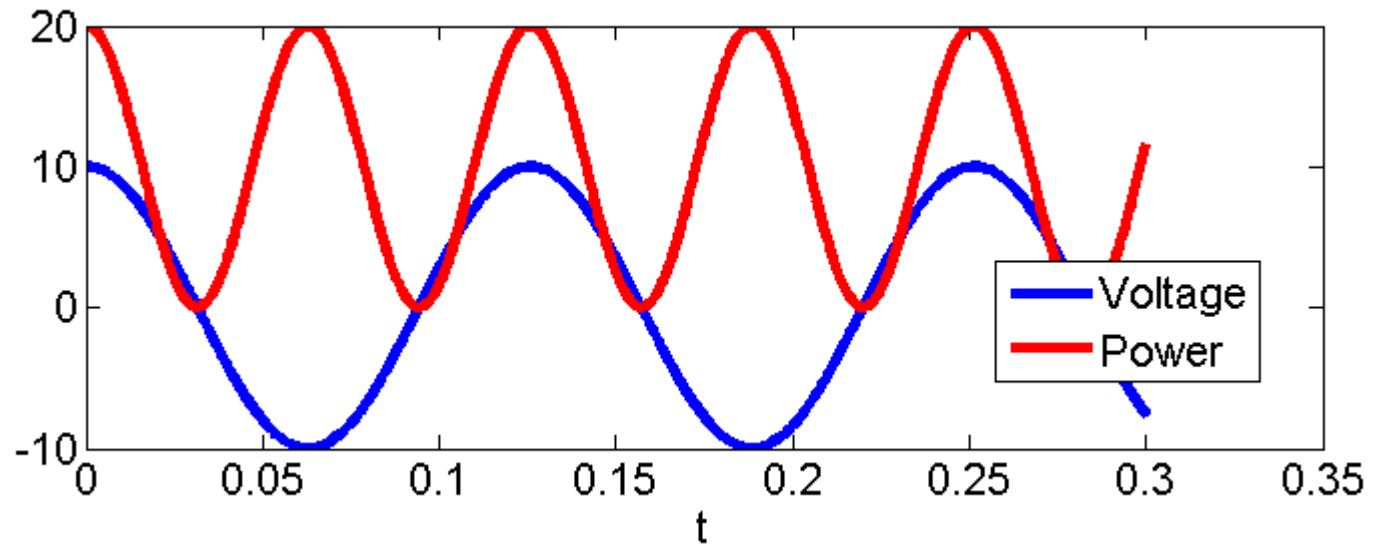

- For the resistor, there is no phasor which represents the power (never goes negative)

Average Power

- Tracking the time function of power with some sort of phasor-like quantity is annoying
 - Frequency changes
 - Sometimes have an offset (e.g. with resistor)
- Often, the thing we care about is the average power, useful for e.g.
 - Battery drain
 - Heat dissipation
- Useful to define a measure of “average” other than the handwavy thing we did before
- Average power given periodic power is:

$$\bar{p} = \int_0^T \frac{1}{T} p(t) dt$$

T is time for 1 period

Power in terms of phasors

- We've seen that we cannot use phasors to find an expression for $p(t)$
- Average power given periodic power is:

$$\bar{p} = \int_0^T \frac{1}{T} p(t) dt \quad T \text{ is time for 1 period}$$

- We'll use this definition of average power to derive an expression for average power in terms of phasors

Average Power

- $\overline{p(t)} = \overline{v(t)i(t)}$
- Note: $\overline{ab} \neq \overline{a}\overline{b}$
 - e.g. $a = 5 \cos(t)$, $b = 4 \cos(t)$
 - Average of each cosine is zero
 - Average of their product is 10
- Our goal will be to get the average power $\overline{p(t)}$ from phasors \hat{V} and \hat{I}
- We'll utilize $\overline{Re[a]Re[b]} = \frac{1}{2} Re[ab^*]$
 - * denotes complex conjugate
 - See extra slides for proof of this identity

Power from Phasors

- $\overline{Re[a]Re[b]} = \frac{1}{2} Re[ab^*]$

- $\overline{p(t)} = \overline{v(t)i(t)}$

- $v(t) = Re[V_o e^{j(\omega t + \theta)}]$

- $i(t) = Re[I_o e^{j(\omega t + \phi)}]$


- $$\begin{aligned}\overline{p(t)} &= \overline{Re[Re[V_o e^{j(\omega t + \theta)}]] Re[Re[I_o e^{j(\omega t + \phi)}]]} \\ &= \frac{1}{2} Re[V_o e^{j(\omega t + \theta)} I_o e^{-j(\omega t + \phi)}] \\ &= \frac{1}{2} Re[V_o I_o e^{j(\theta - \phi)}] \\ &= \frac{1}{2} Re[\hat{V} \hat{I}^*]\end{aligned}$$

Power from Phasors

- Thus, given a voltage phasor \hat{V} and a current phasor \hat{I} , the average power absorbed is

$$p(t) = \frac{1}{2} \operatorname{Re}[\hat{V}\hat{I}^*]$$

Capacitor Example

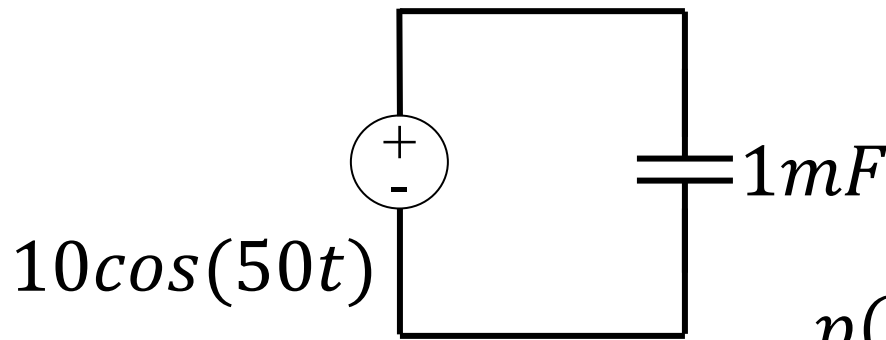

$$i(t) = -0.5 \cos\left(50t + \frac{\pi}{2}\right)$$
$$p(t) = 5\cos(50t) \cos\left(50t + \frac{\pi}{2}\right)$$

- Phasors are:


$$- \hat{V}(t) = 10 \angle 0$$

$$- \hat{I}(t) = 0.5 \angle \frac{\pi}{2}$$

- $\overline{p(t)} = \frac{1}{2} \operatorname{Re} \left[10 \angle 0 \times 0.5 \angle -\frac{\pi}{2} \right]$

$$= \frac{1}{2} \operatorname{Re} \left[5 \angle -\frac{\pi}{2} \right] = 0$$

Resistor Example

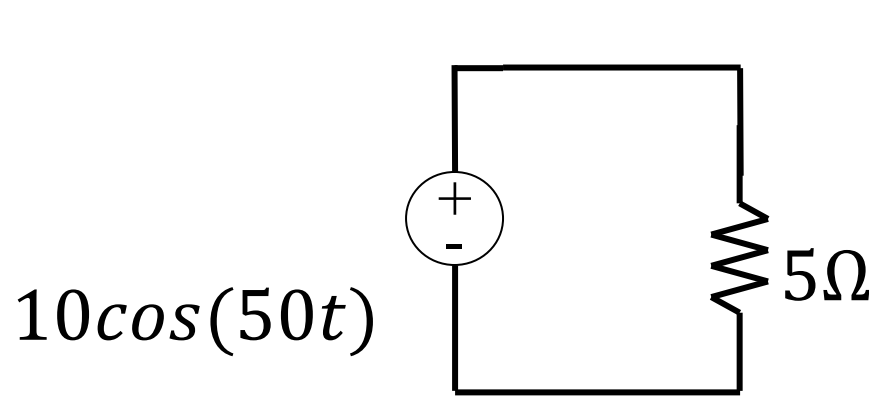

$$p(t) = \frac{1}{2} \operatorname{Re}[\hat{V}\hat{I}^*]$$

- $\hat{V} = 10\angle 0$

Find avg power across resistor

- $\hat{I} = 2\angle 0$


- $\overline{(p(t))} = \frac{1}{2} \operatorname{Re}[20] = 10$

A. 0 Watts

B. 10 Watts

C. 20 Watts

Resistor Example

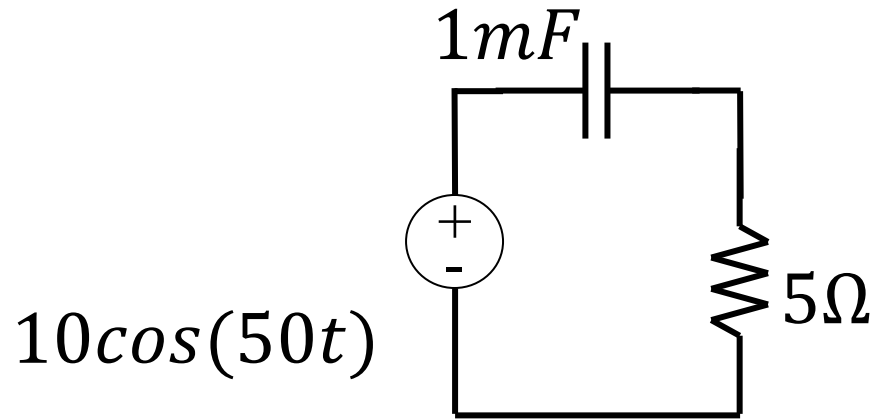

- $Z_{eq} = 5 - 20j$

Find avg power from source

- $\hat{V} = 10\angle 0$


- $\hat{I} = \hat{V} / Z_{eq}$

- $\overline{(p(t))} = \frac{1}{2} Re[\hat{V}\hat{I}^*] = \frac{1}{2} Re\left[\frac{\hat{V}\hat{V}^*}{Z_{eq}^*}\right] = \frac{1}{2} Re\left[\frac{100}{5 + 20j}\right]$
 $= \frac{1}{2} Re\left[\frac{100}{20.6155\angle 1.3258}\right] = \frac{1}{2} Re[1.17 - 4.7j] = 0.58W$

Reactive Power

- So if power dissipated is $\frac{1}{2} \text{Re}[\hat{V}\hat{I}^*]$, then what is $\frac{1}{2} \text{Im}[\hat{V}\hat{I}^*]$?
- Imaginary part is called “reactive power”
- Physical intuition is that it’s power that you put into an element with memory, but which the element eventually gives back

Capacitor Reactive Power Example

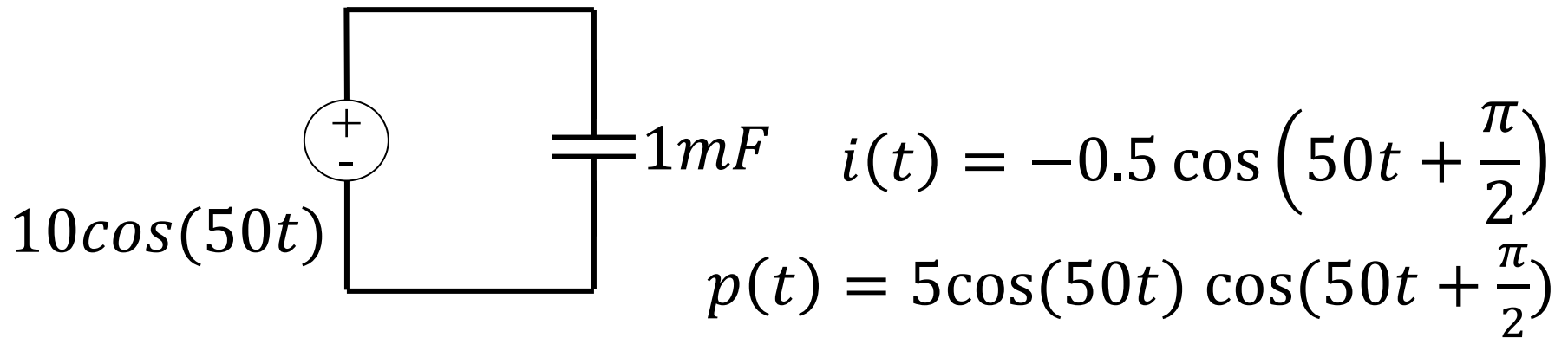

- Phasors are:


$$- \hat{V}(t) = 10 \angle 0$$

$$- \hat{I}(t) = 0.5 \angle \frac{\pi}{2}$$

- $\overline{p(t)} = \frac{1}{2} \text{Im} \left[10 \angle 0 \times 0.5 \angle -\frac{\pi}{2} \right]$

$$= \frac{1}{2} \text{Im} \left[5 \angle -\frac{\pi}{2} \right] = -\frac{5}{2} \text{ W}$$

Graphically

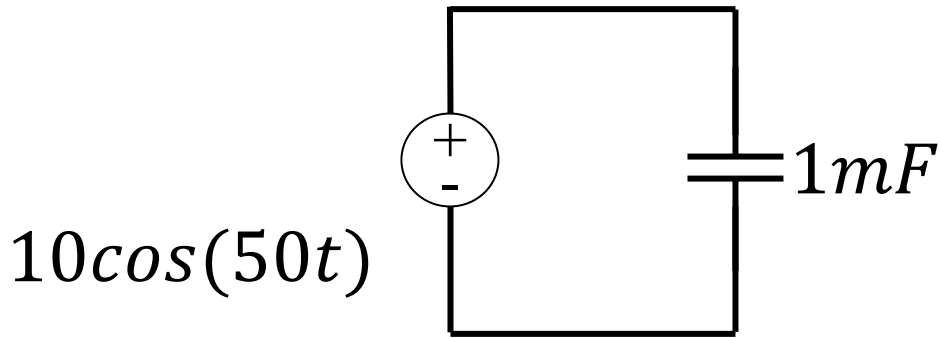


Peak Power: $5/2W$

Min Power: $-5/2W$

Avg Power: $0W$

Avg Reactive Power: $-5/2W$

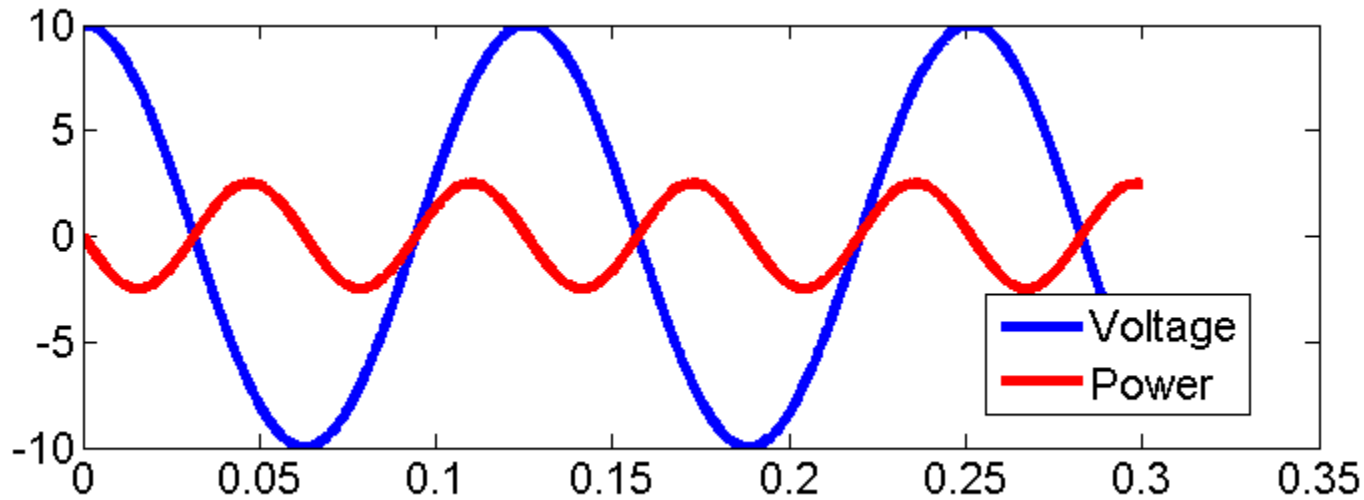

Like a frictionless car with perfect regenerative brakes, starting and stopping again and again and again

Note on Reactive Power

- “Providing” reactive power and “consuming” reactive power are physically the same thing
- Usually we say capacitors “provide” reactive power, which comes from our definition, whereas inductors “consume” reactive power

$$P_{\text{reactive}} = \frac{1}{2} \text{Im}[\hat{V} \hat{I}^*]?$$

- As you’ll see on HW7, capacitors and inductors can be chosen to get rid of reactive power

And that rounds out Unit 2

- We've covered all that needs to be covered on capacitors and inductors, so it's time to (continue) moving on to the next big thing

Back to Unit 3 – Integrated Circuits


- Last Friday, we started talking about integrated circuits
- Analog integrated circuits
 - Behave mostly like our discrete circuits in lab, can reuse old analysis
- Digital integrated circuits
 - We haven't discussed discrete digital circuits, so in order to understand digital ICs, we will first have to do a bunch of new definitions

Digital Representations of Logical Functions

- Digital signals offer an easy way to perform logical functions, using Boolean algebra
- Example: Hot tub controller with the following algorithm
 - Turn on heating element if
 - A: Temperature is less than desired ($T < T_{set}$)
 - **and** B: The motor is on
 - **and** C: The hot tub key is turned to “on”
 - OR
 - T: Test heater button is pressed


Hot Tub Controller Example

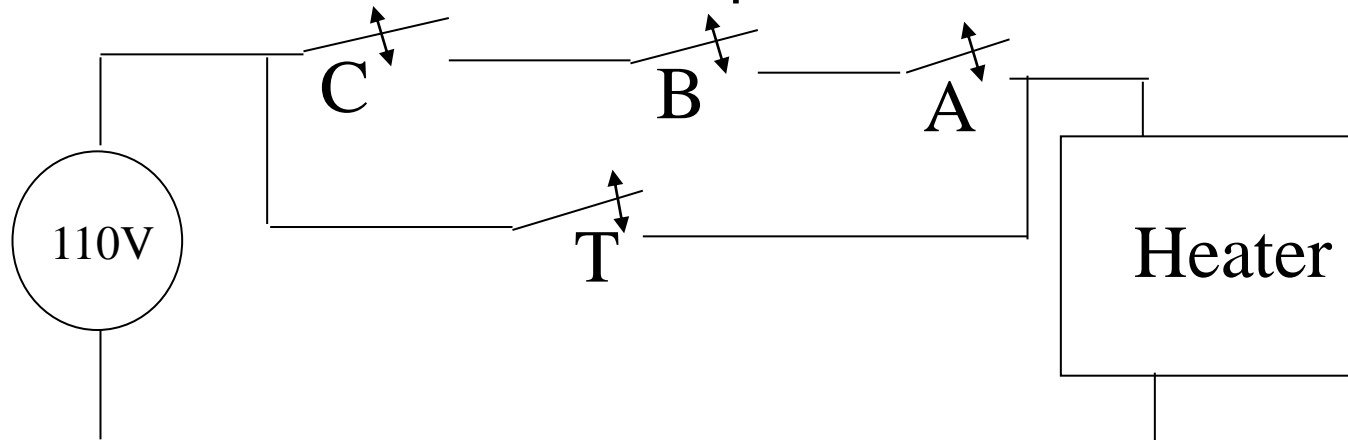- Example: Hot tub controller with the following algorithm
 - Turn on heating element if
 - A: Temperature is less than desired ($T < T_{set}$)
 - **and** B: The motor is on
 - **and** C: The hot tub key is turned to “on”
 - **OR**
 - T: Test heater button is pressed



Hot Tub Controller Example

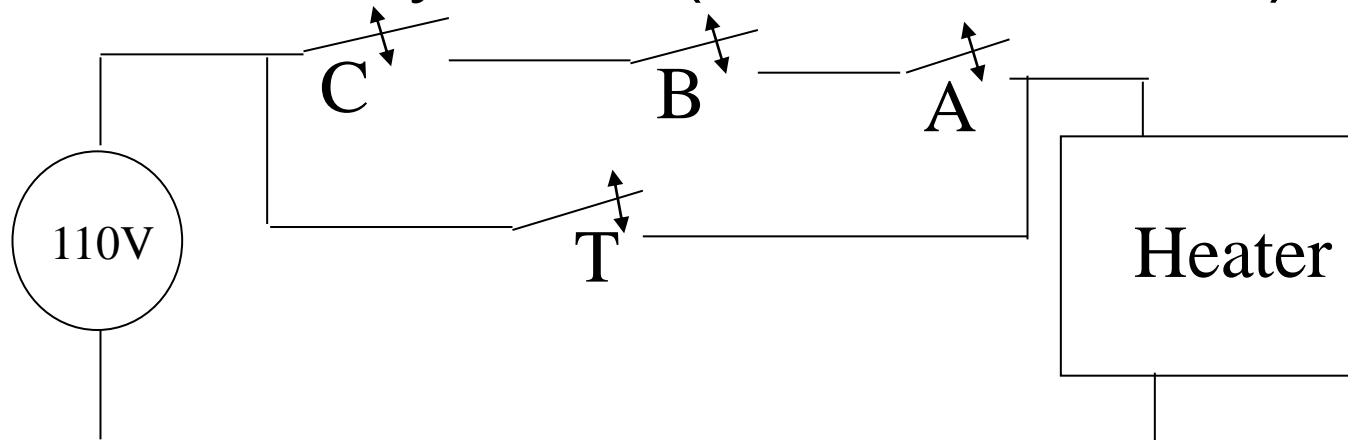- Example: Hot tub controller with the following algorithm
 - A: Temperature is less than desired ($T < T_{set}$)
 - B: The motor is on
 - C: The hot tub key is turned to “on”
 - T: Test heater button is pressed
- Or more briefly: $ON = (A \text{ and } B \text{ and } C) \text{ or } T$



Boolean Algebra and Truth Tables

- We'll next formalize some useful mathematical expressions for dealing with logical functions
- These will be useful in understanding the function of digital circuits

Boolean Logic Functions

- Example: $ON = (A \text{ and } B \text{ and } C) \text{ or } T$
- Boolean logic functions are like algebraic equations
 - Domain of variables is 0 and 1
 - Operations are “AND”, “OR”, and “NOT”
- In contrast to our usual algebra on real numbers
 - Domain of variables is the real numbers
 - Operations are addition, multiplication, exponentiation, etc

Examples

- In normal algebra, we can have
 - $3+5=8$
 - $A+B=C$
- In Boolean algebra, we'll have
 - $1 \text{ and } 0=0$
 - $A \text{ and } B=C$

Have you seen boolean algebra before?

- A. Yes
- B. No

Formal Definitions

- “not” is a unary operator (takes 1 argument)
- Returns 1 if its argument is 0, and 0 if its argument is 1, e.g.
 - not 0=1
- There exist many shorthand ways of writing the not operation e.g.
 - $\bar{0} = 1$
 - $0' = 1$
 - $\neg 0 = 1$
- I will use bar notation for consistency with the book.

Formal Definitions

- “and” is a binary operator [takes 2 arguments] which returns 1 if both if its arguments are 1, and 0 otherwise
- Many ways to write “A and B” in shorthand:

$$AB$$

$$A \cdot B$$

$$A \wedge B$$

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

- As a table, if $Z = AB$, then:

Formal Definitions

- “or” is a binary operator [takes 2 arguments] which returns 0 if either of its arguments are 1, and 0 otherwise
- Common ways to write “A and B” in shorthand:

$$A + B$$

$$A \vee B$$

- As a table, if $Z = A + B$, then:

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

Boolean Algebra and Truth Tables

- Just as in normal algebra, boolean algebra operations can be applied recursively, giving rise to complex boolean functions
- $Z=AB+C$
- Any boolean function can be represented by one of these tables, called a **truth table**

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Boolean Algebra

- Originally developed by George Boole as a way to write logical propositions as equations
- Now, a very handy tool for specification and simplification of logical systems

Simplification Example

- Z : Shine the bat signal
- C : Crime in progress
- B : Want to meet Batman
- T : Test bat signal
- $Z = C + \bar{C}B + \bar{C}\bar{B}T$
- Simpler expression:
 - $Z = C + B + T$

C	B	T	Z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Logic Simplification


- In CS61C and optionally CS150, you will learn a more thorough systematic way to simplify logic expression
- All digital arithmetic can be expressed in terms of logical functions
- Logic simplification is crucial to making such functions efficient
- You will also learn how to make logical adders, multipliers, and all the other good stuff inside of CPUs

Quick Arithmetic-as-Logic Example

- Assuming we have boolean input variables A_1, A_2, B_1, B_2 and boolean output variables Z_1, Z_2
- Let's say that each variable represent one digit of a binary number, we have 16 possibilities

Logic Gates



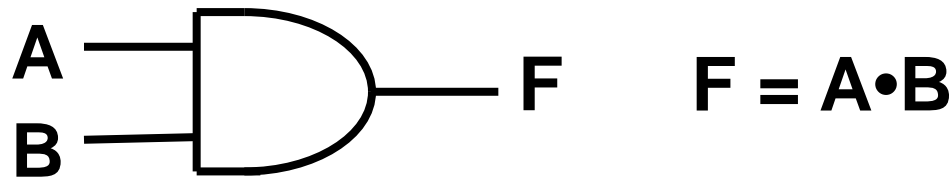
- Logic gates are the schematic equivalent of our boolean logic functions
- Example, the AND gate:



A	B	F
0	0	0
0	1	0
1	0	0
1	1	1


- If we're thinking about real circuits, this is a device where the output voltage is high if and only if both of the input voltages are high

Logic Functions, Symbols, & Notation

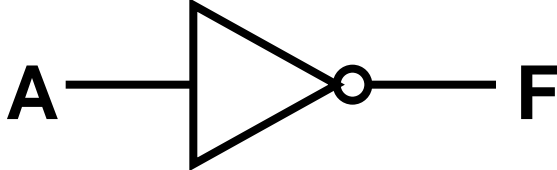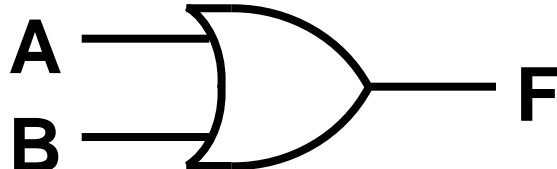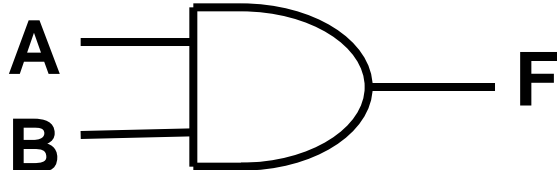
<u>NAME</u>	<u>SYMBOL</u>	<u>NOTATION</u>	<u>TRUTH TABLE</u>															
“NOT”		$F = \bar{A}$	<table border="1"> <thead> <tr> <th>A</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	F	0	1	1	0									
A	F																	
0	1																	
1	0																	
“OR”		$F = A+B$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	F	0	0	0	0	1	1	1	0	1	1	1	1
A	B	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
“AND”		$F = A \cdot B$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	F	0	0	0	0	1	0	1	0	0	1	1	1
A	B	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																

Multi Input Gates

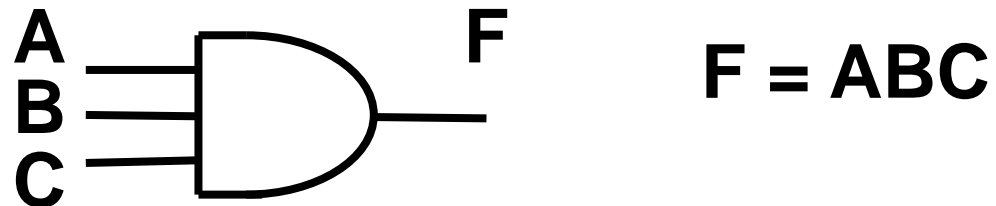- AND and OR gates can also have many inputs, e.g.



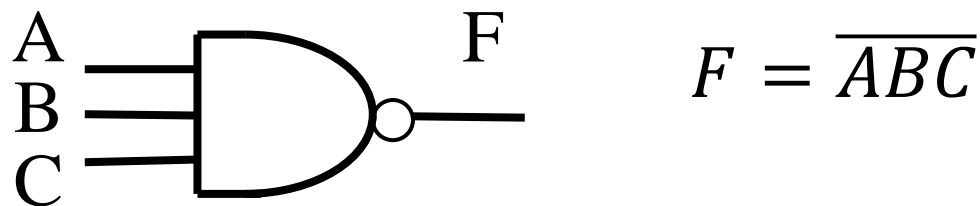- Can also define new gates which are composites of basic boolean operations, for example NAND:




Logic Gates

- Can think of logic gates as a technology independent way of representing logical circuits
- The exact voltages that we'll get will depend on what types of components we use to implement our gates
- Useful when designing logical systems
 - Better to think in terms of logical operations instead of circuit elements and all the accompanying messy math


Hot Tub Controller Example

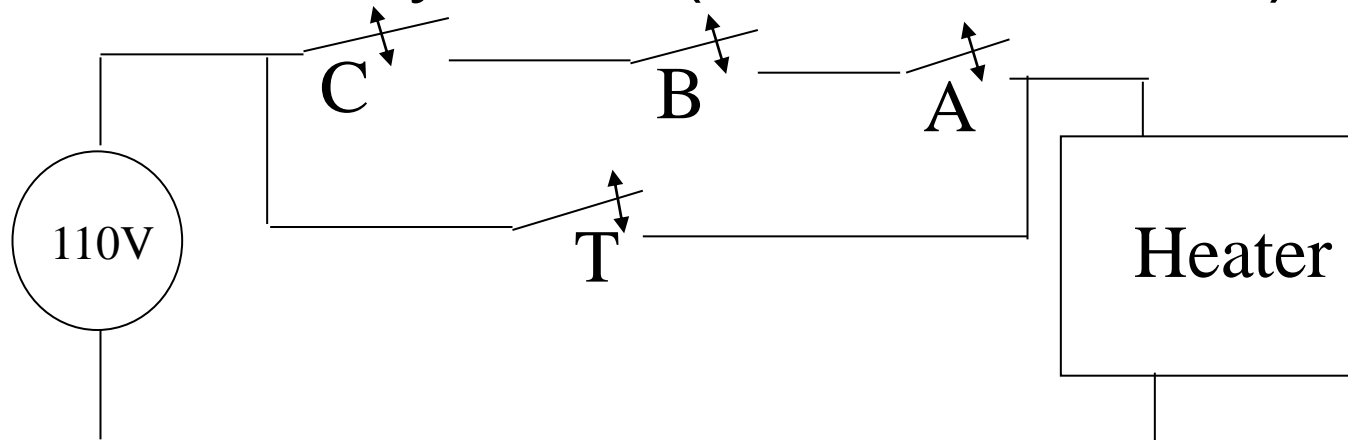- Example: Hot tub controller with the following algorithm
 - A: Temperature is less than desired ($T < T_{set}$)
 - B: The motor is on
 - C: The hot tub key is turned to “on”
 - T: Test heater button is pressed
- Or more briefly: $ON = (A \text{ and } B \text{ and } C) \text{ or } T$



Hot Tub Controller Example

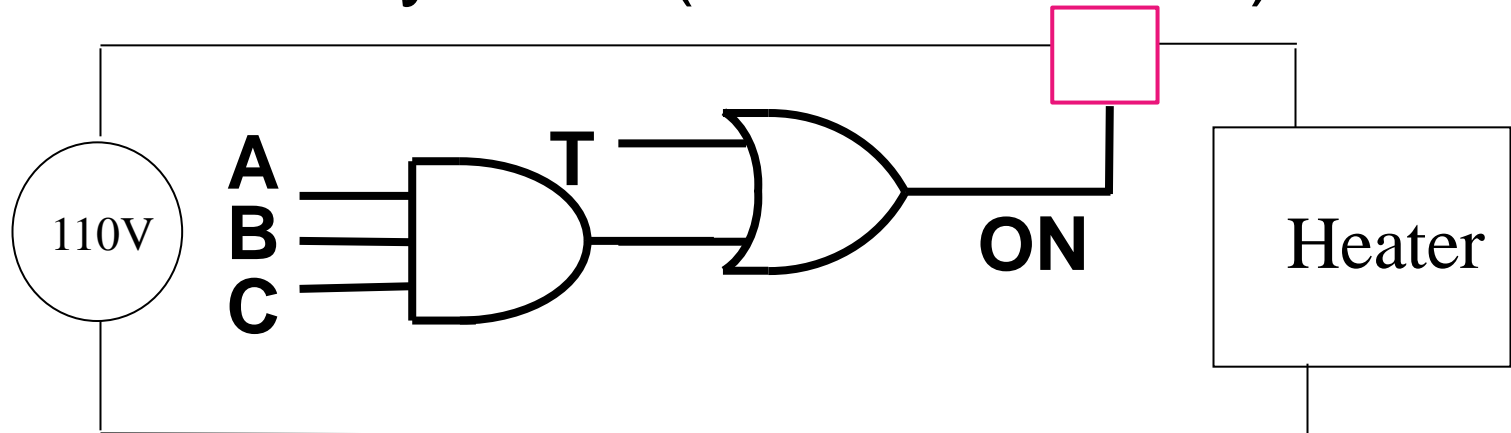- Example: Hot tub controller with the following algorithm
 - A: Temperature is less than desired ($T < T_{set}$)
 - B: The motor is on
 - C: The hot tub key is turned to “on”
 - T: Test heater button is pressed
- Or more briefly: $ON = (A \text{ and } B \text{ and } C) \text{ or } T$



How does this all relate to circuits?


- A digital circuit is simply any circuit where every voltage in the circuit is one of two values
 - V_{low} (typically ground) will represent boolean 0
 - V_{high} (in modern CPUs, approximately 1V, though you can set this on your computer) will represent boolean 1
- In truth, of course, values will vary continuously, but entire design is conceptualized as simply 1s and 0s

The “Static Discipline”

- We can think of the whole circuit as obeying a contract to always provide output voltages V_{low} and V_{high} at all outputs as long as the inputs follow these same rules
- Up to the circuit designer to ensure this specification is met
- In truth, voltages may be a little lower or higher than these contractual values
- However, as long as the output values are close enough, the deviations are unimportant

Many Possible Ways to Realize Logic Gates

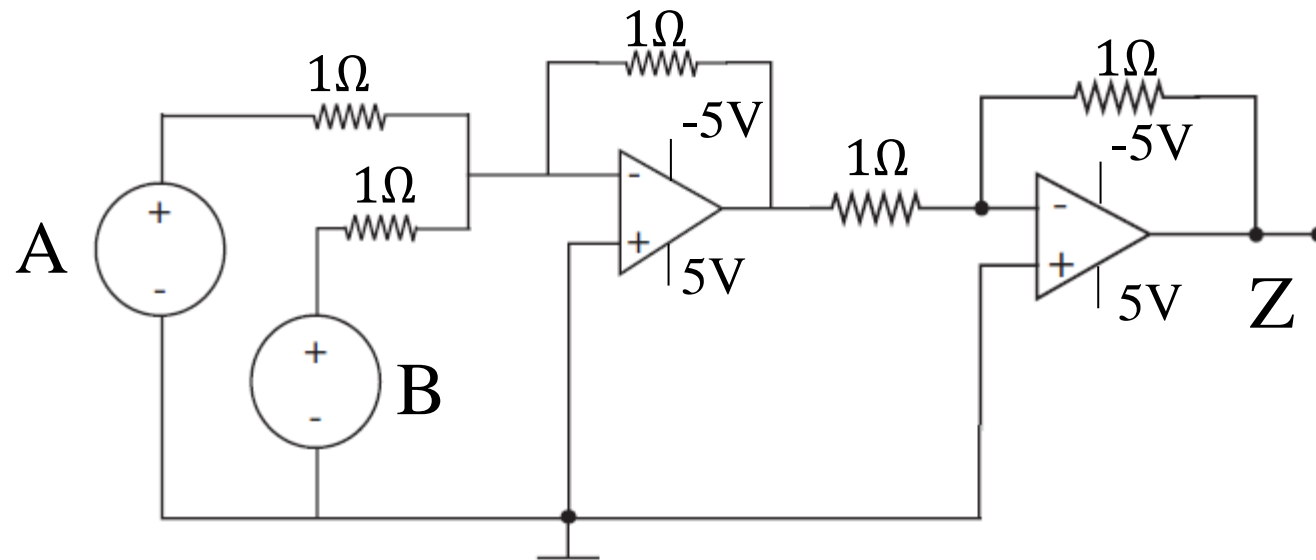- There are many ways to build logic gates, for example, we can build gates with op-amps




$$Z = f(A, B)$$

- Far from optimal
 - 5 resistors
 - Dozens of transistors
- Is this a(n):
 - A. AND gate
 - B. OR gate
 - C. NOT gate
 - D. Something else

Switches as Gates

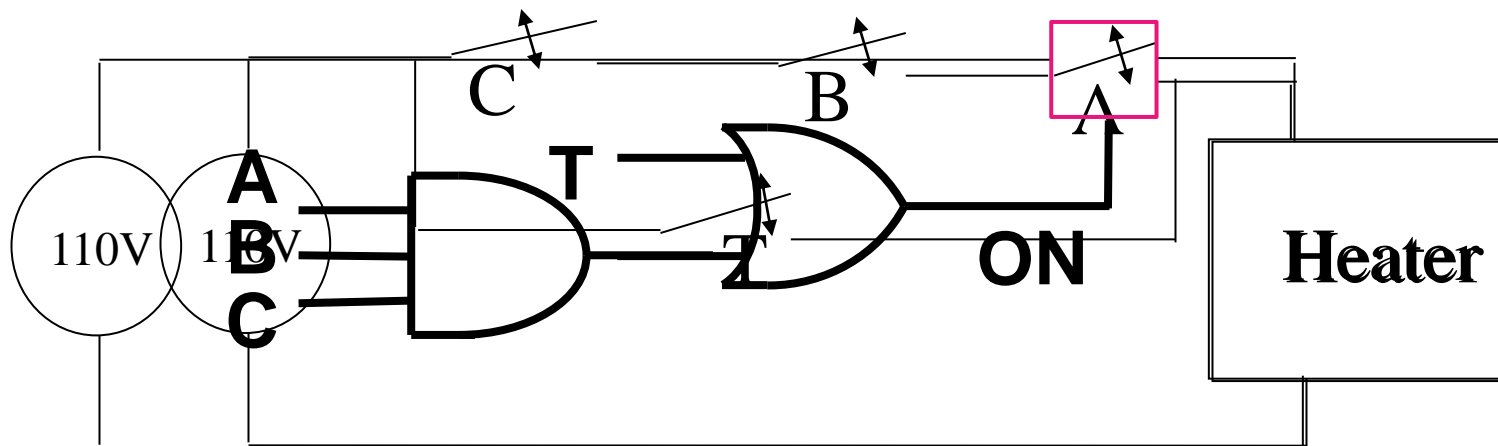- Example: Hot tub controller
- $ON = (A \text{ and } B \text{ and } C) \text{ or } T$
- Switches are the most natural implementation for logic gates




Relays, Tubes, and Transistors as Switches

- Electromechanical relays are ways to make a controllable switch:
 - Zuse's Z3 computer (1941) was entirely electromechanical
- Later vacuum tubes adopted:
 - Colossus (1943) – 1500 tubes
 - ENIAC (1946) – 17,468 tubes
- Then transistors:
 - IBM 608 was first commercially available (1957), 3000 transistors

Electromechanical Relay

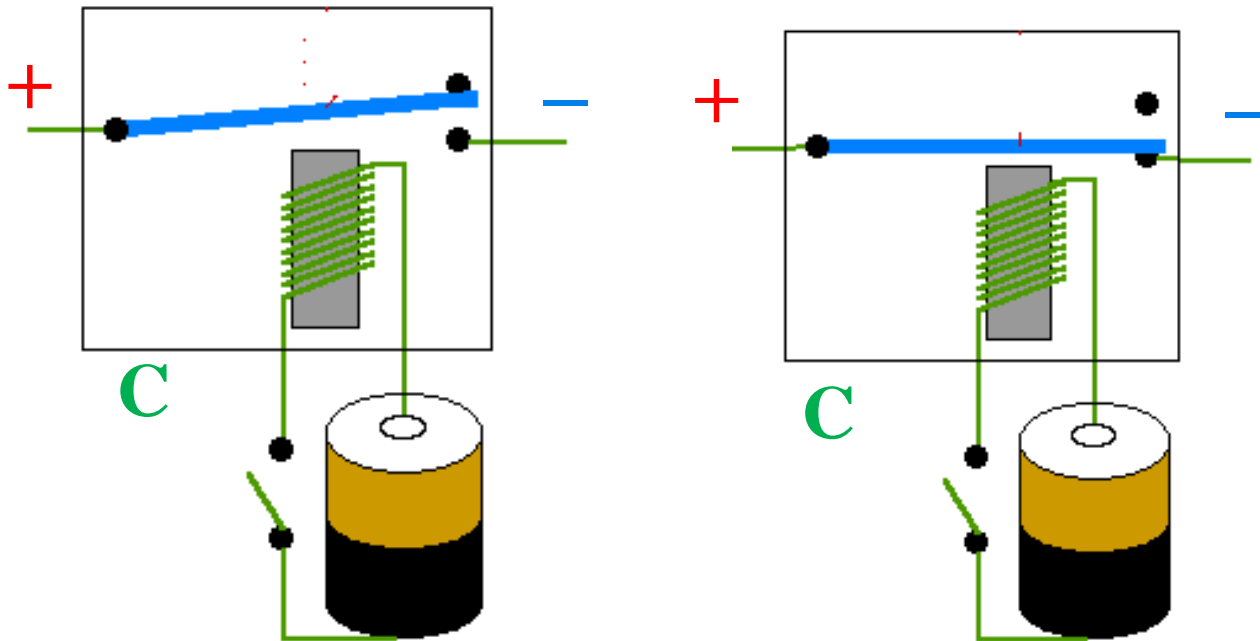- Inductor generates a magnetic field that physically pulls a switch down
- When current stops flowing through inductor, a spring resets the switch to the off position




- Three
Terminals:
+ : Plus
- : Minus
C : Control

Electromechanical Relay Summary

- “Switchiness” due to physically manipulation of a metal connector using a magnetic field
- Very large
- Moving parts
- No longer widely used in computational systems as logic gates
 - Occasional use in failsafe systems

Vacuum Tube

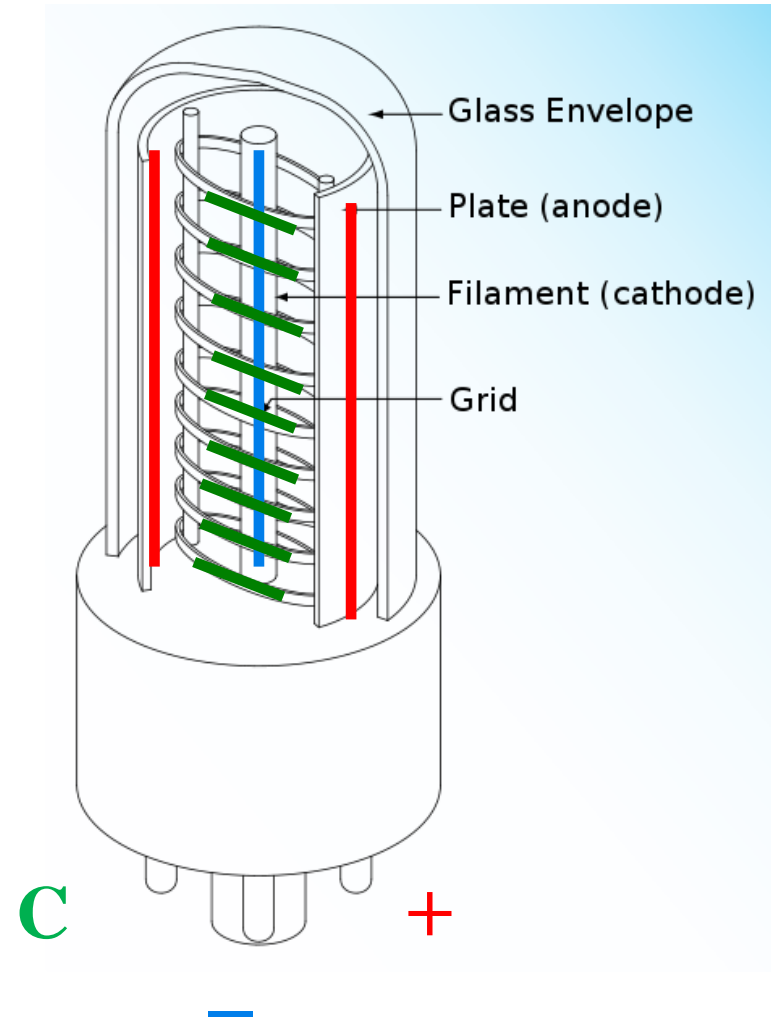- Inside the glass, there is a hard vacuum
 - Current cannot flow
- If you apply a current to the minus terminal (filament), it gets hot
- This creates a gas of electrons that can travel to the positively charged plate from the hot filament
- When control port is used, grid becomes charged
 - Acts to increase or decrease ability of current to flow from – to +




(Wikipedia)

Vacuum Tube Demo

Vacuum Tube Summary


- “Switchiness” is due to a charged cage which can block the flow of free electrons from a central electron emitter and a receiving plate
- No moving parts
- Inherently power inefficient due to requirement for hot filament to release electrons
- No longer used in computational systems
- Still used in:
 - CRTs
 - Very high power applications
 - Audio amplification (due to nicer saturation behavior relative to transistors)

Field Effect Transistor

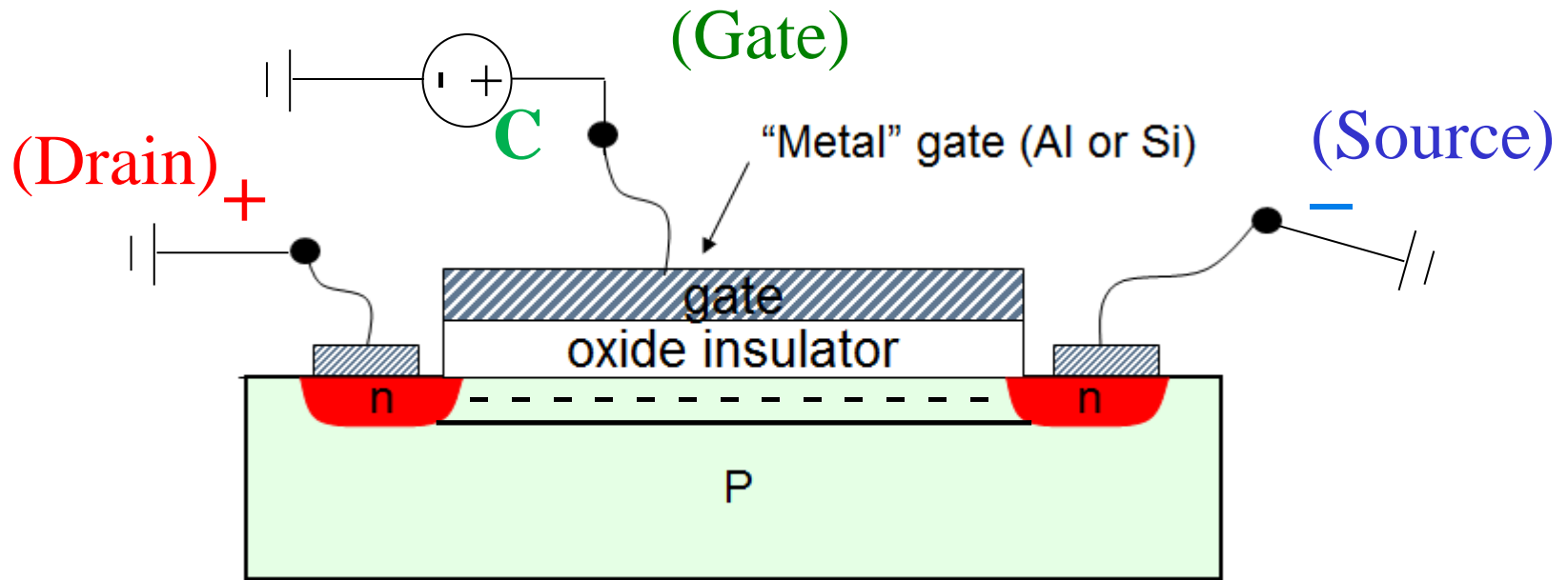


- P is (effectively) a high resistance block of material, so current can barely flow from + to -
- The n region is a reservoir of extra electrons (we will discuss the role of the n region later)
- When V_c is “on”, i.e. V_c is relatively positive, then electrons from inside the P region collect at bottom of insulator, forming a “channel”

Field Effect Transistor

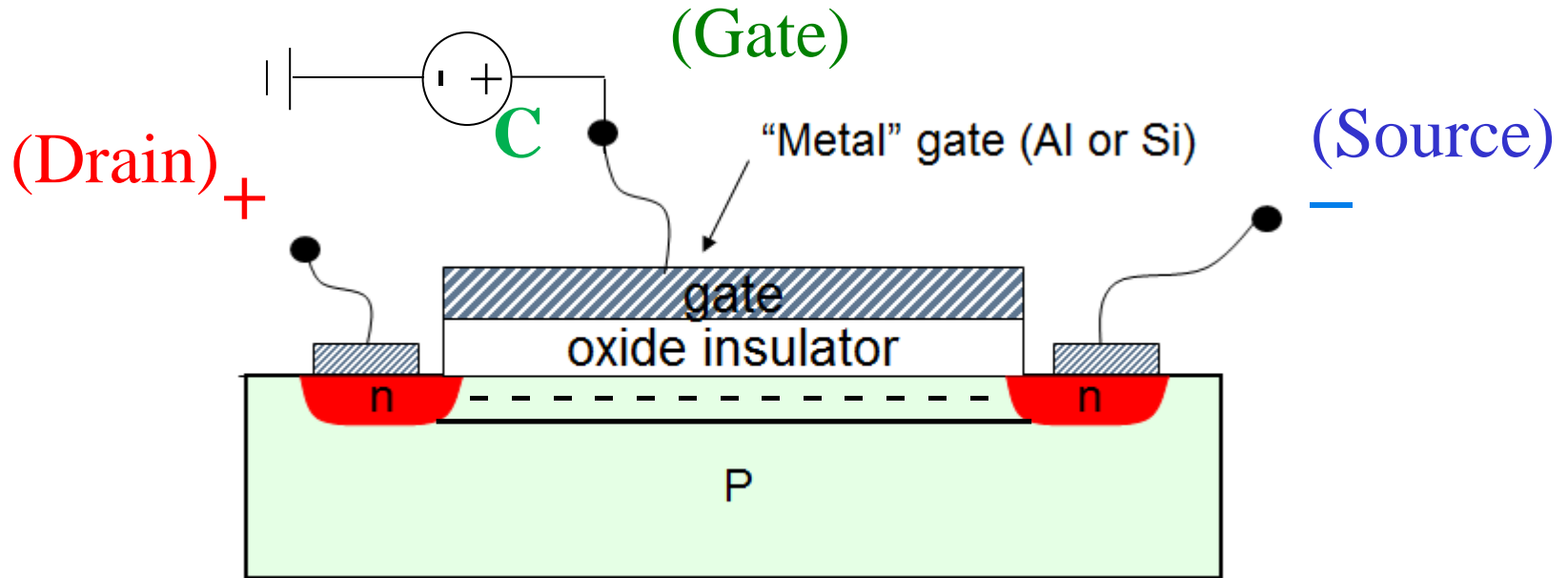

- When the channel is present, then effective resistance of P region dramatically decreases
- Thus:
 - When **C** is “off”, switch is open
 - When **C** is “on”, switch is closed

Field Effect Transistor

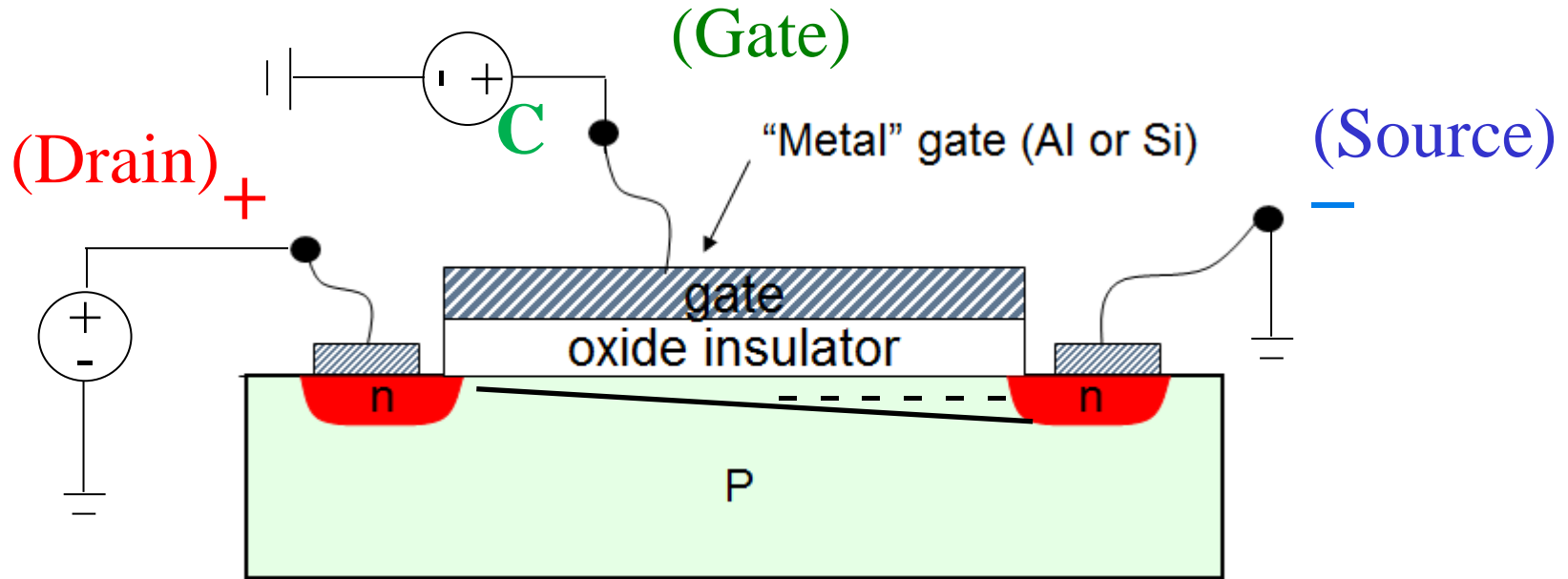



- If we apply a positive voltage to the plus side
 - Current begins to flow from + to -
 - Channel on the + side is weakened
- If we applied a different positive voltage to both sides?

Field Effect Transistor Summary

- “Switchiness” is due to a controlling voltage which induces a channel of free electrons
- Extremely easy to make in unbelievable numbers
- Ubiquitous in all computational technology everywhere



MOSFET Model

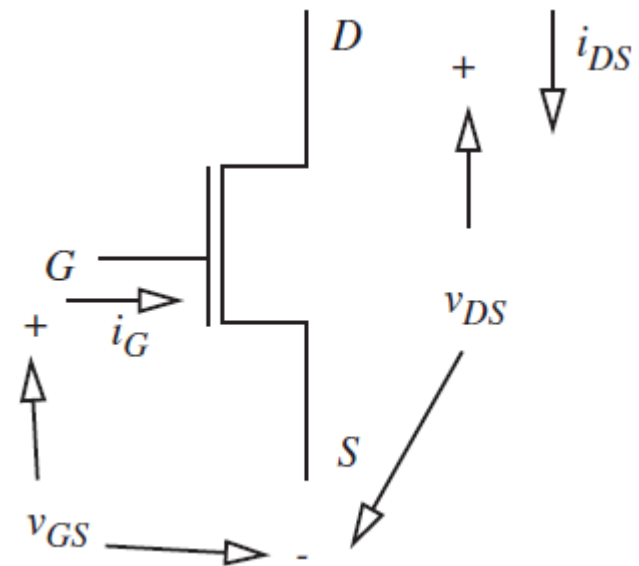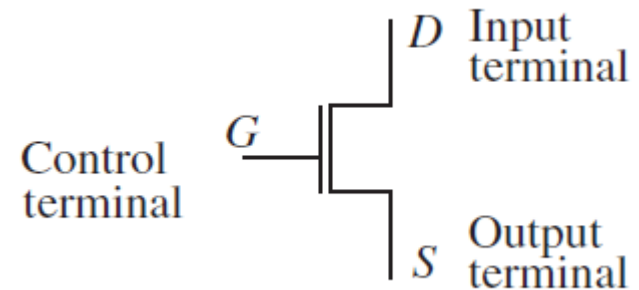- Schematically, we represent the MOSFET as a three terminal device
- Can represent all the voltages and currents between terminals as shown to the right






MOSFET Model

- What do you expect i_G to be?

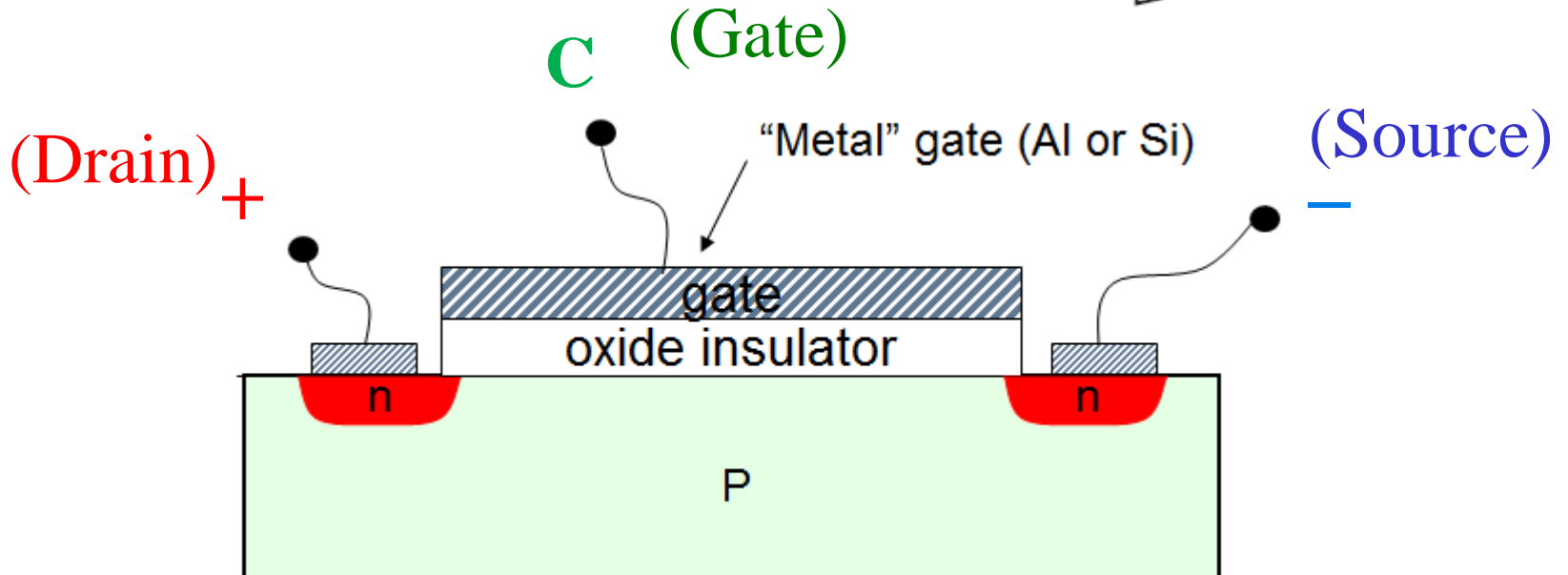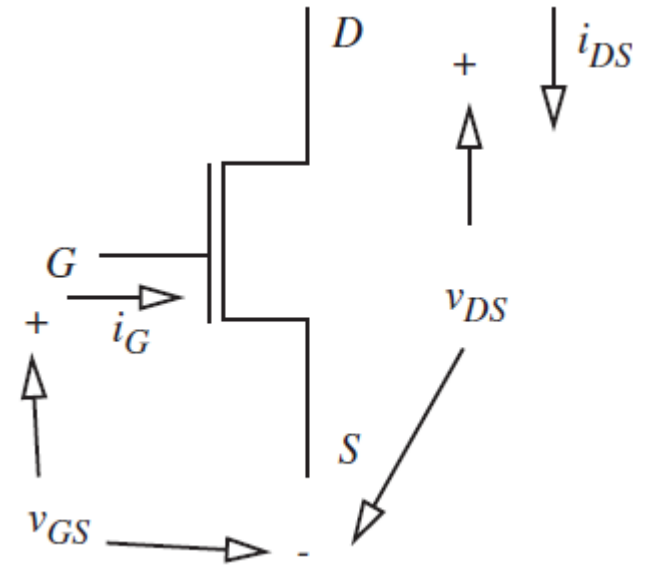


S Model of the MOSFET

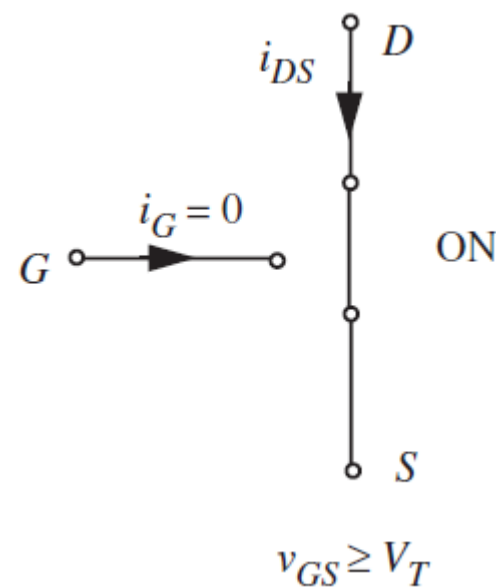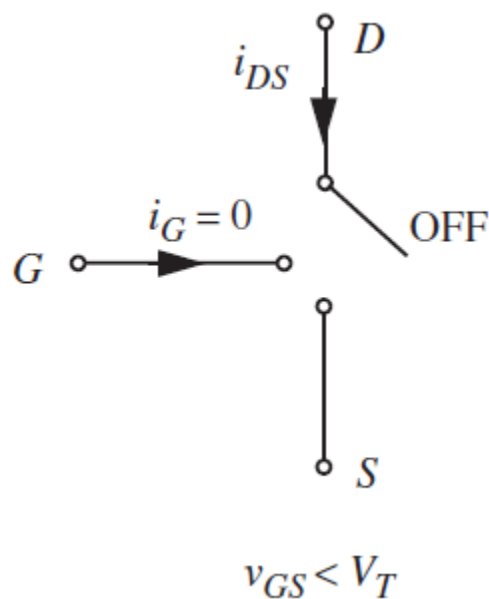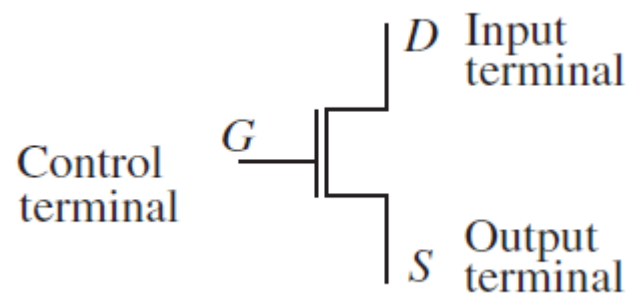- The simplest model basically says that the MOSFET is:
 - Open for $V_{GS} < V_T$
 - Closed for $V_{GS} > V_T$



Building a NAND gate using MOSFETs

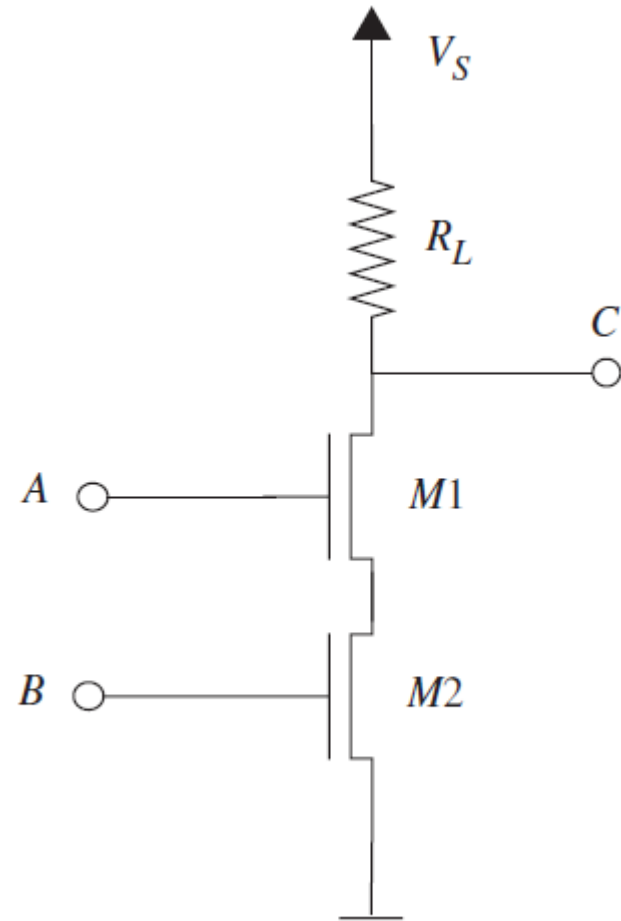- Consider the circuit to the right where V_S
- On the board, we'll show that $C = \overline{AB}$
- Demonstration also on page 294 of the book



That's it for today

- Next time, we'll discuss:
 - Building arbitrarily complex logic functions
 - Sequential logic
 - The resistive model of a MOSFET
- Until then, study