
EE40
Lecture 15
Josh Hug

7/30/2010

Logistics

- HW7 due Tuesday
- HW8 will be due next Friday
- Homeworks will be less mathematically intense starting with the second half of HW7
- Details on Project 2 demo and Mini-Midterm 3 details on Monday

Midterm 2

- I can show you your midterm 2 grade, but problem 5 needs regrading [most people will get 3 to 6 more points]
- At the moment, mean is 102 and standard deviation is 24
- First midterm was mean 103, standard deviation 20
- Some oochness will happen here


Logic Gates and Static Discipline

- (On the board before we started)

iClicker Warmup


- We're going to have a ton of iClicker questions today
- A quick warmup. Have you played Starcraft 2?
 - A. Yes
 - B. No
 - C. Starwhat?

Field Effect Transistor

 


- P is (effectively) a high resistance block of material, so current can barely flow from + to -
- The n region is a reservoir of extra electrons (we will discuss the role of the n region later)
- When V_C is “on”, i.e. V_C is relatively positive, then electrons from inside the P region collect at bottom of insulator, forming a “channel”

Field Effect Transistor

 

- When the channel is present, then effective resistance of P region dramatically decreases
- Thus:
 - When **C** is “off”, switch is open
 - When **C** is “on”, switch is closed

Field Effect Transistor

 

- If we apply a positive voltage to the plus side
 - Current begins to flow from + to -
 - Channel on the + side is weakened
- If we applied a different positive voltage to both sides?

Field Effect Transistor Summary



- “Switchiness” is due to a controlling voltage which induces a channel of free electrons
- Extremely easy to make in unbelievable numbers
- Ubiquitous in all computational technology everywhere

Discussion Today

- In discussion today, we'll go over the physics of MOSFETs for those of you who are curious
- Time permitting, we'll discuss at a future date in class as well (so yeah, it will be slightly redundant)



MOSFET Model

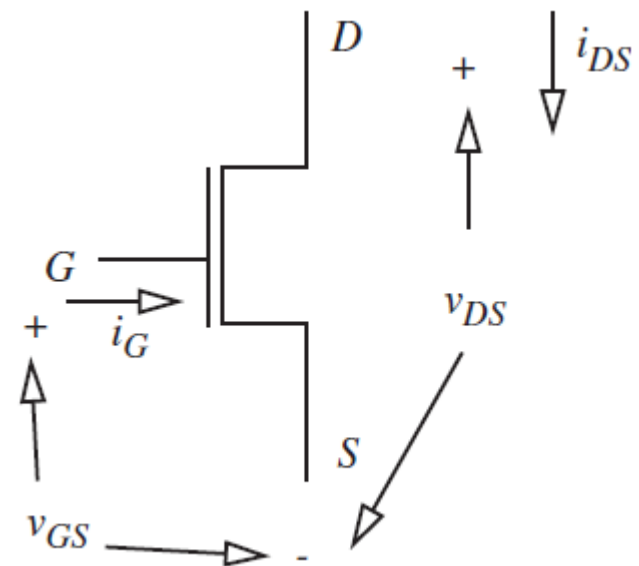 - Schematically, we represent the MOSFET as a three terminal device
- Can represent all the voltages and currents between terminals as shown to the right






MOSFET Model

- What do you expect i_G to be?

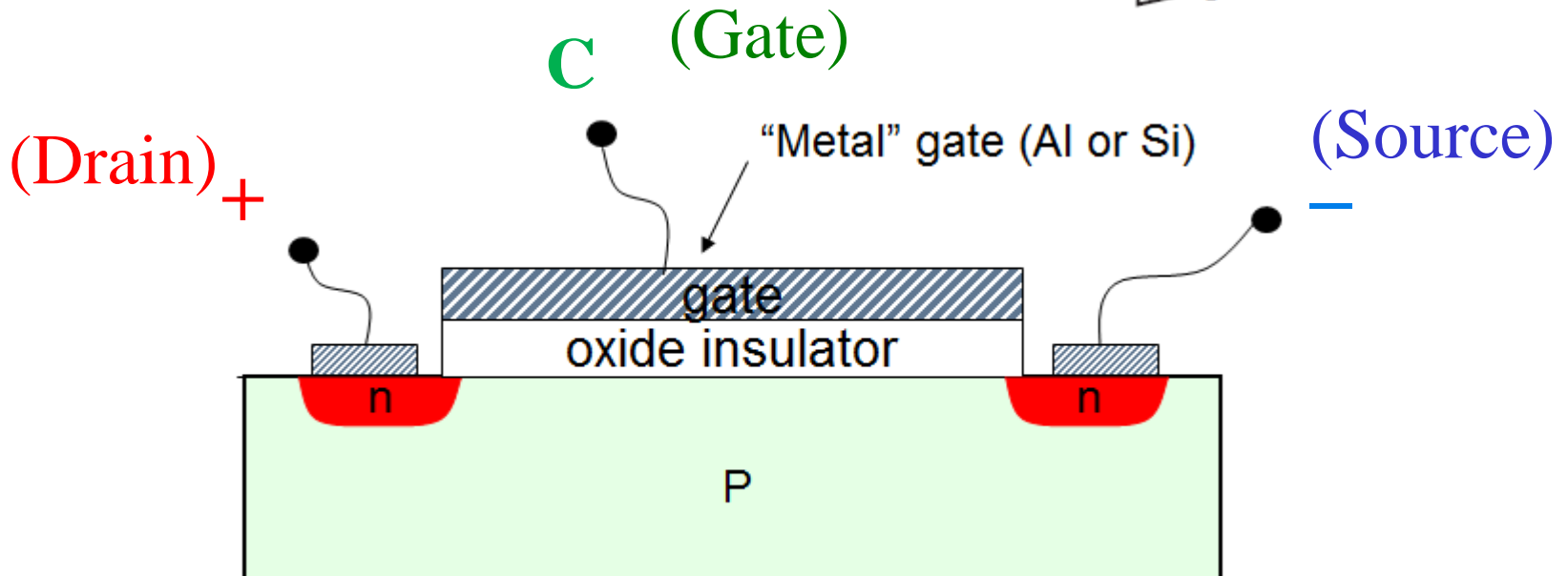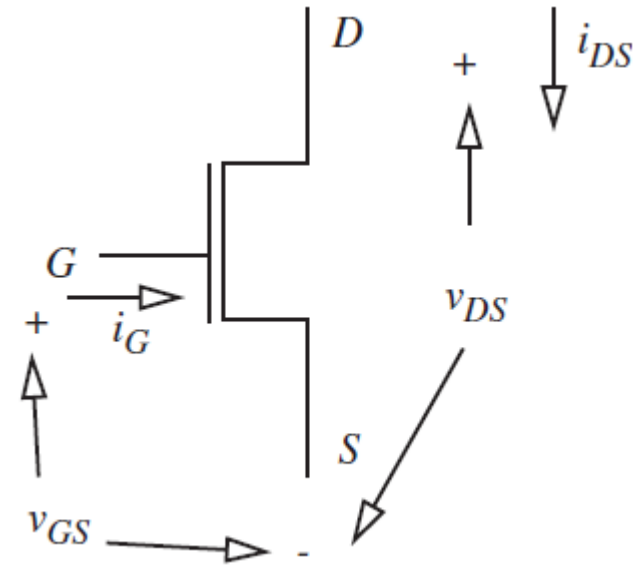



S Model of the MOSFET

   - The simplest model basically says that the MOSFET is:
 - Open for $V_{GS} < V_T$
 - Closed for $V_{GS} > V_T$



Building a NAND gate using MOSFETs

 
 
- Consider the circuit to the right where V_S
- On your worksheet, we'll show that $C = \overline{AB}$
- Demonstration also on page 294 of the book




MOSFET modeling

- MOSFET models vary greatly in complexity
- For example, an “ON” MOSFET has some effective resistance (not an ideal switch)
- We will progressively refine our model of the MOSFET
 - Will add capacitance later today
 - If we have time in the next 2 weeks, we will also talk about using MOSFETs as analog amplifiers which will necessitate an even better model

SR Model of the MOSFET

  

OFF State

 

ON State

$$i_{DS} = \frac{V_{DS}}{R_{ON}}, V_{GS} \geq V_T$$

$$= 0, \quad V_{GS} < V_T$$

[Has nothing to do with SR flip-flop]

NAND with the SR Model

- What is V_C when either of the inputs is low?
- Draw the equivalent circuit when both inputs are high. What is V_C ?


A. V_S

B. 0

C. V_S/R_L

D. $V_S \frac{2R_{ON}}{R_L + 2R_{ON}}$

E. $V_S \frac{R_L}{R_L + 2R_{ON}}$

 


NAND with the SR Model

- Assume static discipline requires $0 < V_{OL} < 0.5V$ and $4.5V < V_{OH} < 5V$
- Assume R_L is $100k\Omega$
- Choose a V_S such that the static discipline for V_{OH} is met:

 - A. $5V$
- B. $4.5V$
- C. $0.5V$
- D. $0V$


$$O_{\text{High}}: V_C = V_S$$
$$O_{\text{Low}}: V_C = V_S \frac{2R_{ON}}{R_L + 2R_{ON}}$$



NAND with the SR Model

- Assume static discipline requires $0 < V_{OL} < 0.5V$ and $4.5V < V_{OH} < 5V$
- Assume $R_L = 10k\Omega$ and $V_S = 5V$
- Choose an R_{ON} and R_L such that V_{OL} meets the static discipline
 
$$O_{\text{High}}: V_C = V_S$$
$$O_{\text{Low}}: V_C = V_S \frac{2R_{ON}}{R_L + 2R_{ON}}$$



Note: R_L is usually called a “Pull-up resistor”

Another SR Model Example


- Replace the left MOSFET with the equivalent circuit when A is high
- What is V_{GS} on the right NMOS if A is high?

A. $5V$

B. $5 \frac{1}{1+9.5}$

C. $5 \frac{1}{1+11}$


D. 0

 

$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Another SR Model Example

 
- When A is on,
$$V_{GS, right} = 5 \frac{1}{1+9.5} = 0.476V$$
- What is V_{OUT} when A is high?
 - A. $5V$
 - B. $5 \frac{1}{1+9.5}$
 - C. $5 \frac{1}{1+11}$
 - D. 0



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$


The power of digital circuits

 - At each stage, circuit **restores** the signal
- Can think of each MOSFET as diverting the 5V or 0V power supply into the next gate
- Tolerant to noise and manufacturing error




The power of digital circuits

 - How much noise could we tolerate on the input of the 2nd gate?
- On the input of the 3rd gate?



$$R_{on} = 1k\Omega$$

$$V_T = 1V$$

 


The power of digital circuits (literally)

- Like all circuits, digital circuits consume power
- Amount of power will be dependent on state of our MOSFET switches

Power Example

 
- What is the power dissipation when $A=1$, $B=1$, $C=0$?
- First, draw circuit with ON MOSFETS replaced with resistors
- Then, calculate P_s



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Power Example

 - In general, power consumption will depend on which inputs are high and which are low
- “Worst case analysis” is when we pick the set of inputs which consumes the most power




$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Static Power

- Using only NMOS to implement our gates will result in a gate which constantly eats up power
 - If you wire such a gate up on a breadboard, it will hum along using power all day
- Later today, we will see a technique called CMOS to avoid this static power dissipation
- But first, let's discuss delay

The SRC Model of an NMOS Transistor

 - So far, our NMOS implementation of logic gates allow for instantaneous switching
- In real life, of course, an NMOS implementation will take some non-zero time to switch




Green:
Inverter
Input

Red:
Inverter
Output



The SRC Model

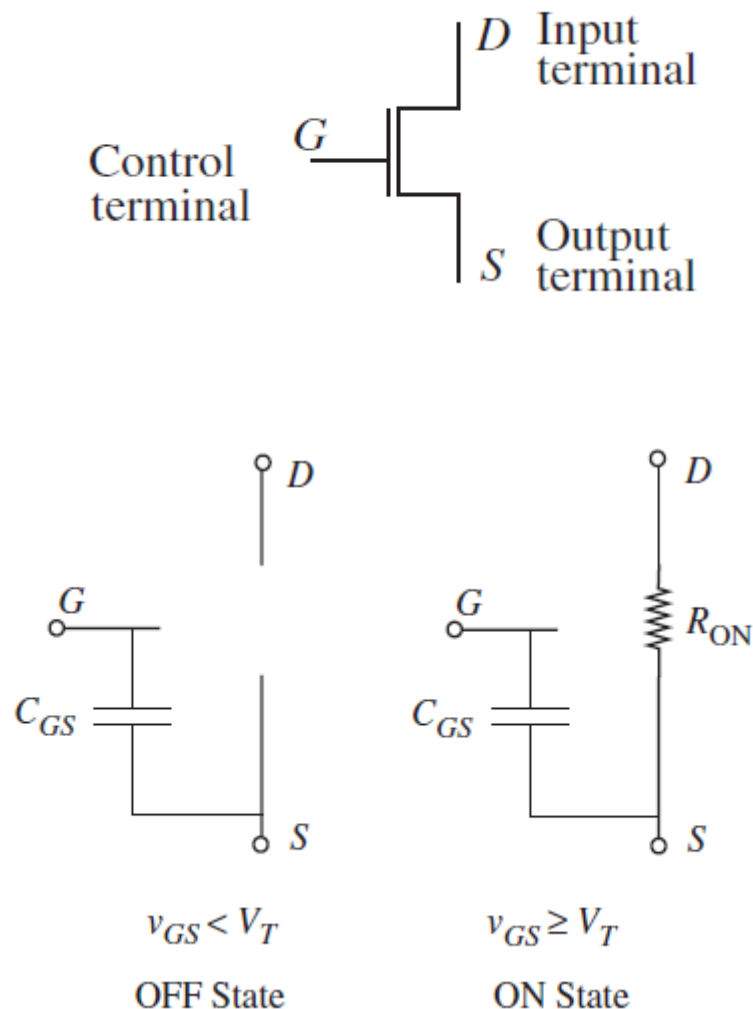- The SRC Model is almost identical to the SR model, except that each gate node has a capacitance
- Like SR model: open when OFF and resistive when ON
- Note that now i_G is non-zero!




The SRC Model

  - Useful for modeling:
 - Gate delay: Takes time to charge up
 - Dynamic power:
 $i_G \neq 0$



$$v_{GS} < V_T$$

OFF State

 


$$v_{GS} \geq V_T$$



ON State

SRC Model

 - Consider our familiar pair of inverters
- We're going to focus on the behavior of our left inverter
- Let's assume that both MOSFETs have a gate capacitance of 1pF or 10^{-12}F



SRC Model of our 2 Inverters

  

- We decide to ignore the function of the gate on the right, keeping it in mind only because we know we'll have to charge it

Analysis of SRC Model


- When the gate voltage V_{IN} has been less than V_T (i.e. the gate capacitor is not charged) for a long time, what is V_{G1} ?

A. $0V$

B. $5V$

C. $5 \frac{1}{1+9.5} V$

D. $5 \frac{1}{(1+9.5)10^{-12}} V$

 


$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Q8

Hug

Analysis of SRC Model

 
- Now assume V_{in} has been low for a long time and thus $V_{G1} = 5V$
- If the logic gate upstream of V_{in} rises above 1V, the SRC model of the left MOSFET says it should instantly switch to “ON”
- Draw the equivalent circuit on the MOSFET worksheet



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Analysis of SRC Model

 - If $V_{G1} = 5V$, and the $1k\Omega$ resistor suddenly appears at $t=0$
- What is $V_{G1}(\infty)$?
 - A. $0V$
 - B. $5V$
 - C. $5 \frac{1}{1+9.5} V$
 - D. $5 \frac{1}{(1+9.5)10^{-12}} V$




$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Timing Analysis of the SRC model

- What is the time constant for the discharge of V_{G1} ?

 
- A. 10^{-12}
- B. $10^{-12} \times 1000$
- C. $10^{-12} \times (9500 + 1200)$
- D. $10^{-12} \times (9500 \parallel 1200)$
- E. $2 \times 10^{-12} \times (9500 + 1200)$



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Timing Analysis of the SRC model

 - Since $V_{G1}(0) = 5V$, $V_{G1}(\infty) = 0.476V$, and $\tau \approx 1ns$, then:
- $V_{G1}(t) = (5 - 0.476)e^{-t/\tau} + 0.476$
- How long will it take for the next inverter in the chain to turn on?




$$R_{on} = 1k\Omega$$

$$V_T = 1V$$

$$\tau = 10^{-12} \times (9500 \parallel 1200) = 1.06 \times 10^{-9}$$

Timing Analysis of the SRC model


 
- $(5 - 0.476)e^{-t_{fall}/\tau} + 0.476 = 1$
- $-\tau \ln(0.1158) = t_{fall}$
- So $t_{fall} = 2.2ns$
- We call this the “**Fall Time**”: gives time for V_{G1} to fall from 5V to 1V



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Fall Time

  
- $(5 - 0.476)e^{-t/\tau} + 0.476 = 1$
- $\tau \approx 10^{-9}$
- Gives: $t_{fall} = 2.2ns$



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Timing Analysis of the SRC model

 
- How do we find the **Rise Time**?
- Have to replace by new equivalent circuit where:
 - Capacitor is initially discharged (0.476 V)
 - Switch is open



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Timing Analysis of the SRC model

 - How do we find the **Rise Time**?
- Have to replace by new equivalent circuit where:
 - Capacitor is initially discharged (0.476 V)
 - Switch is open
- $V_{G1} = (0.476 - 5)e^{-t/\tau} + 5$
- $\tau = 10^{-12} \times 9500 \approx 10ns$



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$


Timing Analysis of the SRC model

- $V_{G1} = (0.476 - 5)e^{-t/\tau} + 5$
 $\tau = 10^{-12} \times 9500 \approx 10ns$

- $(0.476 - 5)e^{-t_{rise}/\tau} + 5 = 1$

$$-\tau \ln(0.884) = t_{rise}$$



- $t_{rise} = 1.2ns$

 

$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Timing Analysis of the SRC model

 
 
- $V_{G1} = (0.476 - 5)e^{-t/\tau} + 5$
- $\tau \approx 10^{-12} \text{ s}$
- $t_{rise} = 1.2 \text{ ns}$



$$R_{on} = 1 \text{ k}\Omega$$
$$V_T = 1 \text{ V}$$

Propagation Delay

  
- Rise and Fall Time are also called “Propagation Delays”




- Gives “delay time” between when the logical input changes and the logical output changes
- Book calls them $t_{pd,1\rightarrow 0}$ and $t_{pd,0\rightarrow 1}$

Reminder of Where We Started

Wanted to study gate delay of:

 

So used SRC model:

 


Which implements:



Giving delay of LEFT gate!


Using Propagation Delays

 - $t_{rise} = t_{pd,0 \rightarrow 1} = 1.2ns$
- $t_{fall} = t_{pd,1 \rightarrow 0} = 2.2ns$
- Suppose A has been zero a long time and switches to 1
 - How long does it take for G_1 to go to 0?
 - How long does it take for OUT to go to 1?




Propagation Delays

 - In general $t_{pd,0 \rightarrow 1}$ is not equal to $t_{pd,1 \rightarrow 0}$
- Thus, we usually just take the maximum and call that the propagation delay of the gate
- $t_{pd} = 2.2ns$
- Means that no matter what input you give the gate, output will be correct within $2.2ns$



Bonus Question for CS61C Veterans

 
- Assume now that the rise and fall times of both gates are $2.2ns$
- Assume that we have a register driving “A” and a register receiving “OUT”
- Assume the registers operate instantaneously
- What is the minimum clock time if this very boring buffer is our longest pipeline stage?



-
- This is where we stopped

Power in the SRC Model


 
- **Static power** in the SRC Model is exactly as SR Model, compare:



- We're also interested in the **dynamic power** while capacitance is charging
- Algebra is a bit involved. We'll outline the concept. Book has a very thorough treatment in sections 11.1 through 11.3



Dynamic Power in NMOS Circuits

  - When our inverter is going from **low to high**, we have the circuit on the left:
- In general, looks like circuit on the right:




Dynamic Power in NMOS Circuits

  - When our inverter is going from **high to low**, we have the circuit on the left:
- In general, looks like circuit on the right:




Dynamic Power

 - Worst case is that inverter is driven by a sequence of 1s and 0s
 - Circuit constantly switching behavior
 - Gate capacitor constantly charging and discharging




Charges up towards V_S

 


Discharges down towards $V_S \frac{R_{ON}}{R_{ON} + R_L}$

 Problem Setup

- V_{in} is
 - 0 for some time T_1
 - Dissipates some energy w_1
 - 1 for some time T_2
 - Dissipates some energy w_2
- $P = \frac{w_1 + w_2}{T_1 + T_2}$
- See 11.1 through 11.3 for derivation



Charges up towards V_S

 


Discharges down towards $V_S \frac{R_{ON}}{R_{ON} + R_L}$

Solution

$$\bar{p} = \frac{V_S^2}{2(R_L + R_{ON})} + \frac{V_S^2 R_L^2 C_L}{(R_L + R_{ON})^2 T}$$

$$p_{\text{static}} = \frac{V_S^2}{2(R_L + R_{ON})}$$
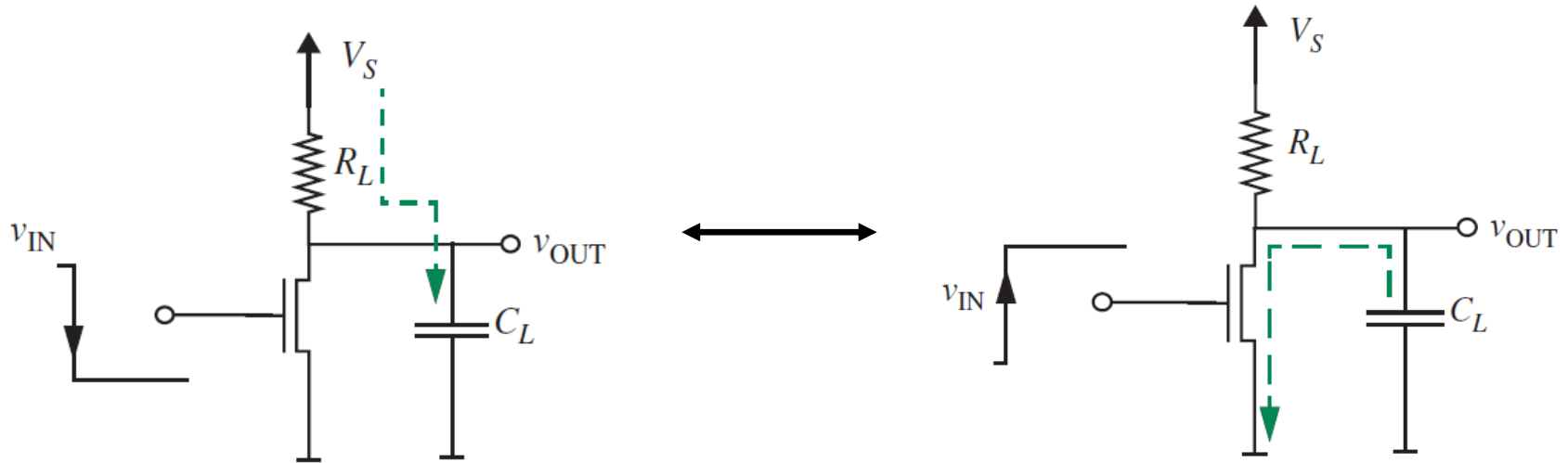
$$p_{\text{dynamic}} = \frac{V_S^2 R_L^2 C_L}{(R_L + R_{ON})^2 T}$$




Avoiding Static Power Loss



- Next we will talk about CMOS, which stands for Complementary MOS
- So far, all of our transistors have been NMOS transistors, where they are on if $V_{GS} \geq V_T$
- Next, we will discuss a new type of FET transistor called a PMOS
- Only difference is that they will be on when $V_{GS} \leq V_T$

PMOS Transistor

 - Drawn with a bubble at the input:
- Usually drawn with source on top and drain on bottom (for reasons that will become clear)
- Just as before, have ON and OFF states, now on when




$$V_{GS} \leq V_T$$

  

Anything logical we can do with NMOS...

- ...we can do with PMOS
- Example, we can build an inverter, try it for 60 seconds or so on the worksheet using a PMOS, 5V source, ground, and resistor
- Assume input signal is 0V or 5V and $V_T = -1V$

Here: R_L acts as a pulldown resistor

 


Analysis of PMOS Logic

- We could go through and repeat everything we did for NMOS, but it would be almost exactly the same thing
- Instead, we're now going to use NMOS and PMOS in a clever way


CMOS Inverter

 - Two complementary implementations of the same logic function
- When V_{IN} is high:
 - Path to ground is closed
 - Path to V_S is open




CMOS Inverter

 - When V_{IN} is high:
 - Path to ground is closed
 - Path to V_S is open
- Huge resistance on open PMOS acts as a pull-up resistor




CMOS Inverter

 - When V_{IN} is low:
 - Path to ground is open
 - Path to V_S is closed
- Huge resistance on open NMOS acts as a pull-down resistor




Static Power in CMOS

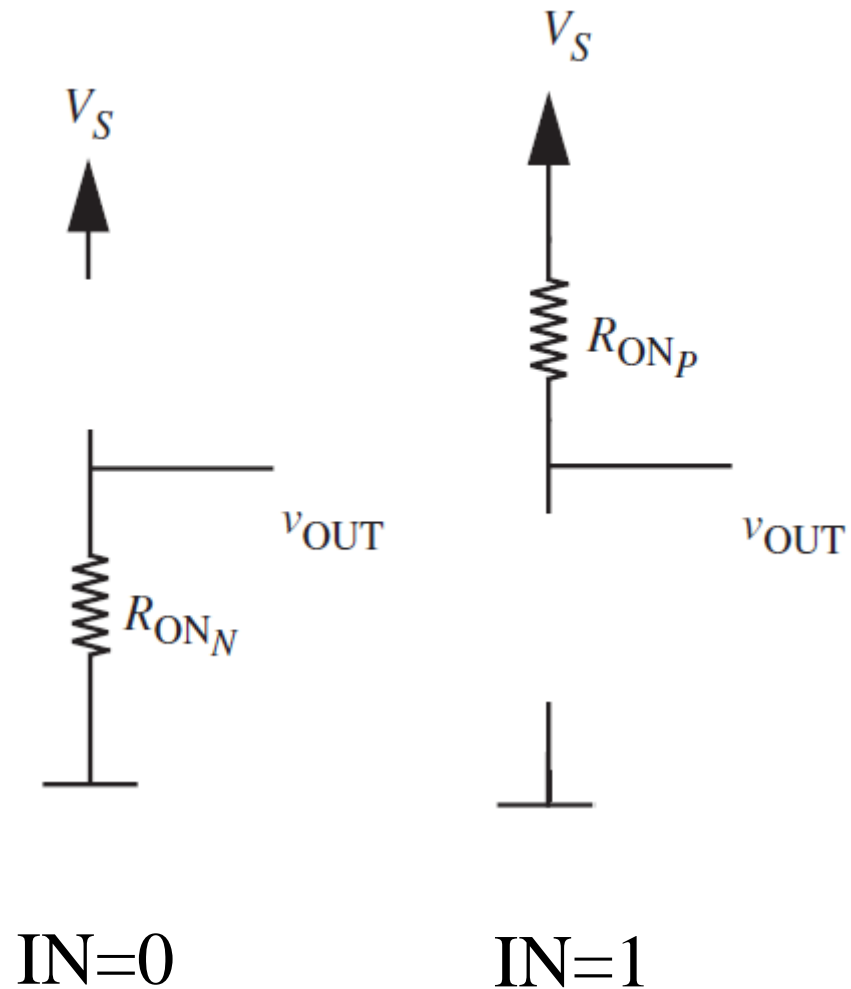- What is the static power consumed by this CMOS inverter when $I_N=0$?
- When $I_N=1$?
- In reality, as gate insulator gets thinner, there is a significant leakage component



Dynamic Power in CMOS

 - **Load power:** Since our CMOS gates will be driving capacitive loads, they will still draw power when switching (since power is provided to the load)




Dynamic Power in CMOS

- **Leakage Power:**

Unless you're careful about timing, both MOSFETs could be closed at the same time

 - Power flows directly from V_S to ground



- Even if timing is perfect, both transistors will at some point be “weakly on” – **subthreshold leakage**

Dynamic Power

- These days, subthreshold leakage is a big issue
 - Thresholds have been reduced to decrease switching times
 - Reduced thresholds mean leakier MOSFETs
- In this class, we won't analyze this case, but be aware that in the world of digital integrated circuits, it plays a big role

CMOS

- CMOS Summary:
 - No need for a pull-up or pull-down resistor
 - Though you can avoid this even with purely NMOS logic (see HW7)
 - Greatly reduced static power dissipation vs. our simple NMOS only logic
 - In reality, thin gate oxides lead to some static non-zero i_G , so static power is not zero
 - Dynamic power is still hugely significant
 - Uses twice the number of transistors as our simple purely NMOS logic



Implementation of Complex Gates Using NMOS and CMOS

- In class today, we've discussed analysis of NMOS and CMOS circuits
- Haven't discussed how to design them
- Luckily, it is easy


That's it for today

Extra Slides

SR Model of the PMOS MOSFET

  

OFF State

 

ON State

$$i_{DS} = \frac{V_{DS}}{R_{ONp}}, V_{GS} \leq V_T$$

$$= 0, V_{GS} > V_T$$

No, has nothing to do with SR flip-flop