
EE40
Lecture 16
Josh Hug

8/02/2010

Logistics

- HW7 due tomorrow
- HW8 will be due Friday
- Mini-midterm 3 next Wednesday
 - 80/160 points will be a take-home set of design problems which will utilize techniques we've covered in class
 - Handed out Friday
 - Due next Wednesday
 - Other 80/160 will be an in class midterm covering HW7 and HW8
- Final will include Friday and Monday lecture
 - Design problems will provide practice

Project 2

- Active filter lab and Booster lab due this week
 - For Booster lab, ignore circuit simulation, though it may be instructive to try the Falstad simulator
- Project 2 due next Wednesday

Design Problems

- **ALL WORK MUST BE DONE COMPLETELY SOLO!**
- Maximum allowed time will be **5 hours**
 - Will be written so that it can be completed in approximately 2 hours
- Allowed resources:
 - May use any textbook (incl. Google Books)
 - Anything posted on the EE40 website
 - Only allowed websites are Google Books, wikipedia, and EE40 websites
 - Not allowed to use other websites like facebook answers, yahoo answers, etc. even if you are reading other people's responses
 - When in doubt, email me or text me
 - We will be very serious about cheating on this!

Example Design Problem

- Design a circuit which will sum three sinusoidal input voltages and attenuate any frequencies above 10,000 Hz by at least 20 dB

Project 2



- For those of you who want to demo Project 2, we'll be doing demos in lab on Wednesday
 - Either at 1 PM after mini-midterm
 - Or at 2 PM during usual lab period
 - Opinions?

Interactive Lecture Question

- Did you like the interactive worksheet intensive MOSFET lecture?
 - A. Yes, it was extremely useful and I highly prefer this type of lecture
 - B. Yes, it was useful, but the usual 1-way lecture is fine
 - C. No real opinion
 - D. Didn't like it
 - E. Hated it

MOSFET Model

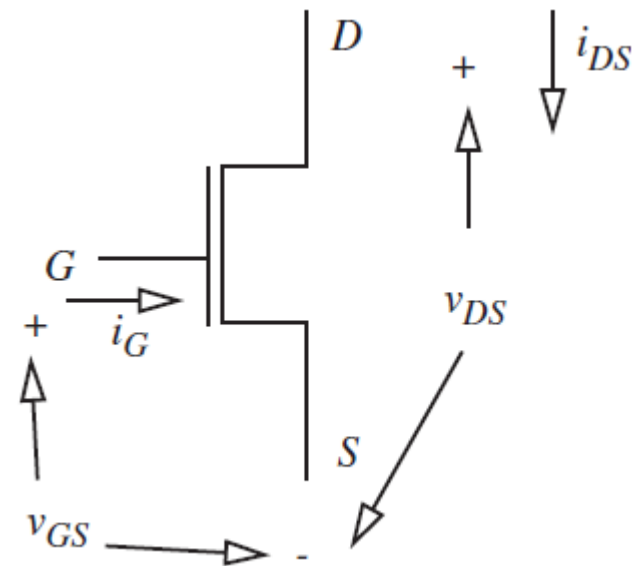 - Schematically, we represent the MOSFET as a three terminal device
- Can represent all the voltages and currents between terminals as shown to the right






MOSFET modeling



- MOSFET models vary greatly in complexity
- **S Model:** Good for explaining MOSFETs to someone with no EE knowledge
- **SR Model:** Includes effective resistance of a MOSFET. Good for understanding how to choose pull-up resistance
- **SR Model:** Include gate capacitance. Good for understanding dynamic power and gate delay

S Model of the MOSFET

   
- The simplest model basically says that the MOSFET is:
 - Open for $V_{GS} < V_T$
 - Closed for $V_{GS} > V_T$



SR Model of the MOSFET

  

OFF State

 

ON State


$$i_{DS} = \frac{V_{DS}}{R_{ON}}, V_{GS} \geq V_T$$

$$= 0, \quad V_{GS} < V_T$$

[Has nothing to do with SR flip-flop]



The SRC Model

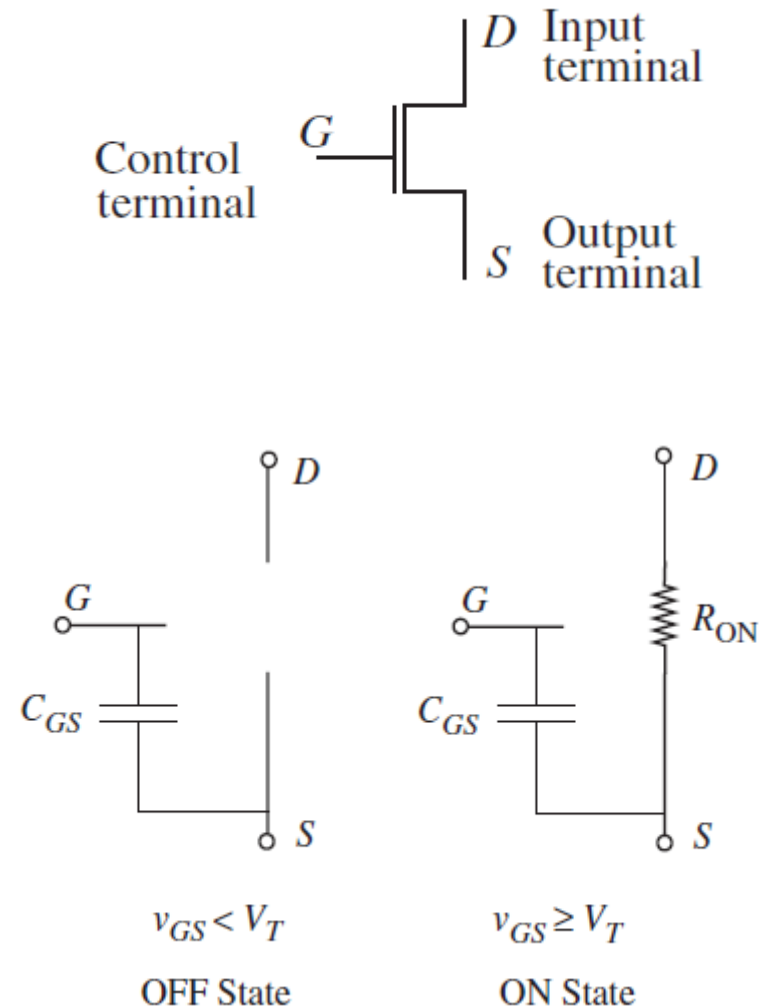- The SRC Model is almost identical to the SR model, except that each gate node has a capacitance
- Like SR model: open when OFF and resistive when ON
- Note that now i_G is non-zero!




The SRC Model

  - Useful for modeling:
 - Gate delay: Takes time to charge up
 - Dynamic power:
 $i_G \neq 0$



$$v_{GS} < V_T$$

OFF State

 


$$v_{GS} \geq V_T$$



ON State

SRC Model

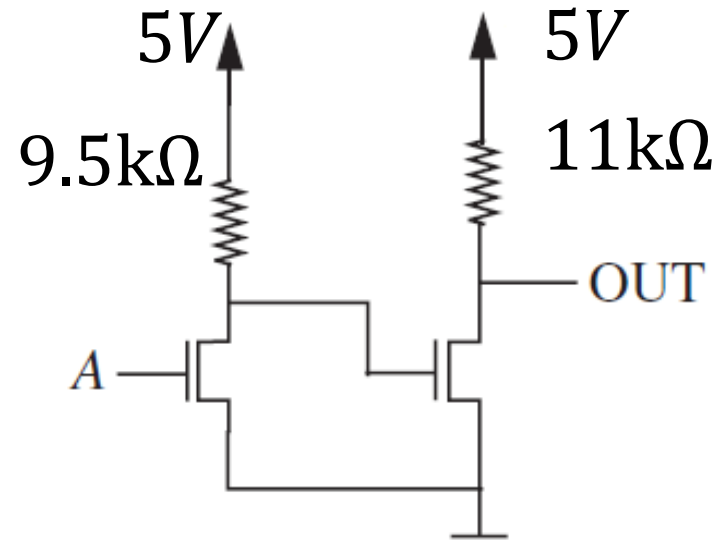- Consider our familiar pair of inverters
- We're going to focus on the behavior of our left inverter
- Let's assume that both MOSFETs have a gate capacitance of 1pF or 10^{-12}F




SRC Model of our 2 Inverters

  

- We decide to ignore the function of the gate on the right, keeping it in mind only because we know we'll have to charge it

Timing Analysis of the SRC model

 - Since $V_{G1}(0) = 5V$,
 $V_{G1}(\infty) = 0.476V$, and
 $\tau \approx 1ns$, then:
- $V_{G1}(t) =$
 $(5 - 0.476)e^{-t/\tau} + 0.476$
- How long will it take for
the next inverter in the
chain to turn on?




$$R_{on} = 1k\Omega$$

$$V_T = 1V$$

$$\tau = 10^{-12} \times (9500 \parallel 1000) = 1.06 \times 10^{-9}$$

Timing Analysis of the SRC model


 
- $(5 - 0.476)e^{-t_{fall}/\tau} + 0.476 = 1$
- $-\tau \ln(0.1158) = t_{fall}$
- So $t_{fall} = 2.2ns$
- We call this the “**Fall Time**”: gives time for V_{G1} to fall from 5V to 1V



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Fall Time

  
- $(5 - 0.476)e^{-t/\tau} + 0.476 = 1$
- $\tau \approx 10^{-9}$
- Gives: $t_{fall} = 2.2ns$



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Timing Analysis of the SRC model

 
- How do we find the **Rise Time**?
- Have to replace by new equivalent circuit where:
 - Capacitor is initially discharged (0.476 V)
 - Switch is open



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Timing Analysis of the SRC model

 - How do we find the **Rise Time**?
- Have to replace by new equivalent circuit where:
 - Capacitor is initially discharged (0.476 V)
 - Switch is open
- $V_{G1} = (0.476 - 5)e^{-t/\tau} + 5$
- $\tau = 10^{-12} \times 9500 \approx 10ns$



$$R_{on} = 1k\Omega$$
$$V_T = 1V$$


Timing Analysis of the SRC model

- $V_{G1} = (0.476 - 5)e^{-t/\tau} + 5$
 $\tau = 10^{-12} \times 9500 \approx 10ns$

- $(0.476 - 5)e^{-t_{rise}/\tau} + 5 = 1$

$$-\tau \ln(0.884) = t_{rise}$$



- $t_{rise} = 1.2ns$

 

$$R_{on} = 1k\Omega$$
$$V_T = 1V$$

Timing Analysis of the SRC model

 
 
- $V_{G1} = (0.476 - 5)e^{-t/\tau} + 5$
- $\tau \approx 10^{-12} \text{ s}$
- $t_{rise} = 1.2 \text{ ns}$



$$R_{on} = 1 \text{ k}\Omega$$
$$V_T = 1 \text{ V}$$

Propagation Delay

  
- Rise and Fall Time are also called “Propagation Delays”




- Gives “delay time” between when the logical input changes and the logical output changes
- Book calls them $t_{pd,1\rightarrow 0}$ and $t_{pd,0\rightarrow 1}$

Reminder of Where We Started


Wanted to study gate delay of:

 

So used SRC model:

 


Which implements:

 

Giving delay of LEFT gate!


Propagation Delays

 - In general $t_{pd,0 \rightarrow 1}$ is not equal to $t_{pd,1 \rightarrow 0}$
- Thus, we usually just take the **maximum** and call that the **propagation delay of the gate**
- $t_{pd} = 2.2ns$
- Means that no matter what input you give the gate, output will be correct within $2.2ns$



Propagation Delay

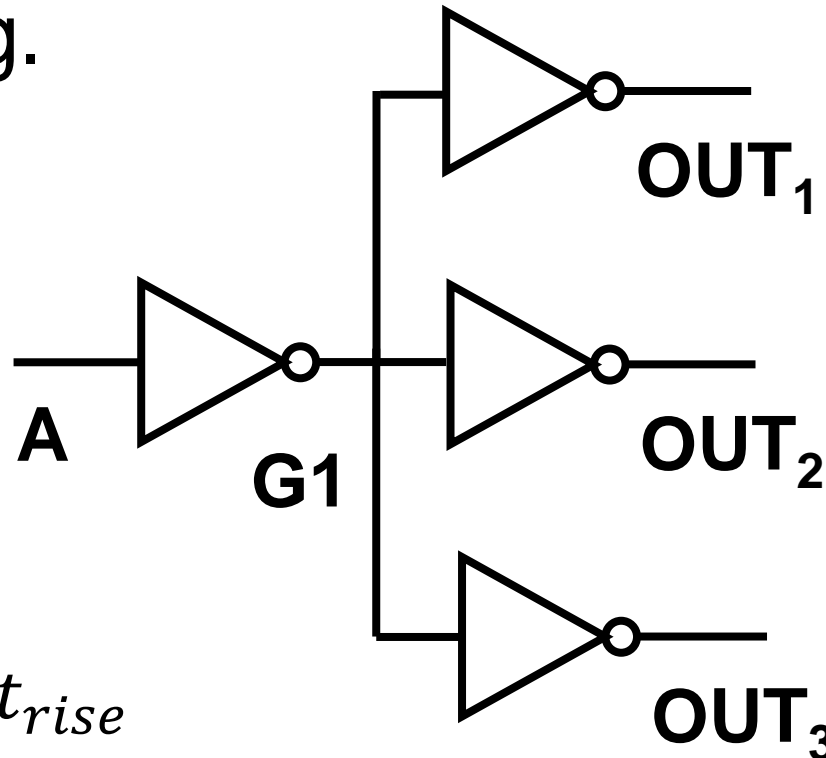
- Is our analysis still correct if we add more output gates?
- No, gate capacitance increases! Takes 3 times as long.



$$-\tau \ln(0.884) = t_{rise}$$

Power in the SRC Model


 
- **Static power** in the SRC Model is exactly as SR Model, compare:



- We're also interested in the **dynamic power** while capacitance is charging
- Algebra is a bit involved. We'll outline the concept. Book has a very thorough treatment in sections 11.1 through 11.3



Dynamic Power in NMOS Circuits

  - When our inverter is going from **low to high**, we have the circuit on the left:
- In general, looks like circuit on the right:




Dynamic Power in NMOS Circuits

  - When our inverter is going from **high to low**, we have the circuit on the left:
- In general, looks like circuit on the right:




Dynamic Power

 - Worst case is that inverter is driven by a sequence of 1s and 0s
 - Circuit constantly switching behavior
 - Gate capacitor constantly charging and discharging




Charges up towards V_S

 


Discharges down towards $V_S \frac{R_{ON}}{R_{ON} + R_L}$

 Problem Setup

- V_{in} is
 - 0 for some time T_1
 - Dissipates some energy w_1
 - 1 for some time T_2
 - Dissipates some energy w_2
- $P = \frac{w_1 + w_2}{T_1 + T_2}$
- See 11.1 through 11.3 for derivation



Charges up towards V_S

 


Discharges down towards $V_S \frac{R_{ON}}{R_{ON} + R_L}$

Solution

$$\bar{p} = \frac{V_S^2}{2(R_L + R_{ON})} + \frac{V_S^2 R_L^2 C_L}{(R_L + R_{ON})^2 T}$$

$$p_{\text{static}} = \frac{V_S^2}{2(R_L + R_{ON})}$$
 
$$p_{\text{dynamic}} = \frac{V_S^2 R_L^2 C_L}{(R_L + R_{ON})^2 T}$$




Avoiding Static Power Loss



- Next we will talk about CMOS, which stands for Complementary MOS
- So far, all of our transistors have been NMOS transistors, where they are on if $V_{GS} \geq V_T$
- Next, we will discuss a new type of FET transistor called a PMOS
- Only difference is that they will be on when $V_{GS} \leq V_T$

PMOS Transistor

 - Drawn with a bubble at the input:
- Usually drawn with source on top and drain on bottom (for reasons that will become clear)
- Just as before, have ON and OFF states, now on when




$$V_{GS} \leq V_T$$

  

Anything logical we can do with NMOS...

 - ...we can do with PMOS
- Example, we can build an inverter, try it for a minute or so on the worksheet using a PMOS, 5V source, ground, and resistor
- Assume input signal is 0V or 5V and $V_T = -1V$




Here: R_L acts as a pull-down resistor

Analysis of PMOS Logic

- We could go through and repeat everything we did for NMOS, but it would be almost exactly the same thing
- Instead, we're now going to use NMOS and PMOS together in a new clever way


CMOS Inverter

 - Two complementary implementations of the same logic function
- When V_{IN} is high:
 - Path to ground is closed
 - Path to V_S is open




CMOS Inverter

 - When V_{IN} is high:
 - Path to ground is closed
 - Path to V_S is open
- Huge resistance on open PMOS acts as a pull-up resistor




CMOS Inverter

 - When V_{IN} is low:
 - Path to ground is open
 - Path to V_S is closed
- Huge resistance on open NMOS acts as a pull-down resistor




Static Power in CMOS

 - What is the static power consumed by this CMOS inverter when $I_N=0$?
- When $I_N=1$?
- In reality, there is a substantial static power component




Static Power in CMOS

 - **Gate Power:** As gate oxides get smaller, gate current grows
- **Subthreshold Leakage Power:** As thresholds are reduced (to increase speed), transistors are never fully OFF, so current always flows from V_S to V_{low}



Dynamic Power in CMOS

 - **Load power:** Since our CMOS gates will be driving capacitive loads, they will still draw power when switching (since power is provided to the load)
- **STL:** Both transistors are again weakly on at intermediate values




Power in CMOS

- Though **subthreshold leakage** is a significant component to MOSFET power (>50%), it involves a more complex MOSFET model we haven't studied
- We'll instead focus on **dynamic load power**
 - Still accounts for vast portion of chip power consumption


Load Power Analysis

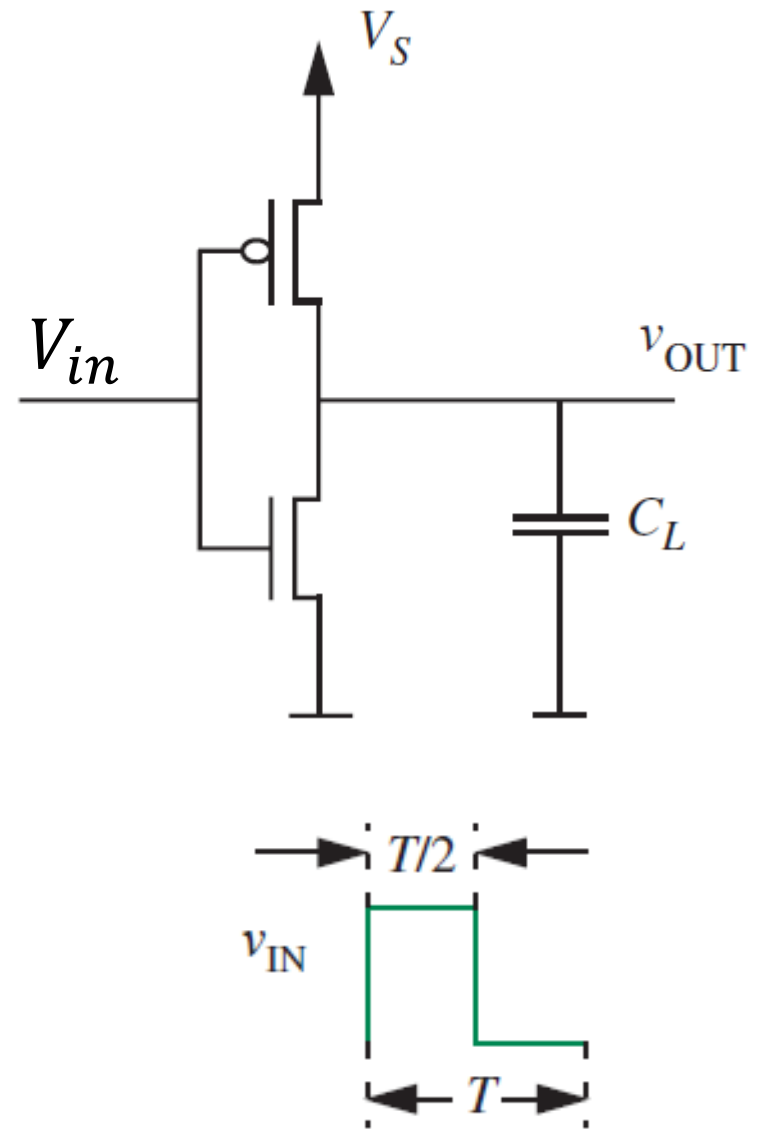- Assume our inverter is driven by a square wave
- Capacitor will be constantly charging and discharging




Load Power Analysis

 
- When input is low, capacitor charges to V_S , energy stored is
 - $\frac{1}{2} C_L V_S^2$
- When input is high, capacitor charges to 0, energy stored is
 - 0




Rising Case

 

 
- From homework, how much energy is dissipated in the resistor as C_L charges to V_S ?



Falling Case

 


 - If capacitor starts with $\frac{1}{2} C_L V_S^2$ Joules of energy, and it all gets dissipated through resistor, then energy dissipated is $\frac{1}{2} C_L V_S^2$



Dynamic Load Power

 - Thus, if clock cycle is long enough, each switching event consumes $\frac{1}{2} C_L V_S^2$ joules of energy
- In T seconds, we consume $C_L V_S^2$
- Power is $\frac{C_L V_S^2}{T} = C_L V_S^2 f$



CMOS

- CMOS Summary:
 - No need for a pull-up or pull-down resistor
 - Though you can avoid this even with purely NMOS logic (see HW7)
 - Greatly reduced static power dissipation vs. our simple NMOS only logic
 - In reality, MOSFETs are never truly off, and static leakage power consumes >50% of chip power
 - Dynamic power is still hugely significant
 - Uses twice the number of transistors as our simple purely NMOS logic

Preview of Tradeoffs in Digital Circuits

- Processor can do more work per second if f is high
 - Increasing V_S and lowering V_T give faster rise and fall times, letting us increase f
 - Dynamic power (and heat) in CMOS scales as $C_L V_S^2 f$
 - Subthreshold leakage power (and heat) gets larger as V_T gets smaller and as heat increases
- Smarter hardware takes more transistors
 - More area means fewer chips per wafer
 - More transistors means more power consumption

Implementation of Complex Gates Using NMOS and CMOS

- In class, we've discussed analysis of NMOS and CMOS circuits
- Haven't discussed how to design them
- Luckily, it isn't very hard

Design of NMOS Circuits

- Gates can be designed which use only NMOS transistors and a pull-up resistor
 - Easy to pick parameters to satisfy static discipline
- The basic idea is to **construct an NMOS network which**:
 - **Provides a path from V_{low} to V_{out} ONLY when logical function is false**
 - When path from V_{low} to V_{out} is not available, then $V_{out} = V_{high}$ through pull-up resistor
- Examples on board

Example on Board


CMOS Design

- In the CMOS case, things are almost exactly the same
- NMOS network which connects V_{low} to V_{out} only when function is false
 - Same network as in NMOS only logic
- PMOS network which connects V_{high} to V_{out} only when function is true
- Examples on board

-
- This is where we stopped

Model Corner Cases

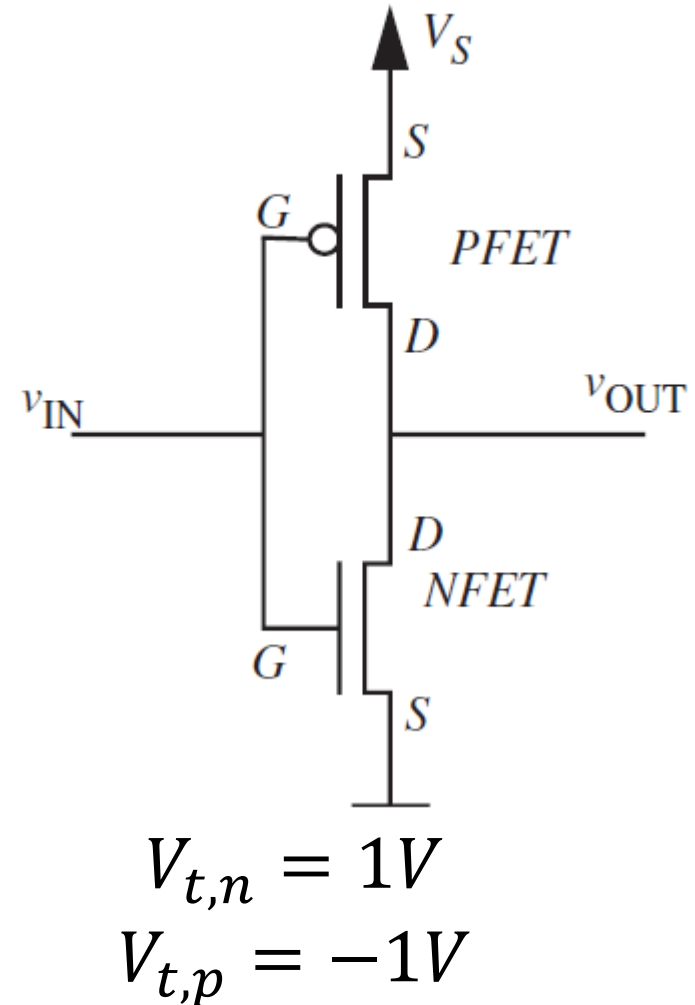- What happens if:
 - $V_{in} = 0.99V$
 - $V_{in} = 1.01V$
 - $V_{in} = 1V$
- Real MOSFET model is more complicated
 - Switch can be semi-on
 - i_{DS} saturates for large V_{DS} [not really a resistor]



Real MOSFET Model

- If we have time this week, we'll discuss a more realistic model of the MOSFET

$$i_{DS} = \begin{cases} K \left[(v_{GS} - V_T)v_{DS} - \frac{v_{DS}^2}{2} \right] & \text{for } v_{GS} \geq V_T \text{ and } v_{DS} < v_{GS} - V_T \\ \frac{K(v_{GS} - V_T)^2}{2} & \text{for } v_{GS} \geq V_T \text{ and } v_{DS} \geq v_{GS} - V_T \\ 0 & \text{for } v_{GS} < V_T. \end{cases}$$


- Useful for understanding invalid input voltages in logic circuits
- More importantly, tells us how we can utilize MOSFETs in analog circuits
 - Op-amps are built from transistors

Nonlinear Elements


- This more realistic MOSFET model is nonlinear
- MOSFETs are three terminal devices, and it will be tough to begin our nonlinear adventure
 - Functionality is similar to what we've seen before (op-amps)
 - Analysis is tough
- We'll instead turn to diodes
 - Interesting new function
 - Analysis is easier
- If we have time, we will talk on Friday or Monday about analog MOSFET circuits

Diode Physical Behavior and Equation


Schematic Device

 

Symbol

 

Qualitative I-V characteristics:

 

Quantitative I-V characteristics:

$$I = I_0(e^{V_D/nV_T} - 1)$$

$$V_T = \frac{kT}{q} = 0.026V$$

$$n: 1 \text{ to } 2$$

$$I_0: 10^{-15}A \text{ to } 10^{-12}A$$

Allows significant current flow
in only one direction

The pn Junction I vs. V Equation

I-V characteristic of PN junctions

In EECS 105, 130, and other courses you will learn why the I vs. V relationship for PN junctions is of the form

$$I = I_0 (e^{V_D/nV_T} - 1) \quad V_T = \frac{kT}{q} = 0.026V$$


where I_0 is a constant related to device area and materials used to make the diode, $q = \text{electronic charge} = 1.6 \times 10^{-19}$, k is Boltzman constant, and T is absolute temperature.
 $kT/q = 0.026V$ at $300^\circ K$, a typical value for I_0 is $10^{-12} - 10^{-15} A$

We note that in forward bias, I increases **exponentially** and is in the μA - mA range for voltages typically in the range of 0.6 - $0.8V$. In reverse bias, the current is essentially zero.

Solving diode circuits

- How do we solve this circuit?
- KCL at the top right node:

$$\frac{V - V_{Th}}{R_{Th}} = I_0 \left(e^{\frac{V}{0.026}} - 1 \right)$$

 

Quantitative I-V characteristics:


$$I = I_0 \left(e^{V_D/V_T} - 1 \right)$$

$n=1$


No algebraic solution!

Load Line Analysis Method

 1. Graph the I - V relationships for the non-linear element and for the rest of the circuit
2. The operating point of the circuit is found from the intersection of these two curves.




$$\frac{V - V_{Th}}{R_{Th}} = I_0 \left(e^{\frac{V}{0.026}} - 1 \right)$$

 

The I - V characteristic of all of the circuit except the non-linear element is called the load line

Load Line Example: Power Conversion Circuits

 
- Converting AC to DC
- Potential applications: Charging a battery




- Can we use phasors?
- Example on board

Piecewise Linear Model


Circuit symbol

 

I-V characteristic

 

Switch model

 

For a Si pn diode, $V_{Don} \cong 0.7 \text{ V}$

RULE 1: When $I_D > 0$, $V_D = V_{Don}$

RULE 2: When $V_D < V_{Don}$, $I_D = 0$

Diode behaves like a voltage source in series with a switch:

- closed in forward bias mode
- open in reverse bias mode

How to Analyze Diode Circuits with Piecewise Linear Model


A diode has only two states:

- **forward biased:** $I_D > 0$, $V_D = 0.7 \text{ V}$
- **reverse biased:** $I_D = 0$, $V_D < 0.7 \text{ V}$

Procedure:

1. Guess the state(s) of the diode(s)
2. Check to see if KCL and KVL are obeyed.
3. If KCL and KVL are not obeyed, refine your guess
4. Repeat steps 1-3 until KCL and KVL are obeyed.

Example:

 

If $v_s(t) > 0.7 \text{ V}$, diode is forward biased
(else KVL is disobeyed – try it)


If $v_s(t) < 0.7 \text{ V}$, diode is reverse biased
(else KVL is disobeyed – try it)

Diode Logic: AND Gate


- Diodes can be used to perform logic functions:

AND gate

 output voltage is high only if
both A and B are high



 Inputs **A** and **B** vary between 0 Volts (“low”) and V_{CC} (“high”) Between what voltage levels does **C** vary?





Diode Logic: OR Gate

- Diodes can be used to perform logic functions:

OR gate

output voltage is high if
either (or both) A and B are high

  Inputs **A** and **B** vary between 0 Volts (“low”) and V_{CC} (“high”) Between what voltage levels does **C** vary?




Diode Logic: Incompatibility and Decay

- Diode Only Gates are Basically Incompatible:


AND gate

 output voltage is high only if both A and B are high



OR gate

 output voltage is high if either (or both) A and B are high



Signal Decays with each stage (Not regenerative)

That's all for today

- Next time, more Diodes and a little more on the more realistic model of MOSFETs