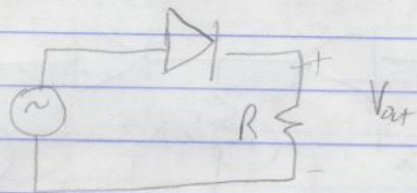



8/4/10!

1.4V $\sin(\omega t)$




E1)

Load line
for $V_{in} = 0.7V$

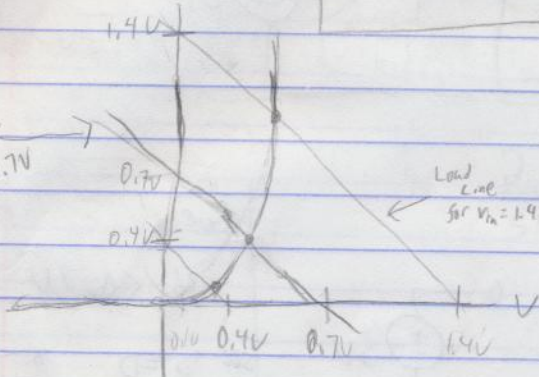


Load line
for $V_{in} = 1.4V$

V_{in}

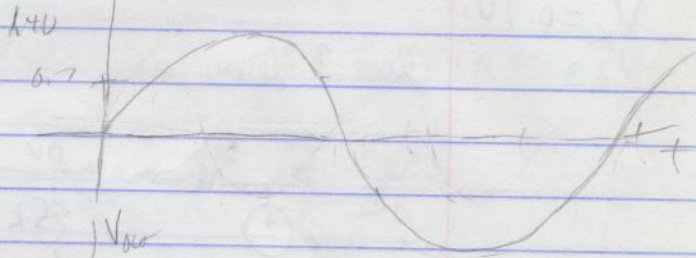


0.8V

V_{out}

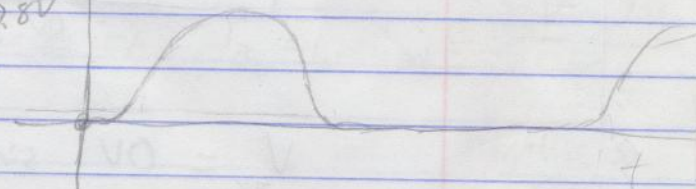


V_D

0.6

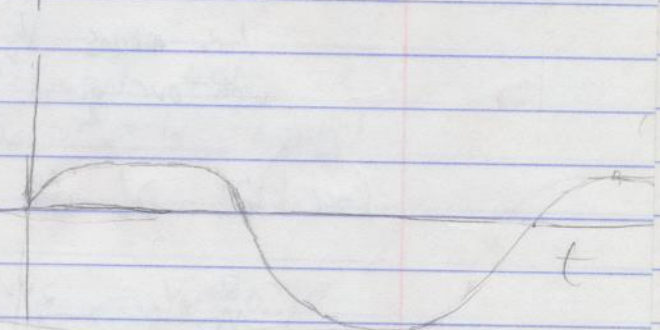


E2) w/ simple model:

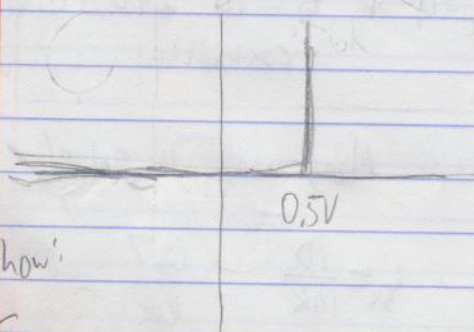

EQ just both are

0.9V

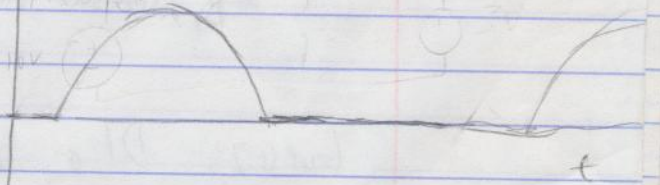

V_D

0.5V




can show:

ON if $V_{in} > 0.5V$


OFF if $V_{in} < 0.5V$

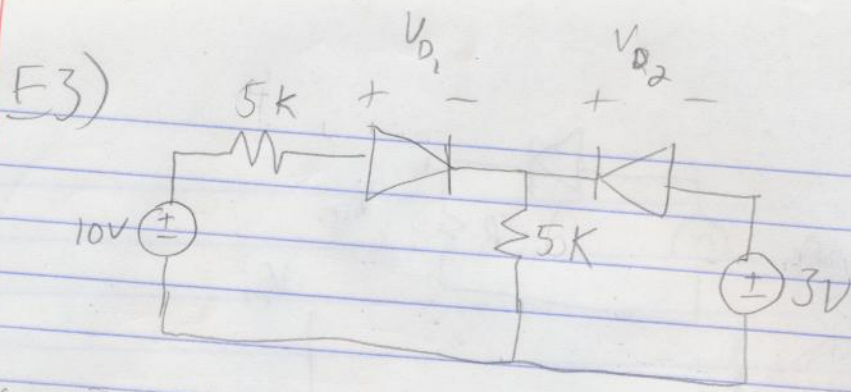See webcast for details
or email me and I'll write it up!



For this problem
 $V_K = 0.7V$.

Guess 1: Both off!

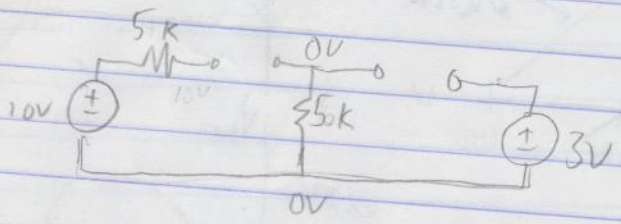


Guess:
 $V_{D1} < 0.7V$ $V_{D2} < 0.7V$
 so: $i_{D1} = 0$ so: $i_{D2} = 0$

$V_{5k} = 0V$ since $i_{5k} = 0$.

This means $V_{D1} = 10V$. But this is a contradiction with our guess.


Guess 2: D1 off, D2 on

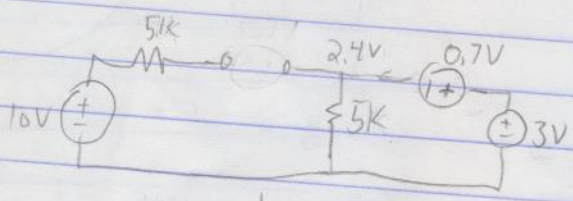

Guess:
 $V_{D1} < 0.7V$ $V_{D2} = 0.7V$
 $i_{D1} = 0$ $i_{D2} > 0$

By similar argument $i_{5k} = 0$, so $V_{D1} = 10 - 2.4V = 7.6V$ - contradiction!

Guess 3: D1 on, D2 off

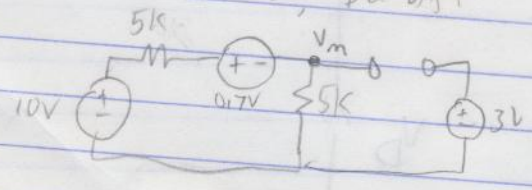


Many ways to solve!
 $i_{5k} = \frac{10}{5k} - \frac{0.7}{10k} = 0.93mA$

$V_m = 0.93mA \cdot 5k = 4.65V$

Guess works! so $V_{D2} = 3 - 4.65V < 0.7V$

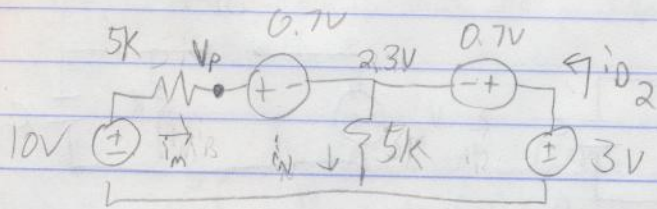But since we're learning, let's do the last one!



Guess!

$$V_{D_1} = 0.7V$$

$$i_{D_1} > 0A$$

$$V_{D_2} = 0.7V$$

$$i_{D_2} > 0A$$

$$i_N = \frac{2.3V}{5k}$$

$$V_p = 2.3V + 0.7V = 3V$$

$$i_M = \frac{1V}{5k} = \dots mA$$

$$i_{D_2} + i_M = i_N \Rightarrow i_{D_2} = i_N - i_M = \frac{2.3V - 7V}{5k}$$

Negative, so
contradiction!


Let's continue discussing our AC circuit. Let's see what happens if we add a capacitor in parallel with our output resistor.



$$V_K = 0.7V$$

Assume $A \gg V_K$

The positive direction

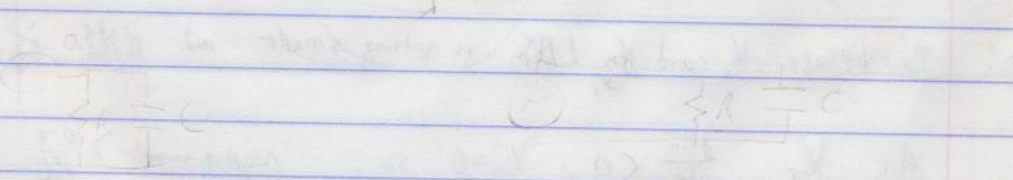


$$V_c = A \sin(\omega t) - 0.5V$$

$$V_c = \frac{V_K}{RC}$$

Valid $V_c < A \sin(\omega t)$

There are 2 possible configurations.

ON:

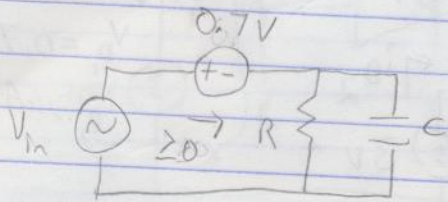

OFF:



Requires that

$$i_D \geq 0 \text{ or by KCL:}$$

$$C \cdot \frac{d(V_{in} - 0.7V)}{dt} + \frac{V_{in} - 0.7}{R} \geq 0$$

Requires that:

$$V_C < V_{in} - 0.7V$$

$$V_C = A \sin(\omega t) - 0.7V$$


OR: $\frac{dV_{in}}{dt} > \frac{0.7 - V_{in}}{RC}$

ON: LHS > RHS

ON: $V_C = V_{in} - 0.7V$

OFF:

$$V_C = V_i (e^{-t/RC})$$

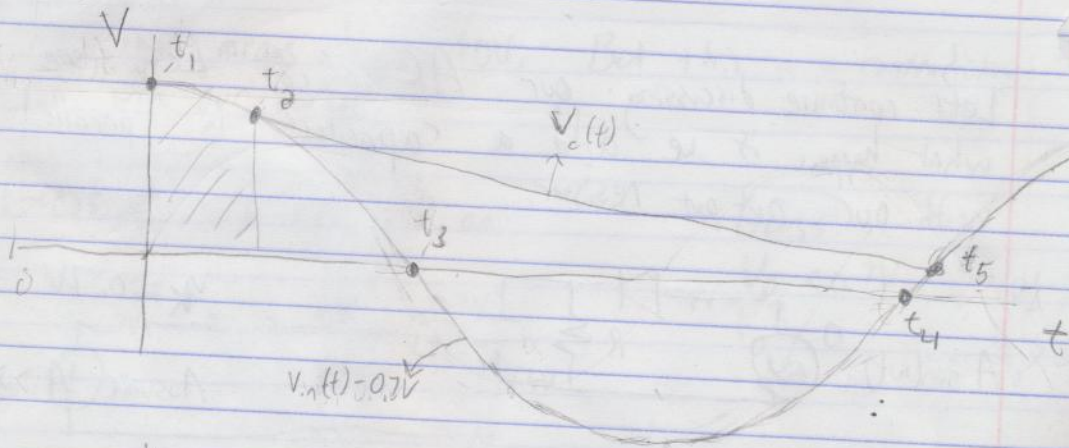

At V_1 : $\frac{dV_{in}}{dt} = 0$, $V_{in} = A$ so: $0 > \frac{0.7 - A}{RC}$ - Yes, since $A > 0.7$

We see: In between V_1 and V_3 , LHS is getting smaller and RHS is getting larger.

At V_3 : $\frac{dV_{in}}{dt} < 0$, $V_{in} = 0$, so negative number $> \frac{0.7}{RC}$ - No!


Since ON at V_1 and OFF at V_3 , we know it must switch to OFF at some V_2 .

Between t_3 and t_5 , diode cannot turn on, this would violate principle that capacitor voltage can't change instantly.


At t_5 , diode cannot remain OFF, since this condition requires that $V_c > A \sin(\omega t) - 0.7V$ and if it stayed OFF it would decay below $A \sin(\omega t) - 0.7V$ which is increasing.

Thus from t_5 to $t_2 + T$, diode is on, and the cycle repeats itself.


Thus it looks like:

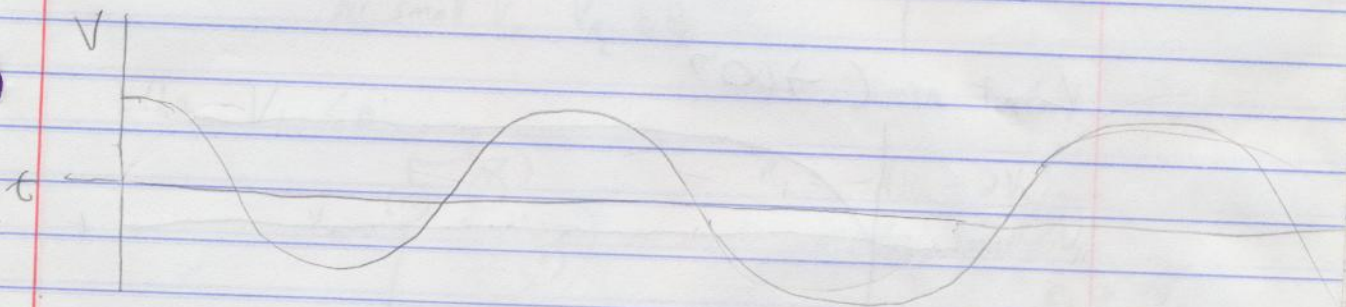

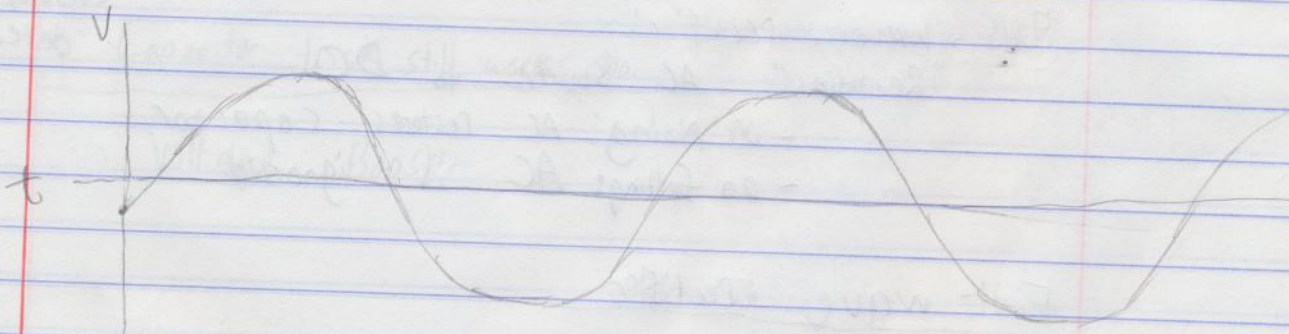
What happens if $V_c = 0$ and we start at $V_n = 0.7V$




What happens as C gets very small?

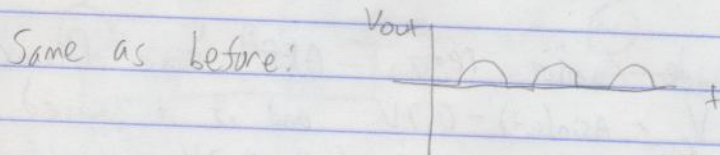

What happens if C gets very large?

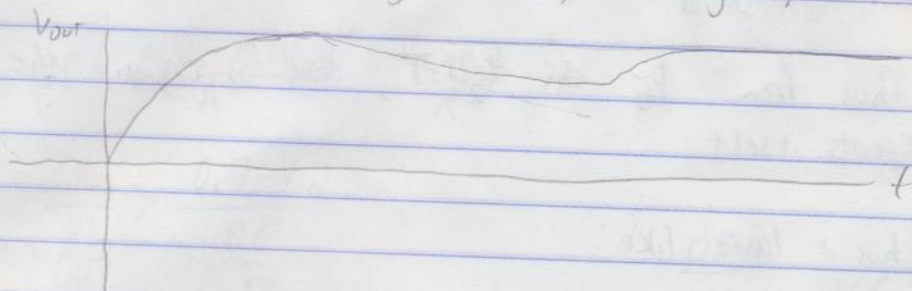

Limit as $C \rightarrow \infty$?

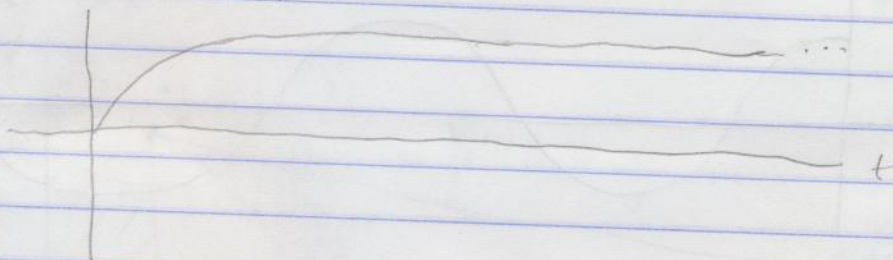

Half-wave rectifier:

"Rectifies" AC source to DC.


- on rising: AC restores capacitor

- on falling: AC is ignored.


can also use
as an
envelope
detector!

Full-wave rectifier

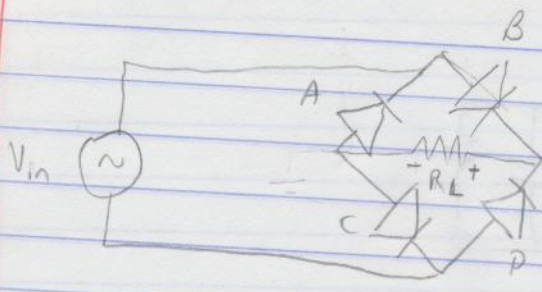Assume $V_{in} \gg V_K$
 so $V_K \approx 0$




When $V_{in} > 0$,

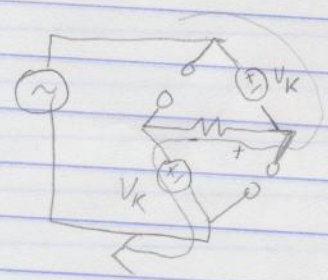

$V_{R_L} = V_{in} - 2V_K$ or
 for small V_K : $V_{R_L} \approx V_{in}$

When $V_{in} < 0$:

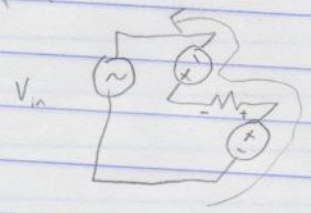

$R_L = -(V_{in} - 2V_K)$
 or for small V_K
 $R_L \approx -V_{in}$

So $R_L \approx |V_{in}|$

Capacitor trick still works too.

Voltage Booster