



The iPhone 4 integrates the antenna into the case

EE40

Lecture 3

Josh Hug

6/25/2010


“Users [are] reporting a drop in signal strength when **the phone is held.**” -BBC

“If you ever experience this on your iPhone 4, avoid gripping it in the lower left corner in a way that covers both sides of the black strip in the metal band, or simply use one of many available cases.”-Apple

Logistical Notes

- Office Hours – Room reservation has been put in, but no word from the people yet. I've got someone looking into it
- HW1 due today at 5 PM in the box in 240 Cory
- No i>Clicker today [couldn't get hardware today]


Nodal Analysis: Example

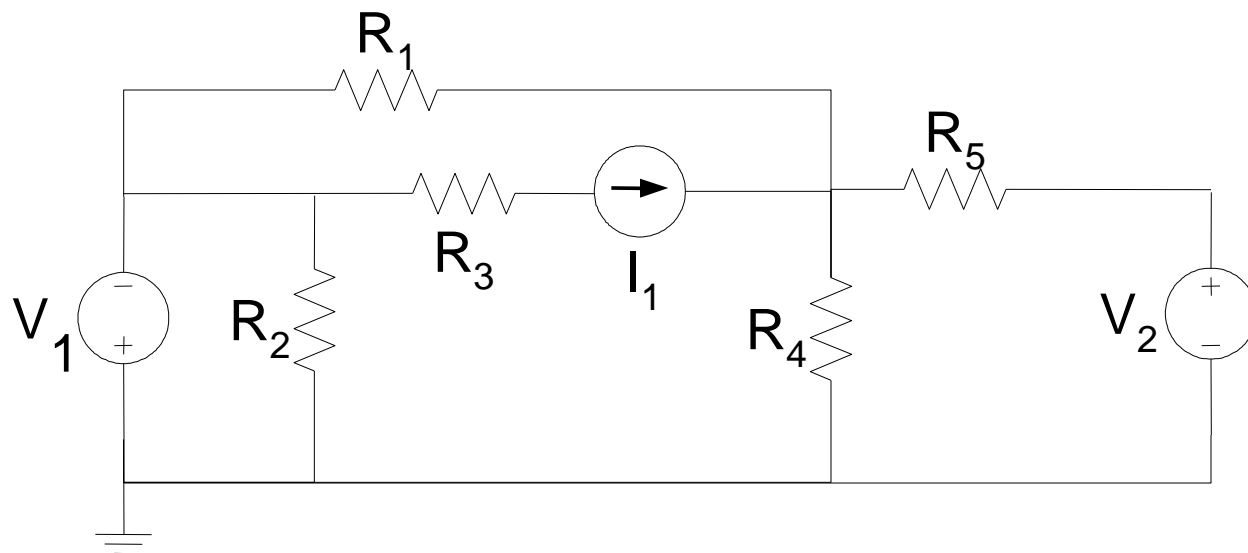

Using the basic method

- 5 unknowns
- 2 KCL equations
- 3 KVL equations

Nodal Analysis: Example

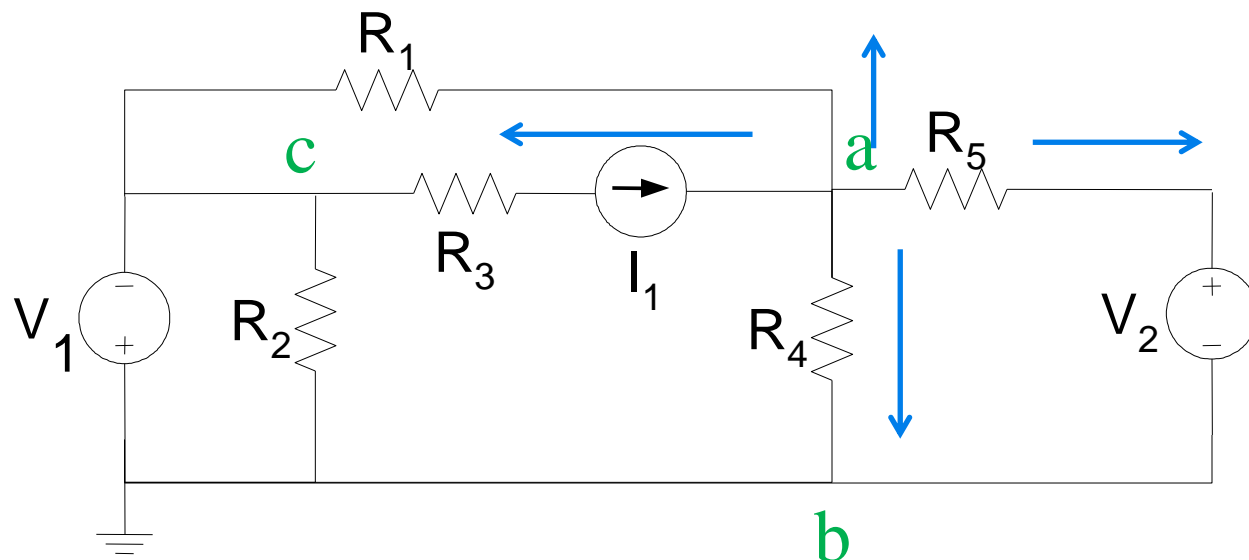

One equation, one unknown


With Node Voltage:

$$\frac{V_a - V_2}{R_5} + \frac{V_a}{R_4} - I_1 + \frac{V_a + V_1}{R_1} = 0$$

$$G_5(V_a - V_2) + G_4V_a - I_1 + G_1(V_a + V_1) = 0$$

$$V_a(G_5 + G_4 + G_1) = G_5V_2 + I_1 - G_1V_1$$

Nodal Analysis: Example

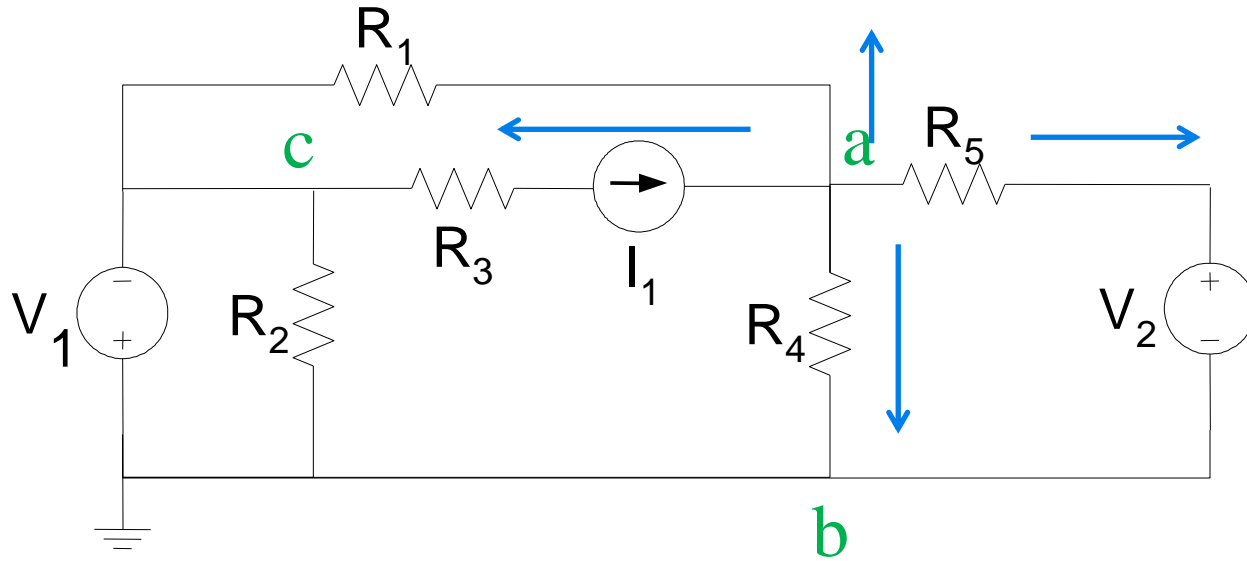

$$V_a(G_5 + G_4 + G_1) = G_5V_2 + I_1 - G_1V_1$$


$$V_a = \frac{G_5V_2 + I_1 - G_1V_1}{G_5 + G_4 + G_1}$$

$$V_a = \frac{R_4(I_1R_1R_5 - R_5V_1 + R_1V_2)}{R_4R_5 + R_1(R_4 + R_5)}$$


It's fine to leave your answer in terms of conductances on HW and exams

Dependent Sources

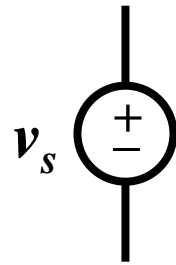- In practice, we'll want to use controllable sources
 - Called “dependent sources” since their output is dependent on something external to the source itself



independent


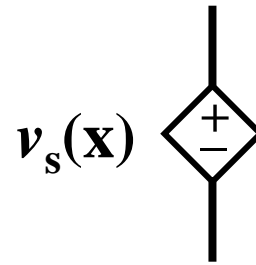


dependent

- In theory, a dependent source could be a function of anything in the universe
 - Intensity of light incident on the source
 - Number of fish within 3 miles

Dependent Sources

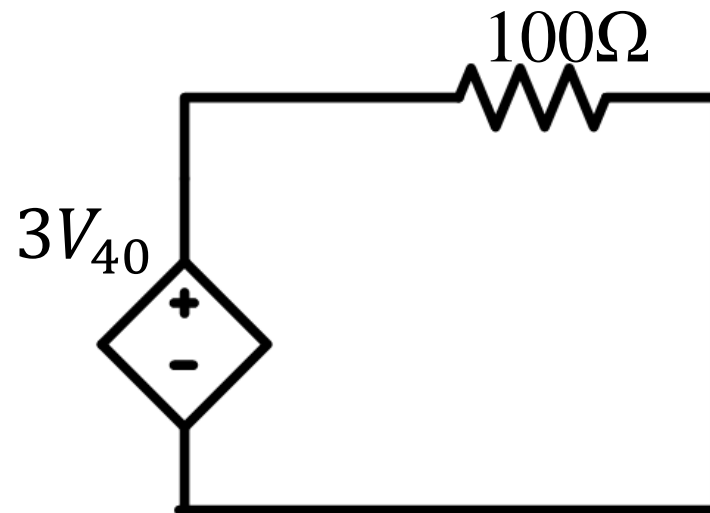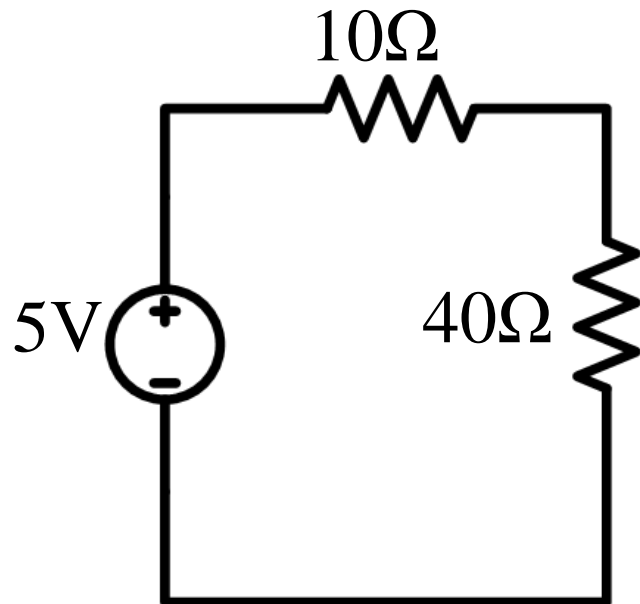- Since we're building electrical circuits, dependent sources have been developed which are functions of other electrical quantities




$$I_{100} = \frac{3V_{40}}{100\Omega} = \frac{3 \times 4V}{100\Omega} = 0.12A$$

Dependent Sources

- Dependent sources allow us to decouple the controller from the controlled
 - Acceleration of the engine affect by gas pedal
 - Gas pedal not affected by engine acceleration
- This is in contrast to our circuits so far where everything is connected

Dependent Sources With Feedback

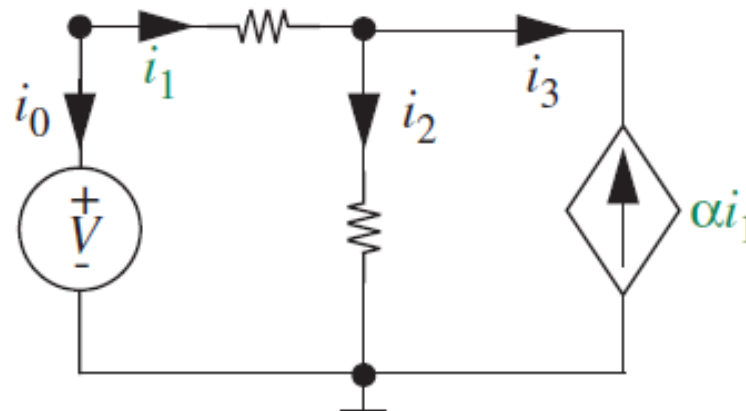- Dependent sources can be coupled to their controller
- This is useful for when the controller needs feedback from the thing being controlled
- Can be a little tricky to analyze




Node Voltage With Dependent Source

$$\frac{V_a - 100}{100} + \frac{V_a}{20} - 4i_1 = 0$$

$$i_1 = -\frac{V_a - 100}{100}$$

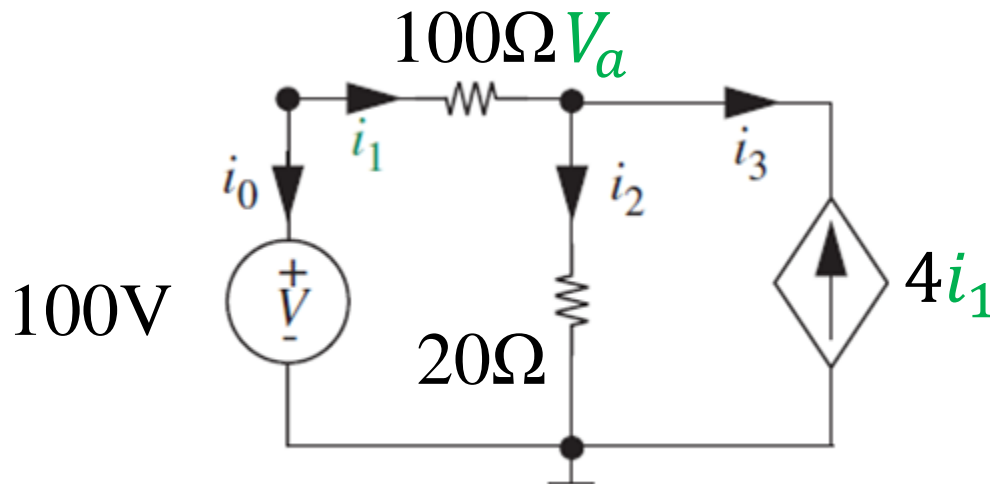- There are two ways to proceed:
 - **Direct substitution (almost always better)**
 - Indirect substitution (tough part of the reading)



Direct Substitution Method for Dependent Sources

$$\frac{V_a - 100}{100} + \frac{V_a}{20} - 4i_1 = 0 \qquad i_1 = -\frac{V_a - 100}{100}$$

$$\frac{V_a - 100}{100} + \frac{V_a}{20} + 4\frac{V_a - 100}{100} = 0$$

$$V_a - 100 + 5V_a + 4V_a - 400 = 0$$

$$10V_a = 500$$


$$V_a = 50$$

Node Voltage With Dependent Source

$$\frac{V_a - 100}{100} + \frac{V_a}{20} - 4i_1 = 0$$

$$i_1 = -\frac{V_a - 100}{100}$$

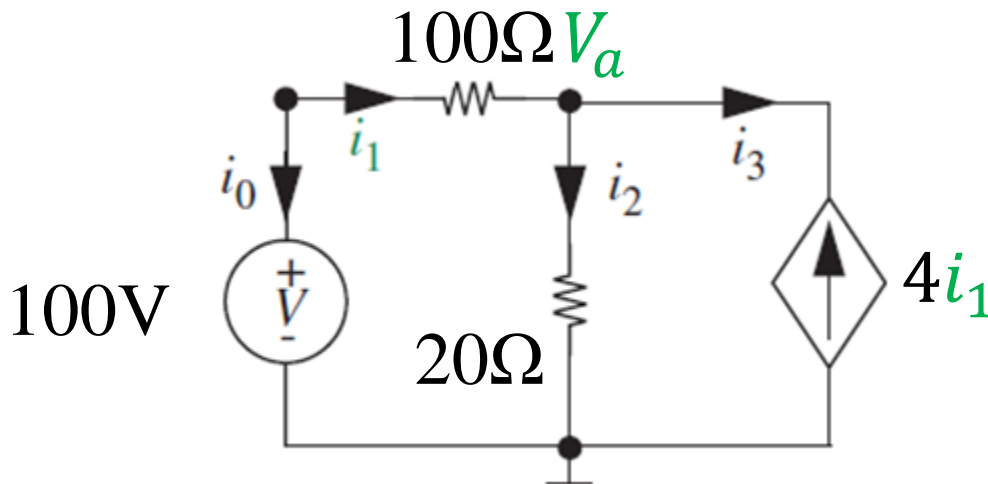- There are two ways to proceed:
 - Direct substitution (almost always better)
 - **Indirect substitution (tough part of the reading)**




? $i = g(i)$?

$I = f(i) = f(g(i))$

?

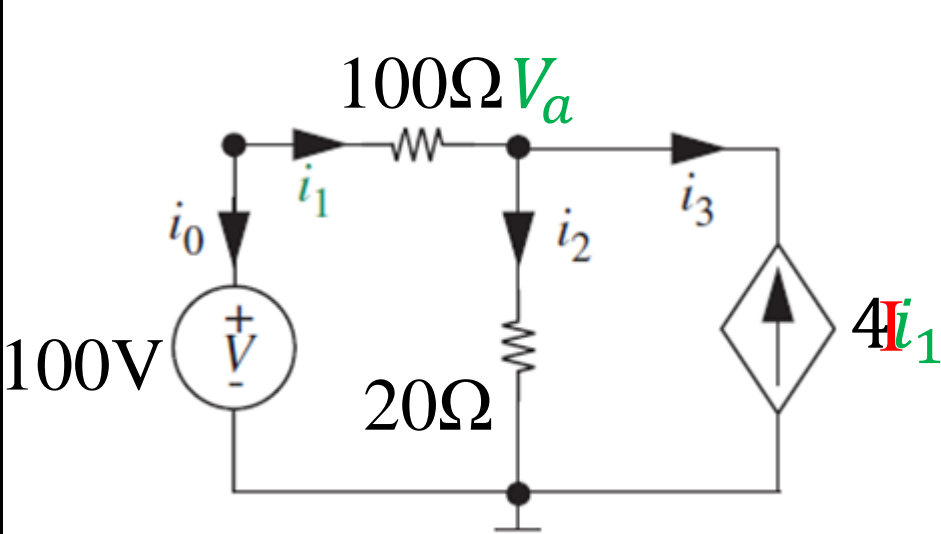Indirect Substitution Method for Dependent Sources



$$\frac{V_a - 100}{100} + \frac{V_a}{20} - 4i_1 = 0$$

Node voltage vs. dummy source

$$V_a = \frac{100 + 100I}{6}$$

Node voltage vs. controlling current

Real source vs. dummy source

$$\frac{I}{4} = i_1$$

$$i_1 = \frac{100 - V_a}{100}$$

$$\frac{I}{4} = \frac{100 - \frac{100 + 100I}{6}}{100}$$

$$I = 2A$$

Summary So Far


- Dependent sources model controllable electrical sources
- Node voltage can be used with dependent sources
 - Controlling input can be seemingly difficult to deal with, e.g. $\frac{V_a - 100}{100} + \frac{V_a}{20} - 4i_1 = 0$
 - Direct Substitution: Replace controlling input with expression in terms of
 - The node voltages you're trying to solve for
 - Known currents if controlling input driven by current source
 - Indirect Substitution: Treat dependent source as a new variable and solve (better in rare cases)

Useful Resistive Circuits

- Wheatstone Bridge
 - Used for measuring unknown resistances
- Strain Gauge
 - Used for measuring weight

Wheatstone Bridge

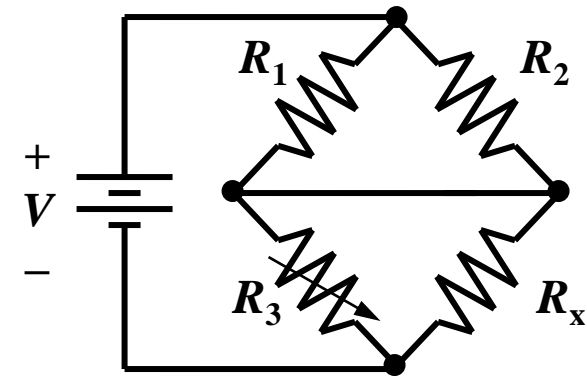- Named for Charles Wheatstone
- Used for measuring resistance of an unknown resistor
- Parts:
 - Known resistors R_1 and R_2
 - Adjustable resistor R_3
 - Unknown resistance R_x
- Basic concept:
 - If $\frac{R_1}{R_3} = \frac{R_2}{R_x}$, then no current will flow in the middle branch




Invented 1833 by Samuel Christie

Hit the charts when remixed by Wheatstone in 1843

Finding the value of R_x

- Adjust R_3 until there is no current in the detector

Then, $R_x = \frac{R_2}{R_1} R_3$

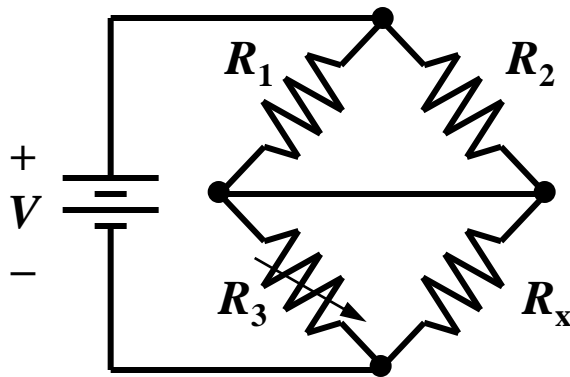

Derivation:

KCL $\Rightarrow i_1 = i_3$ and $i_2 = i_x$

KVL $\Rightarrow i_3 R_3 = i_x R_x$ and $i_1 R_1 = i_2 R_2$

$i_1 R_3 = i_2 R_x$

$$\frac{R_3}{R_1} = \frac{R_x}{R_2}$$


Strain Gauge Intuition

- Resistance is a function of wire length and area
- Weight stretches a wire, changing its shape
- Can theoretically get weight of a load by seeing how resistance varies when a load is added

Resistivity

- Wire resistance: $R = \rho \frac{l}{A}$
- ρ is resistivity, measured in $\Omega \cdot \text{m}$
- Can think of as how tightly molecular lattice holds on to electrons

| Material | ρ |
|----------|-----------------------|
| Copper | 1.68×10^{-8} |
| Aluminum | 2.82×10^{-8} |
| Nichrome | 1.1×10^{-6} |
| Glass | 10^{10} |

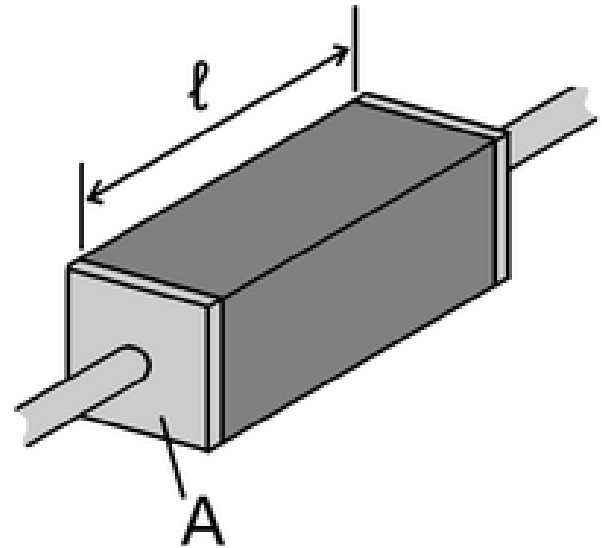

Wire Gauge

| Gauge | Diameter [mm] | Area [mm ²] |
|-------|---------------|-------------------------|
| 10 | 2.58 | 5.26 |
| 14 | 1.62 | 2.08 |
| 16 | 1.29 | 1.31 |

Resistance of 30m, 16 gauge extension cord?

$$1.68 \times 10^{-8} \Omega m \frac{30m}{1.31 \times 10^{-6} m^2}$$


$$0.384 \Omega$$

If carrying 10 amps, how much power dissipated?

$$P = VI = I^2R = 38.4 W$$

Basic Principle

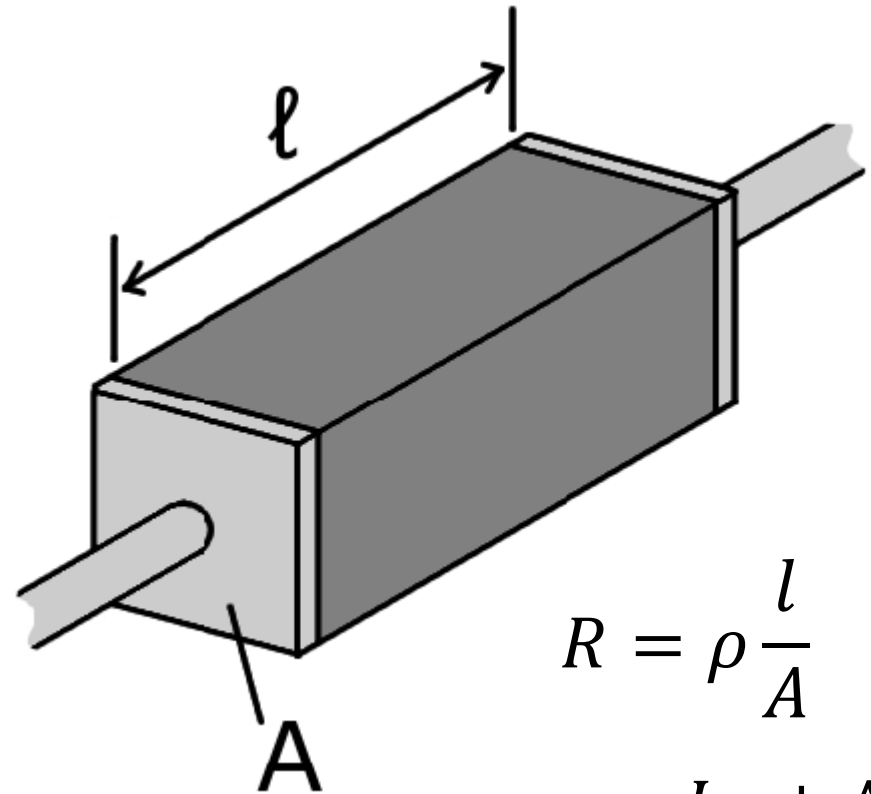- Pull on resistor:
 - $L=L_0+\Delta L$
 - $A=A_0-\Delta A$
 - $V=LA$ [constant]
- Length wins the battle to control resistance
- $R=R_0+\Delta R$



$$R = \rho \frac{l}{A}$$

$$R = R_0 + \Delta R = \rho \frac{L_0 + \Delta L}{A_0 - \Delta A}$$


Define strain $\varepsilon = \frac{\Delta L}{L_0}$

$$\frac{\Delta R}{R_0} = GF \times \varepsilon$$

Where the Gauge Factor relates to how length/area change. $GF \sim 2$


Using Strain to Measure Weight
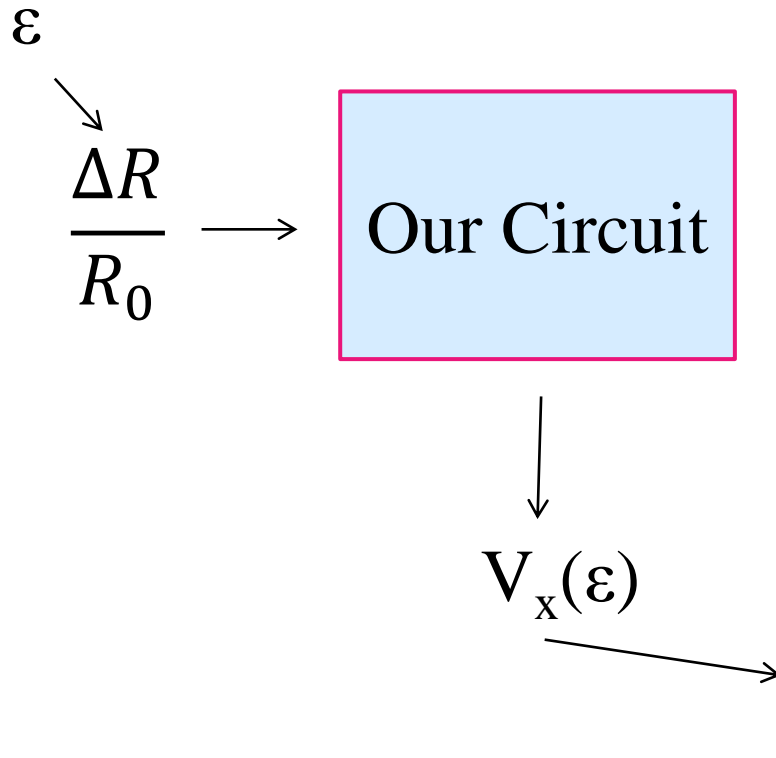
$$\frac{\Delta R}{R_0} = GF \times \varepsilon$$




- We'll attempt to design a circuit which can measure ε
 - Convert $\frac{\Delta R}{R_0}$ into a voltage
- We'll leave it to the mechanical engineers to map ε back to load

Using Strain to Measure Weight

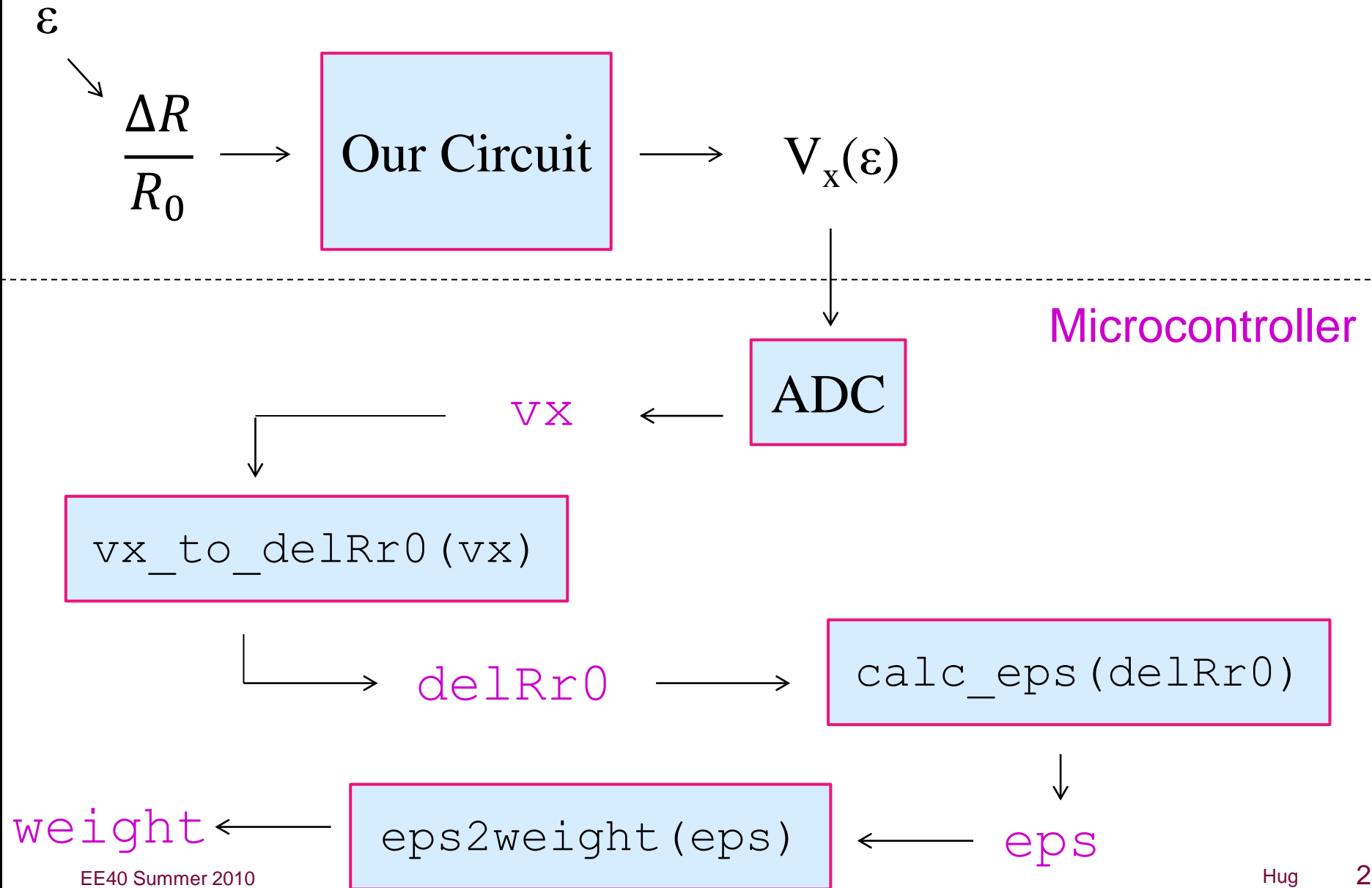


One Possible Design

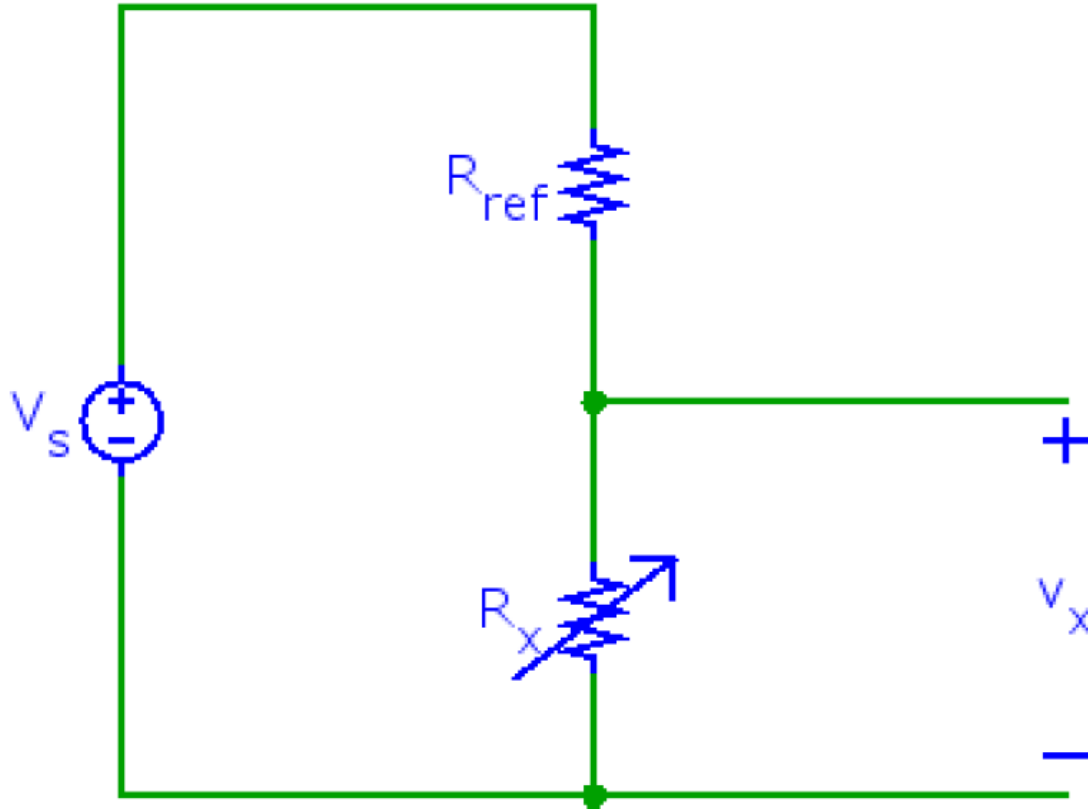

- Here, R_x is a variable resistor, where R_x is dependent on strain
- As strain varies, so will v_x

One Possible Design

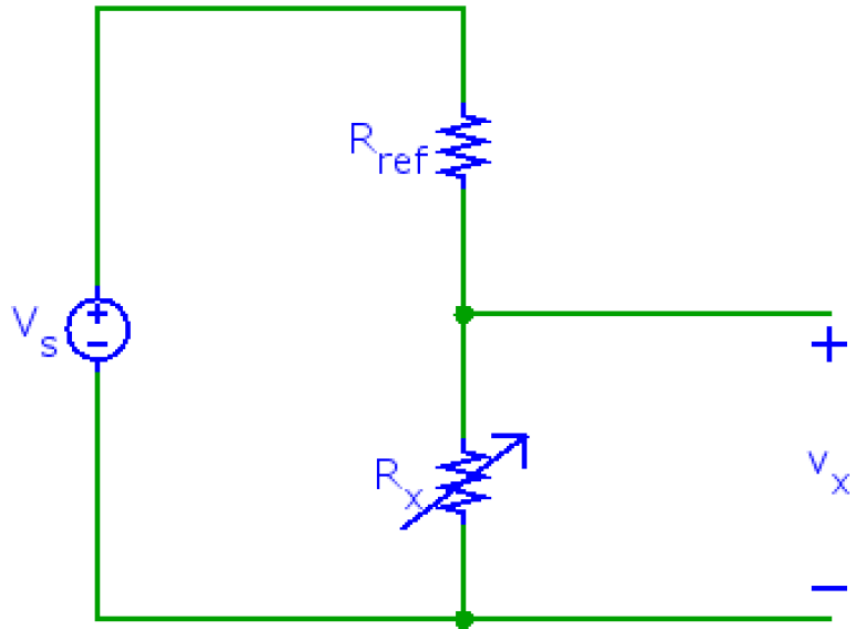

$$\varepsilon = \frac{\Delta R}{R_0} \times \frac{1}{GF}$$

μ Controller calculates ε from known quantities V_x , V_s , R_0 , R_{ref} , GF , and then weight from ε


$$v_x = V_s \frac{R_0 + \Delta R}{R_0 + \Delta R + R_{ref}}$$
$$\cong V_s \frac{R_0 + \Delta R}{R_0 + R_{ref}}$$

v_x is what μ Controller sees

$$\Delta R = \frac{-R_0 V_s + R_0 V_x + R_{ref} V_x}{V_s}$$


$$weight = f(\varepsilon)$$

Better Circuits

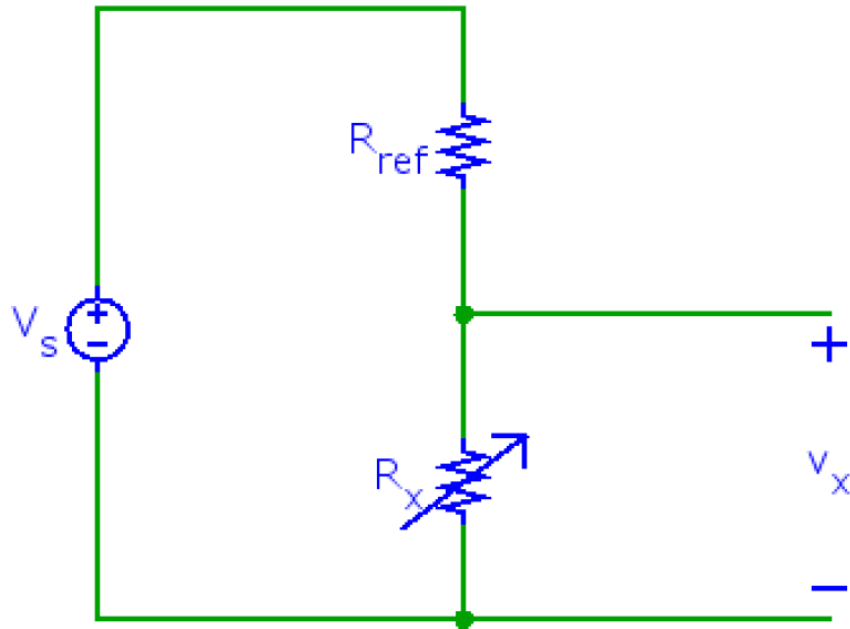


- This will work, but:
 - $V_x \neq 0$ for $\varepsilon = 0$
 - As source voltage varies (e.g. battery gets old), calibration changes – “zero drift”

Improvement #1: Half Bridge

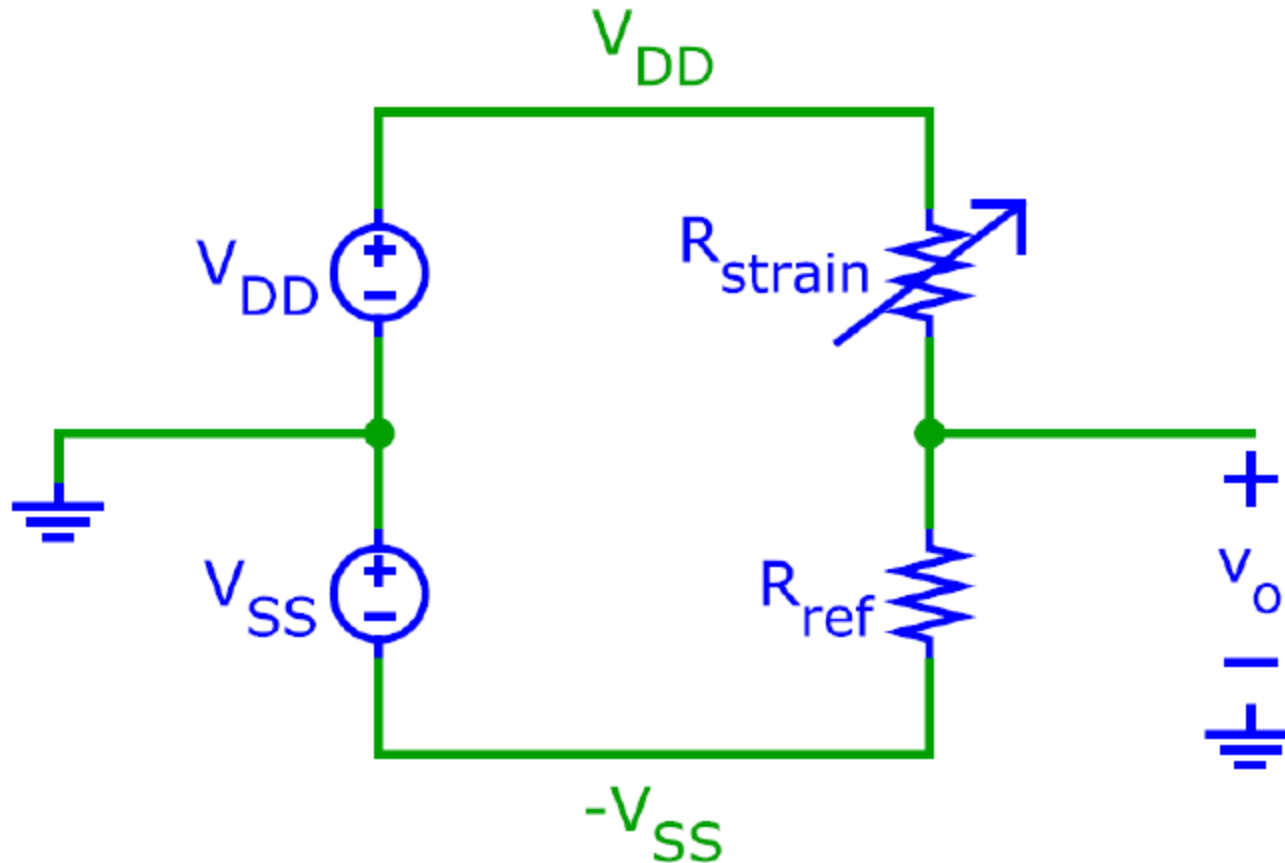

Works, but requires balanced sources

Improvement #2: Full Bridge

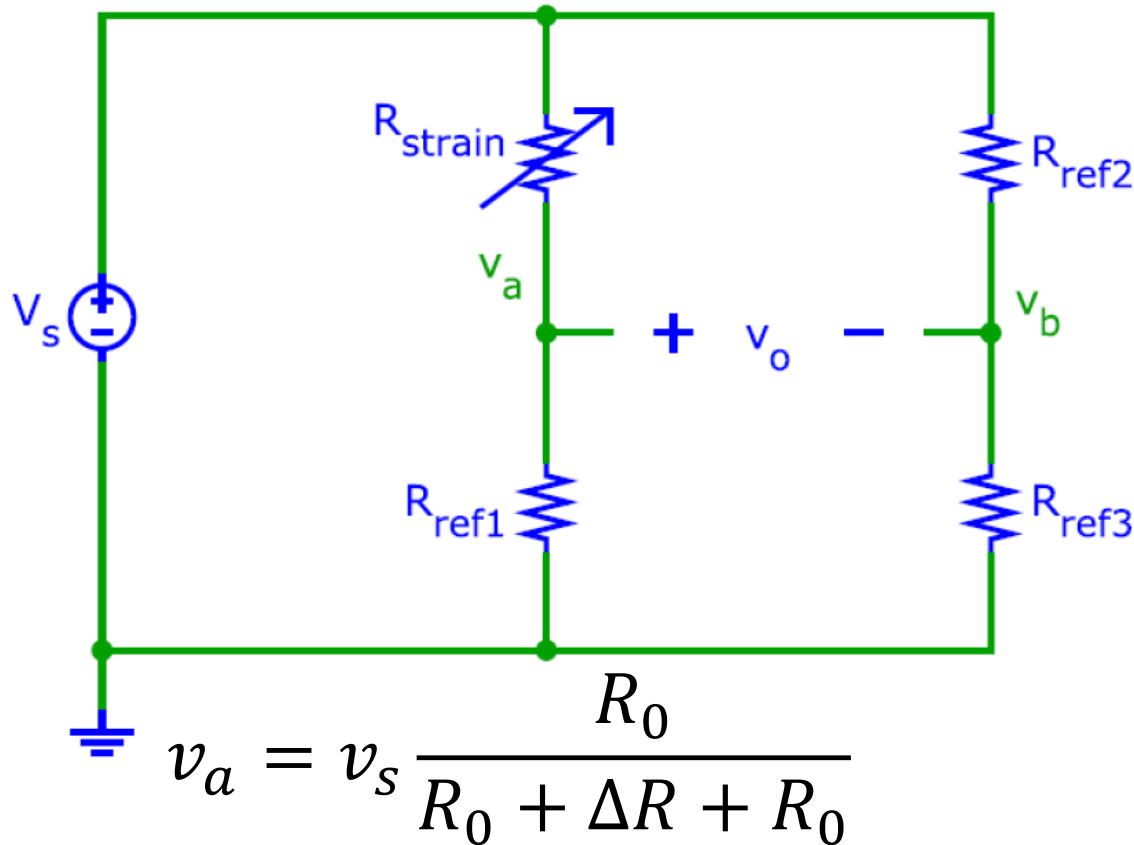

$$R_{\text{strain}} = R_0 + \Delta R$$

$$R_{\text{ref1}} = R_{\text{ref2}} = R_{\text{ref3}} = R_0$$

Want v_o

Use voltage divider

$$v_b = v_s \frac{R_0}{R_0 + R_0} = \frac{v_s}{2}$$

Works, but requires resistors with value equal to R_0

Strain Gauge Summary

- We can map strain (weight) to resistance
- Simplest design (voltage divider) works, but is subject to zero-drift
- More complex circuits give different design tradeoffs
 - Wheatstone-bridge provides arguably the best design
- We will explore these tradeoffs in lab on Wednesday

Useful Resistive Circuit Summary

- The Wheatstone bridge (and other designs) provide us with a way to measure an unknown resistance
- There are resistors which vary with many useful parameters, e.g.
 - Incident light
 - Temperature
 - Strain
- And then... there are always toasters

Back to Circuit Analysis

- Next we'll discuss a few more circuit analysis concepts
 - Superposition
 - Equivalent Resistance
 - Deeper explanation of equivalent resistance
 - For circuits with dependent sources
 - Thevenin/Norton Equivalent Circuits
 - Simulation

Superposition

- Principle of Superposition:
- In any **linear** circuit containing multiple **independent** sources, the current or voltage at any point in the network may be calculated as the **algebraic sum** of the individual contributions of **each source acting alone**.
- A linear circuit is one constructed only of linear elements (linear resistors, and linear capacitors and inductors, linear dependent sources) and independent sources.
- Linear means I-V characteristic of all parts are straight when plotted



Superposition

Procedure:

1. Determine contribution due to **one** independent source
 - Set all other sources to 0:
 - Replace independent voltage source by short circuit
 - independent current source by open circuit
2. Repeat for each independent source
3. Sum individual contributions to obtain desired voltage or current

Easy Example



- Find V_o

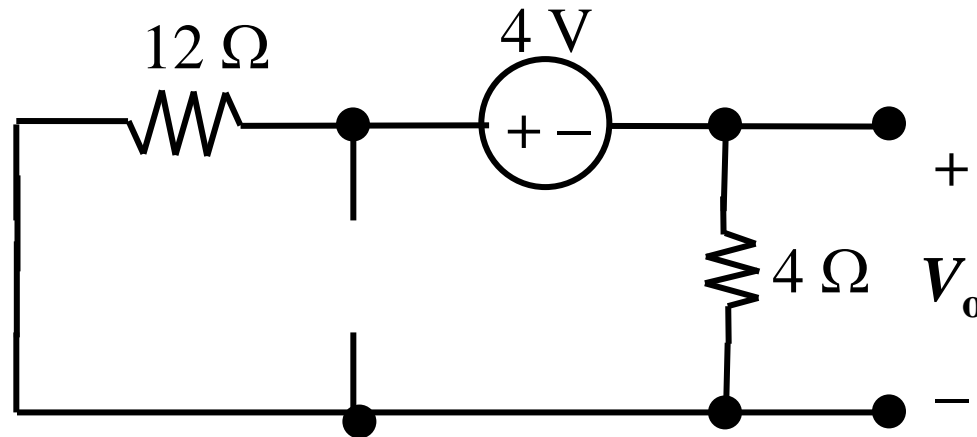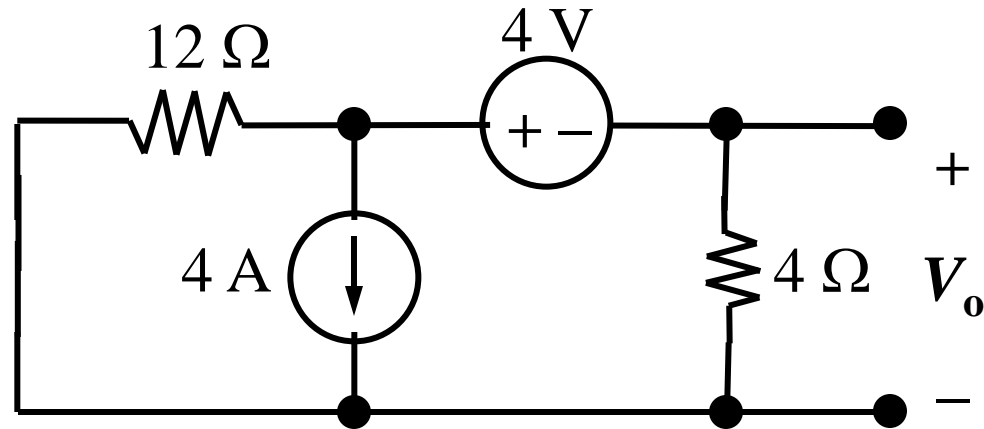

Voltage Divider: $-1\ \text{V}$

Easy Example


- Find V_o

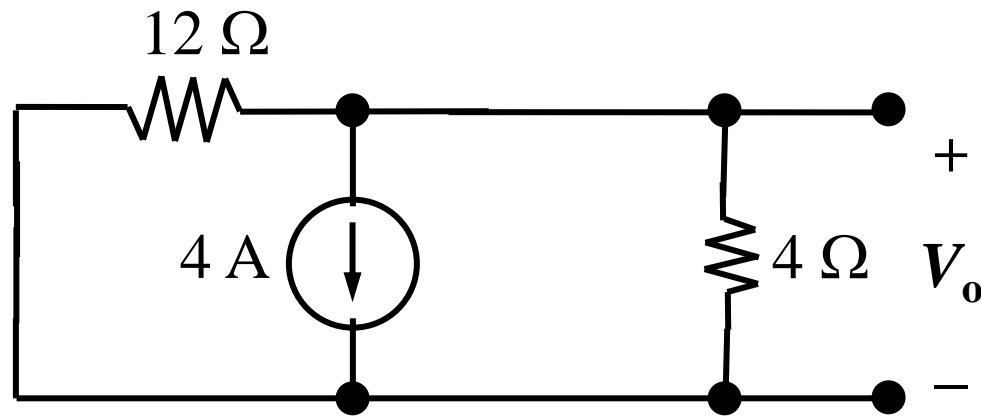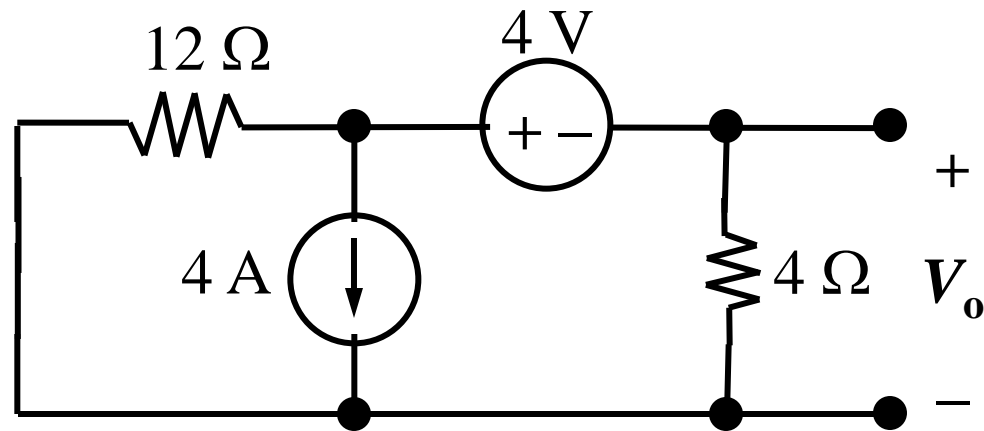

Current Divider: $-(3\ \text{A} * 4\ \Omega) = -12\ \text{V}$

Easy Example

- Find V_o



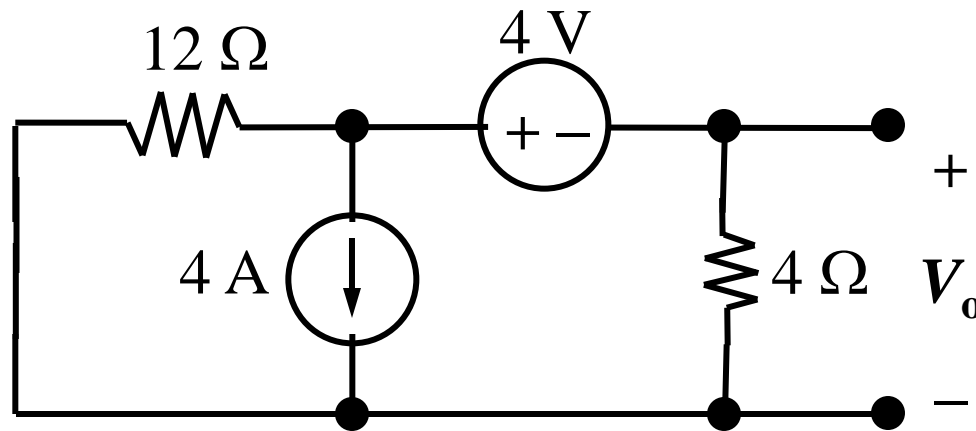


$$V_o = -12\text{V} - 1\text{V} = -13\text{V}$$


Due to current source

Due to voltage source

Hard Example

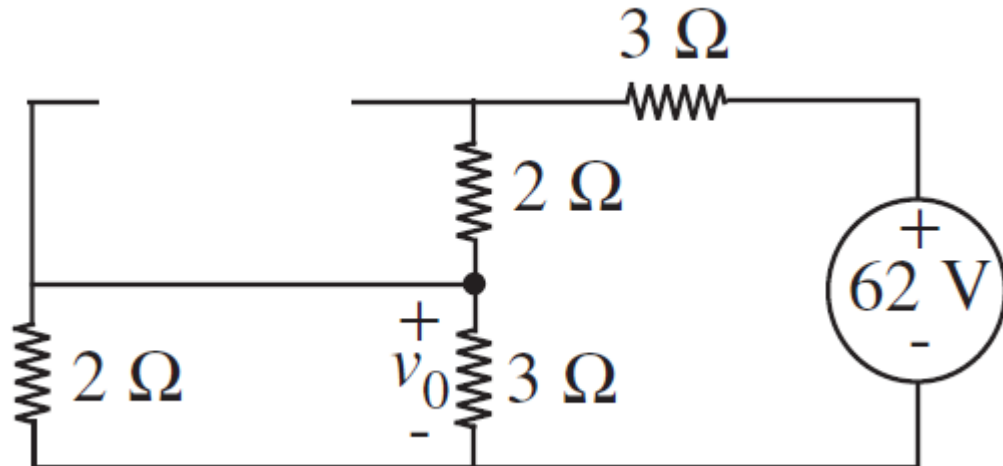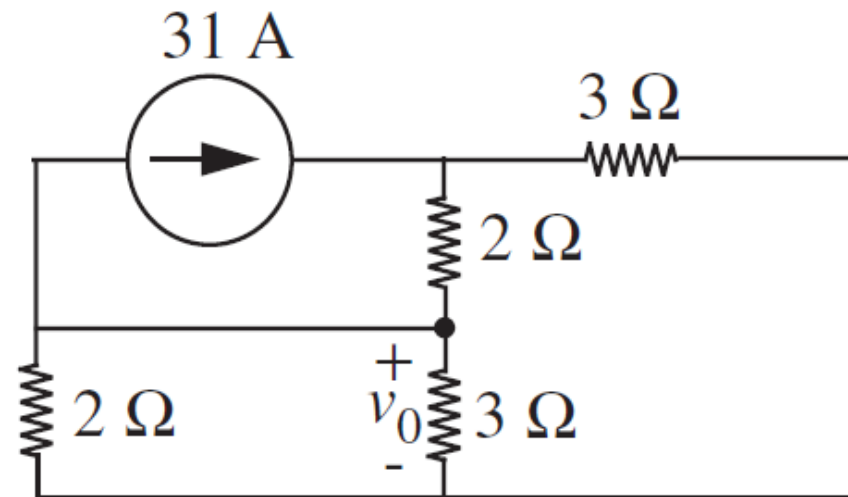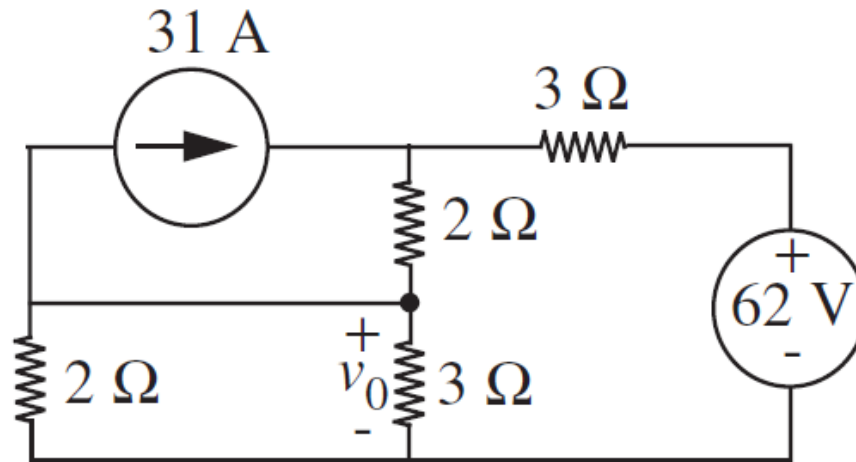

Example

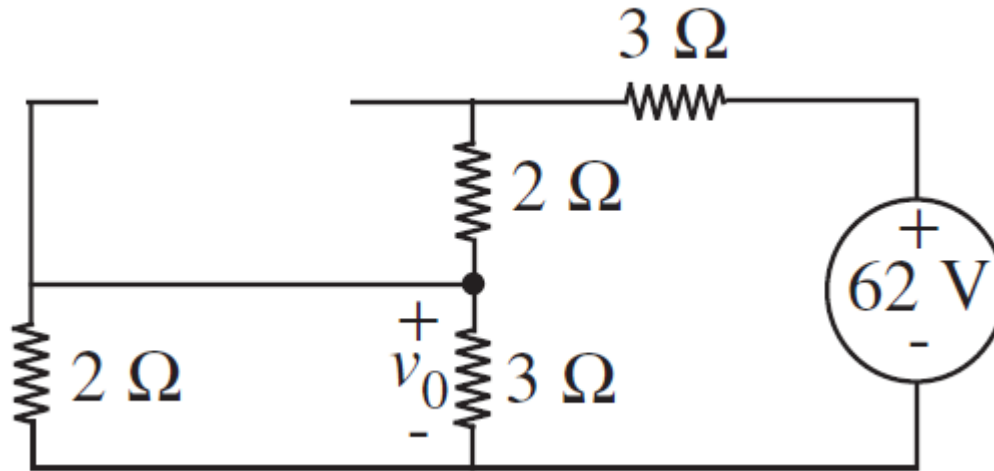


Equivalent resistance:

$$3+2+(3\parallel 2) = 5+(3*2)/(3+2)=6.2\Omega$$

Current is 10A

50V loss through top 5Ω, leaving 12V across v_0

Example

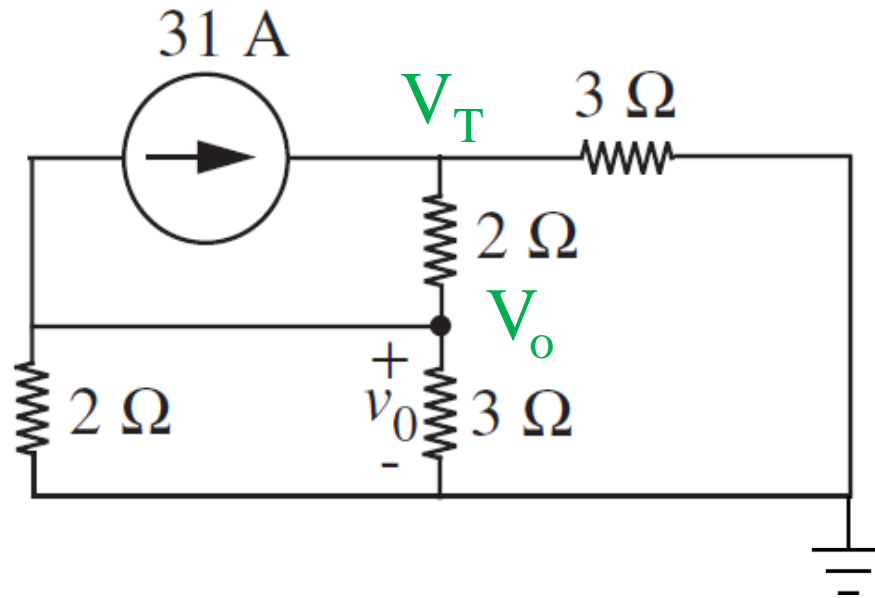


$$\frac{V_o}{3} + \frac{V_o}{2} + 31 + \frac{V_o - V_T}{2} = 0$$

This will work...

$$-31 + \frac{V_T - V_o}{2} + \frac{V_T}{3} = 0$$

But algebra is easier if we pick a better ground


Example

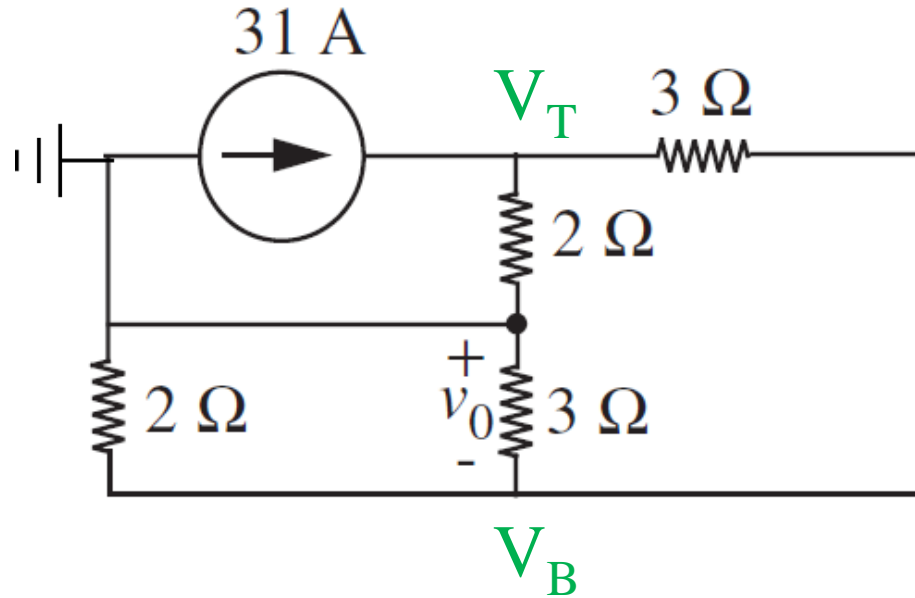


$$\frac{V_B}{2} + \frac{V_B}{3} + \frac{V_B - V_T}{3} = 0 \quad \longrightarrow \quad V_B = \frac{2}{7} V_T$$

$$-31 + \frac{V_T}{2} + \frac{(V_T - V_B)}{3} = 0 \quad \longrightarrow \quad V_B = 12V$$
$$V_0 = -12V$$


Example

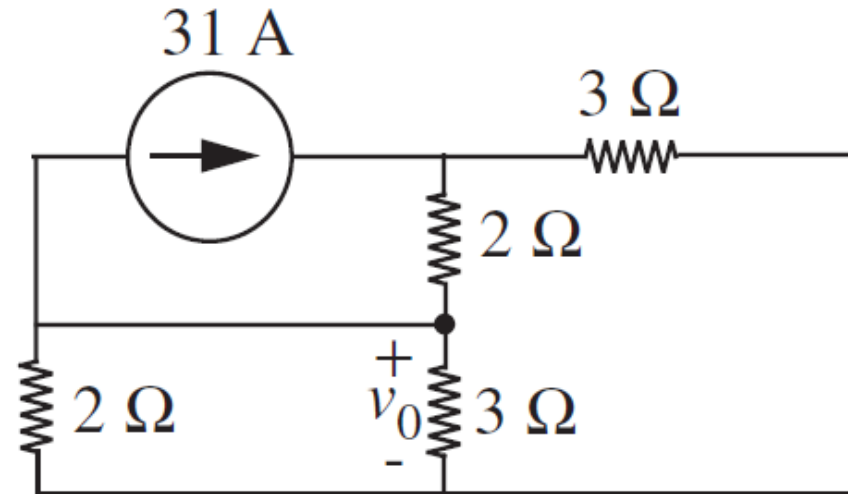

$$V_o = -12V$$

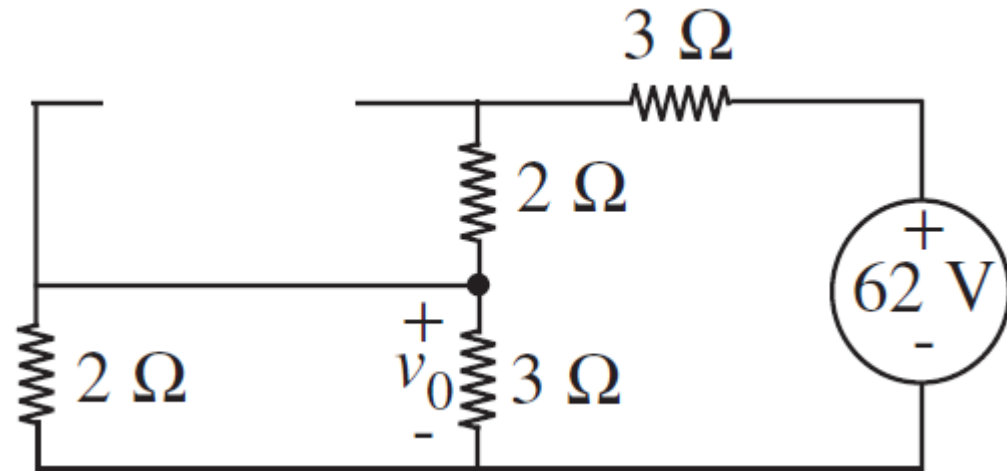

$$V_o = 12V$$

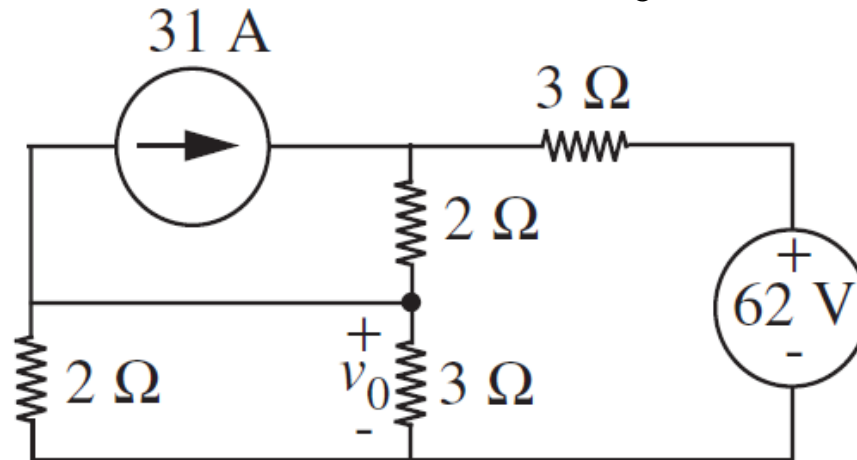


$$V_o = -12V + 12V = 0V$$

Note on Dependent Sources


- You can use superposition in circuits with dependent sources
- However, DON'T remove the dependent sources! Just leave them there.

Equivalent Resistance Review

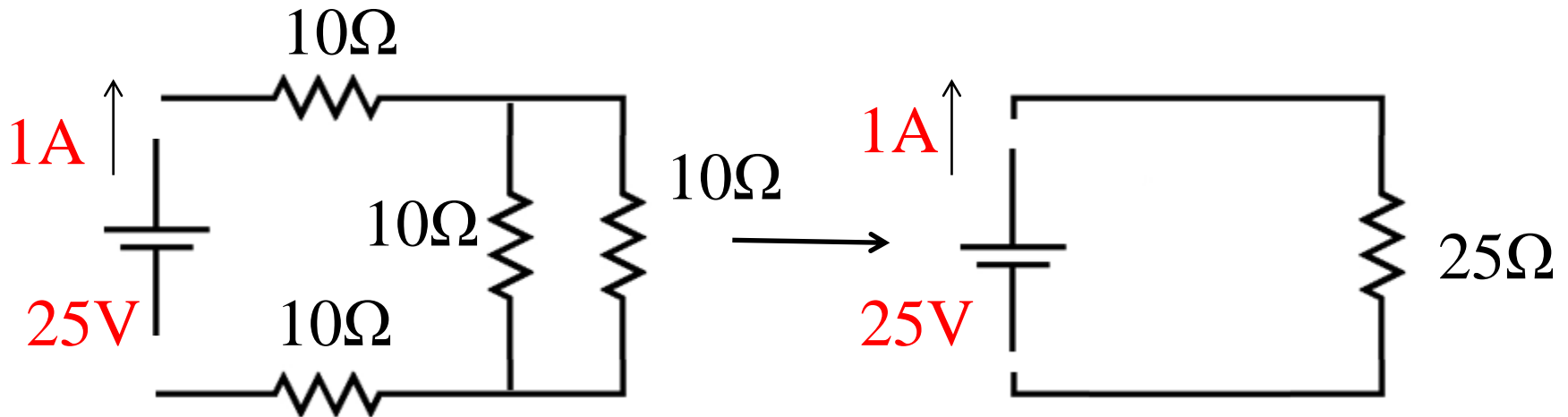
- If you add a source to any two terminals in a purely resistive circuit
 - The added source will “see” the resistive circuit as a single resistor



Alternate Viewpoint

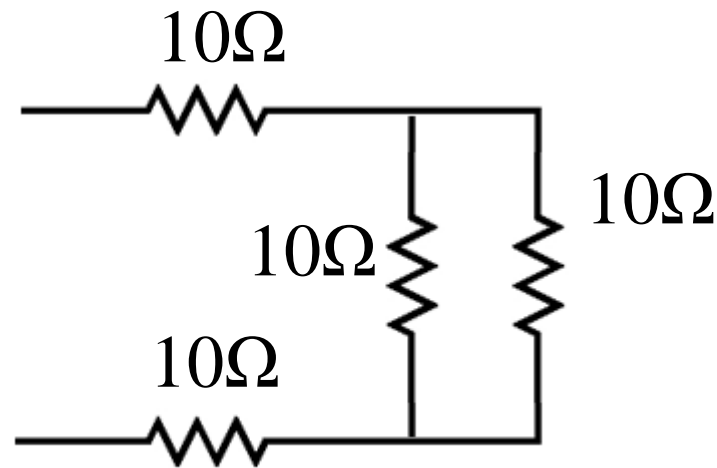


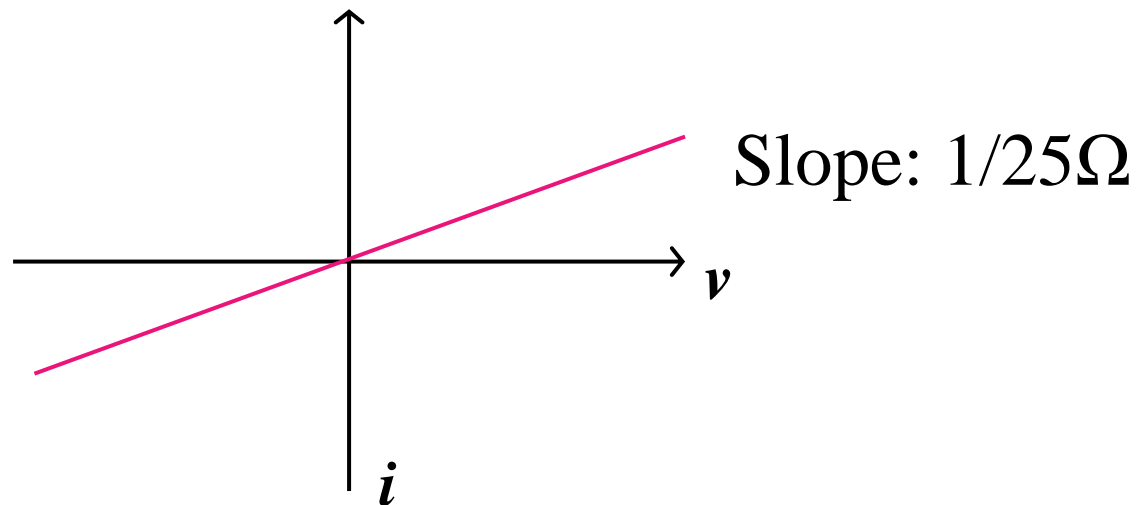We can think of the circuit above as a two terminal circuit element with an I-V characteristic




Equivalent Resistance

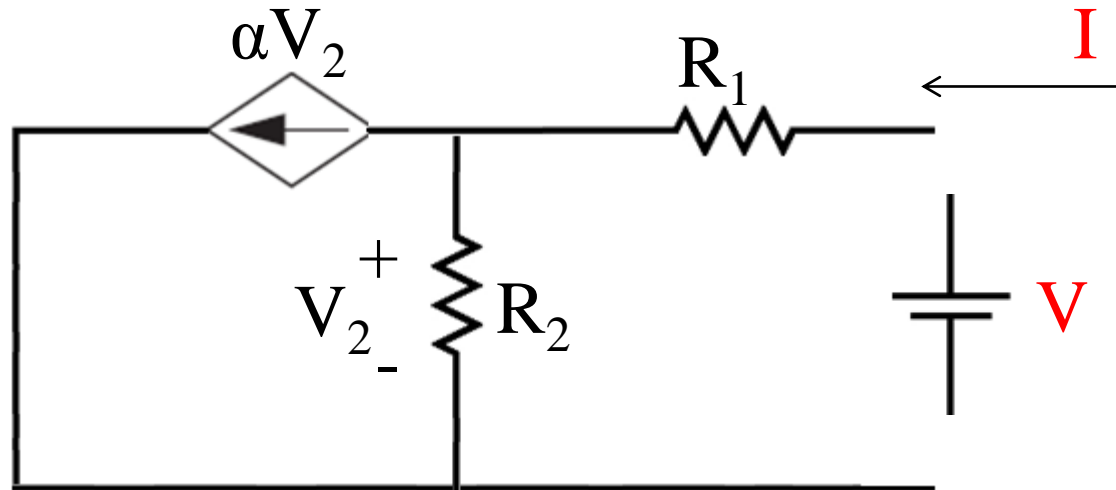- Let's consider the IV characteristic of the following circuit:



$$\frac{V_2 - V}{R_1} + \frac{V_2}{R_2} + \alpha V_2 = 0$$

Equivalent Resistance

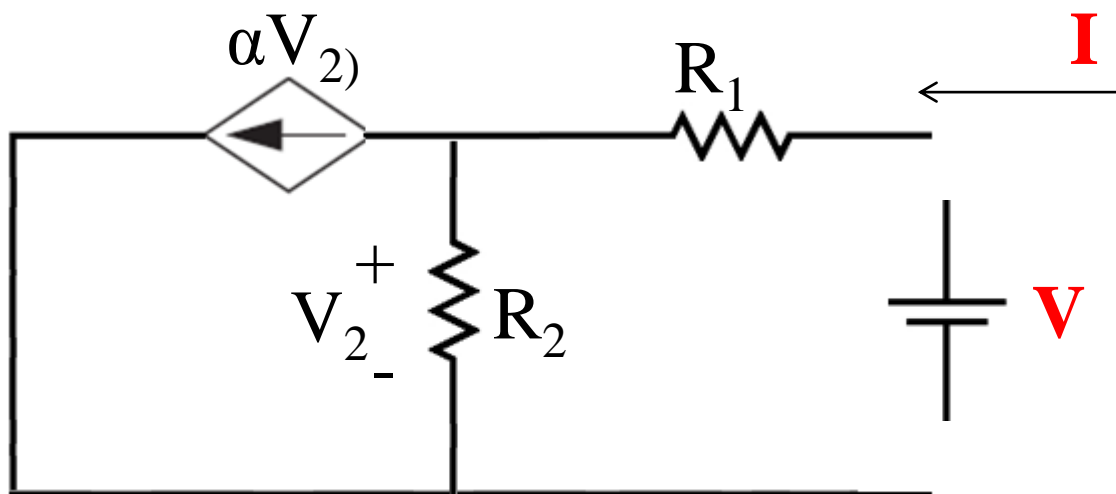



$$\frac{V_2 - V}{R_1} + \frac{V_2}{R_2} + \alpha V_2 = 0$$

$$V_2 = \frac{R_2 V}{R_1 + R_2 + \alpha R_1 R_2}$$

$$I = \frac{V - \frac{R_2 V}{R_1 + R_2 + \alpha R_1 R_2}}{R_1}$$

$$\frac{I}{V} = \frac{1 + \alpha R_2}{R_1 + R_2 + \alpha R_1 R_2}$$

Equivalent Resistance

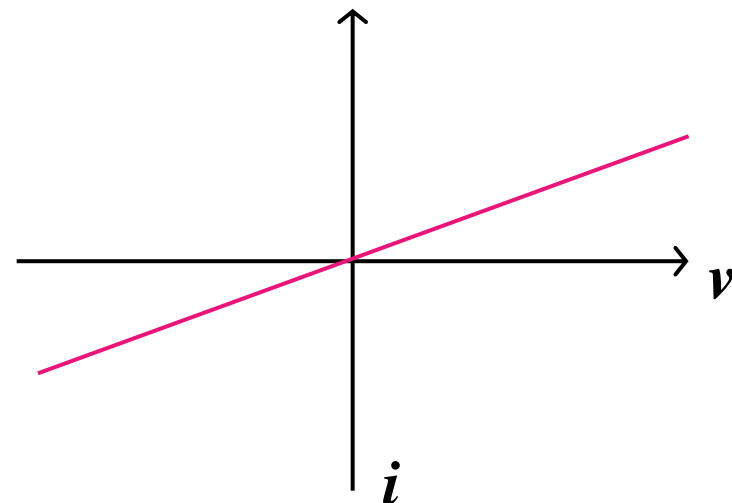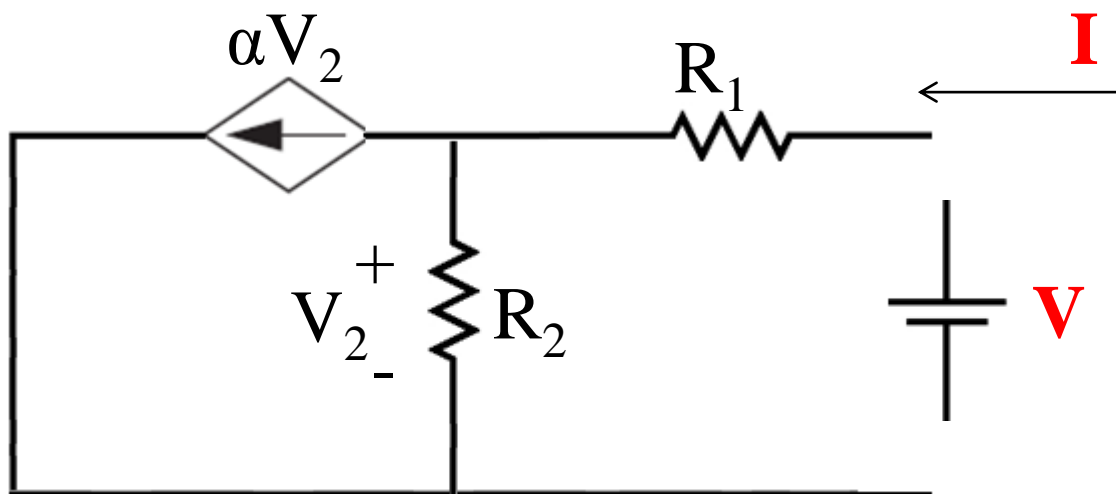


$$\frac{I}{V} = \frac{1 + \alpha R_2}{R_1 + R_2 + \alpha R_1 R_2}$$
$$= 1/R_{\text{eq}}$$

$$\text{Slope: } \frac{1 + \alpha R_2}{R_1 + R_2 + \alpha R_1 R_2}$$


This circuit just acts like a resistor!

Equivalent Resistance Summary So Far

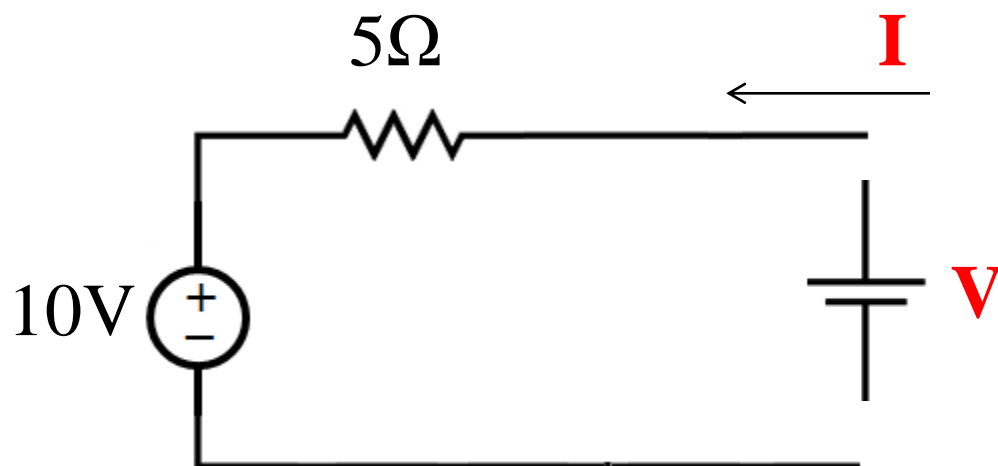- Purely resistive networks have an I-V characteristic that looks just like their equivalent resistance
- **Purely resistive networks which also include dependent sources also act like resistors**
- Let's see what happens with a circuit with an independent source




Equivalent Resistance Summary So Far

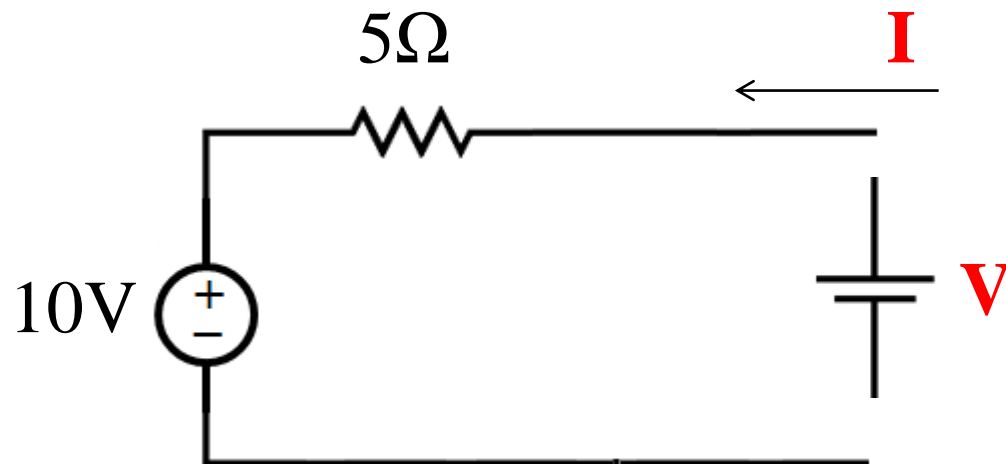


$$I = \frac{V - 10}{5} = \frac{V}{5} - 2$$

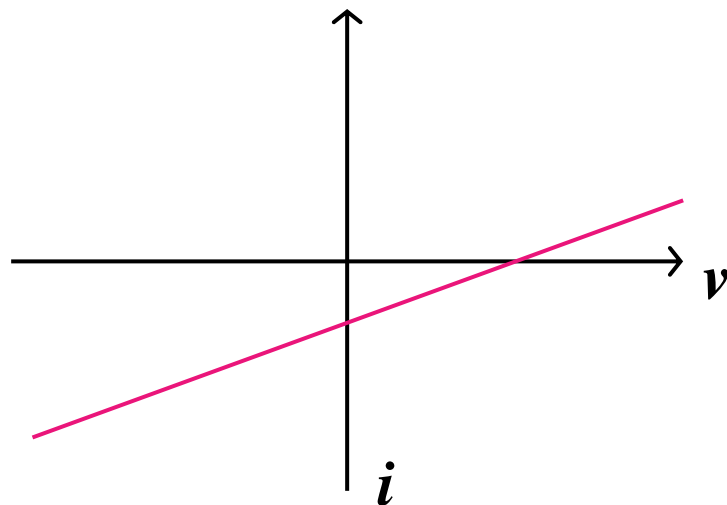
Doesn't match our basic I-V characteristics... good!




Interestingly...

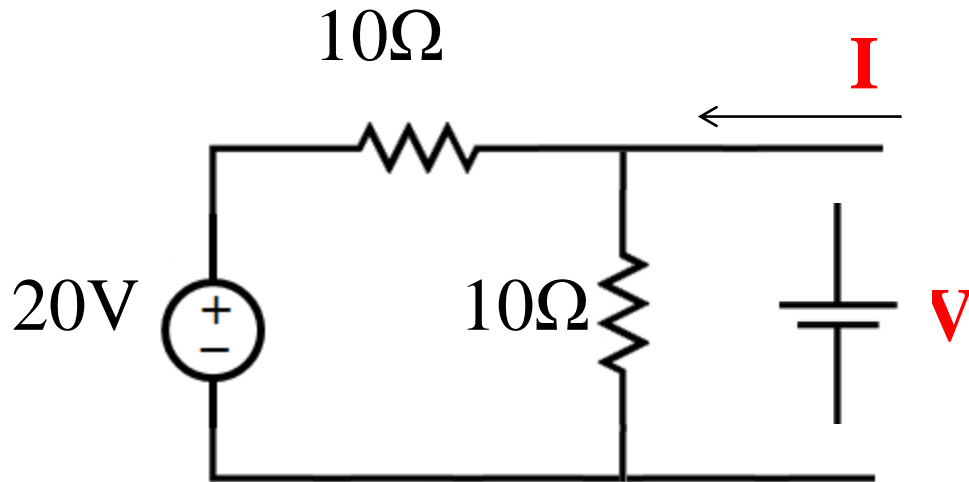

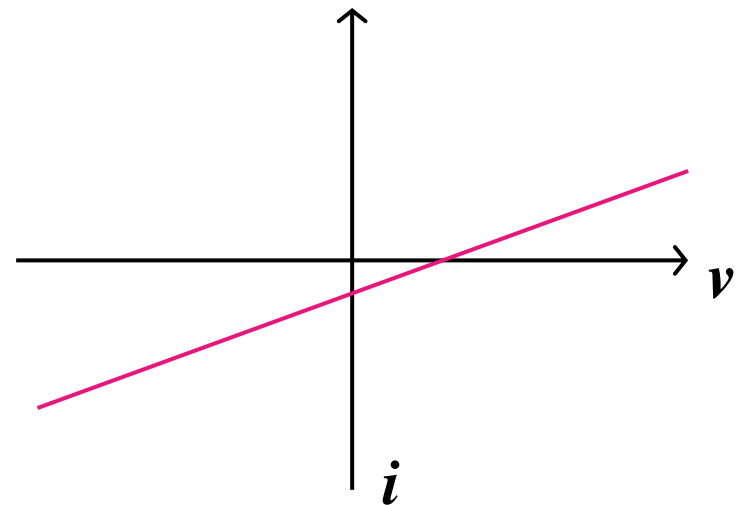
$$I = \frac{V - 20}{10} + \frac{V}{10}$$
$$= \frac{V}{5} - 2$$



Equivalent Circuits

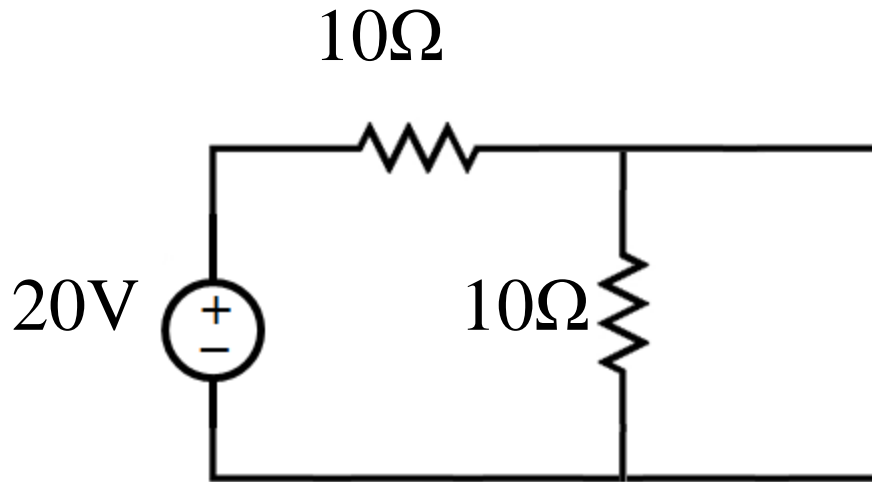

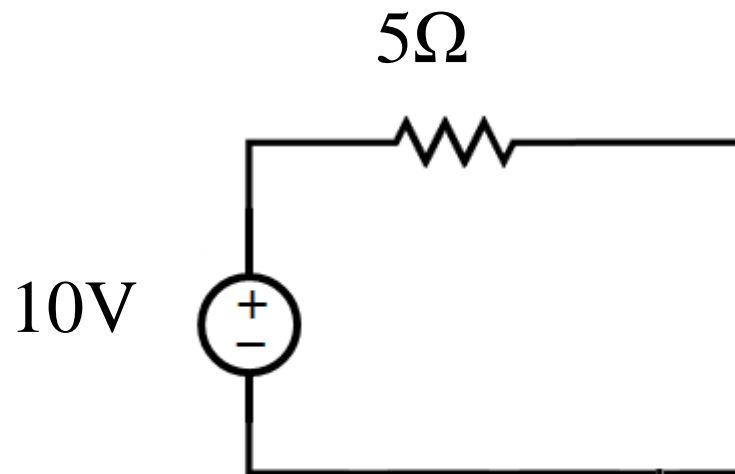Has the exact same I-V characteristic as:




Thevenin Equivalents

- We saw before that we can replace a network of resistors (and dependent sources) with a single equivalent resistance
- Now, we have that **we can replace any circuit we can build so far with a single voltage source and resistor**
 - Not proven, but it's true, trust me
- This two element network is known as a **Thevenin equivalent**
- Generalization of the idea of equivalent resistance

Again: Discovered twice, named after the second guy!

Why is this useful?

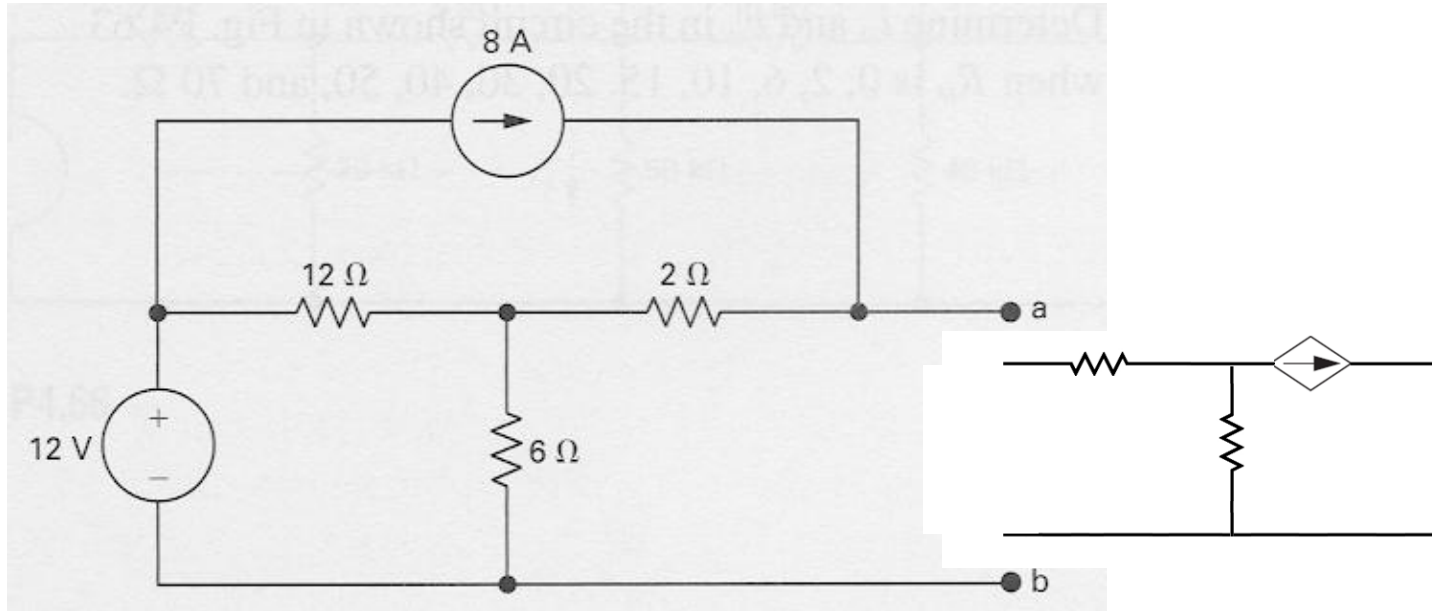


- Can swap out elements and not have to resolve a big circuit again
- Captures the fundamental operation of the circuit as a whole (at chosen two terminals only!)

Thevenin Algorithm for Independently Sourced Circuits

- What you're ultimately doing is finding the I-V characteristic of the circuit
- You can do this by attaching a made up V , and calculating I as on slides 49 and 50
 - Often called a “Test Voltage”
- This is equivalent to:
 - Finding the “open circuit” voltage
 - Finding the “short circuit” current


Calculating a Thévenin Equivalent

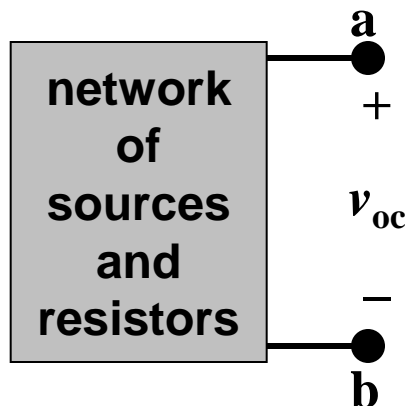1. Calculate the **open-circuit voltage**, v_{oc}



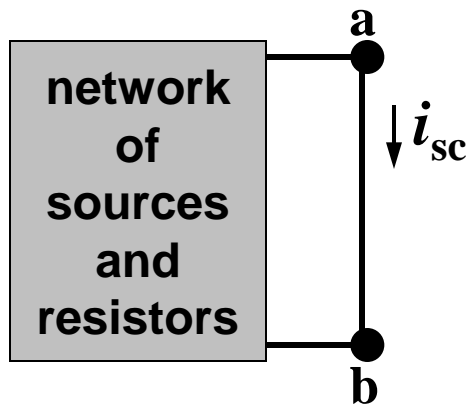
2. Calculate the **short-circuit current**, i_{sc}

- Note that i_{sc} is in the direction of the open-circuit voltage drop across the terminals a,b !



$$V_{Th} = v_{oc}$$
$$R_{Th} = \frac{v_{oc}}{i_{sc}}$$

Example – On the Board

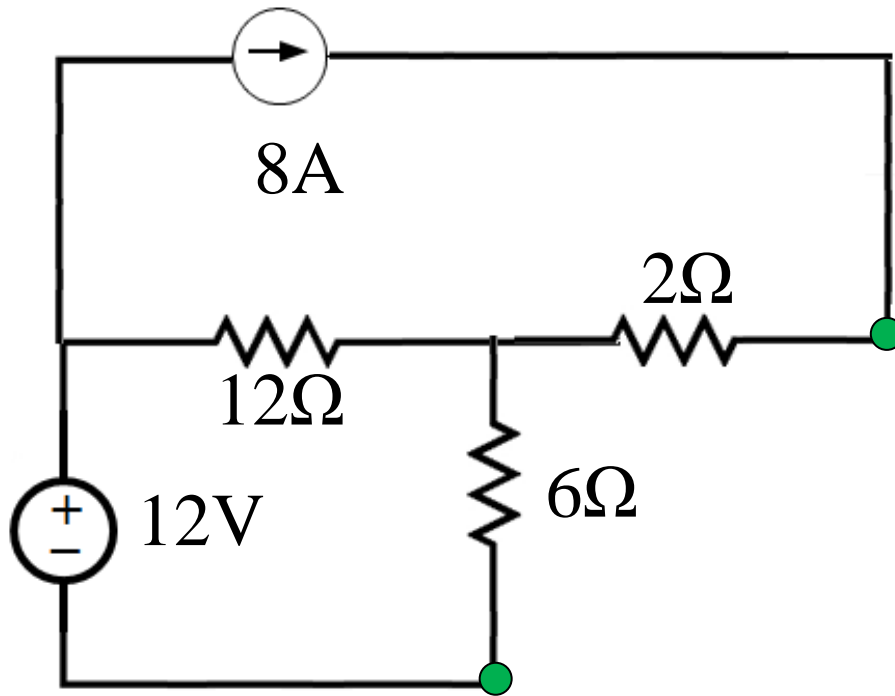

Find the Thevenin Equivalent circuit, by finding


1. V_{OC}
2. I_{SC}

Finding Thevenin Resistance Directly


- If there are no dependent sources in the circuit, we can find the Thevenin Resistance directly
- Algorithm is easy:
 - Set all **independent** sources to zero
 - Voltage source becomes short circuit
 - Current source becomes open circuit
 - Leave dependent sources intact
 - Find equivalent resistance between terminals of interest

Norton Equivalent Circuit

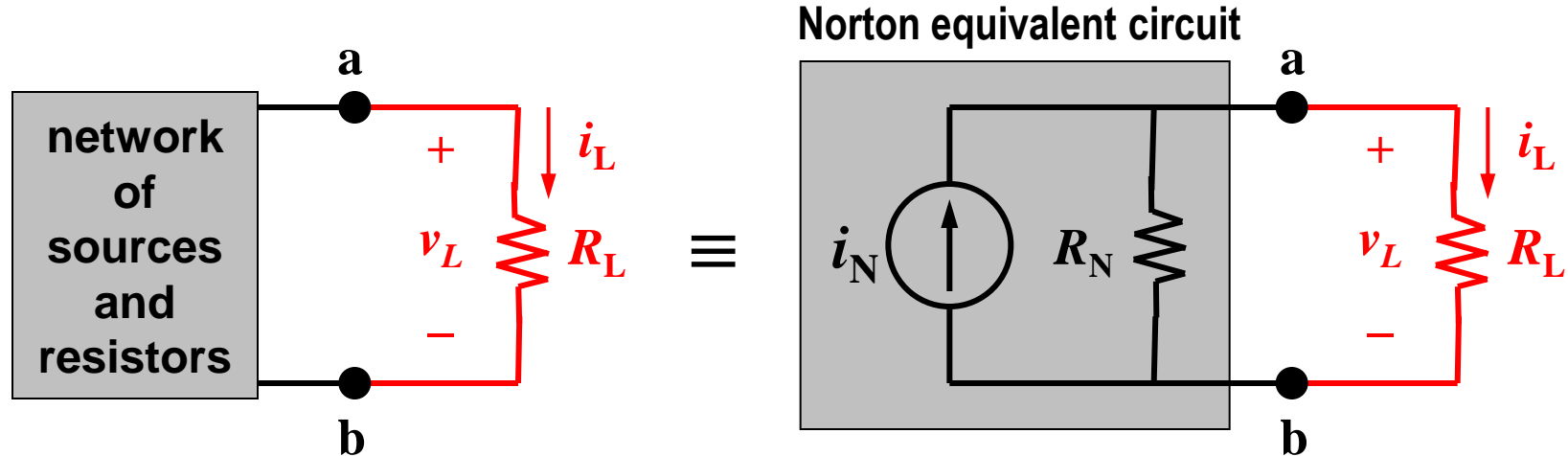- Any network of voltage sources, current sources, and resistors can also be replaced by an equivalent circuit consisting of **an independent current source in parallel with a resistor** without affecting the operation of the rest of the circuit.




Example – On the Board

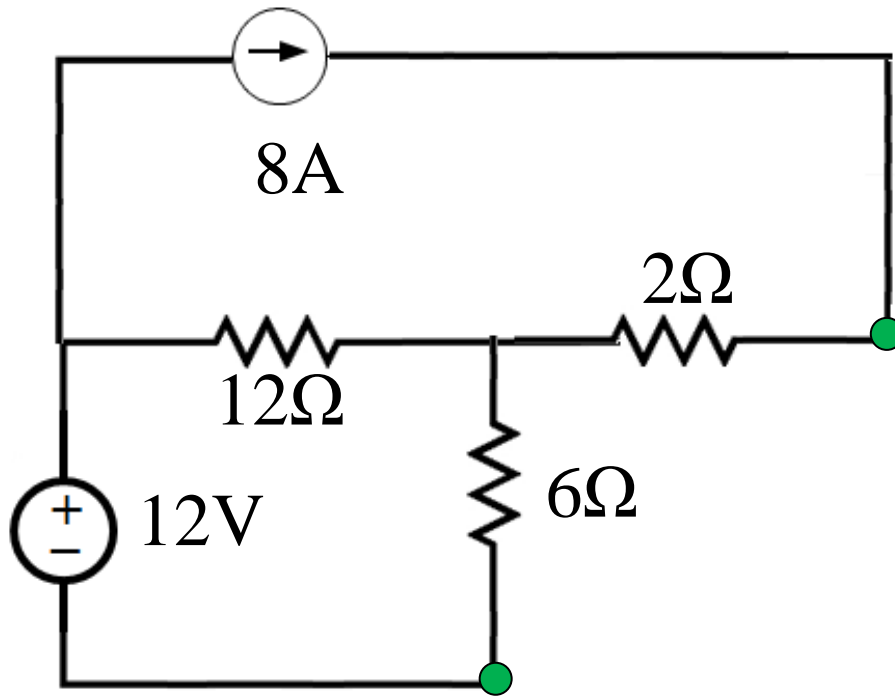


Find the Thevenin Equivalent resistance directly

Finding I_N and R_N

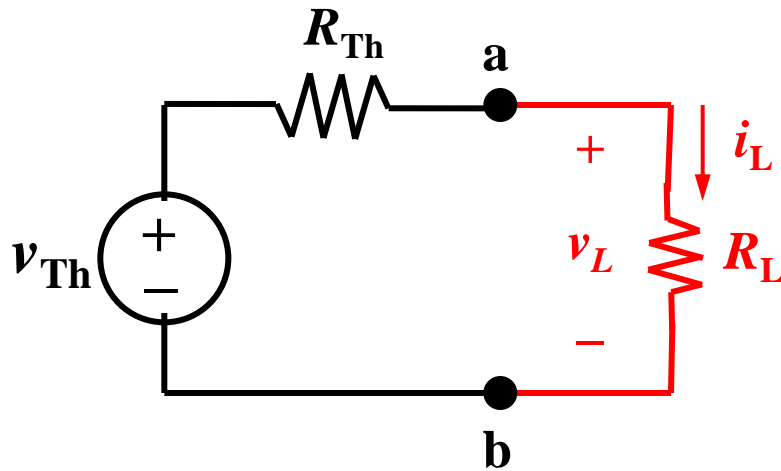- We can derive the Norton equivalent circuit from a Thévenin equivalent circuit simply by making a source transformation:



$$i_L = \frac{v_{Th}}{R_{Th} + R_L}$$

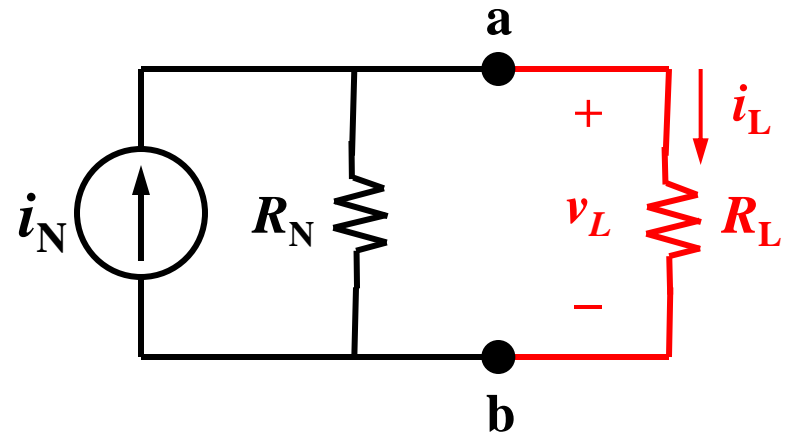

$$i_L = \frac{R_N}{R_N + R_L} i_N$$

$$R_N = R_{Th} = \frac{v_{oc}}{i_{sc}}; \quad i_N = \frac{v_{Th}}{R_{Th}} = i_{sc}$$


Circuit Simulation

- Automated equation solvers use our algorithm:
 - Choose a ground node
 - Assign node voltage labels to all nodes
 - Write out a system of $N-1$ linear equations
 - Solve (using standard linear algebra techniques)
- One pretty handy tool is falstad.com's circuit simulator
- Let's try a live demo

Extra Slides

Delta-Wye Conversion

Equivalent Resistances

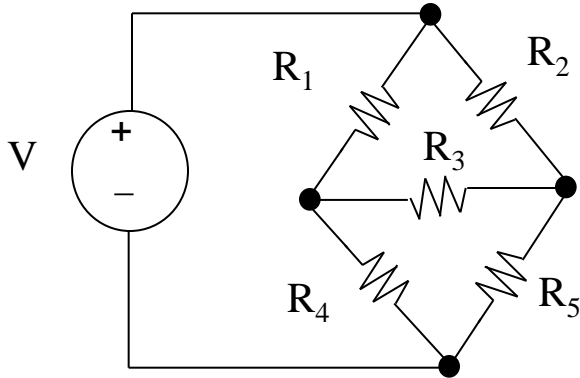

Are there any circuit elements in parallel?

No

Are there any circuit elements in parallel?



No

What do we do?

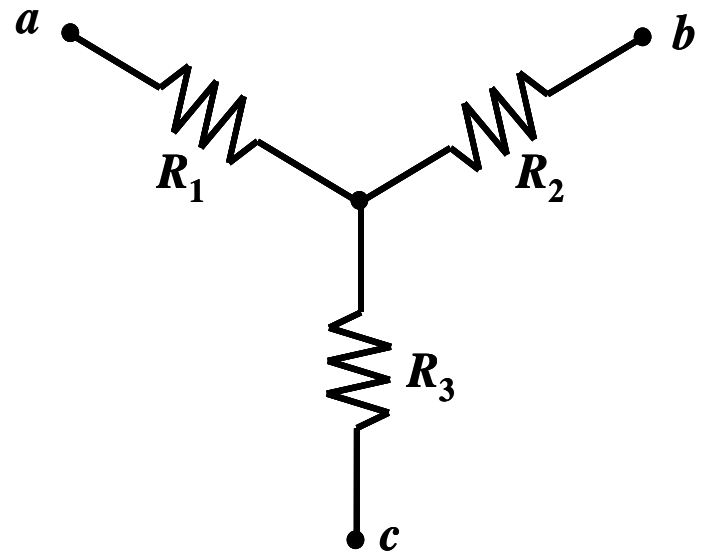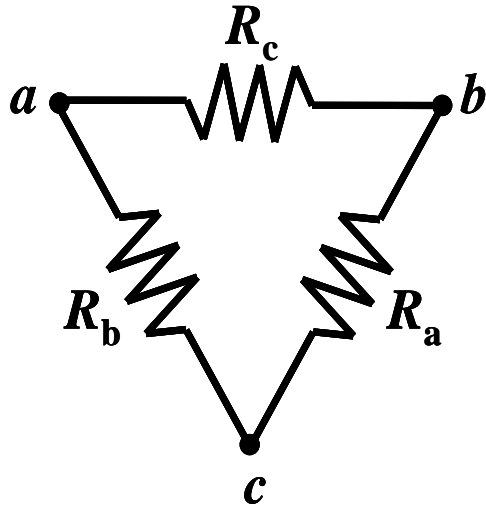1. Be clever and find I-V characteristic directly
2. Apply weirder transformation rules than series or parallel

Y-Delta Conversion

- These two resistive circuits are equivalent for voltages and currents external to the Y and Δ circuits. Internally, the voltages and currents are different.



$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$



Δ -Y and Y- Δ Conversion Formulas

Delta-to-Wye conversion

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$
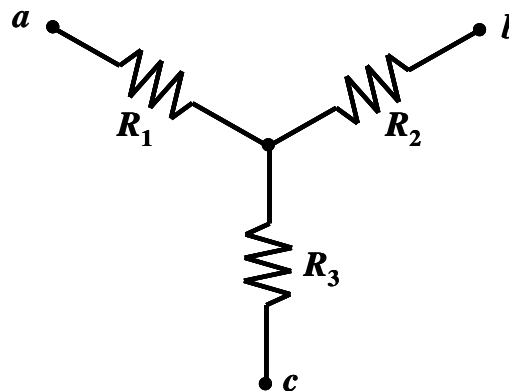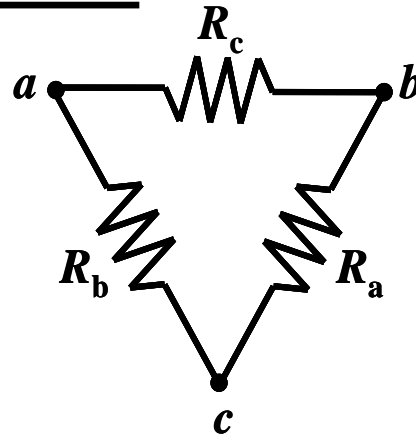
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$



Wye-to-Delta conversion


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Circuit Simplification Example

Find the equivalent resistance R_{ab} :

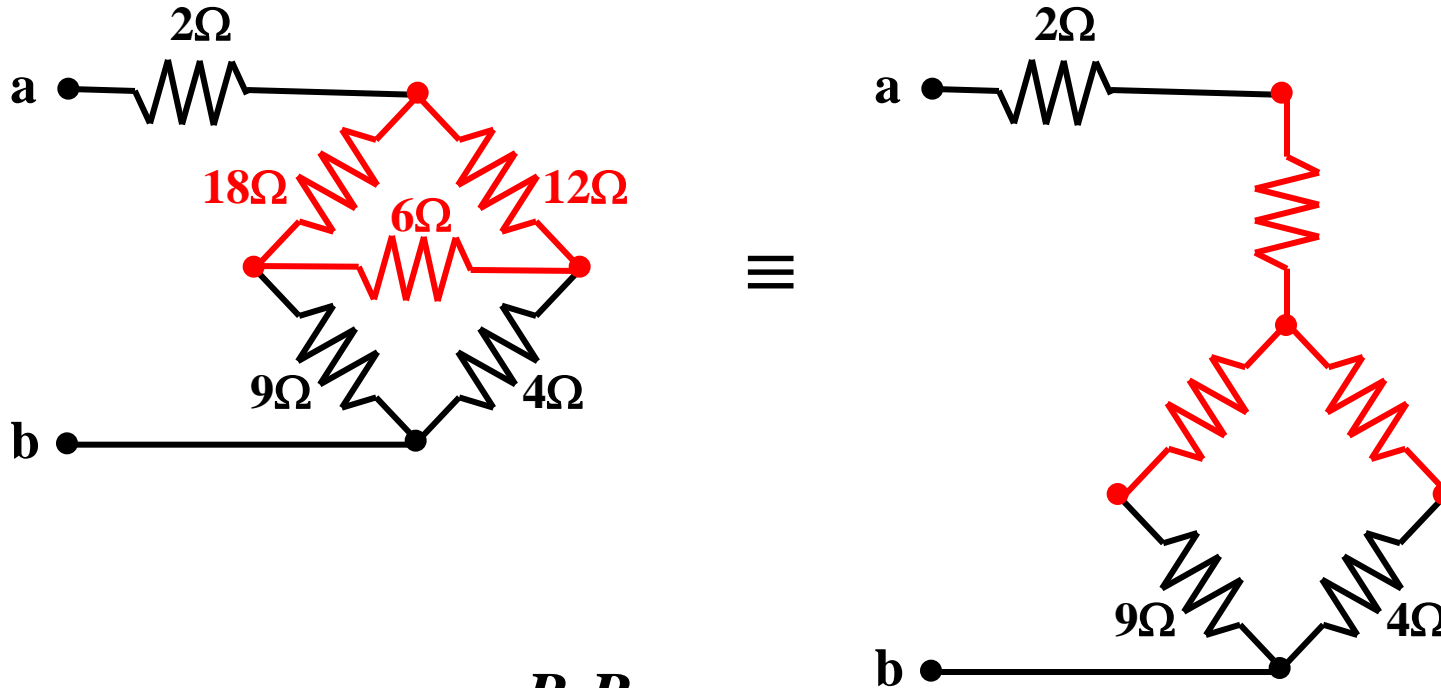

$$R_b = 18$$

$$R_a = 12$$

$$R_c = 6$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$3$$


$$= 6$$

$$R_2 = 2$$


General Versions of Thevenin Slides

Equivalent Resistance Summary So Far

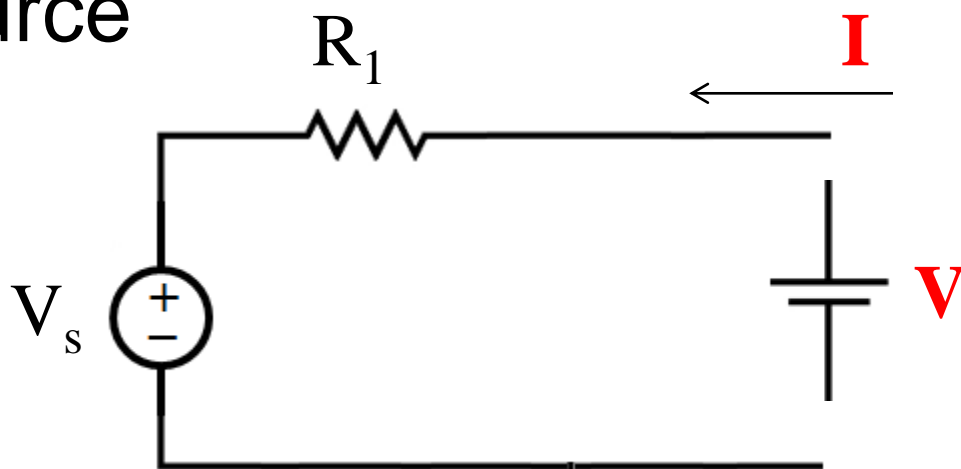- Purely resistive networks have an I-V characteristic that look just like their equivalent resistance
- Networks which include dependent sources also act like resistors
- Let's see what happens with a circuit with a source




Equivalent Resistance Summary So Far

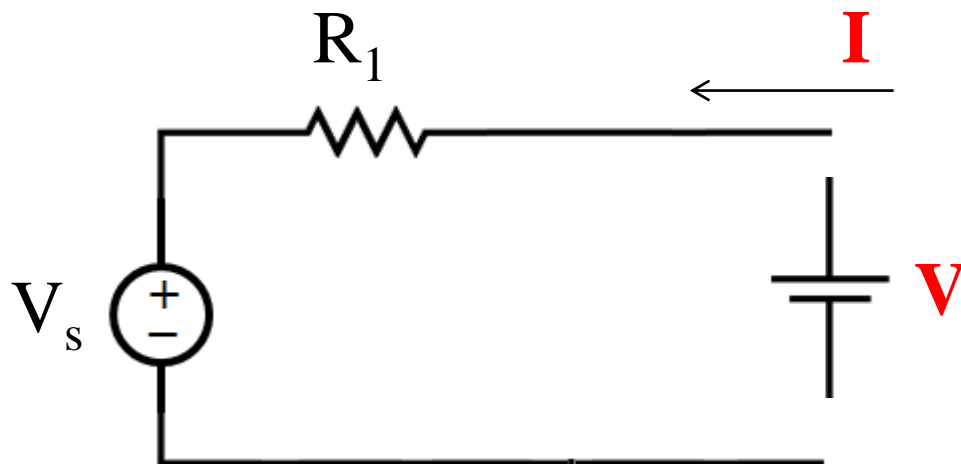


$$I = \frac{V - V_s}{R_1}$$

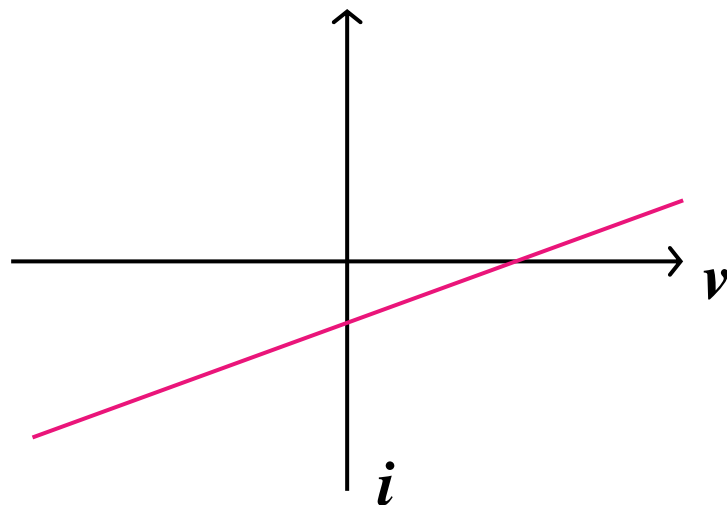
Doesn't match our basic I-V characteristics... good!




Interestingly...

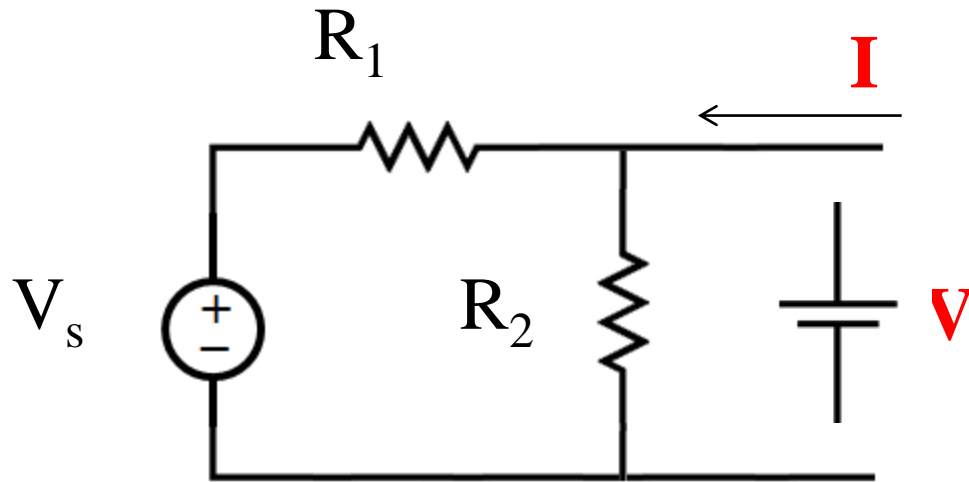
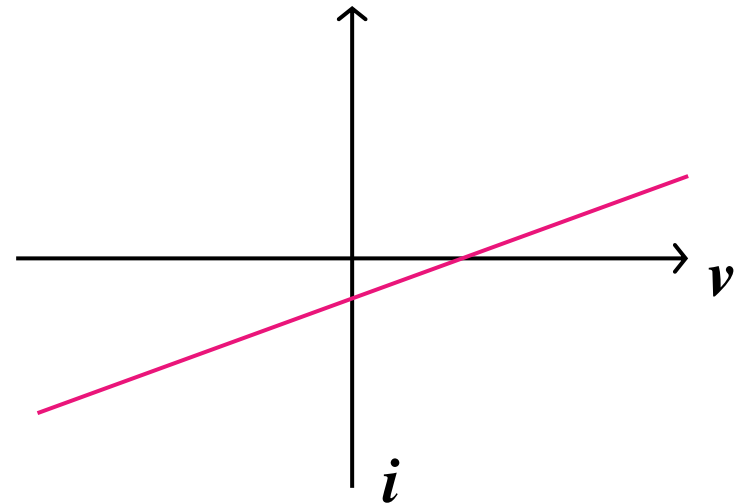
$$I = \frac{V - V_s}{R_1} + \frac{V}{R_2}$$



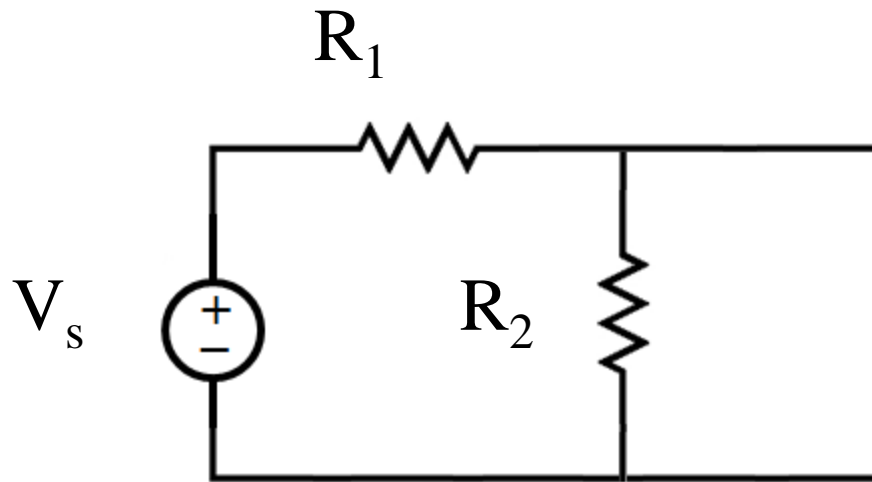

Has the exact same I-V characteristic as:

