


Thevenin Equivalent:

Find 2 of:


- V_{oc}
- I_{sc}
- R_{TH}

V_{oc} :

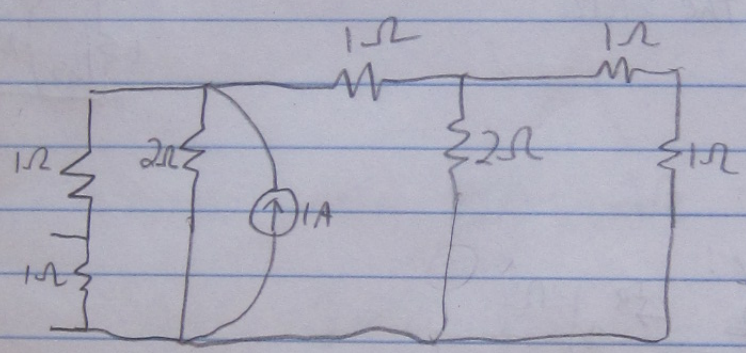
Could do node voltage, but 3 equations, 3 unknowns. Somewhat cumbersome. I prefer superposition.



$$R = ((1+1) \parallel 2) + 1 = 2$$

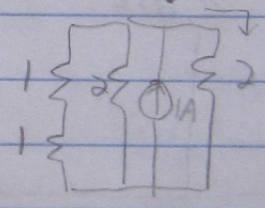


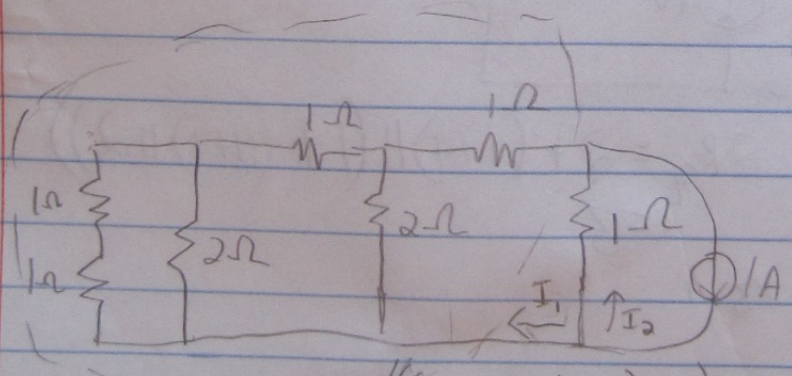Current splits evenly
 $V_0 = \frac{1}{3} A \cdot 1 \Omega = \frac{1}{3} V$



$$R_{eq} = (((1+1) \parallel 2) + 1) \parallel 2 + 1 = 2$$

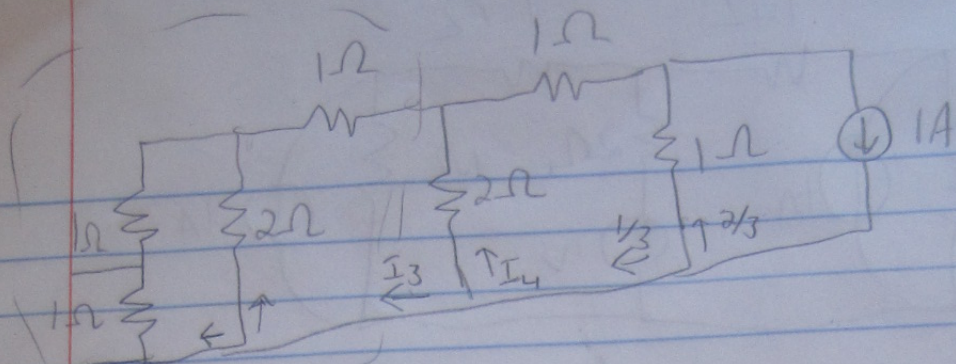Current divider gives us that $I_1 = \frac{1}{3} A$, $I_2 = \frac{2}{3} A$




$$R_{eq} = (((1+1) \parallel 2) + 1) = 2 \Omega$$

Current divider: Each gets half


$$\frac{1}{3} A \cdot \frac{1}{2} = \frac{1}{6} A$$

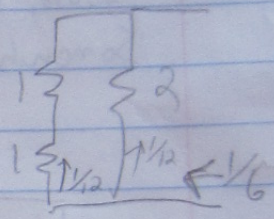Then finally, it obviously splits in half between:
So $\frac{1}{12} A$ goes through the 1Ω .




$$V_0 = -\frac{1}{12} V$$

Finally, the voltage source:

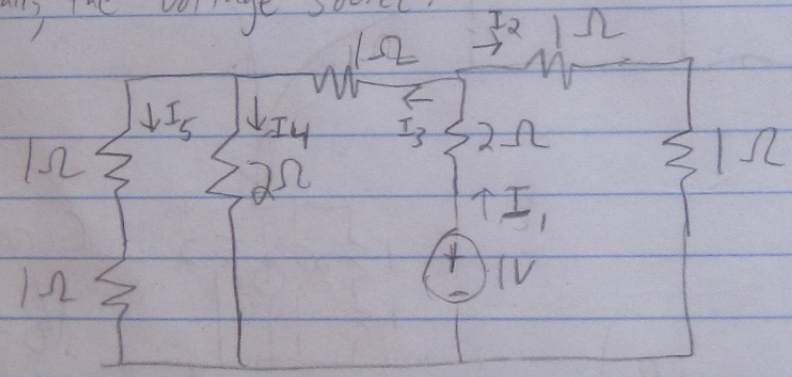

$$R_{eq} = 2 R_{eq} = 2 + (1+1) \parallel (1 + ((1+1) \parallel 2)) = 3$$

$$I_1 = \frac{1}{3} A$$

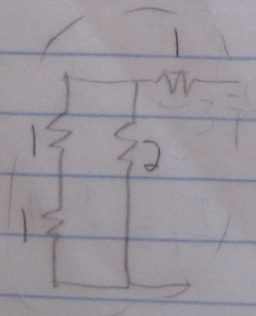


$$R_{eq} = 1 + 2 \parallel 2 = 2$$

Current divider: $\frac{1}{2} I_1 = I_2 = I_3 = \frac{1}{2} \cdot \frac{1}{3} A = \frac{1}{6} A$

Finally, $I_4 = I_5 = \frac{1}{2} \cdot I_3 = \frac{1}{12} A$

$$V_0 = \frac{1}{12} V$$
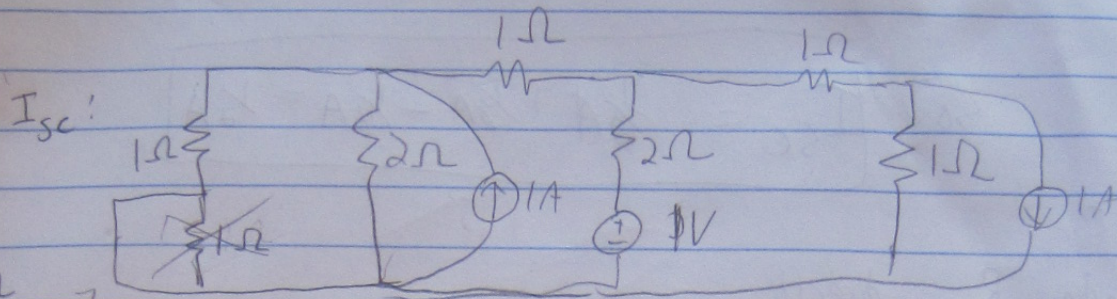
$$V_{oc} = \frac{1}{12}V - \frac{1}{12}V + \frac{1}{3}V = \frac{1}{3}V$$




Ignore 1Ω resistor, since it's shorted.

Superposition:


Left current source:

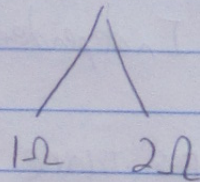Splits between $\frac{1}{3}\Omega$ and $(1 + (2 \parallel (2+1)))$
 2Ω



$$\text{So } 1A \cdot \frac{2}{2+\frac{2}{3}} \cdot \frac{2}{3} = \frac{4}{6+2} = \frac{1}{2}A$$

Right current source:

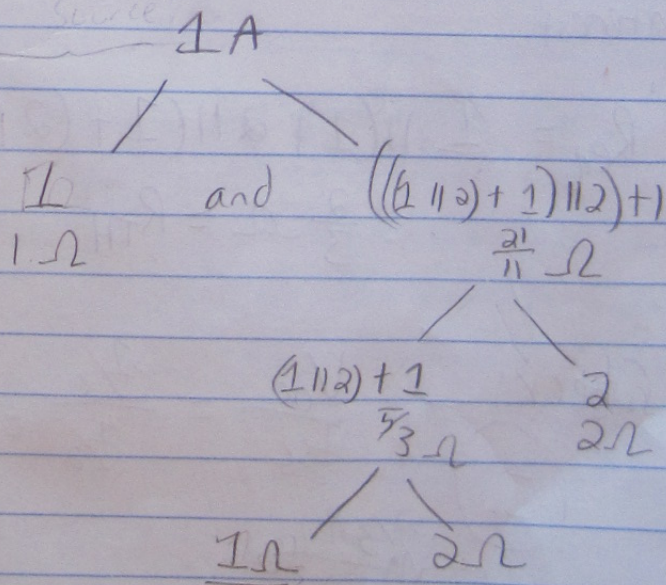

$$\begin{aligned} & \frac{5}{3} \cdot 2 \\ & \frac{5}{3} + 2 \\ & \frac{10}{3} \\ & \frac{10}{3} \\ & = \frac{10}{11} \\ & \frac{10}{11} + 1 = \frac{21}{11} \end{aligned}$$

Current divider:

$$\frac{1}{\frac{21}{11} + 1} \cdot \frac{2}{2+\frac{2}{3}} \cdot \frac{2}{3} = \frac{11}{32} \cdot \frac{2}{11} \cdot \frac{2}{3} = \frac{11}{32} \cdot \frac{6}{11} \cdot \frac{2}{3} = \frac{1}{8}A$$


$$I_{sc} = -\frac{1}{8}A$$

Voltage sources:

Similar math gives you $I_{SC} = 1/8 A$

$$\text{So } I_{SC} = 1/2 A + 1/8 A - 1/8 A = 1/2 A$$

Finding R_{TH} directly:

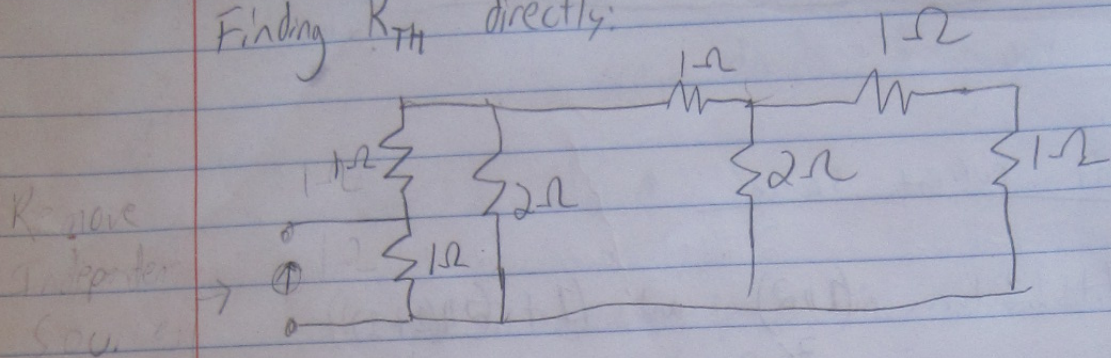


1. First Remove Independent Sources

2. Find equivalent resistance between terminals.

If you get confused about where to start, pretend there's a source across the terminals of interest.


$$R_{eq} = 1 \parallel (1 + 2 \parallel (1 + (2 \parallel (1 + 1))))$$
$$\frac{2}{3} \Omega = R_{TH}$$

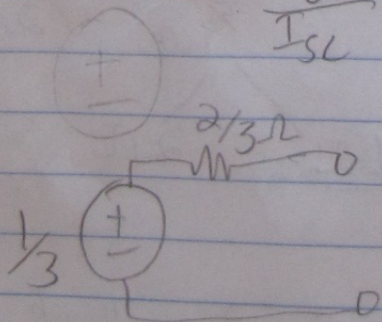Check! $\frac{V_{oc}}{I_{sc}} = \frac{1/3}{1/2} = 2/3 \Omega$



Big crazy Node Voltage Problem

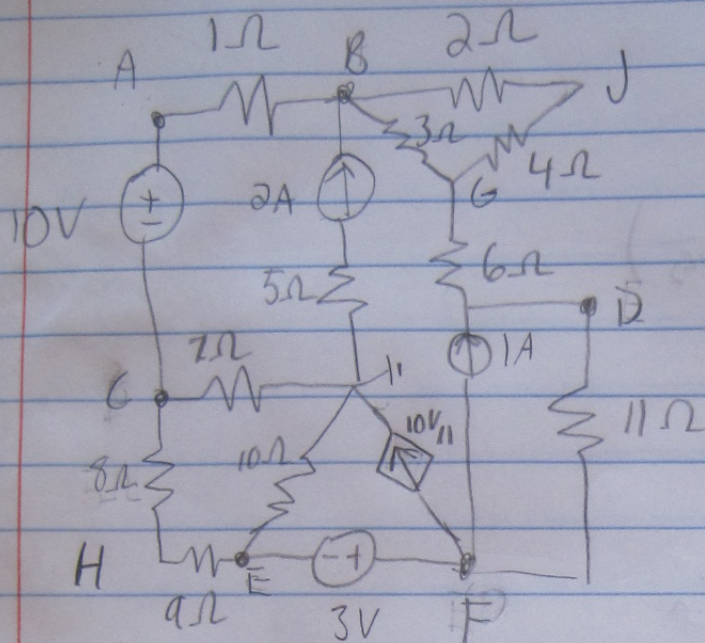Let's assume we don't actually care about node voltages



$$V_G, V_J, V_H$$

$$V_A = V_C + 10V$$

$$V_F = V_E + 3V$$

$$V_H = V_D - V_F$$

$$B: \frac{V_B - V_A}{1\Omega} + \frac{V_B - V_D}{(2+4)\parallel(3+6)} - 2 = 0$$

$$A \& C: \frac{V_A - V_B}{1\Omega} + \frac{V_C - V_E}{8+9} + \frac{V_C}{7} = 0$$

$$E \& F: \frac{V_E - V_C}{8+9} + \frac{V_E}{10} + 10V_{II} + 1 + \frac{V_E - V_D}{11} = 0$$

$$D: \frac{V_D - V_B}{3+6} - 1 + \frac{V_D - V_E}{11} = 0$$

Equations (4 big ones)
7 unknowns

Amazing to solve. This is why we have computers.